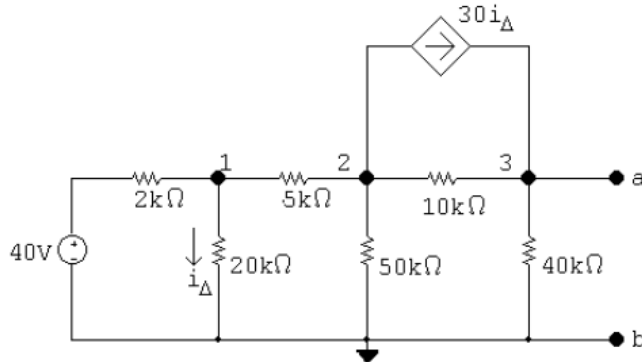


Open book, open notes, and use of a laptop equipped with Freemat is allowed.

1) Find the Thevenin equivalent of the circuit at a-b

P 4.73



The node voltage equations are:

$$\frac{v_1 - 40}{2000} + \frac{v_1}{20,000} + \frac{v_1 - v_2}{5000} = 0$$

$$\frac{v_2 - v_1}{5000} + \frac{v_2}{50,000} + \frac{v_2 - v_3}{10,000} + 30 \frac{v_1}{20,000} = 0$$

$$\frac{v_3 - v_2}{10,000} + \frac{v_3}{40,000} - 30 \frac{v_1}{20,000} = 0$$

In standard form:


$$v_1 \left(\frac{1}{2000} + \frac{1}{20,000} + \frac{1}{5000} \right) + v_2 \left(-\frac{1}{5000} \right) + v_3(0) = \frac{40}{2000}$$

$$v_1 \left(-\frac{1}{5000} + \frac{30}{20,000} \right) + v_2 \left(\frac{1}{5000} + \frac{1}{50,000} + \frac{1}{10,000} \right) + v_3 \left(-\frac{1}{10,000} \right) = 0$$

$$v_1 \left(-\frac{30}{20,000} \right) + v_2 \left(-\frac{1}{10,000} \right) + v_3 \left(\frac{1}{10,000} + \frac{1}{40,000} \right) = 0$$

Solving, $v_1 = 24 \text{ V}$; $v_2 = -10 \text{ V}$; $v_3 = 280 \text{ V}$

$V_{Th} = v_3 = 280 \text{ V}$

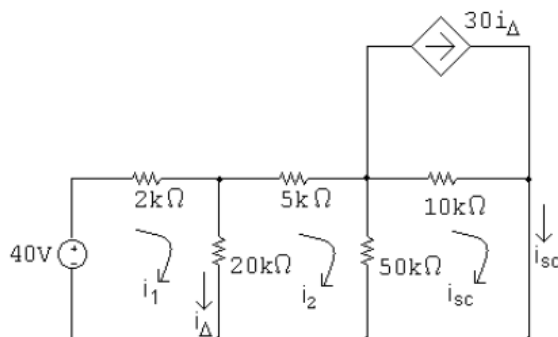

The mesh current equations are:

$$-40 + 2000i_1 + 20,000(i_1 - i_2) = 0$$

$$5000i_2 + 50,000(i_2 - i_{sc}) + 20,000(i_2 - i_1) = 0$$

$$50,000(i_{sc} - i_2) + 10,000(i_{sc} - 30i_{\Delta}) = 0$$

The constraint equation is:

$$i_{\Delta} = i_1 - i_2$$

Put these equations in standard form:

$$i_1(22,000) + i_2(-20,000) + i_{sc}(0) + i_{\Delta}(0) = 40$$


$$i_1(-20,000) + i_2(75,000) + i_{sc}(-50,000) + i_{\Delta}(0) = 0$$

$$i_1(0) + i_2(-50,000) + i_{sc}(60,000) + i_{\Delta}(-300,000) = 0$$

$$i_1(-1) + i_2(1) + i_{sc}(0) + i_{\Delta}(1) = 0$$

Solving, $i_1 = 13.6 \text{ mA}$; $i_2 = 12.96 \text{ mA}$; $i_{sc} = 14 \text{ mA}$; $i_{\Delta} = 640 \mu\text{A}$
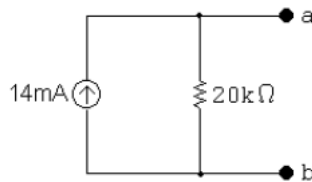
$$R_{Th} = \frac{280}{0.014} = 20 \text{ k}\Omega$$



Finding Rth using a test source: apply 1V source at V3 or Vth. Find io

1) $V1/2 + V1/20 + (V1-V2)/5 = 0$

2) $(V2-V1)/5 + V2/50 + (V2-1)/10 + 30 id = 0$

$id = V1/20$ so swap $1.5V1$ for $30id$ above

3) $io = 1/40 + (1-V2)/10 - 30id = 1/40 + (1-V2)/10 - 1.5V1$

Rearranging

1) $15V1 - 4V2 = 0$

2) $-10V1 + 16V2 + 75V1 = 5, 65V1 + 16V2 = 5$


(freemat) $V1 = .04, V2 = .15$, therefore $io = .025 + (.85)/10 - .06 = 0.05 \text{ mA}$,

so $Rth = Vo/io = 1/.05 = 20 \text{ k Ohms}$

2) The switch has been closed a long time before opening at $t=0$. Find

a. $i_o(t)$

b. $v_o(t)$

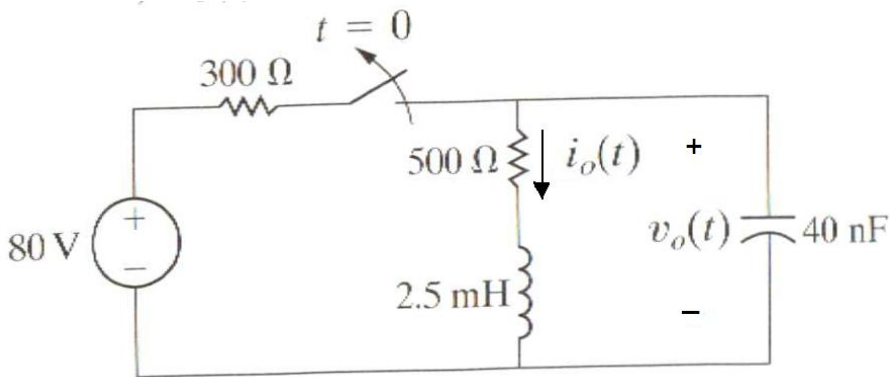

P 8.47 [a] $t < 0$:

$$i_o = \frac{80}{800} = 100 \text{ mA}; \quad v_o = 500i_o = (500)(0.01) = 50 \text{ V}$$

$t > 0$:

$$\alpha = \frac{R}{2L} = \frac{500}{2(2.5 \times 10^{-3})} = 10^5 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(2.5 \times 10^{-3})(40 \times 10^{-9})} = 100 \times 10^8$$

$$\alpha^2 = \omega_o^2 \quad \therefore \text{critically damped}$$

$$\therefore i_o(t) = D_1 t e^{-10^5 t} + D_2 e^{-10^5 t}$$

$$i_o(0) = D_2 = 100 \text{ mA}$$

$$\frac{di_o}{dt}(0) = -\alpha D_2 + D_1 = 0$$

$$\therefore D_1 = 10^5 (100 \times 10^{-3}) = 10,000$$

$$i_o(t) = 10,000 t e^{-10^5 t} + 0.1 e^{-10^5 t} \text{ A}, \quad t \geq 0^+$$

[b] $v_o(t) = D_3 t e^{-10^5 t} + D_4 e^{-10^5 t}$

$$v_o(0) = D_4 = 50$$

$$C \frac{dv_o}{dt}(0) = -0.1$$

OR,

$$V_o(t) = 500 I_o(t) + 0.0025 \frac{dI_o(t)}{dt}$$

$$\frac{dI_o(t)}{dt} = 10000 t (-10^5) \exp(-10^5 t) + 10000 \exp(-10^5 t) + 0.1 (-10^5) \exp(-10^5 t)$$


$$= -10^9 t \exp(-10^5 t) + \quad \text{these two terms cancel out!}$$

$$\text{so } V_o(t) = 500 (10000 t) \exp(-10^5 t) + 50 \exp(-10^5 t) - 25 \times 10^5 t \exp(-10^5 t)$$

$$500(10\,000 e^{-100\,000t} t + 0.1 e^{-100\,000t}) - 2.5 \times 10^6 e^{-100\,000t} t$$

$$= 250\,000t \exp(-100\,000t) + 50 \exp(-100\,000t)$$

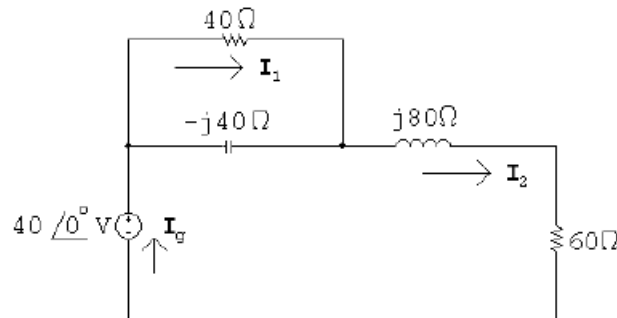P 10.18 [a] $\frac{1}{j\omega C} = -j40\Omega$; $j\omega L = j80\Omega$



$$Z_{\text{eq}} = 40 \parallel -j40 + j80 + 60 = 80 + j60\Omega$$

$$\mathbf{I}_g = \frac{40\angle 0^\circ}{80 + j60} = 0.32 - j0.24 \text{ A}$$

$$S_g = -\frac{1}{2} \mathbf{V}_g \mathbf{I}_g^* = -\frac{1}{2} 40(0.32 + j0.24) = -6.4 - j4.8 \text{ VA}$$

$$P = 6.4 \text{ W (del)}; \quad Q = 4.8 \text{ VAR (del)}$$

$$|S| = |S_g| = 8 \text{ VA}$$

[b] $\mathbf{I}_1 = \frac{-j40}{40 - j40} \mathbf{I}_g = 0.04 - j0.28 \text{ A}$

$$P_{40\Omega} = \frac{1}{2} |\mathbf{I}_1|^2 (40) = 1.6 \text{ W}$$

$$P_{60\Omega} = \frac{1}{2} |\mathbf{I}_g|^2 (60) = 4.8 \text{ W}$$

$$\sum P_{\text{diss}} = 1.6 + 4.8 = 6.4 \text{ W} = \sum P_{\text{dev}}$$

[c] $\mathbf{I}_{-j40\Omega} = \mathbf{I}_g - \mathbf{I}_1 = 0.28 + j0.04 \text{ A}$

$$Q_{-j40\Omega} = \frac{1}{2} |\mathbf{I}_{-j40\Omega}|^2 (-40) = -1.6 \text{ VAR (del)}$$

$$Q_{j80\Omega} = \frac{1}{2} |\mathbf{I}_g|^2 (80) = 6.4 \text{ VAR (abs)}$$

$$\sum Q_{\text{abs}} = 6.4 - 1.6 = 4.8 \text{ VAR} = \sum Q_{\text{dev}}$$

$$\text{P 9.69 } \mathbf{V}_g = 4/0^\circ \text{ V}; \quad \frac{1}{j\omega C} = -j20 \text{ k}\Omega$$

Let \mathbf{V}_a = voltage across the capacitor, positive at upper terminal

Then:

$$\frac{\mathbf{V}_a - 4/0^\circ}{20,000} + \frac{\mathbf{V}_a}{-j20,000} + \frac{\mathbf{V}_a}{20,000} = 0; \quad \therefore \mathbf{V}_a = (1.6 - j0.8) \text{ V}$$

$$\frac{0 - \mathbf{V}_a}{20,000} + \frac{0 - \mathbf{V}_o}{10,000} = 0; \quad \mathbf{V}_o = -\frac{\mathbf{V}_a}{2}$$


$$\therefore \mathbf{V}_o = -0.8 + j0.4 = 0.89/153.43^\circ \text{ V}$$

$$v_o = 0.89 \cos(200t + 153.43^\circ) \text{ V}$$


2) The switch has been closed a long time before opening at $t=0$. Find

a. $i_o(t)$

b. $v_o(t)$

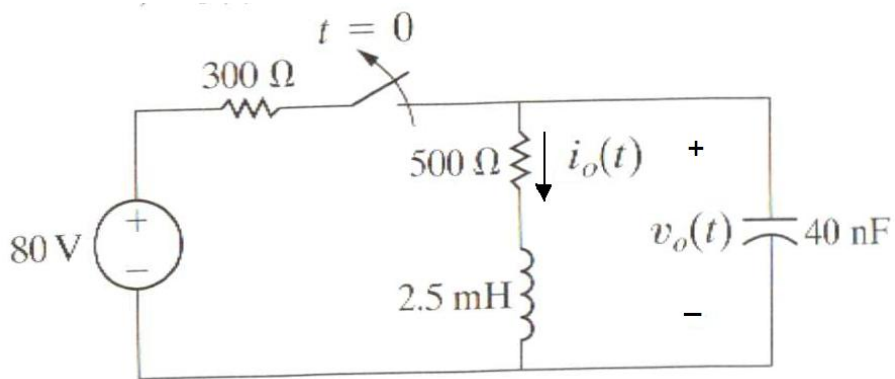

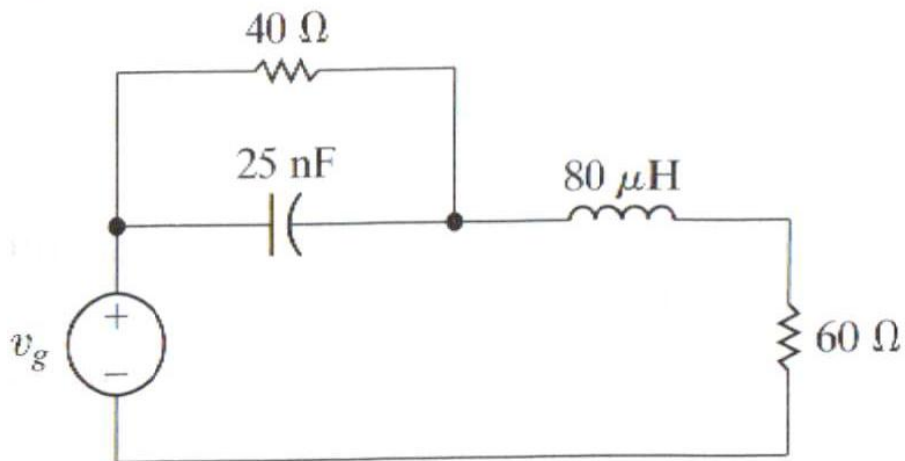- 3) Find the average power, the reactive power and the apparent power supplied by the voltage source in the circuit if $v_g = 40\cos(1000000t)$ Volts (this is magnitude, not rms).



4) The sinusoidal voltage source $v_g = 4\cos(200t)$. If the op-amp is ideal, find the output voltage $v_o(t)$

