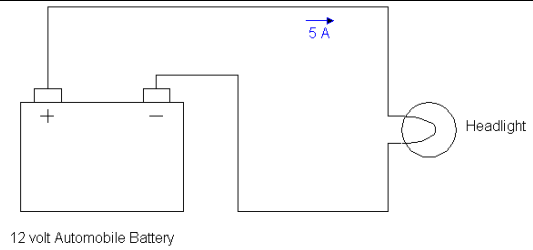


- 1) How much energy is delivered to the headlight if it is left on overnight for 8 hours? Express your answer in kW-hours.




$$P = 5 \times 12 = 60 \text{ W}$$

$$E = P \times t = 60 \times 8 = 480 \text{ W-hours} = .48 \text{ kW-h}$$

- 2) Find  $I$  in the circuit on the right:

$$I = -75/10 = -7.5 \text{ A}$$

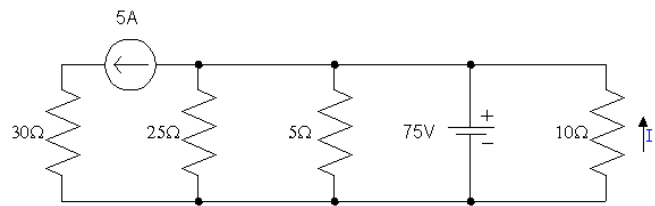

- 3) How much total current is provided by the 75 V source for the circuit shown in Prob 2?

$$\text{KCL: } I = 5 \text{ A} + 3 \text{ A} + 15 \text{ A} + 7.5 \text{ A} = 30.5 \text{ A}$$


- 4) What is the Voltage change across the 5A current source for the circuit in Prob 2? Reference + to the head of the current arrow, and - to the tail.

$$\text{KVL: } -150 + V_{5\text{A}} + 75 = 0, \text{ therefore } V_{5\text{A}} = 75 \text{ Volts}$$

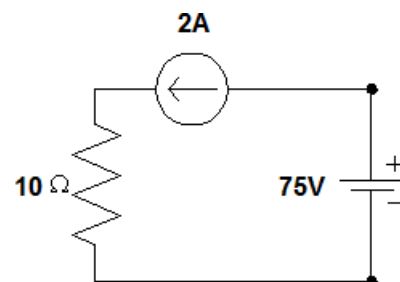- 5) For the circuit on the right, what is the power associated with the current source and the voltage source and indicate whether each is absorbing or releasing power.

$$P_{2\text{A}} = 2 \times 55 = 110 \text{ W (absorbing)}$$

$$P_{40\text{V}} = -2 \times 75 = -150 \text{ W (releasing)}$$




- 6) What is the power associated with the resistor for the circuit in Prob 5?

$$P_{R10} = 2^2 \times 10 = 40 \text{ Watts } P_{R10} = 2^2 \times 10 = 40 \text{ Watts}$$

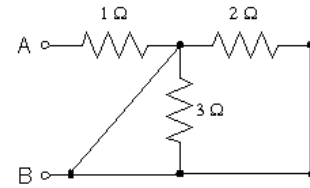
7) What is the equivalent resistance from A to B?

$$R_{eq} = 1 + 0 \parallel 2 \parallel 3 = 1 \text{ Ohm}$$



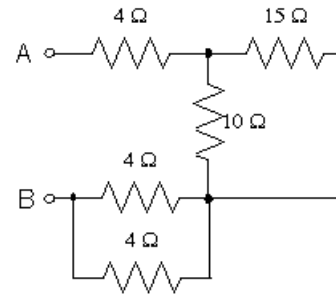
8) What is the equivalent resistance from A to B?

$$\begin{aligned} R_{eq} &= 4 + 10 \parallel 15 + 4 \parallel 4 \\ &= 4 + 150/25 + 2 \\ &= 4 + 6 + 2 \\ &= 12 \text{ Ohm} \end{aligned}$$



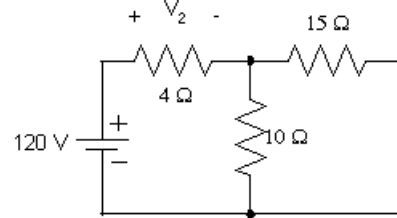
9) Use the Voltage Divider Formula to find  $V_2$

$$V_2 = 120 * 4 / (15 \parallel 10 + 4) = 120 * 4 / 10 = 48V$$



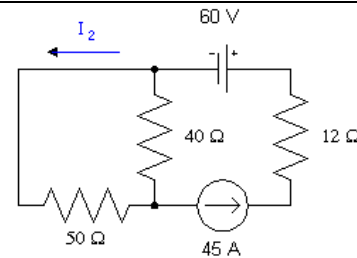
10) Use the Current Divider Formula to find  $I_2$

$$I_2 = 45 * 40 / (50 + 40) = 45 * 40 / 90 = 20A$$



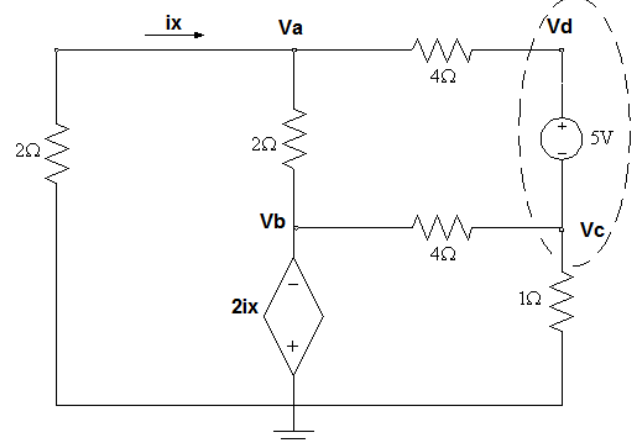11) Write the Node Voltage Equation for the  $V_a$  node in terms of  $V_a$ ,  $V_d$ , and  $V_b$  (ignore the supernode and  $i_x$  for now):

$$\frac{V_a}{2} + \frac{V_a - V_b}{2} + \frac{V_a - V_d}{4} = 0$$








12) Express  $V_d$  in terms of  $V_c$  in the circuit for prob 11, in other words,


$$V_d = V_c + \underline{\quad 5 \quad}$$

13) Write the Node Voltage Equation for the Supernode shown in the above circuit:

$$\frac{V_d - V_a}{4} + \frac{V_c - V_b}{4} + \frac{V_c}{1} = 0$$
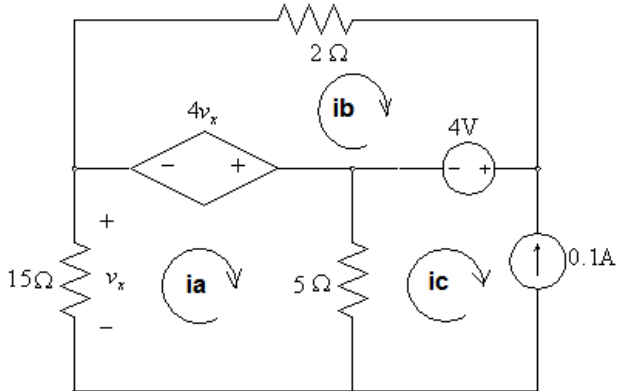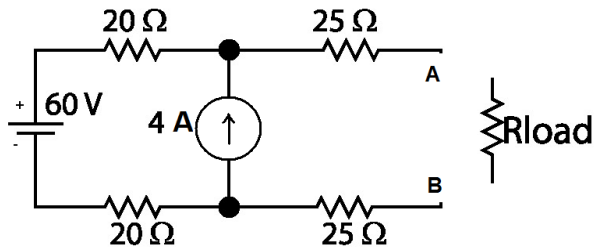
<p>14) Express <math>i_x</math> in terms of <math>V_a</math> for the circuit in #11  <math>i_x = -V_a / 2</math></p>	<p>15) Substitute your answer for 14) for <math>i_x</math> in the dependent source to arrive at an expression for <math>V_b</math> in terms of <math>V_a</math>:</p> $V_b = -2i_x = -2 * -V_a/2 = V_a$
<p>16) For the Mesh Current circuit on the right, express <math>V_s</math> in terms of <math>i_a</math>:</p> $V_s = -15 i_a$	
<p>17) Express the mesh current for Mesh A without using <math>V_s</math> (substitute answer for #16):</p> $15 i_a - 4*(-15i_a) + 5( i_a - i_c) = 0$ $80 i_a - 5 i_c = 0$	<p>18) Express the mesh current for Mesh B without using <math>V_s</math> (substitute your answer for #16)</p> $4*(-15i_a) + 2i_b + 4 = 0$ $60 i_a + 2 i_b = -4$
<p>19) By inspection, what is the current <math>i_c</math>?</p> $i_c = -.1 \text{ A}$	
<p>20) What is the Thevenin Voltage of the Circuit shown:</p> <p>(no current flows thru 25 Ohm resistors)</p> $V_{th} = V_{4A} = 60 + 4*(20+20) = 220V$	
<p>21) What is the Thevenin Resistance of the circuit from Problem 20?</p> <p>(4A source is like open cct, 60V src like short)</p> $R_{th} = 20 + 25 + 20 + 25 = 90 \text{ Ohms}$	<p>22) What value of <math>R_{load}</math> will result in maximum power transferred to the load resistor?</p> $R_{load} = R_{th} = 90 \text{ Ohms}$
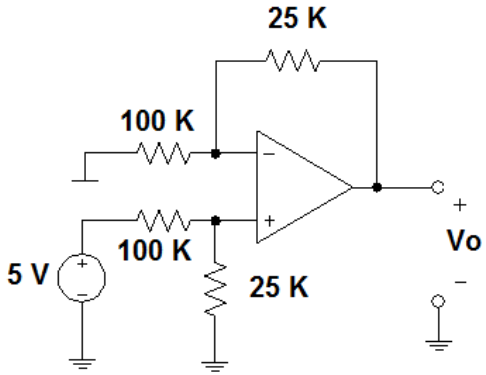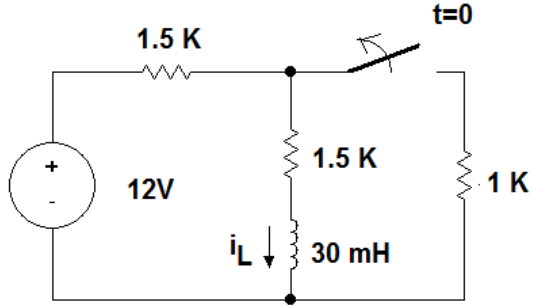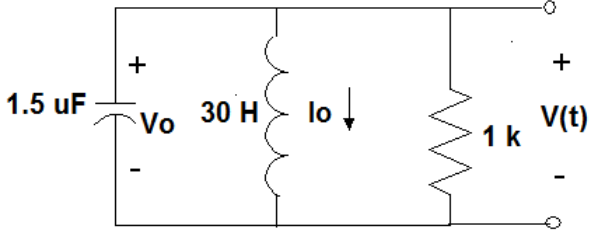
<p>23) What is the value of <math>V_+</math> at the Op-Amp input?</p> $V_+ = 5V \cdot \frac{25}{100 + 25} = 1V$	
<p>24) Assuming the Op-amp is in its linear range, what is the value of <math>V_-</math> ?</p> $V_- = 1V$	<p>25) Still assuming linearity, what is the output voltage <math>V_o</math>?</p> $V_- / 100 + (V_- - V_o) / 25 = 0$ $V_- + 4(V_- - V_o) = 0$ $V_o = 5V_- / 4 = 1.25V$
<p>26) For the circuit at right, prior to <math>t=0</math> the switch has been closed a long time. What is the resistance seen by the 12V supply before the switch opens?</p> <p>Prior to <math>t=0</math>, <math>R_{eq} = 1.5 + 1.5 \parallel 1 = 1.5 + 1.5/2.5</math></p> $R_{eq} = 2.1 \text{ K-Ohm}$	
<p>27) What is the current through the inductor before the switch opens?</p> $i_L(0^-) = (12 / 2.1) \cdot \frac{1}{1 + 1.5} = 2.287 \text{ mA}$	<p>28) What is the final value of current through the inductor after the switch has been open a long time?</p> $i_L(f) = 12V / 3k = 4 \text{ mA}$
<p>29) What is the time constant for the R-L circuit after the switch opens?</p> $\tau = L / R = 30 \text{ mH} / 3 \text{ kOhm} = 10 \text{ microsec}$	<p>30) Write the equation for inductor current as a function of time</p> $i(t) = i(f) + (i(0) - i(f)) e^{-t/\tau} = 4 + (2.287 - 4) e^{-t/\tau} = 4 - 1.73 e^{-10^5 t}$
<p>31) For the parallel RLC circuit shown, find <math>\alpha</math>, <math>\omega_o</math>, <math>s_1</math>, and <math>s_2</math></p> $\alpha = 1/(2RC) = 1/(2 \cdot 1000 \cdot 1.5 \times 10^{-6}) = 333$ $\omega_o = \sqrt{1/LC} = \sqrt{1/(2 \cdot 1.5 \times 10^{-6})} = 149$ $s_1 = -333 + \sqrt{333^2 - 149^2} = -35$ $s_2 = -333 - \sqrt{333^2 - 149^2} = -631$	
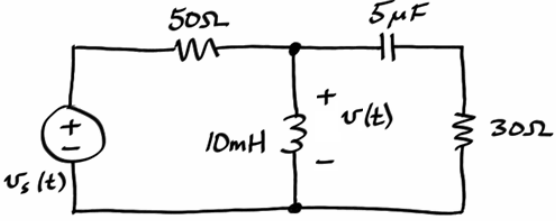
<p>32) Is the circuit over, under or critically damped? overdamped</p>	<p>33) If <math>V_0 = 10V</math> and <math>I_0 = 2 \text{ mA}</math>, calculate <math>v</math>, and <math>dv/dt</math> at <math>t=0^+</math></p> <p><math>v(0^+) = 10</math>  <math>dv/dt \text{ at } t=0^+ = i_c/C = (-2 - (10V/1K)) / C</math>  <math>= -12\text{mA}/1.5\mu\text{F} = -8000 \text{ V/s}</math></p>
<p>34) Suppose <math>v(t) = 220\cos(50t - 67^\circ)</math> volts</p> <p>a) What is the radian frequency, <math>\omega</math> in Rad/sec? <math>\omega = 50 \text{ R/s}</math></p> <p>b) What is the frequency in Hz? <math>f = \omega/2\pi = 50/6.28 = 7.96 \text{ Hz}</math></p> <p>c) What is the period, <math>T</math>? <math>T = 1/f = .1256 \text{ sec}</math></p> <p>d) What is the rms value of <math>v(t)</math>? <math>V_{\text{rms}} = 220/\sqrt{2} = 155.6</math></p>	<p>35) Complex Math</p> <p>a) Convert <math>50 - 45j</math> to polar form  <math>\text{Mag} = \sqrt{50^2 + 45^2} = 67.2</math>  <math>\text{Phi} = \text{atan}(-45/50) = -41.9 \text{ degrees}</math></p> <p>b) Convert <math>30/\underline{25}</math> to rectangular form  <math>\text{Ans} = 27.1 + 12.6j</math></p> <p>c) Find <math>(25/\underline{-60}) / (40 + 10j)</math> in phasor form:  <math>\text{Ans} = .606 \underline{-74}</math></p>
<p>36) For the AC circuit to the right, find <math>Z_c</math> and <math>Z_L</math> <math>\omega = 2\pi \cdot 1000 = 6283</math></p> <p><math>Z_c = -j/(\omega C) = -31.8j</math></p> <p><math>Z_L = j\omega L = 62.8j</math></p>	 <p><math>v_s(t) = 70 \cos(2\pi \cdot 1000t + 30^\circ) \text{ V}</math></p>
<p>37) Find the equivalent impedance of the parallel branches for the circuit in problem 36:</p> <p><math>Z_p = Z_L    (30 + Z_c) = 62.8j \cdot (30 - 31.8j) / (30 + 31j)</math>  <math>= (1997 + 1884j) / (30 + 31j) = 63.6/\underline{-2.89}</math></p>	<p>38) Find an expression for the phasor voltage <math>V</math> across the 10 mH inductor:</p> <p><math>V = V_s Z_p / (50 + Z_p) =</math>  <math>= 70/\underline{30} \cdot 63.6/\underline{-2.89} / 113/\underline{-1.6} = 39.3/\underline{28.7}</math></p>
<p>39) Convert your answer to 38) into the time domain:</p> <p><math>v(t) = 39.3 \cos(2 \pi 1000t + 28.7)</math></p>	<p>40) If the current into a load is <math>I = 40/\underline{35}</math> and the Voltage is <math>V = 10/\underline{-20}</math>, Determine the:</p> <p>a) Average power <math>P</math>: <math>= \frac{1}{2} \cdot 40 \cdot 10 \cdot \cos(-20 - 35)</math>  <math>= 200 \cos(-55) = 115 \text{ W}</math></p> <p>b) Reactive power <math>Q</math>: <math>= 200 \sin(-55) = -164 \text{ var}</math></p>

c) Complex Power S: = 115 -164j VA

41) A 3 phase Y-source has phase voltages:  
 $V_{an} = 120\angle 50^\circ$ ,  $V_{bn} = 120\angle 170^\circ$ ,  $V_{cn} = 120\angle -40^\circ$   
 Find the line voltages  $V_{ab}$ ,  $V_{bc}$ , and  $V_{ca}$   
 $V_{ab} = 207\angle 20^\circ$   
 $V_{bc} = 207\angle 140^\circ$   
 $V_{ca} = 207\angle -70^\circ$

42) Write the mesh equation for mesh 2 in the transformer circuit on the right:

$$j6 I_2 + j3I_1 - j4I_2 + 10I_2 = 0$$

or,

$$(j3)I_1 + (10 + j2) I_2 = 0$$

