
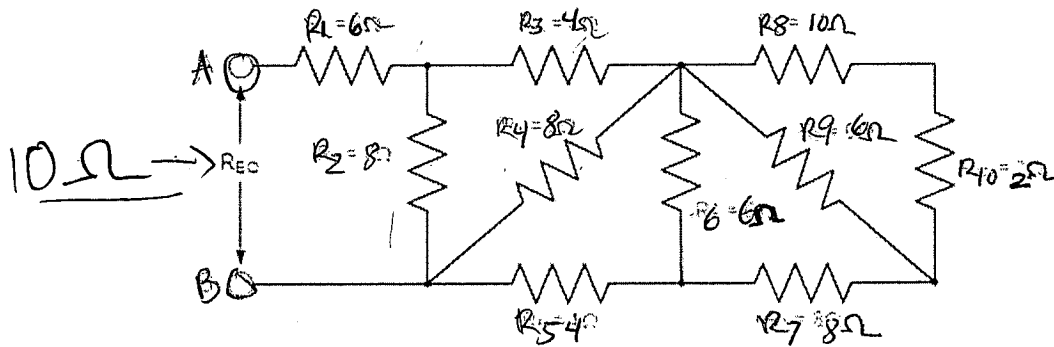


Closed Book. One double sided sheet of notes and a calculator are allowed.





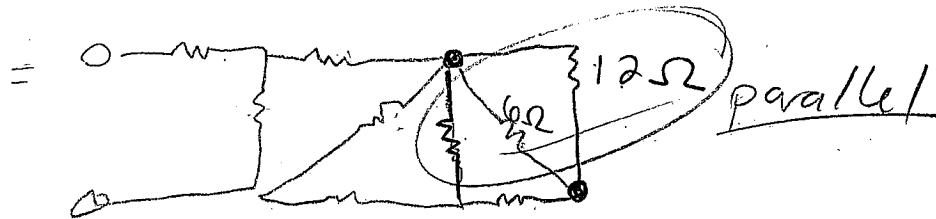
1) Find the effective resistance Req in the network below (it's easier than it may look at first).



$R_8, R_{10} \rightarrow$  series  
 $10 + 2\Omega = 12\Omega$




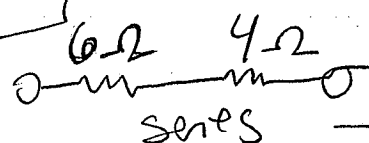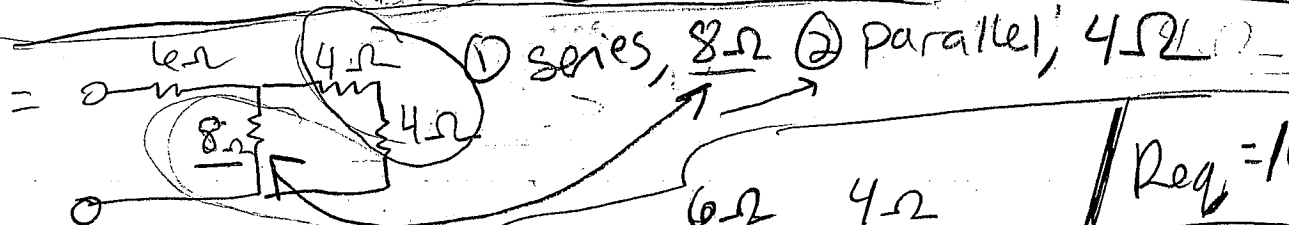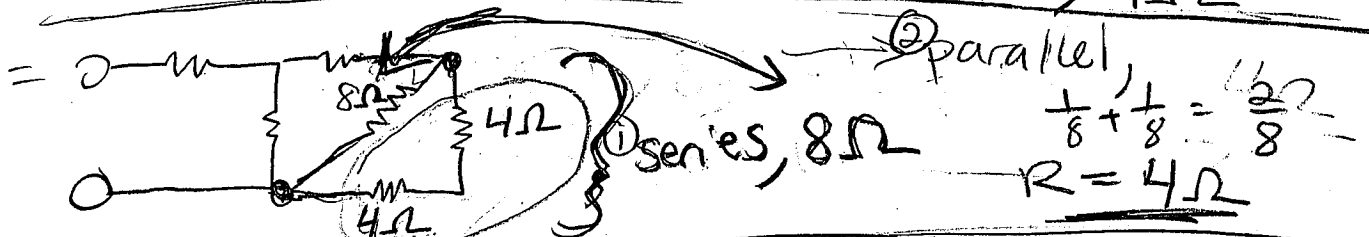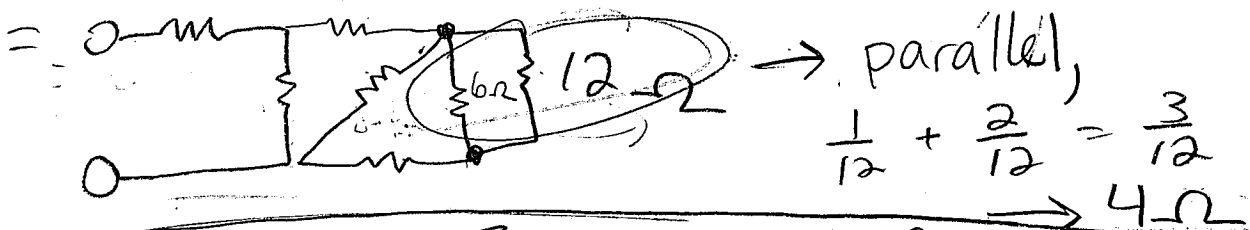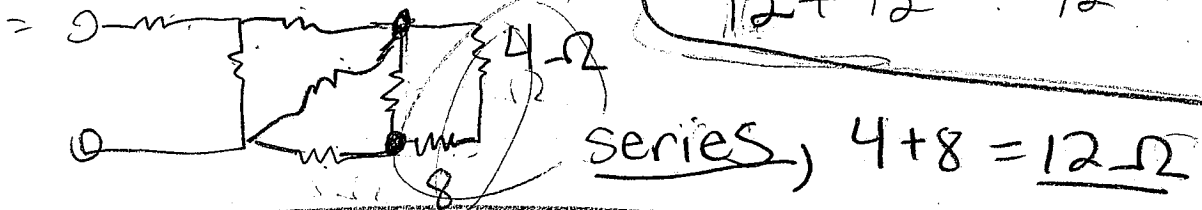$\frac{2}{12} + \frac{1}{12} = \frac{3}{12} \rightarrow 4\Omega$



**$Req = 10\Omega$**

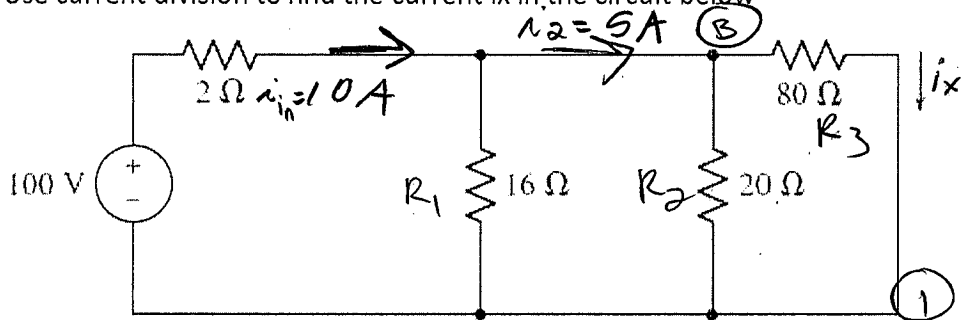2) Use current division to find the current  $i_x$  in the circuit below



$R_2, R_3$   
parallel

$$\frac{1}{80} + \frac{4}{80} = \frac{5}{80}$$

$$\frac{80}{5} = 16\Omega$$



②  $\rightarrow 10\Omega = R_{eq}$

$$V = RI \rightarrow I = \frac{V}{R} = \frac{100}{10}$$

$$I_{in} = 10A$$


③ Current - divider

$$\textcircled{A} \quad i_2 = i_{in} \left[ \frac{R_1}{R_1 + R_2} \right] = 10A \left[ \frac{16\Omega}{32\Omega} \right] = 5A$$


$$\textcircled{B} \quad i_x = i_2 \left[ \frac{R_2}{R_2 + R_3} \right] = 5A \left[ \frac{20\Omega}{100\Omega} \right] = 1A$$

$$i_x = 1.0A$$

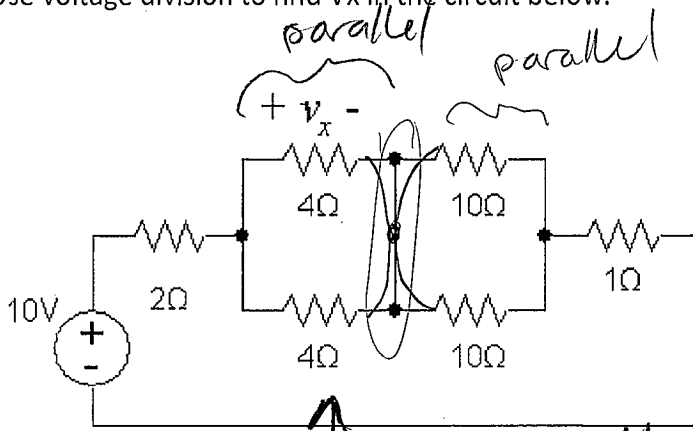3) Use voltage division to find  $V_x$  in the circuit below.



same voltage, parallel

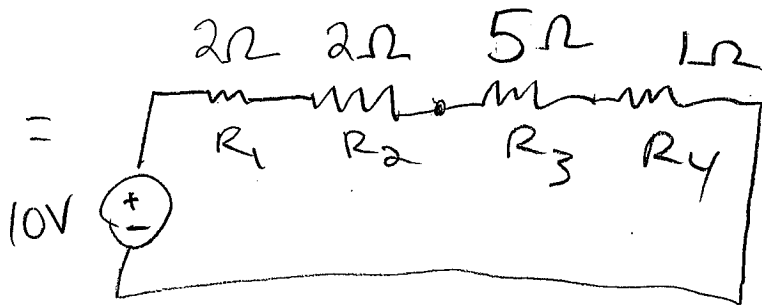

$$V_x = V_{in} \left[ \frac{R_2}{R_1 + R_2 + R_3 + R_4} \right]$$

$$= 10V \left[ \frac{2}{2+2+5+1} \right] = \frac{10 \cdot 2}{10}$$


$$V_x = 2.0V$$

4) Find

a) the current  $i_1 = 1.25 \text{ mA}$

b) the power associated with the dependent source. Is it absorbing or delivering power?

$P = -6.25 \text{ mW}$   
delivering

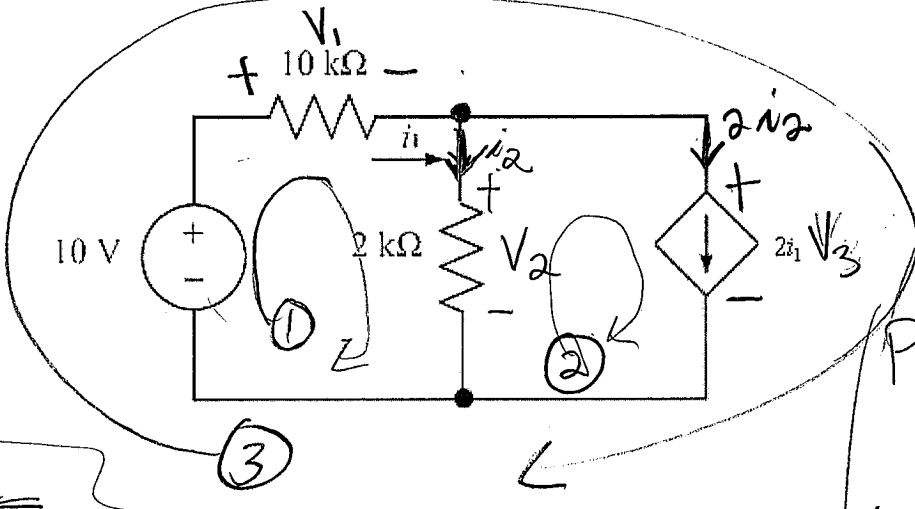

KCL

$$i_1 = i_2 + 2i_1 \rightarrow i_2 = -i_1$$

$$P = +IV \text{ (Passive)}$$

$$= (2)i_1(V_3)$$

$$= (2)(1.25 \text{ mA})(-2.5 \text{ V})$$

$P = -6.25 \text{ mW}$   
delivering

KVL

$$1) -10 \text{ V} + V_1 + V_2 = 0$$

$$2) -V_2 + V_3 = 0$$

$$3) -10 \text{ V} + V_1 + V_3 = 0$$

OL

$$V_1 = R_1 I_1 = (10 \text{ k}\Omega) i_1$$

$$V_2 = R_2 I_2 = (2 \text{ k}\Omega) i_2$$

$$= (2 \text{ k}\Omega) (-i_1)$$

$$1) -10 \text{ V} + 10,000 i_1 - 2000 i_1 = 0 \rightarrow i_1 = \frac{10 \text{ V}}{8000 \Omega} = 1.25 \text{ mA}$$

$$2) 2000 i_1 + V_3 = 0 \rightarrow V_3 = -2000 i_1 = -2 \text{ k}\Omega (1.25 \text{ mA})$$

$$3) -10 \text{ V} + 10,000 i_1 + V_3 = 0 \rightarrow V_3 = -2.5 \text{ V}$$

$i_1 = 1.25 \text{ mA}$  ✓

$V_3 = -2.5 \text{ V}$  ✓