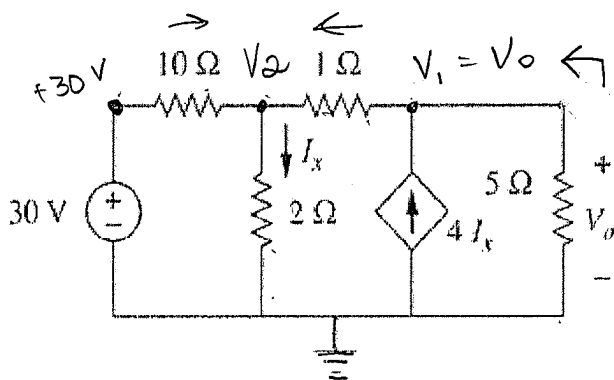


Closed Book, one double sided sheet of notes allowed, and a calculator.

Time limit: 1 hour and 20 minutes.

- 1) Write the Nodal Equations needed to solve for V_o in the following circuit. Reduce your equations to matrix form suitable for entering into FreeMat. You do not have to solve the equations.



$$\begin{cases} V_1 = V_o \\ I_x = \frac{V_2 - 0}{2} \end{cases}$$

$$V_2) \quad \frac{30 - V_2}{10} + \frac{V_1 - V_2}{1} - I_x = 0$$

$$V_1) \quad -\frac{(V_1 - V_2)}{1} + \frac{0 - V_o}{5} + 4I_x = 0$$

$$\rightarrow V_2) \quad 30 - V_2 + 10V_o - 10V_2 - 5V_2 = 0$$

$$\rightarrow V_1) \quad -5V_o + 5V_2 - V_o + 10V_2 = 0$$

equations

$$V_2) \quad -10V_2 + 10V_o = -30 \rightarrow -8V_2 + 5V_o = -15$$


$$V_1) \quad 15V_2 - 6V_o = 0 \rightarrow 5V_2 - 2V_o = 0$$

$$\text{Matrix } A = \begin{vmatrix} -8 & 5 \\ 5 & -2 \end{vmatrix}$$


$$b = \begin{vmatrix} -15 \\ 0 \end{vmatrix}$$

$$A \setminus b = \begin{bmatrix} V_2 \\ V_o \end{bmatrix}$$

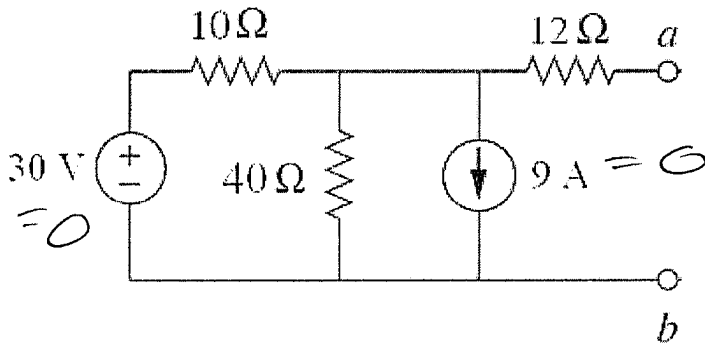
- 2) Find the Thévenin or "lookback" resistance at a-b for the following circuit. You do not need to find the Thévenin voltage.



turn off
independent
sources

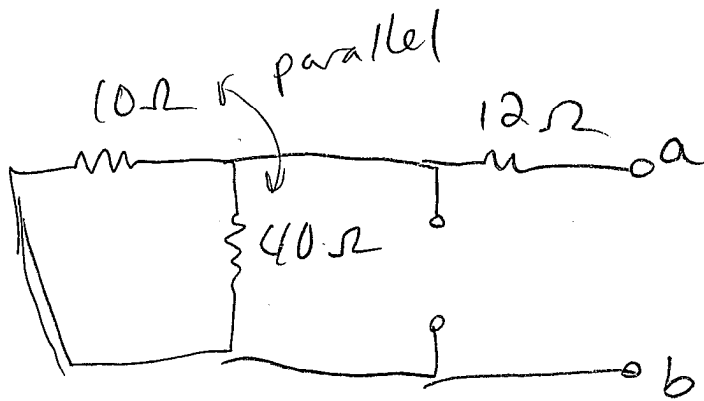

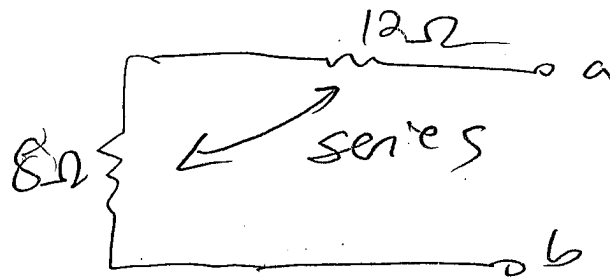
$$\frac{1}{4} \cdot \frac{1}{10} + \frac{1}{40} = \frac{1}{R_{eq}} \Rightarrow \frac{5}{40} = \frac{1}{R_{eq}} \Rightarrow R_{eq} = 8\Omega$$





$$R_{th} = 20\Omega$$

lookback resistance

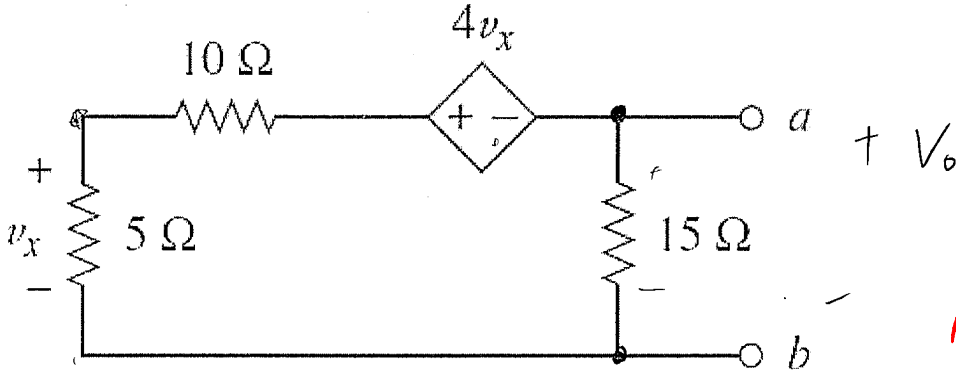3) Find the Thévenin equivalent circuit with respect to terminals a and b .



ASC for test SRC

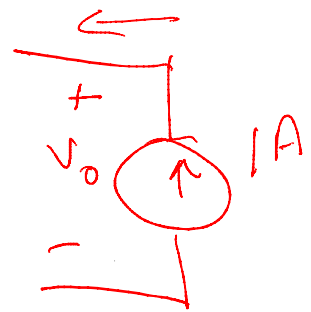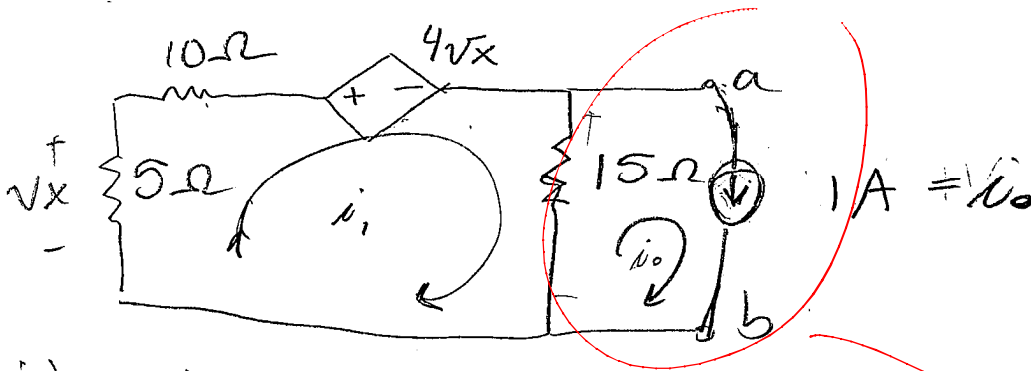

$$i_1) 5i_1 + 10i_1 + 4v_x + 15(i_1 - i_o) = 0$$

$$v_x = -5i_1, i_o = 1$$

$$\Rightarrow 15i_1 - 20i_1 + 15i_1 - 15 = 0$$

$$10i_1 = 15$$


$$i_1 = \frac{15}{10} = \frac{3}{2}$$

$$V_o = 15 \left(\frac{3}{2} - \frac{2}{2} \right) = 15 \left(\frac{1}{2} \right)$$


$$R_{th} = \frac{V_o}{-i_o} = \frac{15/2}{-1} = -15/2 \Omega$$

$$V_{th} = 0$$

No ind. sources

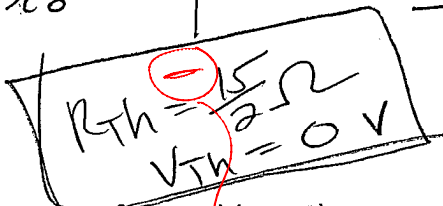


(turn over for problem 4)

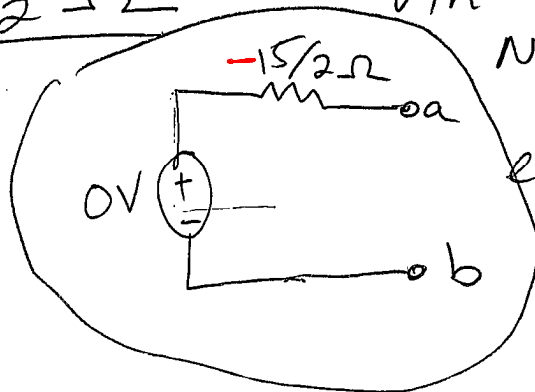

equivalent

score -3

4) Find V_o for the ideal op-amp.

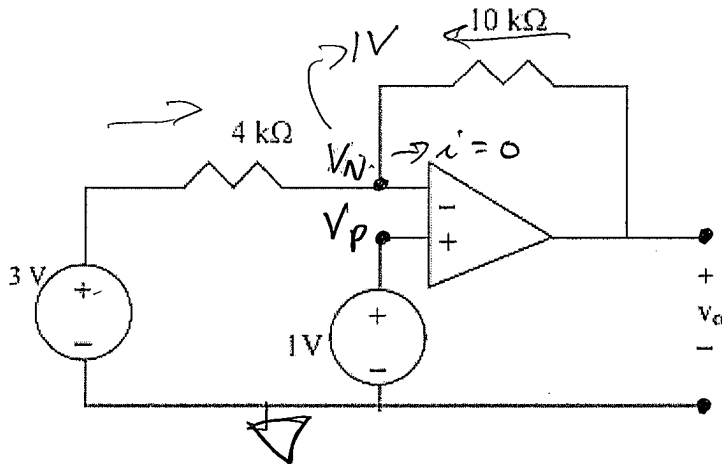

$$V_N = V_P = 1V$$

KCL @ V_N

$$\frac{3 - V_N}{4} + \frac{V_o - V_N}{10} = 0 \Rightarrow V_N = 1V$$

$$\frac{1 - 1}{4} + \frac{V_o - 1}{10} = 0$$

$$5 + V_o - 1 = 0$$

$$V_o = -4V$$