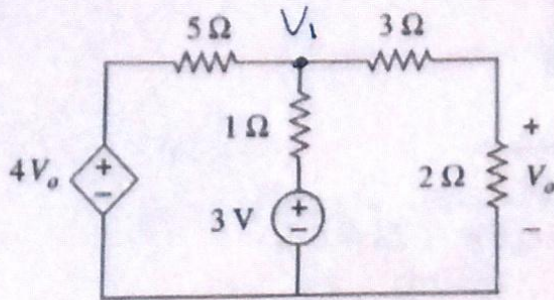


Closed Book, double sided sheet of notes allowed

- 1) Write the Nodal Equations needed to solve for V_o in the following circuit. Reduce your equations to matrix form suitable for entering into FreeMat. You do not have to solve the equations.



$$\textcircled{V_1} \left[\frac{V_1 - 4V_0}{5} + \frac{(V_1 - 3)}{1} + \frac{V_1 - V_0}{3} = 0 \right] \times 15$$

$$3V_1 - 12V_0 + 15V_1 + 5V_1 - 5V_0 = 45$$

$$\underline{-17V_0 + 23V_1 = 45}$$

$$\textcircled{V_0} \left[\frac{V_0 - V_1}{3} + \frac{V_0}{2} = 0 \right] \times 6$$


$$2V_0 - 2V_1 + 3V_0 = 0$$

$$\underline{5V_0 - 2V_1 = 0}$$


$$A = \begin{bmatrix} -17 & 23 \\ 5 & -2 \end{bmatrix}$$

$$B = \begin{bmatrix} 45 \\ 0 \end{bmatrix}$$

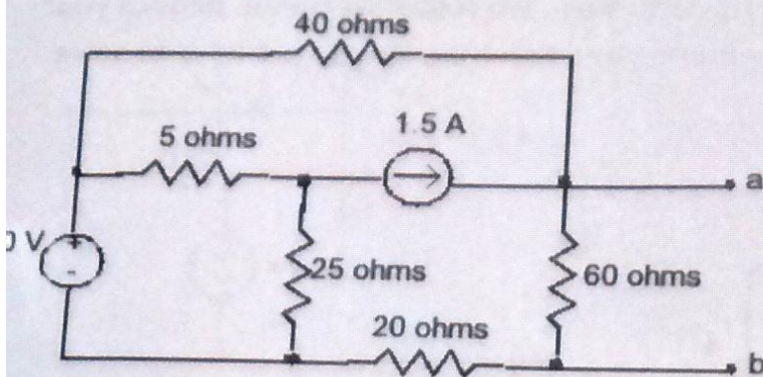2) Find the Thévenin or "lookback" resistance at a-b for the following circuit. You do not need to find the Thévenin voltage.



TURN OFF INDEPENDENT SOURCES

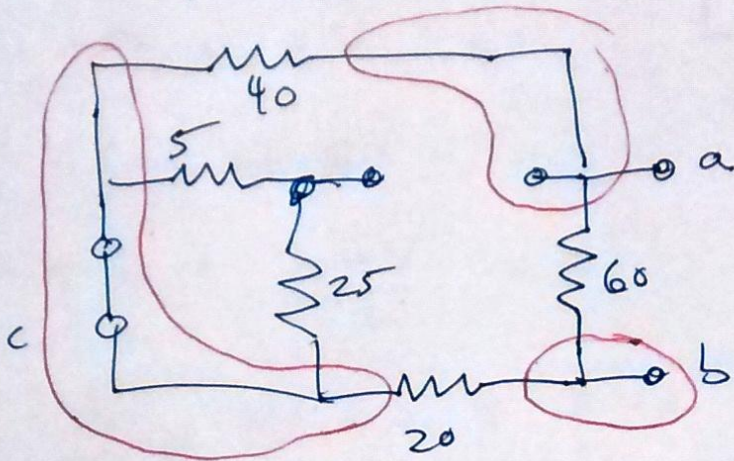


Find R_{ab}

5 + 25 are parallel to a short ckt
 so you can ignore

$$R_{ab} = (40 + 20) \parallel 60 = \underline{30 \Omega}$$

3) Find the Thévenin equivalent circuit with respect to terminals *a* and *b*.

① Find V_{th} with Mesh Analysis

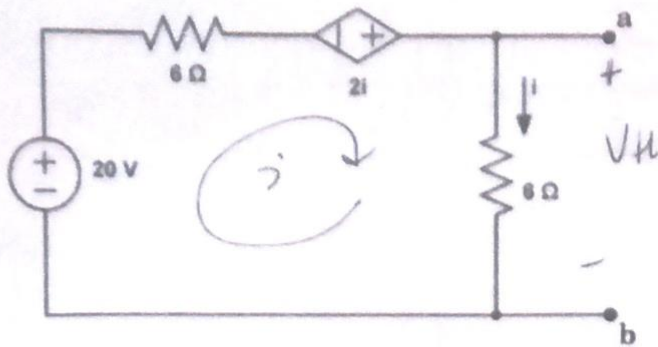

i is only mesh current


$$-20 + 6i - 2i + 6i = 0$$

$$10i = 20$$

$$i = 2A$$

$$\rightarrow V_{th} = 6i = 12V$$

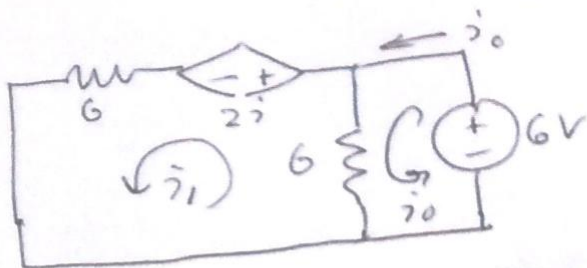② Find R_{th} - Turn off 20V src, connect 6V src
Find i_0 , $R_{th} = \frac{6}{i_0}$



$$\textcircled{1} 6(i_1 - i_0) + 2i + 6i_1 = 0$$

$$i = (i_0 - i_1)$$

$$-4i_0 + 10i_1 = 0$$

$$\textcircled{2} -6 + 6(i_0 - i_1) = 0$$

$$i_0 - i_1 = 1$$

$$\begin{bmatrix} -4i_0 + 10i_1 = 0 \\ 4i_0 - 4i_1 = 4 \end{bmatrix}$$

$$6i_1 = 4, i_1 = \frac{2}{3}, i_0 = \frac{5}{3}$$

$$R_{th} = \frac{6}{5/3} = \frac{18}{5} = 3.6\Omega$$

(turn over for problem 4)

Alternate: Find I_{NORTON}

$$R_{TH} = \frac{V_{TH}}{I_N}$$



Short at *a-b* $\rightarrow i = 0$
 $\rightarrow 2i = 0$


$\rightarrow I_N$ all the way around

$$-20 + 6I_N = 0$$

$$I_N = \frac{20}{6} = \frac{10}{3}$$

$$R_{TH} = \frac{12}{10/3} = 3.6\Omega$$

4) Find V_o for the ideal op-amp.

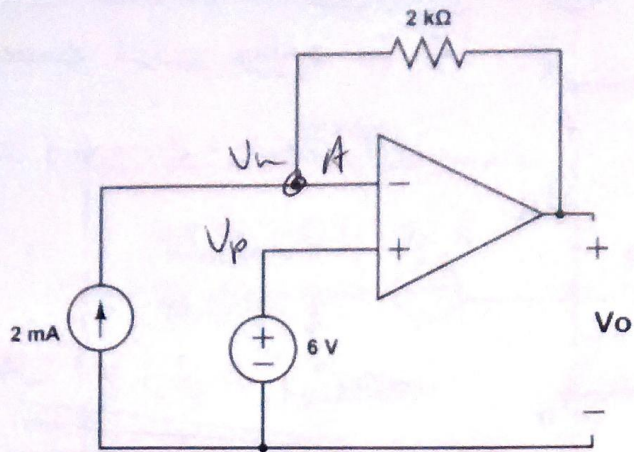

Negative Feedback

$$\rightarrow V_p = V_n = 6V$$

KCL at A:

$$+2 + \frac{V_o - V_n}{2} = 0$$

$$\frac{V_o}{2} = \frac{V_n}{2} - 2 = \frac{6}{2} - 2 = 2$$

$$\therefore V_o = 2 \cdot 2 = \underline{\underline{4V}}$$