

A11


1.

$$A = \begin{bmatrix} I_1 & I_2 \\ 27 + 16j & -(26 + 13j) \\ 13 - 14j & -(12 - 16j) \end{bmatrix} \quad b = \begin{bmatrix} k \\ 0 \\ 150 \end{bmatrix}$$

$A \setminus b \dots$ $I_1 = -26 - 52j$ (A)

$I_2 = -24 - 58j$ (A)

2. THEVENIN PHASOR

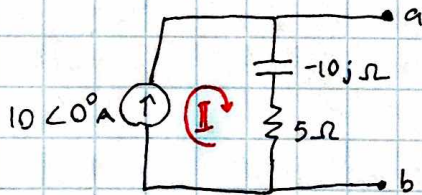


$$R_{TH} = 5 - 10j = 5\sqrt{5} \angle -63.43$$

$$I = 10 \angle 0 = 10$$

$$V_{ab} = I R_{TH} = 10 (5\sqrt{5} \angle -63.43) = 50\sqrt{5} \angle -63.435$$

$$V_{ab} = 111.803 \angle -63.435^\circ \text{ (V)}$$

2) NORTON PHASOR

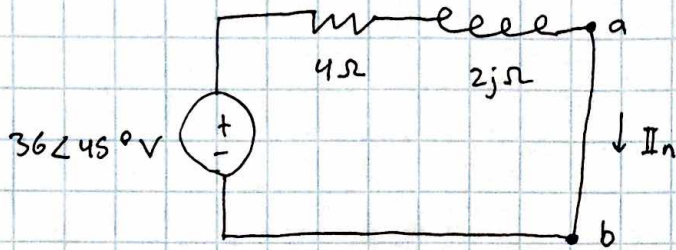


$$I_n = \frac{V}{R_T}$$

$$V = 36 \angle 45^\circ$$

$$R_T = 4 + 2j = 2\sqrt{5} \angle 26.565^\circ$$

$$I_n = 8.050 \angle 18.43^\circ \text{ (A)}$$

3)

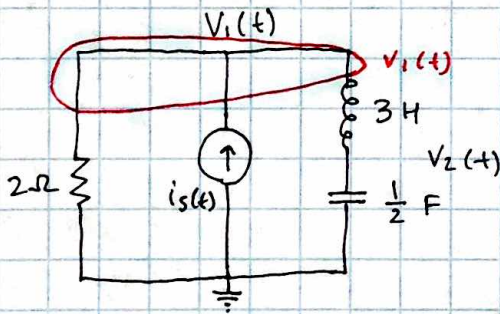

$$i_s(t) = 8 \cos(2t + 40^\circ) \text{ A} = 8 \angle 40^\circ$$

$$\omega = 2$$

$$Z_L = j\omega L = 6j$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j} = -j$$

$$Z_T = 5j$$

$$V_1(t): \frac{V_1}{2} - 8 \angle 40^\circ + \frac{V_1}{5j} = 0$$

$$V_1 \left(\frac{1}{2} + \frac{1}{5j} \right) = 8 \angle 40^\circ$$


$$V_1 \left(\frac{\sqrt{29}}{10} \angle -21.8^\circ \right) = 8 \angle 40^\circ$$

$$V_1 = \frac{8 \angle 40^\circ}{\frac{\sqrt{29}}{10} \angle -21.8^\circ}$$

$$V_1 = 14.86 \angle 61.80^\circ$$

$$V_1(t) = 14.86 \cos(2t + 61.80^\circ) \text{ (V)}$$

4.

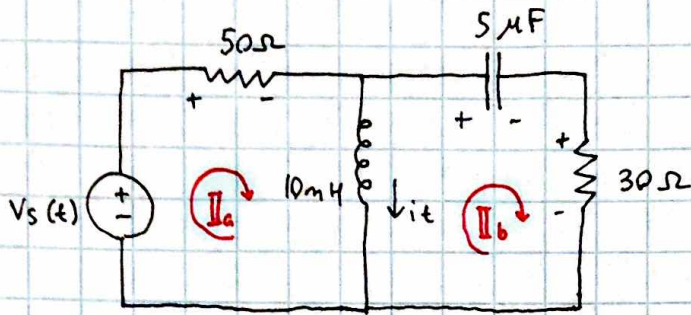

$$V_s(t) = 70 \cos(2000\pi t + 30^\circ) \text{ V} \quad \omega = 2000\pi$$

$$V_s(t) = 70 \angle 30^\circ = 35\sqrt{3} + 35j$$

$$Z_L = j\omega L = 20\pi j$$

$$Z_C = (j\omega C)^{-1} = -\frac{100}{\pi} j$$

$$\text{I}_a: -(35\sqrt{3} + 35j) + 50\text{I}_a + (\text{I}_a - \text{I}_b)20\pi j = 0$$

$$(50 + 20\pi j)\text{I}_a - (20\pi j)\text{I}_b = 35\sqrt{3} + 35j$$

$$\text{I}_b: (\text{I}_b - \text{I}_a)20\pi j + \left(-\frac{100}{\pi}j\right)\text{I}_b + 30\text{I}_b = 0$$

$$-20\pi j \text{I}_a + \left(30 + 20\pi j - \frac{100}{\pi}j\right)\text{I}_b = 0$$

$$\begin{array}{cc|c} \text{I}_a & \text{I}_b & K \\ \hline 50 + 20\pi j & -20\pi j & 35\sqrt{3} + 35j \\ -20\pi j & 30 + 20\pi j - \frac{100}{\pi}j & 0 \end{array}$$


$$\text{I}_a = 0.5252 + 0.3215j$$

$$\text{I}_b = 0.2240 + 0.8684j$$

$$i(t) = \text{I}_a - \text{I}_b = 0.312 - 0.5469j = 0.6244 \angle -61.16^\circ$$

$$i(t) = 0.6244 \cos(2000\pi t - 61.16^\circ) \text{ A}$$

5.

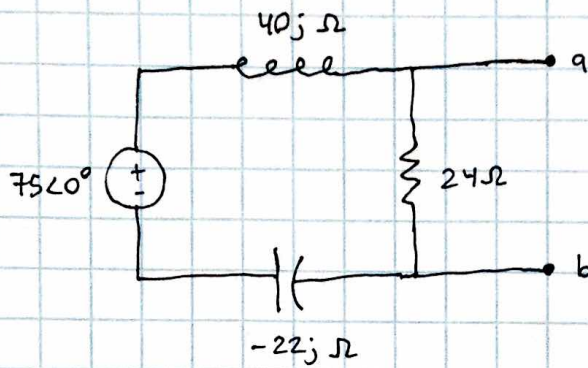
VOLTAGE DIVIDER $V_{ab} = V_{24}$

$$V_{ab} = 75 \left(\frac{24}{40j - 22j + 24} \right) V$$

$$V_{ab} = 48 - 36j = 60 \angle -36.87^\circ$$

$$V_{TH} = 60 \angle -36.87^\circ$$

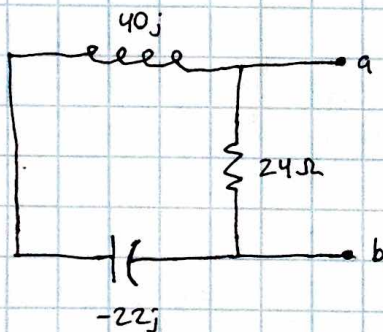Z_{TH} IS LOOK BACK IMPEDANCE WITH $75\angle 0^\circ$
SOURCE TURNED OFF




$$Z_{TH} = 24 \parallel 40j - 22j$$

$$Z_{TH} = \frac{24 \cdot 18j}{24 + 18j}$$

$$Z_{TH} = \frac{216}{25} + \frac{288j}{25}$$

$$Z_{TH} = 8.64 + 11.52j$$

6.

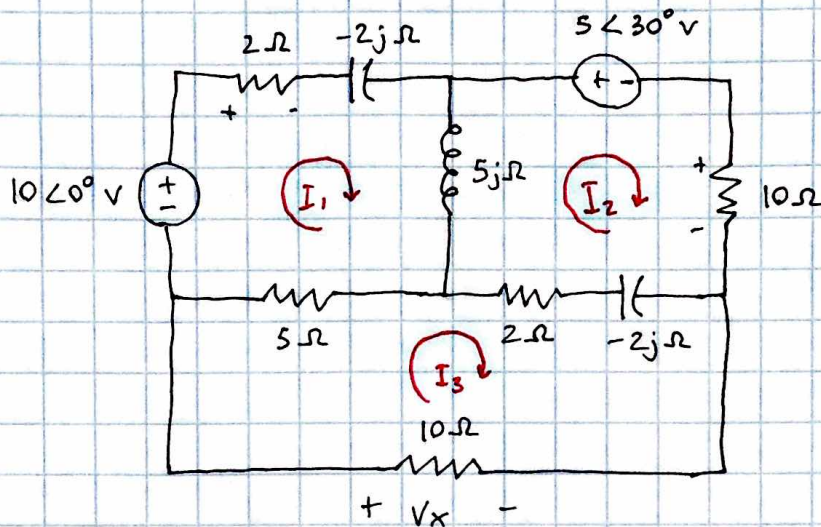

$$\begin{aligned}
 I_1: \quad & -10 + 2I_1 - 2jI_1 + (I_1 - I_2)5j + (I_1 - I_3)5 = 0 \\
 & -10 + \cancel{2I_1} - \cancel{2jI_1} + \cancel{5jI_1} - \cancel{5jI_2} + \cancel{5I_1} - \cancel{5I_3} = 0 \\
 & \underline{(2 - 2j + 5j + 5)I_1 + (-5j)I_2 + (-5)I_3 = 10}
 \end{aligned}$$

$$\begin{aligned}
 I_2: \quad & (I_2 - I_1)5j + (5\angle 30^\circ) + 10I_2 + (I_2 - I_3)(-2j) + (I_2 - I_3)2 = 0 \\
 & \cancel{5jI_2} - \cancel{5jI_1} + \cancel{10I_2} + \cancel{-2jI_2} + \cancel{2jI_3} + \cancel{2I_2} - \cancel{2I_3} = -(5\angle 30^\circ) \\
 & \underline{(-5j)I_1 + (5j + 10 - 2j + 2)I_2 + (2j - 2)I_3 = -\frac{5\sqrt{3}}{2} - \frac{5}{2}j}
 \end{aligned}$$


$$\begin{aligned}
 I_3: \quad & 10I_3 + (I_3 - I_1)5 + (I_3 - I_2)2 + (I_3 - I_2)(-2j) = 0 \\
 & \cancel{10I_3} + \cancel{5I_3} - \cancel{5I_1} + \cancel{2I_3} - \cancel{2I_2} - \cancel{2jI_3} + \cancel{2jI_2} = 0 \\
 & \underline{(-5)I_1 + (-2 + 2j)I_2 + (10 + 5 + 2 - 2j)I_3 = 0}
 \end{aligned}$$

$$\left[\begin{array}{ccc|c}
 I_1 & I_2 & I_3 & k \\
 7+3j & -5j & -5 & 10 \\
 -5j & 12+3j & -2+2j & -\frac{5\sqrt{3}}{2} - \frac{5}{2}j \\
 -5 & -2+2j & 17-2j & 0
 \end{array} \right] \quad \begin{aligned}
 I_3 &= 0.4221 - 0.1065j \\
 V_x &= -10 \cdot I_3
 \end{aligned}$$

$$V_x = -10 \cdot I_3 = -4.2209 + 1.0645j$$

$$\boxed{V_x = 4.353 \angle 165.8^\circ \text{ V}}$$

7.

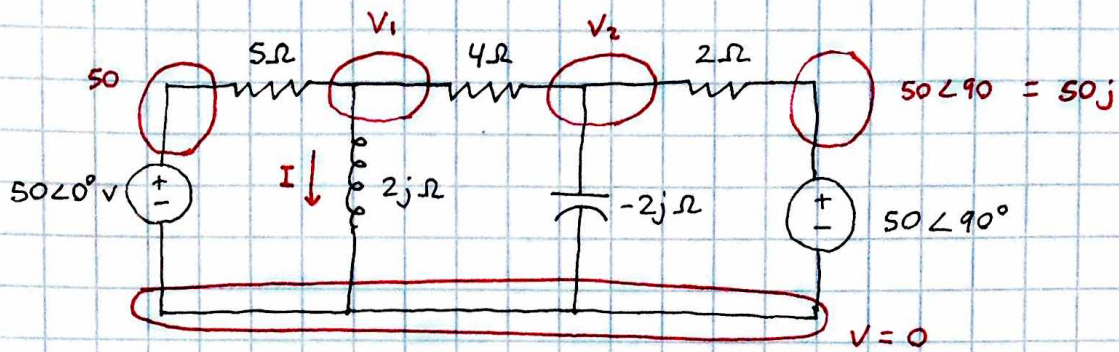

$$V_1: \frac{V_1 - 50}{5} + \frac{V_1}{2j} + \frac{V_1 - V_2}{4} = 0$$

$$\frac{V_1}{5} - \frac{50}{5} + \frac{V_1}{2j} + \frac{V_1}{4} - \frac{V_2}{4} = 0$$

$$\left(\frac{1}{5} + \frac{1}{2j} + \frac{1}{4}\right)V_1 - \frac{1}{4}V_2 = 10$$

$$V_2: \frac{V_2 - V_1}{4} + \frac{V_2}{-2j} + \frac{V_2 - 50j}{2} = 0$$

$$\frac{V_2}{4} - \frac{V_1}{4} - \frac{1}{2j}V_2 + \frac{1}{2}V_2 - 25j = 0$$


$$\left(-\frac{1}{4}\right)V_1 + \left(\frac{1}{4} - \frac{1}{2j} + \frac{1}{2}\right)V_2 = 25j$$

$$\begin{bmatrix} V_1 & V_2 & K \\ \frac{1}{20} + \frac{1}{2j} & -\frac{1}{4} & 10 \\ -\frac{1}{4} & \frac{3}{4} - \frac{1}{2j} & 25j \end{bmatrix} \quad \begin{array}{l} V_1 = 7.5472 + 23.58j \\ V_2 = 20.7547 + 27.36j \end{array}$$

$$I = \frac{V_1}{2j} = \frac{7.5472 + 23.58j}{2j} = 11.7925 - 3.7736j$$

$$I = 12.38 \angle -17.74^\circ \text{ A}$$

8.

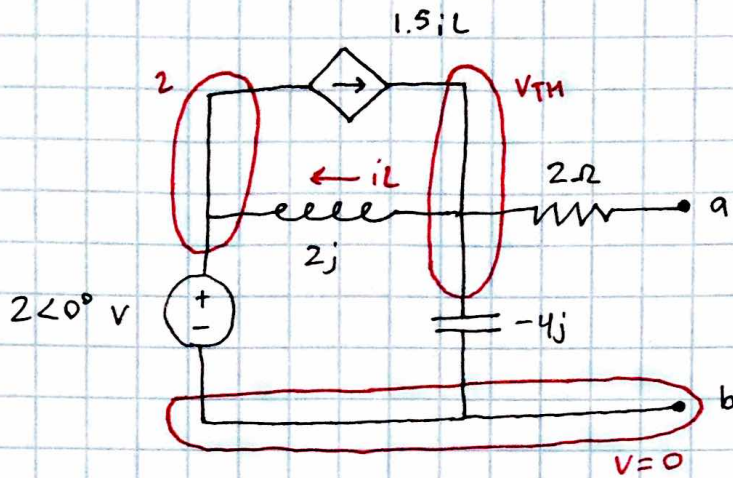


$$V_{TH}: -1.5i_L + i_L + \frac{V_{TH}}{-4j} = 0$$

$$\text{CONS: } \frac{V_{TH} - 2}{2j} = i_L$$

$$\left[\begin{array}{cc|c} V_{TH} & i_L & K \\ -\frac{1}{4j} & -\frac{1}{2} & 0 \\ 1 & -2j & 2 \end{array} \right] \quad \begin{array}{l} V_{TH} = 1 \text{ V} \\ i_L = \frac{1}{2}j \end{array}$$

$$\boxed{V_{TH} = 1 \angle 0^\circ}$$

8.

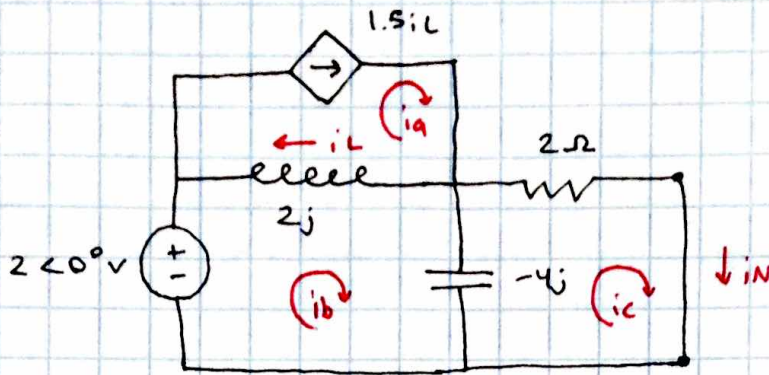

$$i_a: \quad i_a = 1.5i_L \rightarrow \underline{i_a - 1.5i_L = 0}$$

$$i_b: \quad -2 + 2j(ib - ia) - 4j(ib - ic) = 0$$

$$2jib - 2jia - 4jib + 4jic = 2$$

$$\underline{-2jia - 2jib + 4jic = 2}$$

$$i_c: \quad -4j(ic - ib) + 2ic = 0$$

$$-4jic + 4jib + 2ic = 0$$

$$\underline{4jib + (2 - 4j)ic = 0}$$

$$\text{CONS:} \quad i_a - i_b = i_L \rightarrow \underline{i_a - i_b - i_L = 0}$$

$$\left[\begin{array}{cccc|c} i_a & i_b & i_c & i_L & K \\ 1 & 0 & 0 & -1.5 & 0 \\ -2j & -2j & 4j & 0 & 2 \\ 0 & 4j & 2-4j & 0 & 0 \\ 1 & -1 & 0 & -1 & 0 \end{array} \right] \quad i_c = \frac{1}{4} + \frac{1}{4}j$$

$$i_c = i_N = \frac{1}{4} + \frac{1}{4}j \quad Z_{TH} = \frac{V_{TH}}{i_N} = \frac{1}{\frac{1}{4} + \frac{1}{4}j}$$

$$\boxed{Z_{TH} = 2.828 \angle -45.00^\circ \Omega}$$