

**Part I. Drills -- 1 point each**

**Note: All magnitudes are RMS**

1) What is the phase sequence of each of these sets of voltages?

a)  $v_a = 339 \cos 377t$  V  
 $v_b = 339 \cos (377t - 120^\circ)$  V  
 $v_c = 339 \cos (377t + 120^\circ)$  V

b)  $v_a = 679 \cos 377t$  V  
 $v_b = 679 \cos (377t + 120^\circ)$  V  
 $v_c = 679 \cos (377t + 240^\circ)$  V

2) If the phase voltages of a Y-connected source are as follows, find the line voltages  $V_{ab}, V_{bc}, V_{ca}$

$v_{AN} = 169.71 \cos (\omega t + 60^\circ)$  V,  
 $v_{BN} = 169.71 \cos (\omega t + 180^\circ)$  V,  
 $v_{CN} = 169.71 \cos (\omega t - 60^\circ)$  V.


3) If the phase currents of a Delta connected source are as follows, find the line currents  $I_a, I_b, I_c$

$I_{AB} = 339 \cos 377t$  V  
 $I_{BC} = 339 \cos (377t - 120^\circ)$  V  
 $I_{CA} = 339 \cos (377t + 120^\circ)$  V


4) Convert the Delta load to a Y,

and the Y load to a Delta

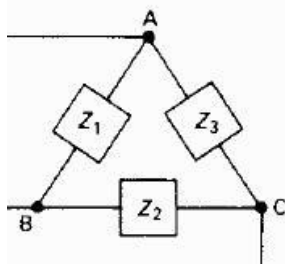
a)  $Z_1 = 2.4 - j0.7$ ,  $Z_2 = 8 + j6$ ,  $Z_3 = 20 + j0$



b)

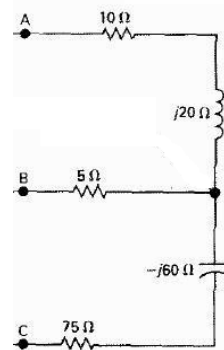

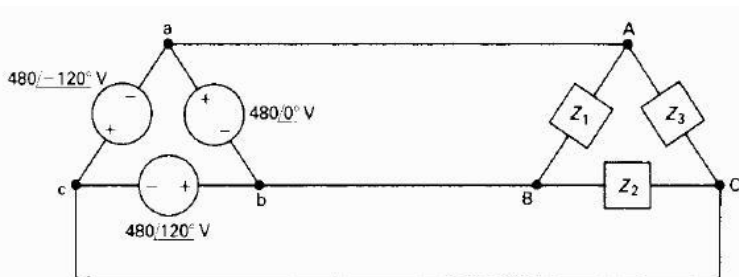5) For the Delta-Delta circuit shown, the load impedances  $Z_1 = Z_2 = Z_3 = 10 \angle 53.13^\circ$ . Find the phase currents  $I_{AB}, I_{BC}$  and  $I_{CA}$ , and the line currents  $I_a, I_b, I_c$ . Draw the voltage-current phasor diagram with all three quantities (line voltage, line and phase currents) on it.




## Part II. Assisted Problem Solving – 2 pts

6)

The magnitude of the phase voltage of an ideal balanced, three-phase, Y-connected source is 240 V. The source is connected to a balanced Y-connected load by a distribution line that has an impedance of  $0.2 + j1.6 \Omega/\phi$ . The load impedance is  $23.8 + j5.4 \Omega/\phi$ . The phase sequence of the source is abc. Use the a-phase voltage of the source as the reference. Specify the magnitude and phase angle of the following quantities: (a) the three line currents, (b) the three line voltages at the source, (c) the three phase voltages at the load, and (d) the three line voltages at the load.

Plan

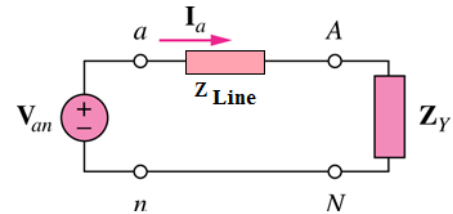- 1) Remember this is 240 Vrms.
- 2) Draw a single phase loop of this Y-Y system starting at  $V_{an}$ , going over line aA to the load and label the impedances of the line and the load. It will look something like this




- 3)  $V_{an} = 240\angle 0^\circ$ , so you can find  $I_a$  using Ohm's law ( $I_b$  and  $I_c$  by symmetry  $\pm 120^\circ$ )
- 4)  $V_{AN} = I_a * Z_Y$  (the rest by symmetry)
- 5) use the chart to find  $V_{AB}$ ,  $V_{BC}$ , and  $V_{CA}$

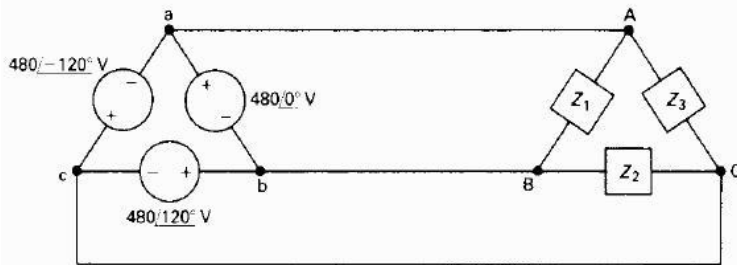7) Repeat problem 5 with

$$Z_1 = 2.4 - j0.7, \quad Z_2 = 8 + j6, \quad Z_3 = 20 + j0$$

Draw the voltage-current phasor diagram with all three quantities (line voltage, line and phase currents) on it.



PLAN

- 1) This is not a balanced system, however, the delta configuration allows us to compute each phase current in the load as the line voltage divided by the load impedance.
- 2) Find each phase current in the load (Ohm's law)
- 3) use KCL to derive the line currents
- 4) draw the phasor diagram as before in problem 5

## Part III. Unassisted Problem Solving – 3 points

8)

A balanced  $\Delta$ -connected load having an impedance of  $216 + j63 \Omega/\phi$  is connected in parallel with a balanced Y-connected load having an impedance of  $50\angle 0^\circ \Omega/\phi$ . The parallel loads are fed from a line having an impedance of  $0.5 + j4.0 \Omega/\phi$ . The magnitude of the line-to-neutral voltage of the Y-load is 750 V.

- a) Calculate the magnitude of the current in the line feeding the loads.
- b) Calculate the magnitude of the phase current in the  $\Delta$ -connected load.
- c) Calculate the magnitude of the phase current in the Y-connected load.
- d) Calculate the magnitude of the line voltage at the sending end of the line.