


ENGR 12

Assignment 14

SOLUTIONS

Part I. Drills -- 1 point each

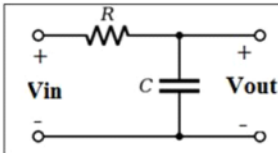
1) A series RC lowpass filter requires a cutoff frequency of 8 kHz. Use $R = 10 \text{ k}\Omega$ and compute the value of C required.



$$\omega_0 = 1/RC = 8000 * 2\pi, \quad RC = 1/(16000\pi),$$


$$C = 19.894\mu\text{s} / 10\text{k}\Omega, \quad \underline{C = 1.98 \text{ nF}}$$

2) A series RL highpass filter with a cutoff frequency of 2 kHz is needed. Using $R = 5 \text{ k}\Omega$, compute
a) L , b) $|H(\omega)|$ at 200 Hz, c) Phase($H(\omega)$) at 200 Hz

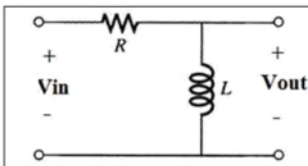

a) $\omega_0 = R/L = 2000 * 2\pi, \quad L = R/(4000\pi) = 5000/(4000\pi), \quad \underline{L = 397 \text{ mH}}$
 b) when $\omega = 200 * 2\pi, \quad H(\omega) = 1/(1 + R/(j\omega L)) = 0.0099 + 0.0990i$
 $H(200) = 0.100 \angle 84.29, \quad \underline{|H(\omega)| = 0.1}$
 c) phase($H(\omega)$) = 84.29 degrees

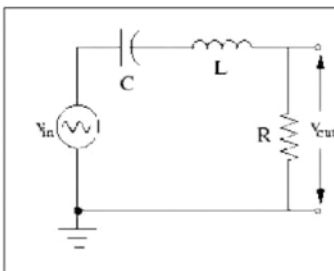3) A series RLC has a $0.1 \mu\text{F}$ capacitor. Find R and L for a bandpass filter with a center frequency of 12 kHz and a Q of 6



$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s} = 12000 * 2\pi, \quad LC = 1/(24000\pi)^2, \quad \underline{L = 1.76 \text{ mH}}$$

$$Q = \frac{\text{Peak energy stored in the circuit}}{\text{Energy dissipated by the circuit in one period at resonance}} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 CR}$$

$$Q = \omega_0 * L / R = 6, \quad R = \omega_0 * L / Q = 24000\pi * 0.00176 / 6, \quad \underline{R = 22.1 \Omega}$$

4) Show that $\omega_0 = \sqrt{\omega_1 \omega_2}$ for the series RLC circuit

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$


$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

$\omega_1 = 69376, \quad \omega_2 = 81942, \quad \omega_0 = 75398$ and the original $\omega_0 = 24000\pi = 75398$

Part II. Assisted Problem Solving – 2 pts

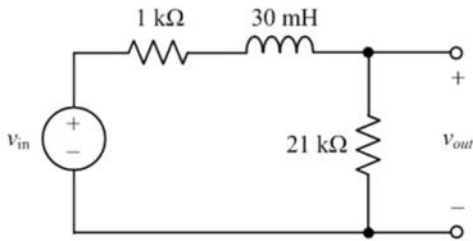6) Find the transfer function V_{out}/V_{in} and the corner frequency ω . What kind of filter is it? Plot the magnitude and phase of $H(\omega)$ using Freemat or WolframAlpha.



Plan


- 1) Replace the inductor with $j\omega$ (0.03)
- 2) Use the voltage divider formula to derive $H(\omega)$
- 3) Then find $H(\omega)$ by taking V_{out}/V_{in}
- 4) Plot the magnitude and phase of $H(\omega)$ using Freemat. Something like this:

```
w = [0:100:1e6];
H = 21000 ./ (1000 + j*w*(0.3));
semilogx(w, abs(H));
[copy and paste plot into word, then...]
semilogx(w, angle(H)*180/pi)
```


make sure to use ./ to divide the two terms of H

Solution to 6)

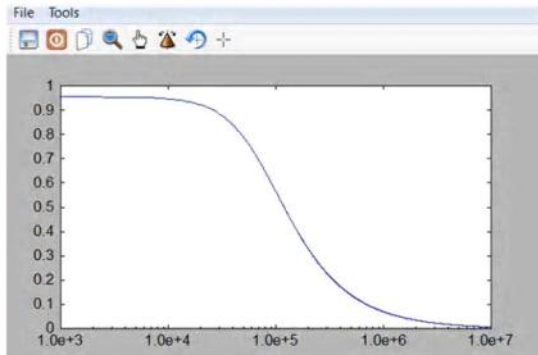
```
w = [1000:1000:10e6];
H = 21000 ./ (22000 + j*w*(0.3));
semilogx(w, abs(H));
```



semilogx(w, angle(H)*180/pi)

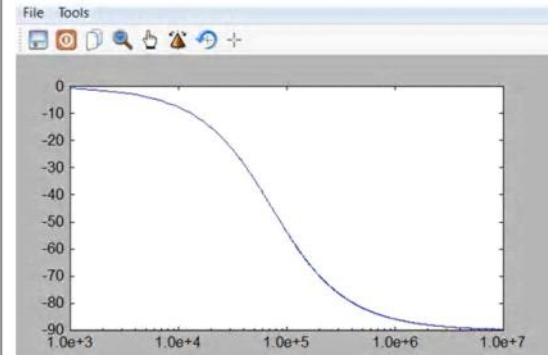

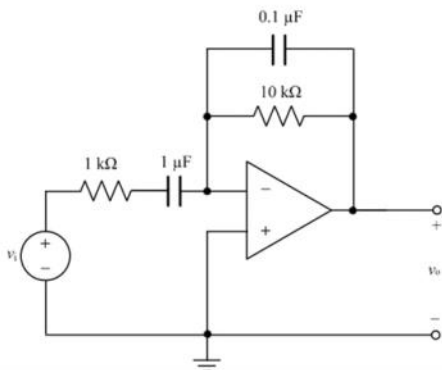7) Find the transfer function V_o/V_i for the following circuit



PLAN

- 1) Note that this is an inverting amplifier
- 2) Determine the values of R_s and R_f and use the formula from Chapter 5 (that's $V_o = -(R_f/R_s) V_i$)
- 3) Simplify your formula for $H(\omega)$ if necessary
- 4) Plot the magnitude and phase of $H(\omega)$ using Freemat

Solution to 7)

$$H(\omega) = -Z_f/Z_s =$$

$$Z_f = 10000 \parallel (1/(j\omega C_f)) \quad (\text{where } C_f = 0.1 \mu\text{F})$$

$$= \frac{10000}{10000 + \frac{1}{j\omega C_f}} = \frac{10000 \cdot 1 \cdot 10^7}{j\omega} = \frac{1 \cdot 10^7}{j\omega + 1000}$$



$$Z_s = 1000 + (1/(j\omega C_s)) \quad (\text{where } C_s = 1 \mu\text{F})$$

$$= 1000 + \frac{1}{j\omega C_s} = 1000 + \frac{1 \cdot 10^6}{j\omega} = \frac{1000j\omega + 1 \cdot 10^6}{j\omega}$$

$$H(\omega) = -(Z_f)/(Z_s)$$



$$= -\frac{\frac{1 \cdot 10^7}{j\omega + 1000}}{\frac{1000j\omega + 1 \cdot 10^6}{j\omega}} = \frac{-j\omega (1 \cdot 10^7)}{(1000j\omega + 1 \cdot 10^6)(j\omega + 1000)}$$

$$\frac{-10000j\omega}{(j\omega + 1000)(j\omega + 1000)} = \frac{-10000j\omega}{(1 \cdot 10^6 - \omega^2 + 2000j\omega)}$$

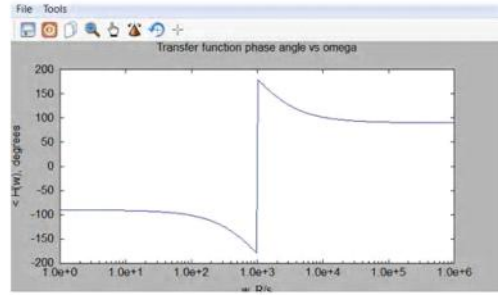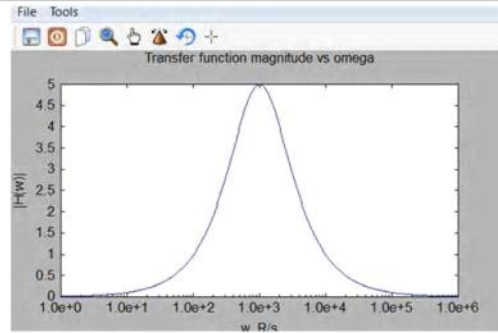

Part III. Unassisted Problem Solving – 3 points

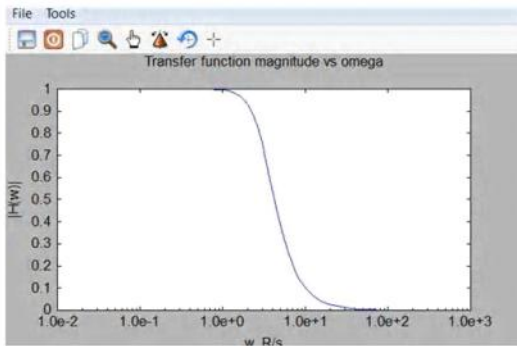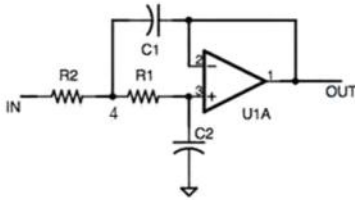8) Find the transfer function for this circuit given R1=R2=110 k, C1= 4uF, C2= 2 uF. Determine the cutoff frequency and plot the magnitude in Freemat. Hint: since there is negative feedback, terminal 3 will have the same voltage as 2.



Solution:

Call terminal 4 (V4) the center node between R2 and R1
Note that V2 = Vout and V3 = Vout

Then,

$$1) \quad (V_{in} - V_4)/R_2 + (V_3 - V_4)/R_1 + (V_2 - V_4)/Z_{C1} = 0$$

$$\text{or, } (V_{in} - V_4)/R_2 + (V_{out} - V_4)/R_1 + (V_{out} - V_4)/Z_{C1} = 0$$

$$\text{or, } V_{in} = R_2 \cdot \left[\frac{V_4}{R_2} + \frac{(V_4 - V_{out})}{R_1} + \frac{(V_4 - V_{out})}{Z_{C1}} \right]$$

and

$$2) \quad (V_3 - V_4)/R_1 + V_3/Z_{C2} = 0$$

$$\text{or, } (V_{out} - V_4)/R_1 + V_{out}/Z_{C2} = 0$$

solving 2) for V4:

$$3) \quad V_4 = R_1 \cdot V_{out} (1/R_1 + 1/Z_{C2}) = V_{out} (1 + R_1/Z_{C2})$$

Substituting 3) into 1)

$$V_{in} = R_2 \cdot V_{out} \cdot \left[\frac{(1 + R_1/Z_{C2})}{R_2} + \frac{R_1/Z_{C2}}{R_1} + \frac{(R_1/Z_{C2})}{Z_{C1}} \right]$$

$$H(\omega) = V_{out}/V_{in} = 1 / \left[\frac{(1 + R_1/Z_{C2})}{R_2} + \frac{R_1/Z_{C2}}{R_1} + \frac{(R_1/Z_{C2})}{Z_{C1}} \right]$$

$$= 1 / \left[1 + j\omega R_1 C_2 + j\omega R_2 C_2 - \omega^2 R_1 R_2 C_1 C_2 \right]$$

$$H(\omega) = \frac{1}{1 - \omega^2 R_1 R_2 C_1 C_2 + j\omega C_2 (R_1 + R_2)}$$

when $\omega = 0$, $H(\omega) = 1$, when $\omega = \infty$, $H(\omega) = 0 \rightarrow$ low pass filter

note the steeper rolloff of this filter due to the ω^2 term.

To find the cutoff frequency, set magnitude of H to $1/\sqrt{2}$

$$|H(w)| = .7071 = \frac{1}{1 - w^2 R_1 R_2 C_1 C_2 + jwC_2(R_1 + R_2)} \quad \text{when}$$

$$|1 - w^2 R_1 R_2 C_1 C_2 + jwC_2(R_1 + R_2)| = 1.414$$

or

$$(1 - w^2 R_1 R_2 C_1 C_2)^2 + (wC_2(R_1 + R_2))^2 = 2$$

or

$$1 - 2w^2 R_1 R_2 C_1 C_2 + (w^2 R_1 R_2 C_1 C_2)^2 + (wC_2(R_1 + R_2))^2 = 2$$

Substituting in values for R and C gives

$$w^4 = 106.72$$

$$w = 3.214$$