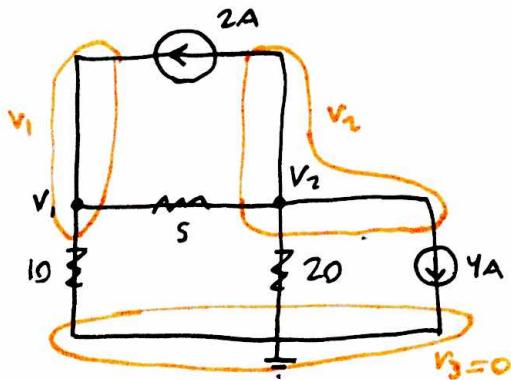


HENRY CARDENAS  
TOM REBOLD  
ENGR 12  
4 MARCH 2015

A4

1)



$$V = iR \quad i = \frac{V}{R}$$

$V_1$ : OUT IS POSITIVE

$$V_1: -2 + \frac{V_1 - V_2}{5} + \frac{V_1}{10} = 0$$

$$-20 + 2(V_1 - V_2) + V_1 = 0$$

$$-20 + 2V_1 - 2V_2 + V_1 = 0$$

$$3V_1 - 2V_2 = 20$$

$$V_2: +2 + \frac{V_2}{20} + 4 + \frac{V_2 - V_1}{5} = 0$$


$$120 + V_2 + 4V_2 - 4V_1 = 0$$

$$-4V_1 + 5V_2 = -120$$

$$4V_1 - 5V_2 = 120$$

$$V_1 = -20 \quad V_2 = -40$$

2)

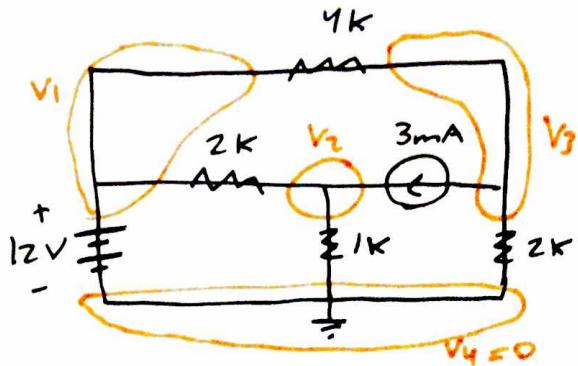

$$V_1: \frac{V_1 - V_3}{4} + \frac{V_1 - V_2}{2} \dots V_1 = 12V$$

$$V_2: \frac{V_2 - 12}{2} - 3 + \frac{V_2}{1} = 0$$


$$V_2 - 12 - 6 + 2V_2 = 0$$

$$3V_2 = 18 \quad \boxed{V_2 = 6V}$$

$$V_3: \frac{V_3}{2} + 3 + \frac{V_3 - 12}{4} = 0$$

$$2V_3 + 12 + V_3 - 12 = 0$$

$$\boxed{V_3 = 0V}$$

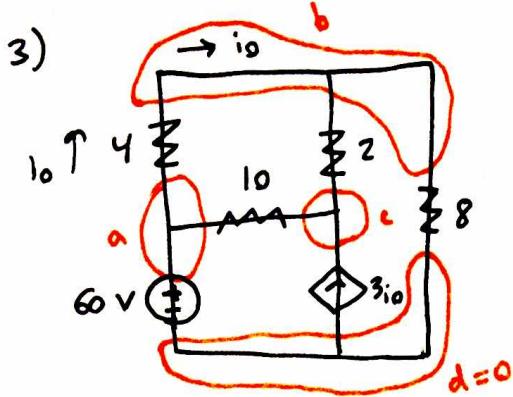


$$V_a = 60V$$

$$V_b: 7V_b - 4V_c + 0i_o = 120$$

$$V_c: -5V_b + 6V_c - 30i_o = 60$$

$$\text{constraint: } V_b + 0V_c + 4i_o = 60$$

$V_b = 53.08$	$V_c = 62.88$	$i_o = 1.73A$
---------------	---------------	---------------

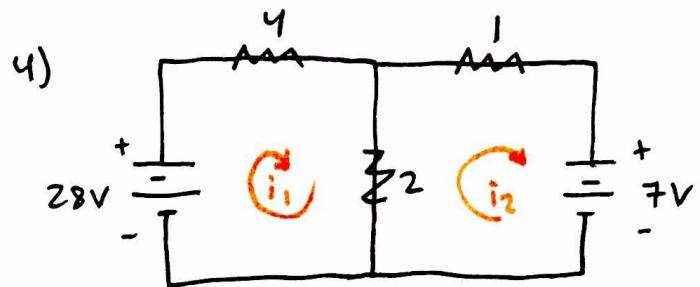

$$i_1: -28 + 4i_1 + 2(i_1 - i_2) = 0$$

$$i_2: 2(i_2 - i_1) + i_2 + 7 = 0$$

$$4i_1 + 2i_1 - 2i_2 = 28$$


$$6i_1 - 2i_2 = 28$$

$$2i_2 - 2i_1 + i_2 = -7$$

$$-2i_1 + 3i_2 = -7$$

$i_1 = 5A$	$i_2 = 1A$
------------	------------

5)

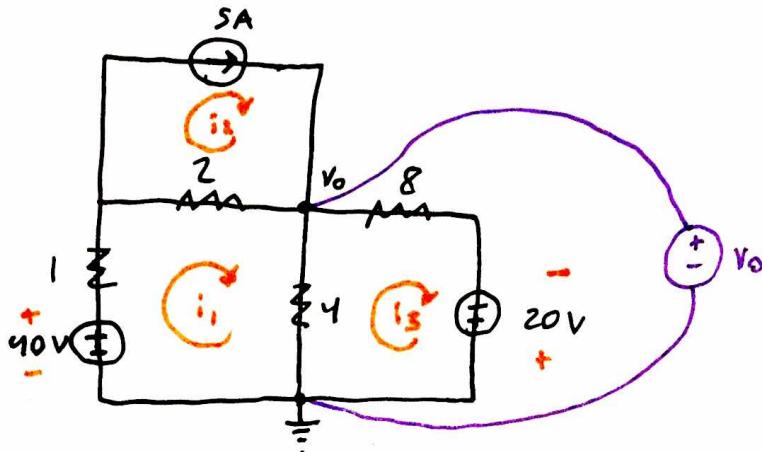

$$i_1 : -40 + i_1 + 2(i_1 - i_2) + 4(i_1 - i_3) = 0$$

$$-40 + i_1 + 2i_1 - 2i_2 + 4i_1 - 4i_3 = 0$$

$$i_2 : 5A$$

$$i_1 : -40 + i_1 + 2i_1 - 10 + 4i_1 - 4i_3 = 0$$

$$7i_1 - 4i_3 = 60$$

$$i_3 : 4(i_3 - i_1) + 8i_3 - 20 = 0$$

$$4i_3 - 4i_1 + 8i_3 - 20 = 0$$


$$-4i_1 + 12i_3 = 20$$

$$i_1 = 10A \quad i_3 = 5A$$

$$\text{KVL: } 4(i_3 - i_1) + V_o = 0 \rightarrow -20 + V_o = 0$$

$$V_o = 20V$$

6)

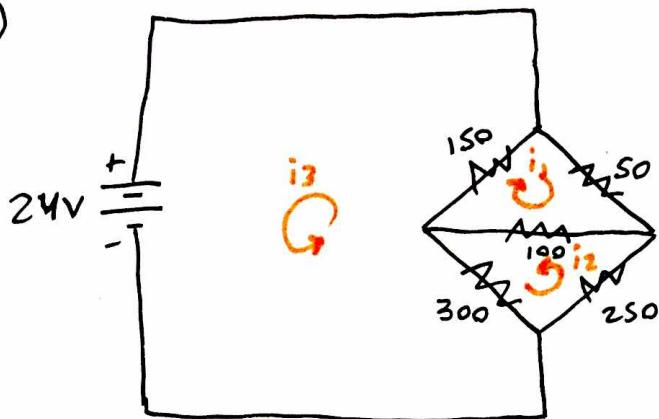

$$i_3: 300(i_3 - i_2) + 150(i_3 + i_1) + 24 = 0$$

$$300i_3 - 300i_2 + 150i_3 + 150i_1 = -24$$

$$150i_1 - 300i_2 + 450i_3 = -24$$

$$i_2: 250i_2 + 100(i_2 + i_1) + 300(i_2 - i_3) = 0$$

$$250i_2 + 100i_2 + 100i_1 + 300i_2 - 300i_3$$

$$100i_1 + 650i_2 - 300i_3 = 0$$


$$i_1: 150(i_1 + i_3) + 50i_1 + 100(i_1 + i_2) = 0$$

$$150i_1 + 150i_3 + 50i_1 + 100i_1 + 100i_2 = 0$$

$$300i_1 + 100i_2 + 150i_3 = 0$$

$i_1 = 93.8 \text{ mA}$     $i_2 = -77.2 \text{ mA}$     $i_3 = -136.1 \text{ mA}$

6

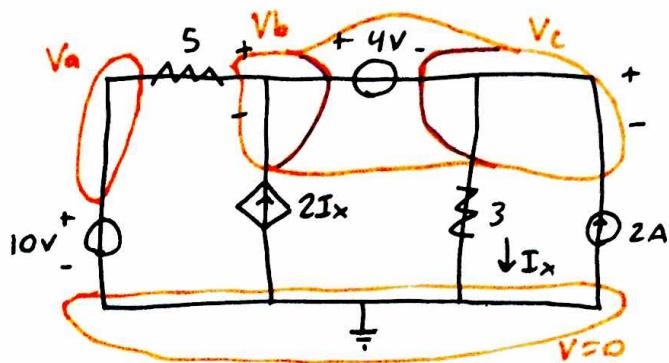

$$V_A = 10V$$

$$V = iR \quad i = \frac{V}{R}$$

$$SN: \frac{V_B - 10}{5} + I_x - 2I_x - 2 = 0$$

$$KVL: -V_B + 4 + V_C = 0$$

$$CONS. \frac{V_C}{3} = I_x$$

$$SN: V_B - 10 - 5I_x - 2 = 0$$

$$V_B + 0V_C - 5I_x = 12$$


$$V_B + 0V_C - 5I_x = 20$$

$$-V_B + V_C + 0I_x = -4$$

$$0V_B + V_C - 3I_x = 0$$

$$I_x = -8A$$

7.

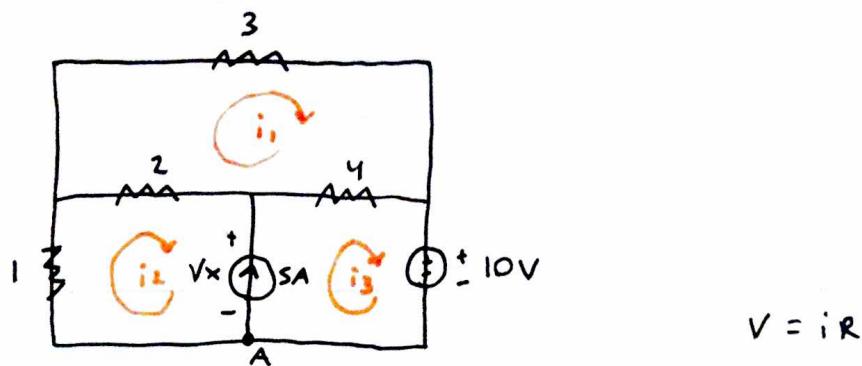

$$V = iR$$

$$i_1: 2(i_1 - i_2) + 3i_1 + 4(i_1 - i_3) = 0$$

$$i_{23}: i_2 + 2(i_2 - i_1) + 4(i_3 - i_1) + 10 = 0$$

$$\text{CONS @ A: } 5 - i_3 + i_2 = 0$$

ALGEBRA:

$$2i_1 - 2i_2 + 3i_1 + 4i_1 - 4i_3 = 0$$

$$\underline{9i_1 - 2i_2 - 4i_3 = 0}$$

$$i_2 + 2i_2 - 2i_1 + 4i_3 - 4i_1 + 10 = 0$$

$$\underline{-6i_1 + 3i_2 + 4i_3 = -10}$$

$$\underline{0i_1 + i_2 - i_3 = -5}$$

$$i_1 = -1.48 \quad i_2 = -5.56 \quad i_3 = -0.56$$


KVL  $i_3$  LOOP:

$$-V_x + 4(i_3 - i_1) + 10 = 0$$

$$V_x = 4(i_3 - i_1) + 10$$

$$\boxed{V_x = 13.70V}$$

8)

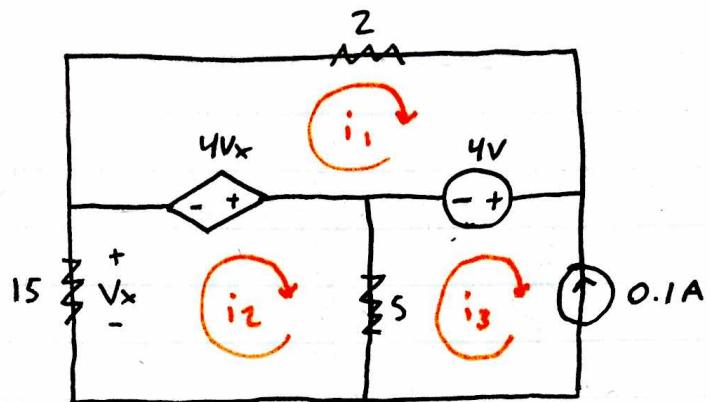USE MC TO AVOID SUPERNODE  $V = iR$ 

$$i_1: 4V_x + 2i_1 + 4 = 0$$

$$i_2: -V_x - 4V_x + 5(i_2 - i_3) = 0$$

$$i_3: i_3 = -0.1A$$

$$\text{CONS. } 15i_2 = -V_x$$

$$i_2: -5V_x + 5i_2 - 5i_3 = 0$$

$$\begin{bmatrix} V_x & i_1 & i_2 & i_3 & C \\ 4 & 2 & 0 & 0 & -4 \\ -5 & 0 & 5 & -5 & 0 \\ 0 & 0 & 0 & 1 & -0.1 \\ 1 & 0 & 15 & 0 & 0 \end{bmatrix}$$

$$V_x = 0.0938V$$