


ENGR 12

Assignment 6

SOLUTIONS


Part I. Drills -- 1 point each

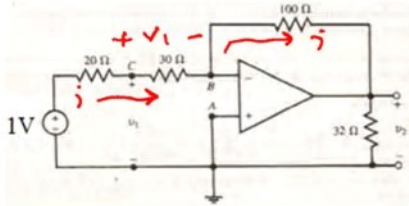1) For the following circuit: What type of Op-Amp circuit is it? Inverting then, find  $V_1$  and  $V_2$



$$\begin{aligned}
 v_p = v_n = 0 \\
 i = \frac{1-0}{20+30} = \frac{0-v_2}{100} \\
 v_2 = \frac{-100}{50} = -2V.
 \end{aligned}
 \left. \begin{array}{l} \text{KVL } -1 + 20i + v_1 = 0 \\ v_1 = 1 - 20i = \\ v_1 = 1 - \frac{20}{50} = \underline{\underline{.6V}} \end{array} \right\}$$

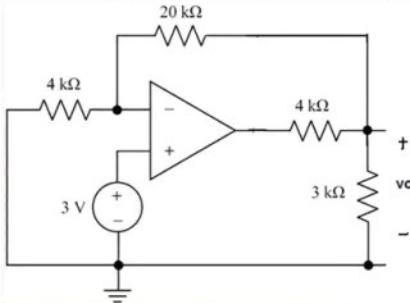
2) For the following circuit: What type of Op-Amp circuit is it? Non-Inv then, find  $V_o$



$$\begin{aligned}
 v_p = +3 = v_n \\
 v_n - 0 + \frac{v_n - v_o}{20} = 0 \\
 5v_n + v_n - v_o = 0 \\
 v_o = 6v_n = \underline{\underline{18V}}
 \end{aligned}$$

we assume linear operation since  $\pm V_{cc}$  not provided.

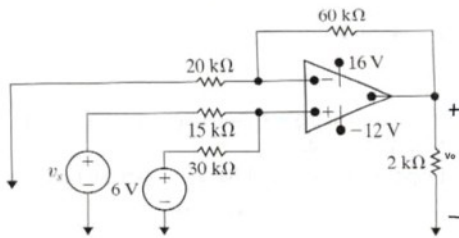3) For the following circuit: What type of Op-Amp circuit is it? Summing then, find  $V_o$




$$\begin{aligned}
 1) \text{ NV at } v_p: \\
 \frac{v_s - v_p}{15} + \frac{6 - v_p}{30} = 0, \quad 3v_p = 2v_s + 6 \\
 v_p = \frac{2}{3}v_s + 2 \\
 2) \text{ NV at } v_n: \\
 \frac{v_n}{20} + \frac{v_n - v_o}{60} = 0, \quad 4v_n = v_o
 \end{aligned}$$

$$\begin{aligned}
 3) \text{ Assume linear } (v_n = v_p = \frac{2}{3}v_s + 2) \\
 v_o = 4v_n = 4(\frac{2}{3}v_s + 2), \quad v_o = \underline{\underline{\frac{8}{3}v_s + 8}}
 \end{aligned}$$

$$4) \text{ Linear Range: } v_o = 16 \text{ when } \frac{8}{3}v_s = 8, \quad v_s = 3V, \quad v_o = -12 \text{ when } \frac{8}{3}v_s = -20, \quad v_s = \underline{\underline{-7.5V}}$$

$$\therefore \text{ OpAmp is Linear when } \underline{\underline{-7.5 < v_s < 3}}$$

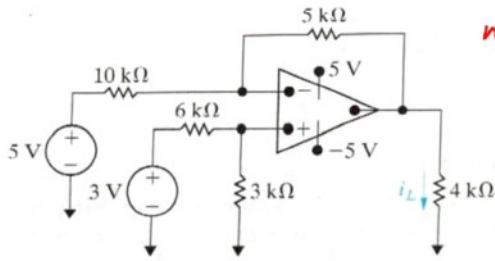- 4) For the following circuit: What type of Op-Amp circuit is it? Difference then, find  $i_L$  in micro-Amperes




note:  $\frac{10}{5} = \frac{6}{3} \therefore$  use simple formula:

$$V_o = \frac{R_b}{R_a} (V_b - V_a) = \frac{5}{10} (3 - 5) = \underline{\underline{-1V}}$$

$$i_L = \frac{V_o}{4k} = \underline{\underline{-0.25 \mu A}}$$

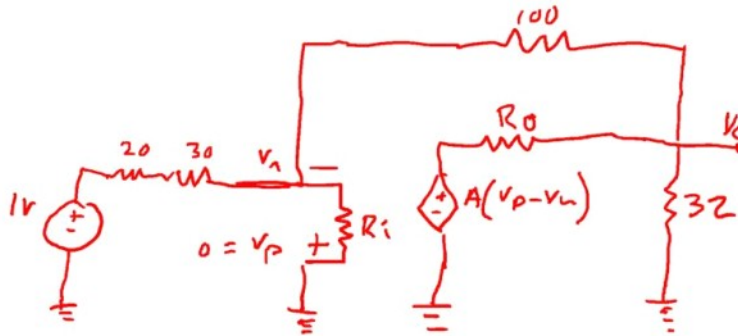- 5) Repeat #1 using non-ideal op-amp model. Take  $A = 100000$ ,  $R_i = 500 \text{ k}\Omega$ ,  $R_o = 75 \text{ }\Omega$  [ a CHALLENGE!!! ]



$$1) \text{ Nodal } v_n: \frac{v_n - 1}{20} + \frac{v_n - v_o}{100} + \frac{v_n}{R_i} = 0, \quad 2v_n - 2 + v_n - v_o + \frac{100v_n}{R_i} = 0$$

$$2) \text{ Nodal } v_o: \frac{v_o - v_n}{100} + \frac{v_o - A(0 - v_n)}{R_o} + \frac{v_o}{32} = 0$$

$$8v_o - 8v_n + \frac{800}{R_o} (v_o + Av_n) + 25v_o = 0$$

$$1) \quad v_n \left( 3 + \frac{100}{R_i} \right) - v_o = 2, \quad (R_i = 500k) \rightarrow v_o = v_n (3.0002) - 2$$

$$2) \quad v_n \left( -8 + \frac{800}{R_o} A \right) + v_o \left( 8 + \frac{800}{R_o} + 25 \right) = 0, \quad \left( \begin{matrix} R_o = 75 \\ A = 100000 \end{matrix} \right) \rightarrow v_n (-1.067 \times 10^6) + 43.67 v_o = 0$$


$$\text{Substituting: } v_n (1.067 \times 10^6) + 43.67 (3.0002 v_n - 2) = 0$$

$$v_n = \frac{+87.34}{(43.67 \cdot 3.0002 + 1.067 \times 10^6)} = +8.184 \times 10^{-5} \text{ V}$$

$$\underline{\underline{v_o = -1.9998 \text{ V}}}$$

Part II. Assisted Problem Solving – 2 pts each

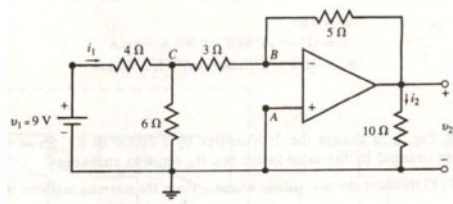6 Find  $V_c$ ,  $i_1$ ,  $R_{in}$  (input Resistance seen by 9V source),  $v_2$ ,  $i_2$



$$v_B = v_A = 0$$

$$\text{NVC: } v_C - 9 + \frac{v_C}{6} + \frac{v_C}{3} = 0$$

$$3v_C + 2v_C + 4v_C = 27, \quad v_C = 3$$


$$i_1 = \frac{9-3}{4} = 1.5$$

$$R_{in} = \frac{9}{i_1} = \frac{9}{1.5} = 6\Omega$$

$$14V \text{ Amp} \rightarrow v_2 = -\frac{5}{7} v_C = -5V$$

$$i_2 = \frac{v_2}{10} = -0.5A \text{ (going "up")}$$

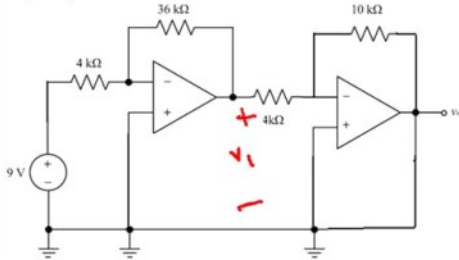7 Find  $V_o$  for the following 2 stage amplifier. What is the total gain of the amplifier? ( $G = v_o/v_{in}$ )



Both inverting Op Amps.


$$v_1 = -\frac{36}{4} v_{in} = -81v$$

$$v_o = -\frac{10}{4} (-81) = 202.5$$

$$G_{ain} = \frac{v_{out}}{v_{in}} = \frac{202.5}{9} = 22.5$$

Part III. Unassisted Problem Solving – 3 points each

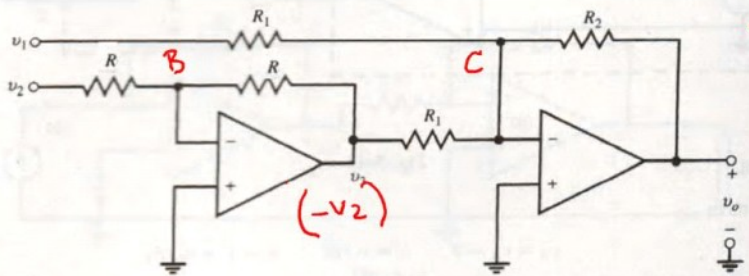8) Find  $v_o$  for the following circuit:



2) NVC: note  $v_C = 0$  too

$$\frac{v_C - v_1}{R_1} + \frac{v_C - v_2}{R_1} + \frac{v_C - v_o}{R_2} = 0$$

mult by  $R_1 R_2$ :

$$v_C R_2 + (v_C + v_2) R_2 + R_1 (v_C - v_o) = R_2 v_1$$

( $v_C = 0$ )

$$v_2 R_2 - v_1 R_2 = R_1 v_o$$

$$v_o = \frac{(v_2 R_2 - v_1 R_2)}{R_1}$$

1) 1st: Inv, 2nd Summ  
note  $v_B = 0$ :  $v_3 = -\frac{R}{R} v_2 = -v_2$

$$v_o = \frac{R_2}{R_1} (v_2 - v_1)$$