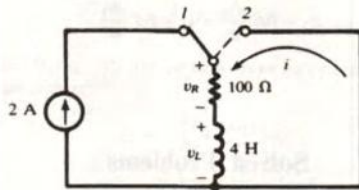


ENGR 12

Assignment 8 SOLNS

Part I. Drills -- 2 point each

1) Switch at 1 a long time, moves to 2 at t=0




This is a NATURAL response

For the circuit above, find the:

- a) initial current $i_L(0^-)$ 2 A
- b) final current $i_L(\infty)$ 0
- c) Effective R seen by inductor ($t > 0$) 100 ohm
- d) time constant for $t > 0$.04 sec
- e) $i_L(t) = 2e^{-25t}$ A
- f) $v_L(t) = \frac{L di}{dt} = -200e^{-25t}$ V

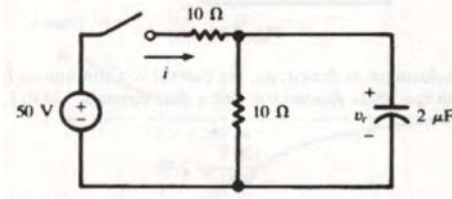2) Switch has been open a long time, closes at t=0




This is a STEP response

For the circuit above, find the:

- a) initial voltage $V_C(0^-)$ 0
- b) final voltage $V_C(\infty)$ 25V
- c) Reff seen by capacitor ($t > 0$) 5 Ohm
- d) time constant for $t > 0$ 10 usec
- e) $v_C(t) = 25 - 25e^{-100000t}$ V
- f) $i_C(t) = \frac{C dv_C}{dt} = 2\mu F * (-25) * (-100000) e^{-100000t} = 5e^{-100000t}$ A

Part II. Assisted Problem Solving – 1.5 pts each

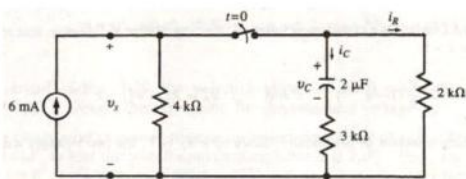
3. Switch has been closed and opens at t=0. Find V_C , I_C , I_R and V_S for $t > 0$



This is a NATURAL response

- 1) $V_C(0^-) = V_S(0^-) = .006 * (4 || 2) = 8$ V
- 2) $R_{eq} = 5$ k
- 3) $\tau = .01$
- 4) $V_C(t) = 8e^{-100t}$ V
- 5) $I_C(t) = \frac{C dv_C}{dt} = -1.6e^{-100t}$ mA
- 6) $I_R(t) = -I_C(t) = +1.6e^{-100t}$ mA
- 7) $V_S(t) = 24V$ constant for $t > 0$

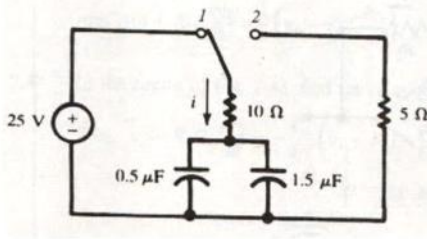4. For $t < 0$, switch had been at 2 a long time. At $t = 0$, switch goes to 1. At $t = 60$ micro-seconds, switch goes back to 2. Find $i(t)$ for $t > 0$



This is a ___STEP/Natural/STEP___ response

- 1) $V_c(0^-) = 0$
- 2) $C_{eq} = .5 + 1.5 = 2 \mu F$
- 3) $V_c(\infty)$ (for $t < 0 < 60$) = 25V
- 4) $R_{eq} = 10 \text{ Ohm}$
- 5) τ for $t < 0 < 60 \text{ usec} = 20 \text{ usec}$
- 6) $V_c(t)$ for $t < 0 < 60 = 25 - 25e^{-50000t}$ parallel caps
- 7) $V_c(60 \text{ usec}) = 25(1 - e^{-50000(60 \times 10^{-6})}) = 23.75 \text{ V}$
- 8) For second switch throw ($t > 60 \text{ usec}$):
- 9) $V_c(60 \text{ usec}) = 23.75 \text{ V}$
- 10) $R_{eq} = 15 \text{ Ohm}$
- 11) τ for $t > 60 \text{ usec} = 15 * 2 \times 10^{-6} = 30 \text{ usec}$
- 12) $V_c(t > 60 \text{ usec}) = 23.75e^{-33333(t-60 \text{ usec})} \text{ V}$
- 13) Finally, use $V_c(t)$ to find $i(t)$:

Region I : $0 < t < 60 \text{ usec}$:

$$i(t) = C \frac{dV_c}{dt} = 2\mu F(1.25 \times 10^{-6}) = 2.5e^{-50000t} \text{ A}$$

Region II: $60 \text{ usec} < t < \infty$

$$i(t) = 2\mu F(23.75)(-33333) e^{-33333(t-60 \text{ usec})} \\ = -1.583e^{-33333(t-60 \text{ usec})} \text{ A}$$

Notice that we must use $(t - 60 \text{ usec})$ for region II because we need the exponent to equal zero at $t = 60 \text{ usec}$ to match the values of V_c at the instant of switching. In other words,

$$V_c(60 \text{ usec}^-) = V_c(60 \text{ usec}^+)$$


and this will only work if we use $t - 60 \text{ usec}$ for the second exponential.

Part III. Unassisted Problem Solving – 2 points each

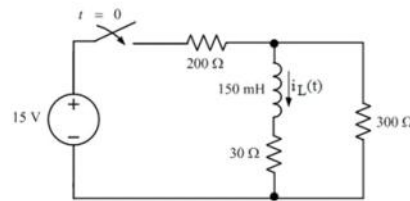5) The switch has been open a long time. At $t = 0$ the switch closes. Find $i_L(t)$ for $t > 0^+$

This is a ___STEP___ response

See SOLN Video: <http://www.rose-hulman.edu/CLEO/video/player.php?id=38&embed>




- a) $i_L(0) = 0$,
- b) In the steady state, inductor is short, and voltage source sees $200 + (30 \parallel 300) \text{ Ohm} = 227.27$, so $i_{\text{source}} = 15/227.27 = .066 \text{ A}$, and i_L sees only part of that thru the current divider, so $i_L(\infty) = .066 * 300/330 = 60 \text{ mA}$
- c) $R_{eq} = 200 \parallel 300 + 30 = 150 \text{ Ohm}$
- d) $\tau = L/R = .150/150 = .001 \text{ sec}$
- e) $i_L(t) = 60 - 60 e^{-1000t} \text{ mA}$

6)

In the circuit the switch has been closed for a long time before opening at $t = 0$.

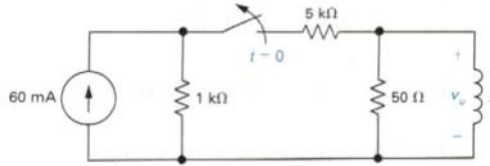- (a) Find the value of L so that $v_o(t)$ equals $0.25 v_o(0^+)$ when $t = 5$ ms.
 (b) Find the percentage of the stored energy that has been dissipated in the 50Ω resistor when $t = 5$ ms.



This is a NATURAL response

a) The solution for $i_L(t) = I_0 e^{-t/\tau}$ (where I_0 is initial current thru inductor)

and the solution for $V_o(t) = \frac{L di_L}{dt} = \frac{L I_0}{\tau} e^{-t/\tau}$, in other words, same time constant as $i_L(t)$

We are given at 5ms $V_o(5ms) = 0.25 V_o(0^+) = V_o(0^+) e^{-0.005/\tau}$.

Therefore, we only need to solve $0.25 = e^{-\frac{0.005}{\tau}}$, or, taking log of both sides,

$$-\frac{0.005}{\tau} = \log(.25) = -1.386, \text{ or, } \tau = 3.607 \text{ ms} = L/R = L/50, \text{ (Req} = 50 \text{ Ohm for } t > 0)$$

so $L = R * \tau = 180.4 \text{ mH}$

b) Lets solve for $i_L(t)$. First, we'll need I_0 . Before switch opened, Inductor is a short. Due to current divider, $I_0 = 60 * 1/(1+5) = 10 \text{ mA}$. Therefore:

$$i_L(t) = 10 e^{-t/\tau} \text{ mA} = 10 e^{-277.2t}$$

$$i_L(0) = 10 \text{ mA and } i_L(5ms) = 10 e^{-277.2(0.005)} = 2.5 \text{ mA (as in V, we are .25 of original value)}$$

$$\text{Energy in Inductor} = w(t) = \frac{1}{2} L i_L(t)^2$$

$$\text{Ratio of energy in inductor at 5 ms vs 0 ms} = \frac{\frac{1}{2} L i_L(5ms)^2}{\frac{1}{2} L i_L(0)^2} = \frac{2.5^2}{10^2} = .0625 \text{ or } 6.25\%$$

The energy lost in inductor has been dissipated in the 50Ω resistor, so the resistor has dissipated $100 - 6.25 = 93.75\%$