

ENGR 12


Assignment 9

SOLUTIONS

Part I. Drills -- 1 point each


Determine the type of response (under, critical, over-damped) for these 2nd order circuits:

1)

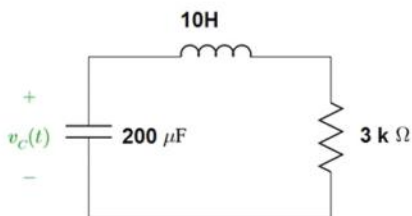

Series, Natural
 $\alpha = \frac{3k}{2 \cdot 10} = 150$
 $\omega_0 = \frac{1}{\sqrt{LC}} = 22.36$
 $\alpha > \omega_0$
OVER



2)

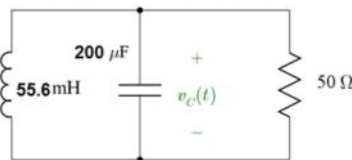

Parallel, Natural
 $\alpha = \frac{1}{2RC} = 50$
 $\omega_0 = \frac{1}{\sqrt{LC}} = 300$
 $\omega_0 > \alpha$
UNDER damped

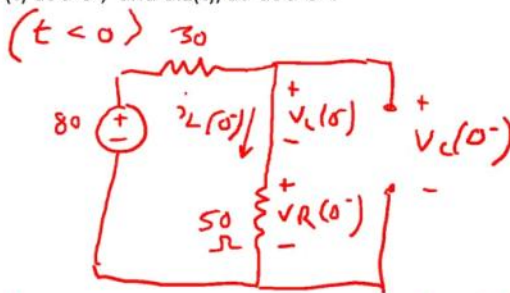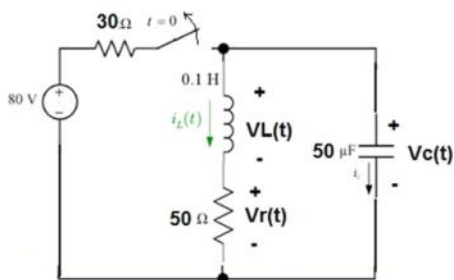3) For the following circuit, the switch is initially closed and has been for a long time.

Find the initial values of $V_c(t)$, $i_L(t)$, $V_L(t)$ and $V_r(t)$ at $t=0^-$, and $di_L(t)/dt$ at $t=0^+$.



$V_L(0^-) = 0$, $i_L(0^-) = \frac{80V}{8\Omega} = 1A$, $V_c(0^-) = i_L(0^-) \cdot 50 = 50V$
 $V_r(0^-) = V_c(0^-) = 50V$


4) Derive the formula for the inductor current $i_L(t)$ in problem 3 for $t > 0$.

Series, Natural: $\alpha = \frac{R}{2L} = 250$, $\omega_0 = \frac{1}{\sqrt{LC}} = 447.2$, Under damped, $\omega_d = 370.8$

$i(0^+) = 1A = B_1$

$\frac{di(0^+)}{dt} = \frac{V_L(0^+)}{L} = 0 = -\alpha B_1 + \omega_d B_2$
 $= -250B_1 + 370.8 B_2$

$B_2 = 250(1A) / 370.8 = 0.674$

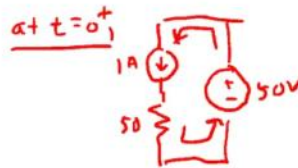

$$\therefore i_L(t) = e^{-250t} (-\alpha \beta_1 + \omega_d \beta_2) = e^{-250t} (\beta_1 \cos 370.8t + \beta_2 \sin 370.8t)$$

$$i_L(t) = e^{-250t} (\cos 370.8t + 0.674 \sin 370.8t)$$

5) Derive the formula for the capacitor voltage $V_C(t)$ in problem 3 for $t > 0$.

$$\text{KVL: } -V_R - V_L + V_C = 0, \quad V_C = V_L + V_R = L \frac{di_L}{dt} + i_L R$$

$$V_C = 0.1 \left(e^{-250t} (-539.3 \sin(370.8t) - 0.0808 \cos(370.8t)) \right) + \left(e^{-250t} (\cos(370.8t) + 0.674 \sin(370.8t)) \right) \cdot 50$$

$$V_C = e^{-250t} (50 \cos(370.8t) - 20.2 \sin(370.8t)) \text{ Volts}$$

6) What value of the inductor in problem 3 would make the circuit critically damped?

$$\frac{R}{2L} = \frac{1}{\sqrt{LC}} \Rightarrow \frac{50}{2L} = \frac{1}{\sqrt{L \cdot 50 \mu\text{F}}} \Rightarrow \frac{L}{25} = \frac{\sqrt{L \cdot 50 \mu\text{F}}}{1}$$

$$\frac{L^2}{625} = L \cdot 50 \mu\text{F} \Rightarrow L^2 = 12500 \mu\text{F} \cdot L \Rightarrow L = 125 \text{ mH}$$

Part II. Assisted Problem Solving – 2 pts

7) The natural voltage response of a parallel RLC circuit is $v(t) = 75e^{-8000t}(\cos 6000t - 4\sin 6000t)$ Volts, for $t > 0$

If the inductor is 400 mH, find the values of C, R, V_0 , I_0 , and $i_L(t)$.

$$\alpha = +8000 = \frac{1}{2RC}$$

$$\omega_d = 6000 = \sqrt{\omega_0^2 - \alpha^2}, \quad 36 \times 10^6 = \omega_0^2 - 8000^2$$

$$\omega_0 = \sqrt{100 \times 10^6} = 10000 = \frac{1}{\sqrt{LC}}$$

$$LC = \frac{1}{100 \times 10^6}, \quad C = \frac{1}{L(100 \times 10^6)} = \frac{1}{40 \times 10^6} = 25 \text{ nF}$$

n: $\times 10^{-9}$

PLAN

- 1) note that this is underdamped
- 2) compare the equation to the formula for underdamped and notice where different parameters appear and match them up using algebra where needed.

$$\alpha = \frac{1}{2RC} = 8000, \quad R = \frac{1}{2(8000C)} = 2500 \Omega$$

$$V_0 = 75 e^{-8000t} (\cos 0 - 4 \sin 0)$$


$$= 75$$

$$I_0 + I_L(t) : \text{skip !!}$$

Part III. Unassisted Problem Solving – 3 points

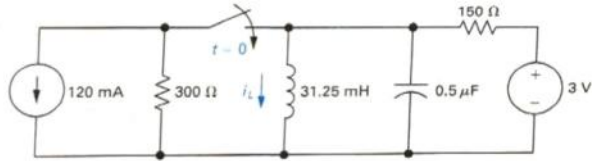
8)

The switch in the circuit has been open a long time before closing at $t = 0$. Find $i_L(t)$ for $t \geq 0$.



Parallel, STEP

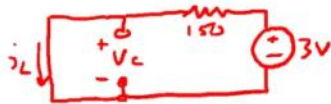1) Circuit at $t = 0^-$ (steady state before switch closes)



$$i_L(0^-) = \frac{3}{150} = .02 \text{ A}$$

$$V_C(0^-) = 0 \text{ V (V across a short)}$$

2) Circuit at $t = 0^+$

V_C stays at 0V

i_L stays at 20 mA


$$\frac{di_L}{dt} = \frac{V_L}{L} = \frac{V_C}{L} = 0 \text{ A/s}$$



0V across 300 ohm \rightarrow 0A through it

3) Circuit at $t = \infty$

$V_C = V_L = V_{300} = 0 \text{ V}$

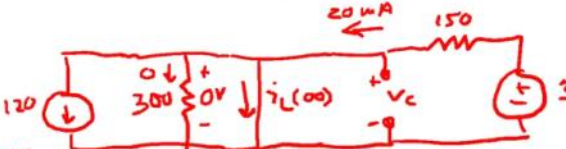

KCL $i_L + 120 = 20, i_L(\infty) = -100 \text{ mA}$

$$3) R_{eq} = 300 \parallel 150 = 100 \Omega$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 100 \cdot .5 \times 10^{-6}} = 10000$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 9000$$

$\alpha > \omega_0 \rightarrow$ OVER DAMPED

$$s_1 = -10000 + \sqrt{10000^2 - 8000^2} = -10000 + 6000 = -4000$$

$$s_2 = -10000 - 6000 = -16000$$

$$4) i_L(0^+) = .02 = I_{\infty} + A_1 + A_2 \rightarrow A_1 + A_2 = .02 + .1 = .12 \text{ A} = 120 \text{ mA}$$

$$\frac{di_L}{dt}(0^+) = 0 = s_1 A_1 + s_2 A_2, -4000 A_1 - 16000 A_2 = 0, A_1 = -4 A_2$$

$$-4 A_2 + A_2 = .12, -3 A_2 = .12, A_2 = -.04 \text{ A} = -40 \text{ mA}$$

$$A_1 = .16 \text{ A} = 160 \text{ mA}$$

$$i_L(t) = -100 + 160 e^{-4000t} - 40 e^{-16000t} \text{ mA}$$