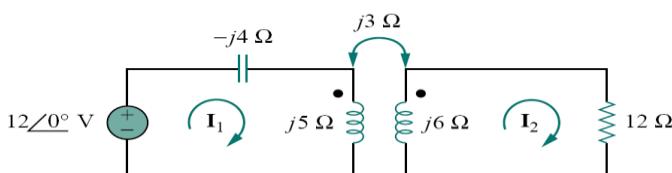


## Linear Transformer “Dot” Rule:


If a current enters the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **positive** at the dotted terminal of the second coil.

Complete the two mesh equations for each circuit:




$$-12 - 4j I_1 + 5j I_1 \text{ _____} = 0$$

$$6j I_2 + 12 I_2 \text{ _____} = 0$$

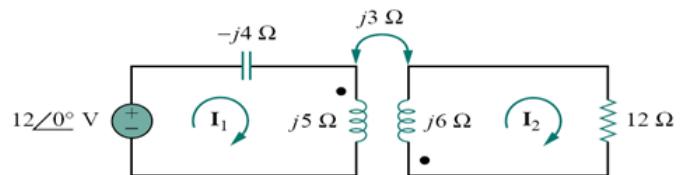


$$-12 - 4j I_1 + 5j I_1 \text{ _____} = 0$$

$$6j I_2 + 12 I_2 \text{ _____} = 0$$

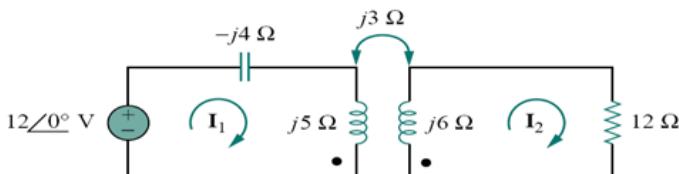


$$-12 - 4j I_1 + 5j I_1 \text{ _____} = 0$$

$$6j I_2 + 12 I_2 \text{ _____} = 0$$

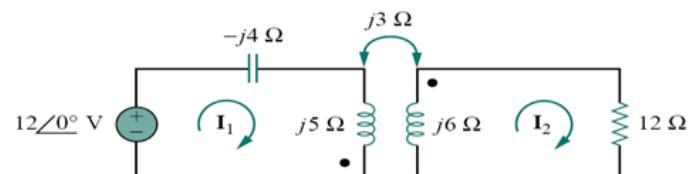


$$-12 - 4j I_1 + 5j I_1 \text{ _____} = 0$$

$$6j I_2 + 12 I_2 \text{ _____} = 0$$

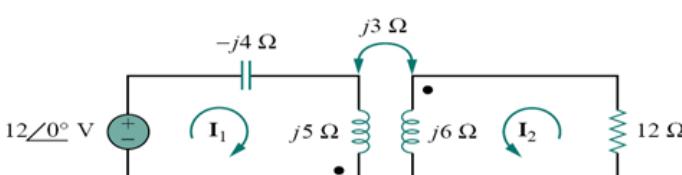

$$-12 - 4j I_1 + 5j I_1 \text{ _____} = 0$$


$$6j I_2 + 12 I_2 \text{ _____} = 0$$

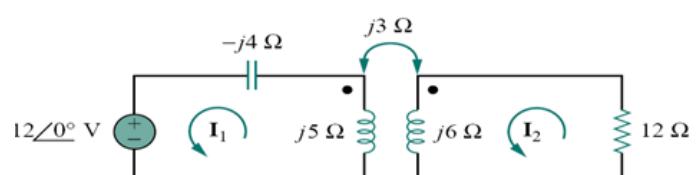


$$12 - 4j I_1 + 5j I_1 \text{ _____} = 0$$

$$6j I_2 + 12 I_2 \text{ _____} = 0$$


## Ideal Transformer “Dot” Rule:

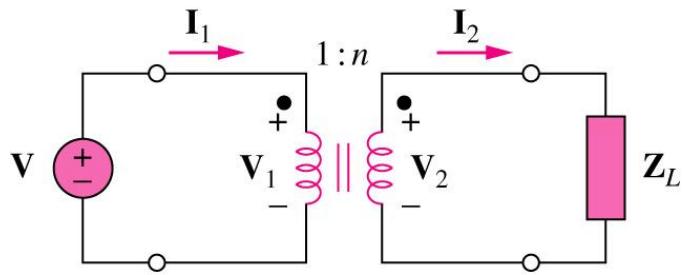

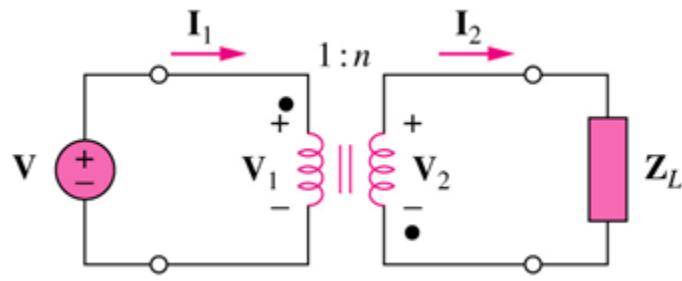
$$\frac{\mathbf{V}_2}{\mathbf{V}_1} = \frac{N_2}{N_1} = n \quad \frac{\mathbf{I}_2}{\mathbf{I}_1} = \frac{N_1}{N_2} = \frac{1}{n}$$


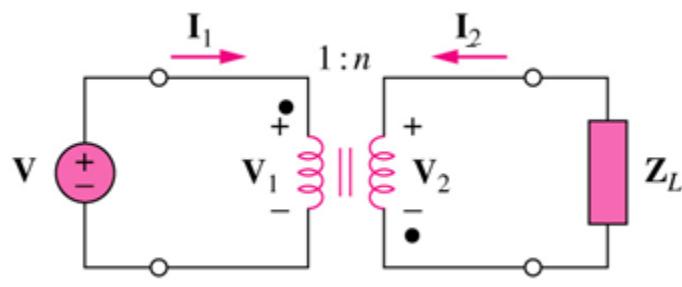
$$\frac{\mathbf{V}_2}{\mathbf{V}_1} = -\frac{N_2}{N_1} = -n \quad \frac{\mathbf{I}_2}{\mathbf{I}_1} = -\frac{N_1}{N_2} = -\frac{1}{n}$$


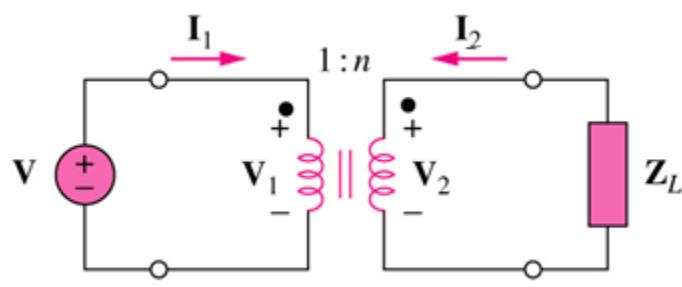
$$\frac{\mathbf{V}_2}{\mathbf{V}_1} = -\frac{N_2}{N_1} = -n \quad \frac{\mathbf{I}_2}{\mathbf{I}_1} = \frac{N_1}{N_2} = \frac{1}{n}$$



$$\frac{\mathbf{V}_2}{\mathbf{V}_1} = \frac{N_2}{N_1} = n \quad \frac{\mathbf{I}_2}{\mathbf{I}_1} = -\frac{N_1}{N_2} = -\frac{1}{n}$$