

EE2003

Circuit Theory

Chapter 13

Magnetically Coupled Circuits

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Magnetically Coupled Circuit

Chapter 13

13.1 What is a transformer?

13.2 Mutual Inductance

13.3 Energy in a Coupled Circuit

13.4 Linear Transformers

13.5 Ideal Transformers


13.6 Applications

13.1 What is a transformer? (1)

- It is an electrical device designed on the basis of the concept of magnetic coupling
- It uses magnetically coupled coils to transfer energy from one circuit to another
- It is the key circuit elements for stepping up or stepping down ac voltages or currents, impedance matching, isolation, etc.

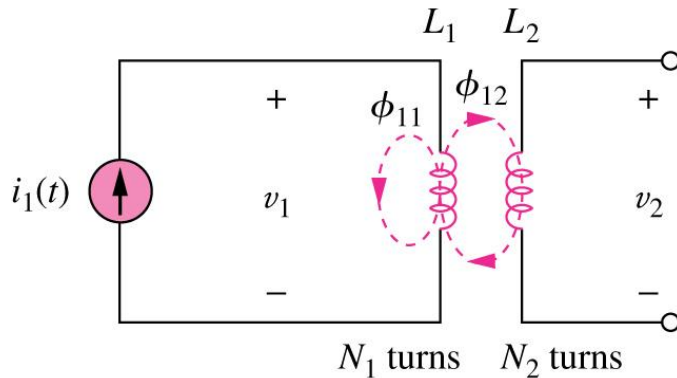
13.2 Mutual Inductance (1)

- It is the ability of one inductor to induce a voltage across a neighboring inductor, measured in henrys (H).



$$v_2 = M_{21} \frac{di_1}{dt}$$

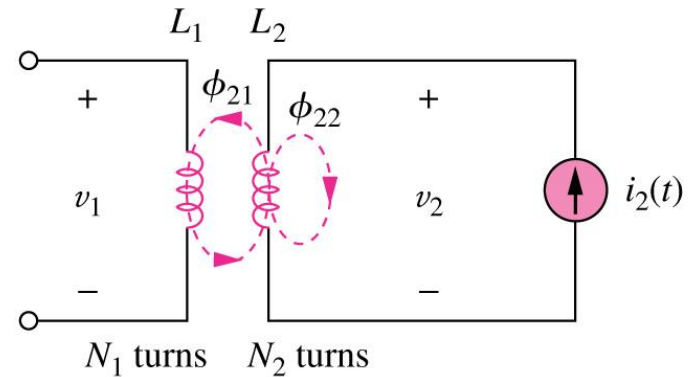The open-circuit mutual voltage across coil 2



$$v_1 = M_{12} \frac{di_2}{dt}$$

The open-circuit mutual voltage across coil 1

13.2 Mutual Inductance (2)

- If a current enters the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is positive at the dotted terminal of the second coil.


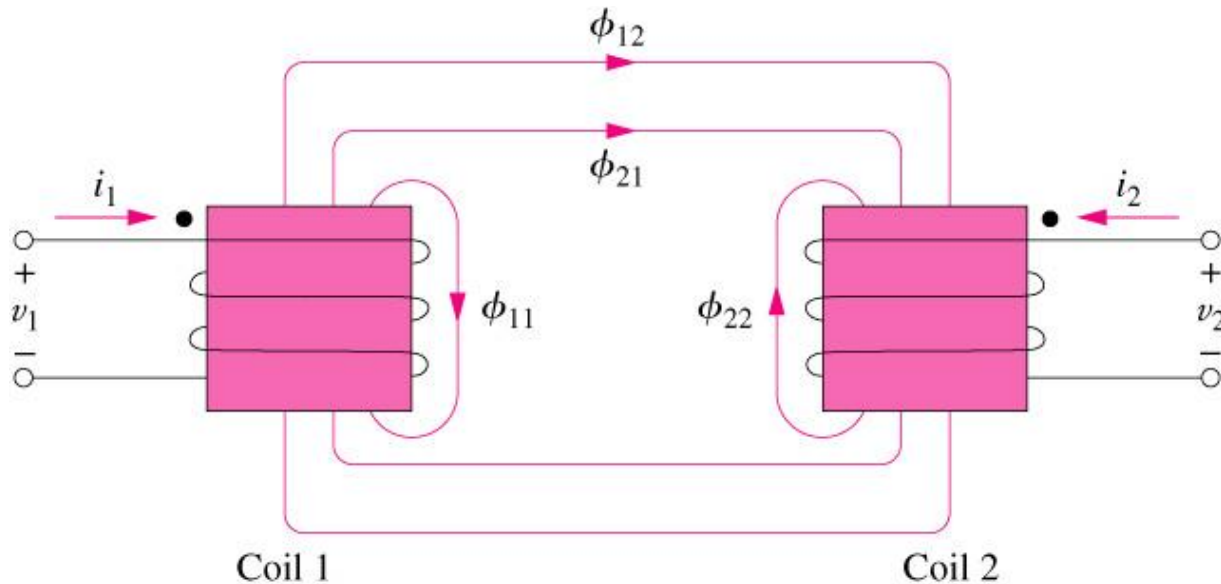
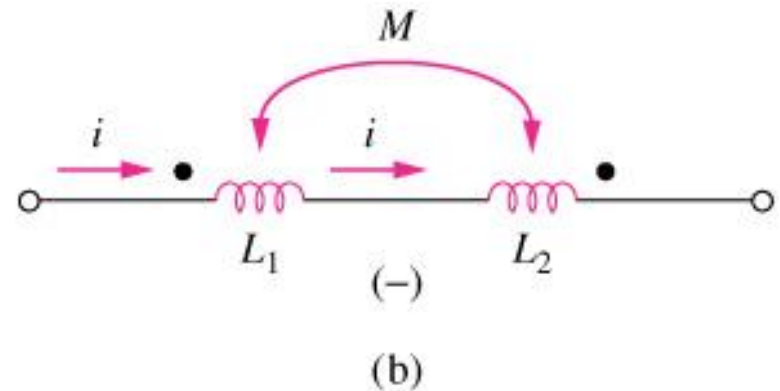


Illustration of the dot convention.

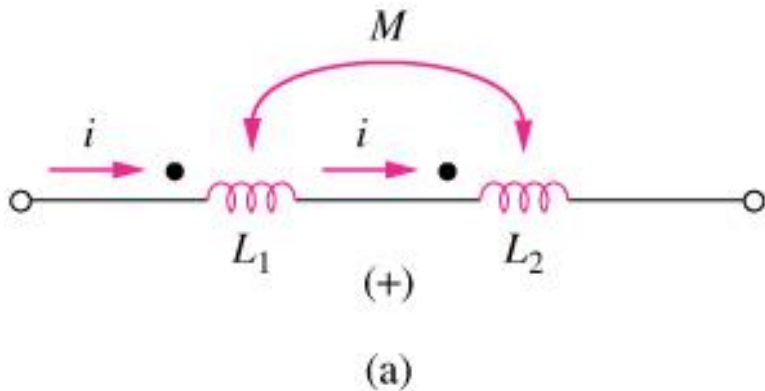13.2 Mutual Inductance (3)

Dot convention for coils in series; the sign indicates the polarity of the mutual voltage; (a) series-aiding connection, (b) series-opposing connection.




$$L = L_1 + L_2 + 2M$$

(series - aiding connection)


$$L = L_1 + L_2 - 2M$$

(series - opposing connection)

13.2 Mutual Inductance (4)

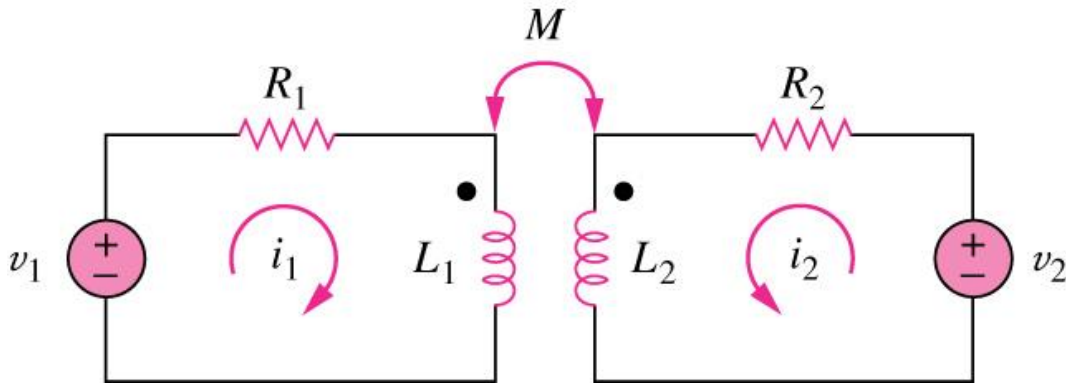

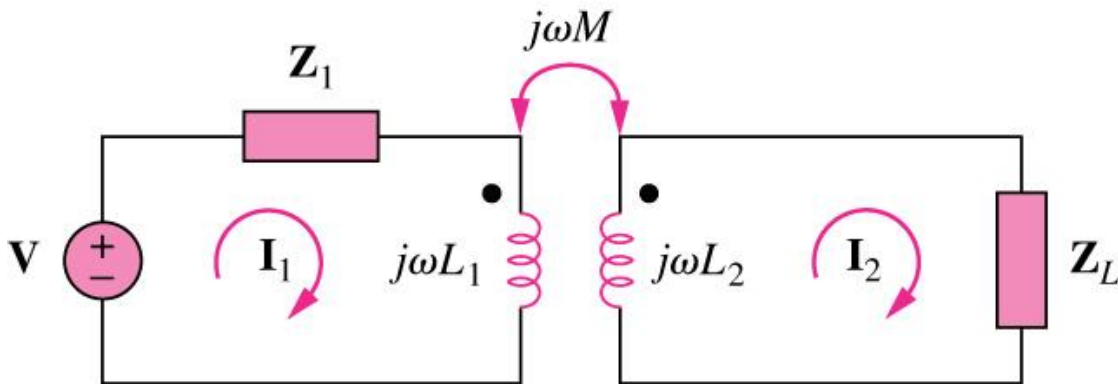Time-domain
analysis of a circuit
containing coupled
coils.




Frequency-domain
analysis of a circuit
containing coupled
coils

13.2 Mutual Inductance (5)

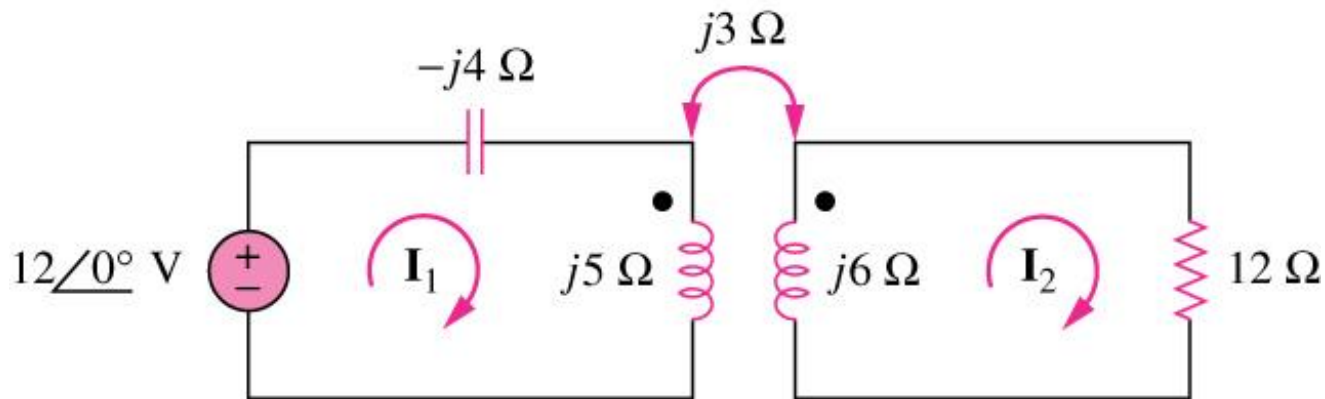Example 1


Calculate the phasor currents I_1 and I_2 in the circuit shown below.



Ans: $I_1 = 13.01 \angle -49.39^\circ \text{ A}$; $I_2 = 2.91 \angle 14.04^\circ \text{ A}$

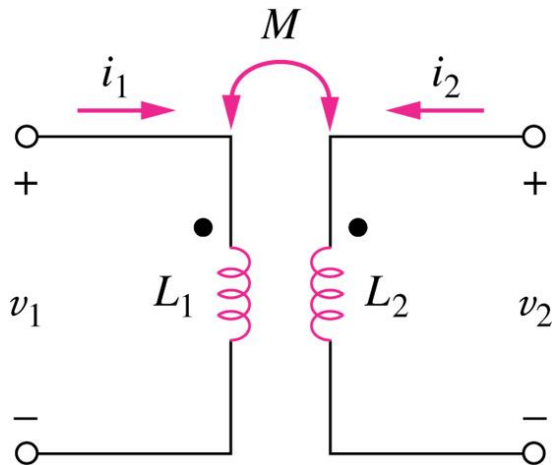13.3 Energy in a Coupled Circuit (1)

- The coupling coefficient, k , is a measure of the magnetic coupling between two coils; $0 \leq k \leq 1$.



$$M = k \sqrt{L_1 L_2}$$


- The instantaneous energy stored in the circuit is given by

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M I_1 I_2$$

13.3 Energy in a Coupled Circuit (2)

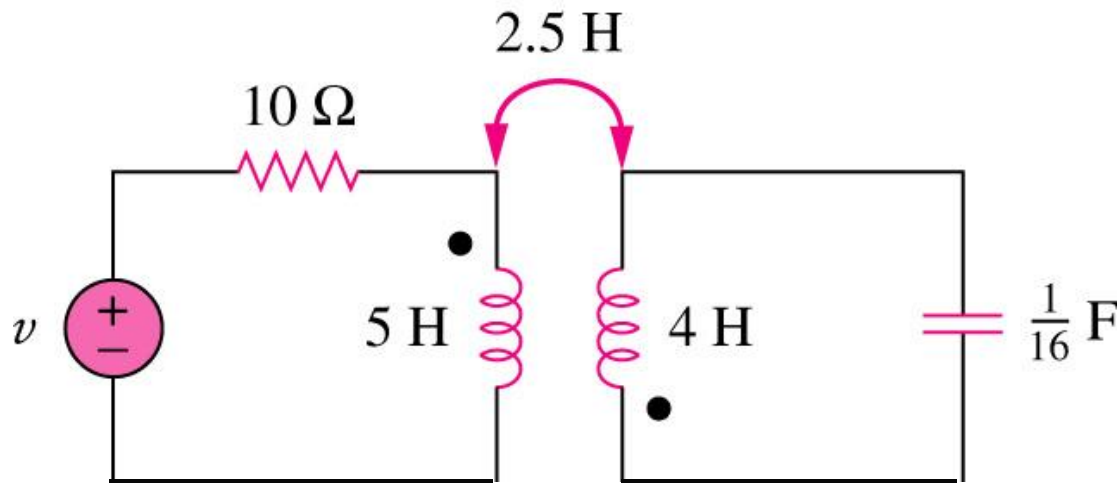Example 2


Consider the circuit below. Determine the coupling coefficient. Calculate the energy stored in the coupled inductors at time $t = 1\text{ s}$ if $v = 60\cos(4t + 30^\circ)\text{ V}$.



*Refer to in-class illustration, textbook Ans: $k=0.56$; $w(1)=20.73\text{ J}$

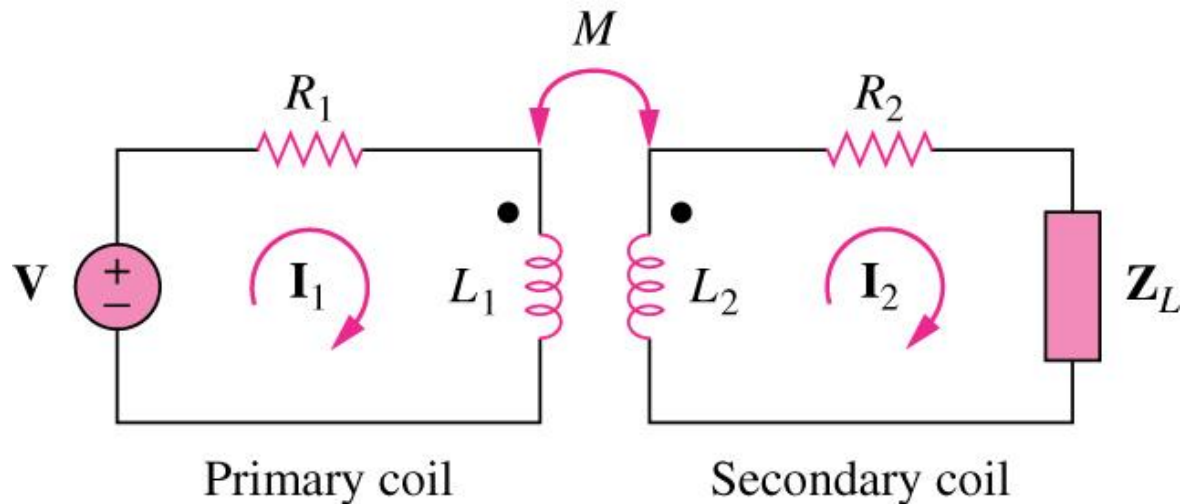13.4 Linear Transformer (1)

- It is generally a four-terminal device comprising two (or more) magnetically coupled coils




$$Z_{\text{in}} = \frac{V}{I_1} = R_1 + j\omega L_1 + Z_R, \quad Z_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L} \text{ is reflected impedance}$$

13.4 Linear Transformer (2)

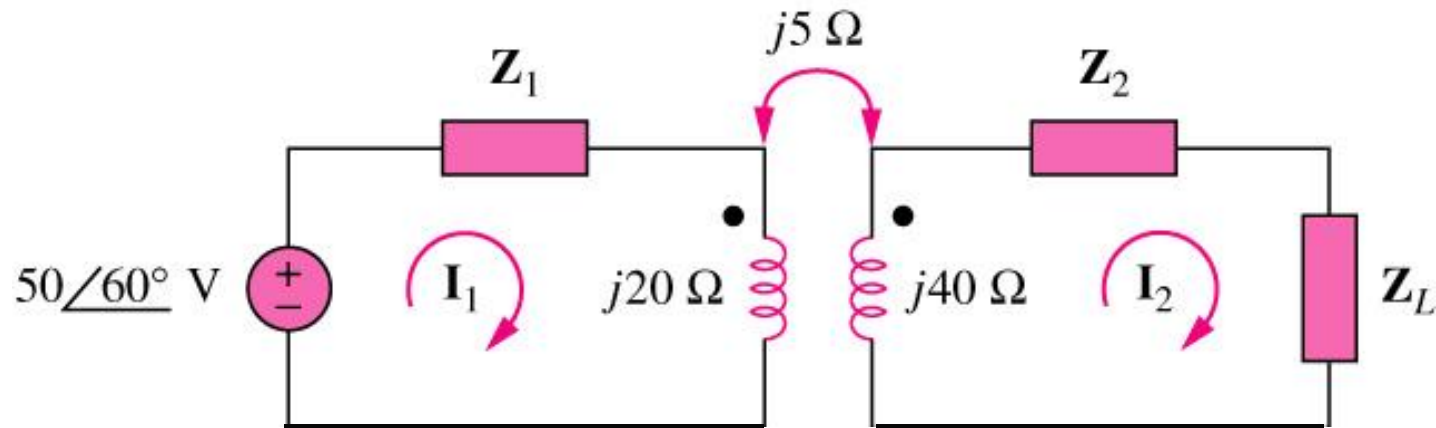Example 3

In the circuit below, calculate the input impedance and current I_1 . Take $Z_1=60-j100\Omega$, $Z_2=30+j40\Omega$, and $Z_L=80+j60\Omega$.




Ans: $Z_{in} = 100.14\angle -53.1^\circ\Omega$; $I_1 = 0.5\angle 113.1^\circ\text{A}$


*Refer to in-class illustration, textbook

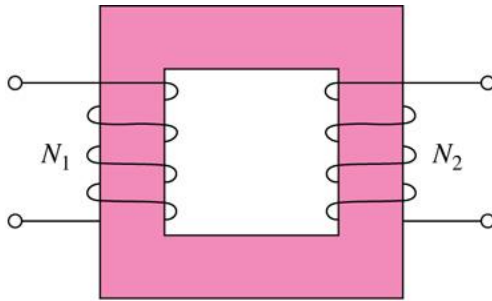13.5 Ideal Transformer (1)

- An ideal transformer is a unity-coupled, lossless transformer in which the primary and secondary coils have infinite self-inductances.




(a)

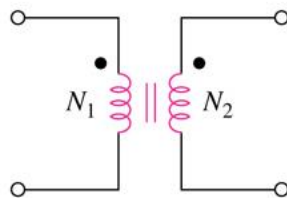

(b)

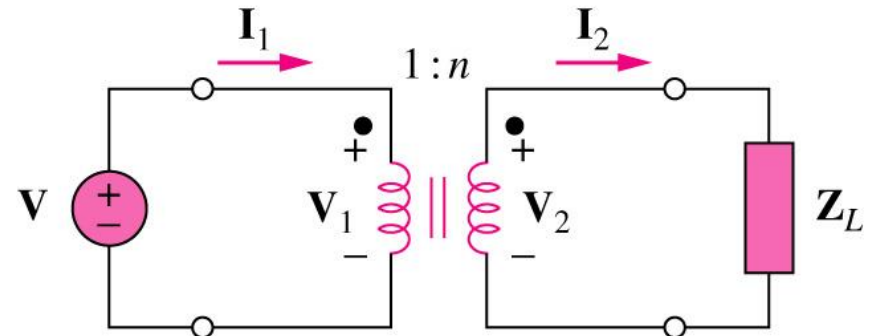- (a) **Ideal Transformer**
(b) **Circuit symbol**



$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n \quad \frac{I_2}{I_1} = \frac{N_1}{N_2} = \frac{1}{n}$$

- $V_2 > V_1 \rightarrow$ step-up transformer**
 $V_2 < V_1 \rightarrow$ step-down transformer

Example 4

An ideal transformer is rated at 2400/120V, 9.6 kVA, and has 50 turns on the secondary side.

Calculate:


- (a) the turns ratio,
- (b) the number of turns on the primary side, and
- (c) the current ratings for the primary and secondary windings.

Ans:

- (a) This is a step-down transformer, $n=0.05$**
- (b) $N_1 = 1000$ turns**
- (c) $I_1 = 4A$ and $I_2 = 80A$**

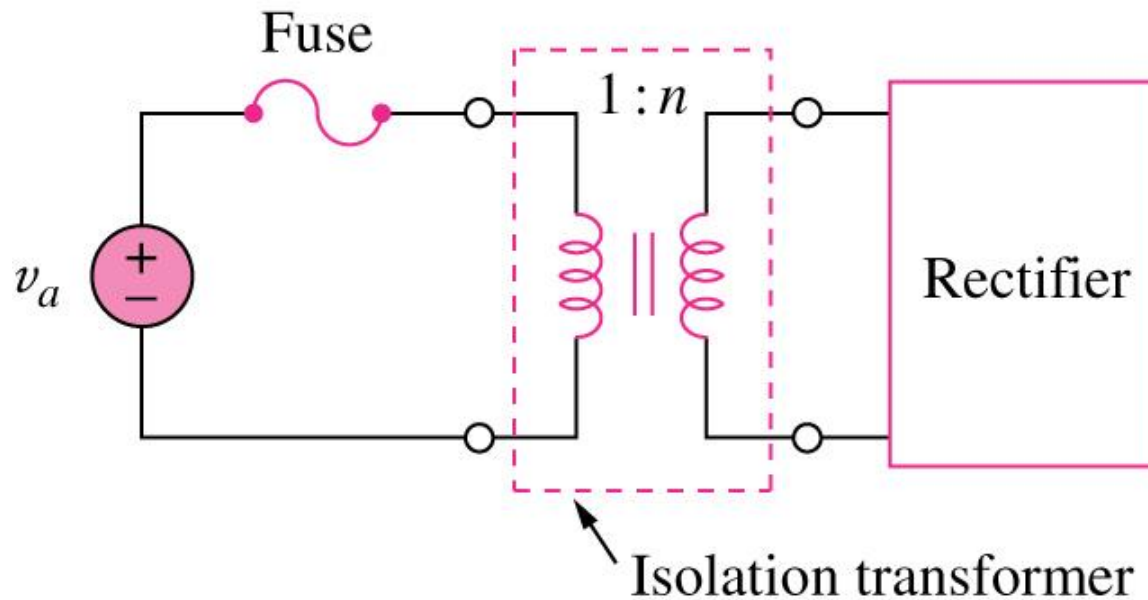
13.6 Applications (1)

- Transformer as an Isolation Device to isolate ac supply from a rectifier



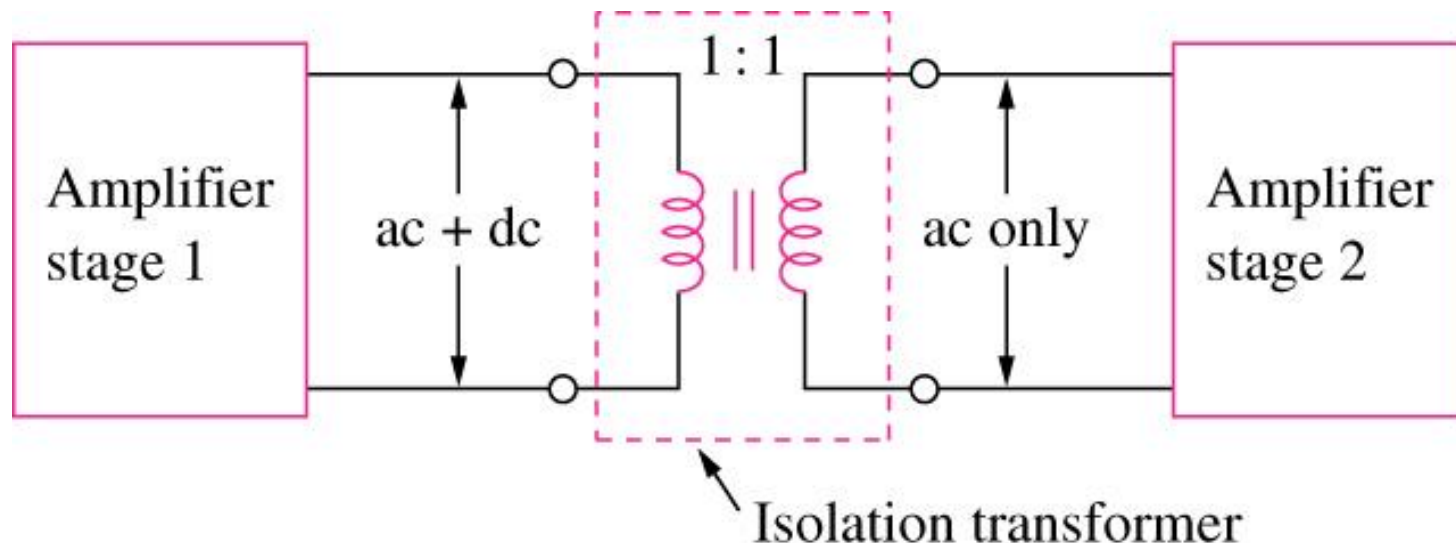13.6 Applications (2)



- Transformer as an Isolation Device to isolate dc between two amplifier stages.



13.6 Applications (3)

- Transformer as a Matching Device

Using an ideal transformer to match the speaker to the amplifier

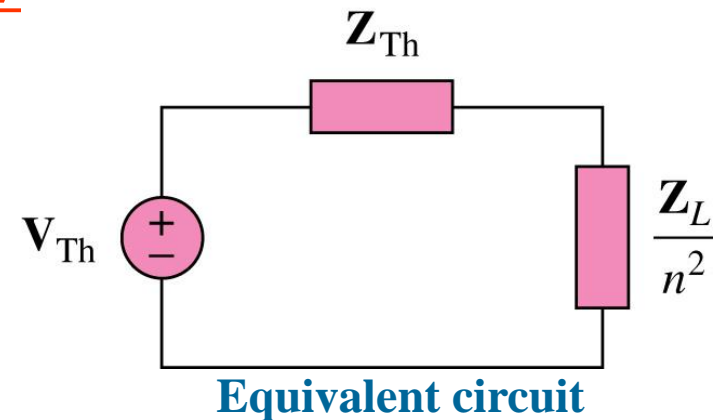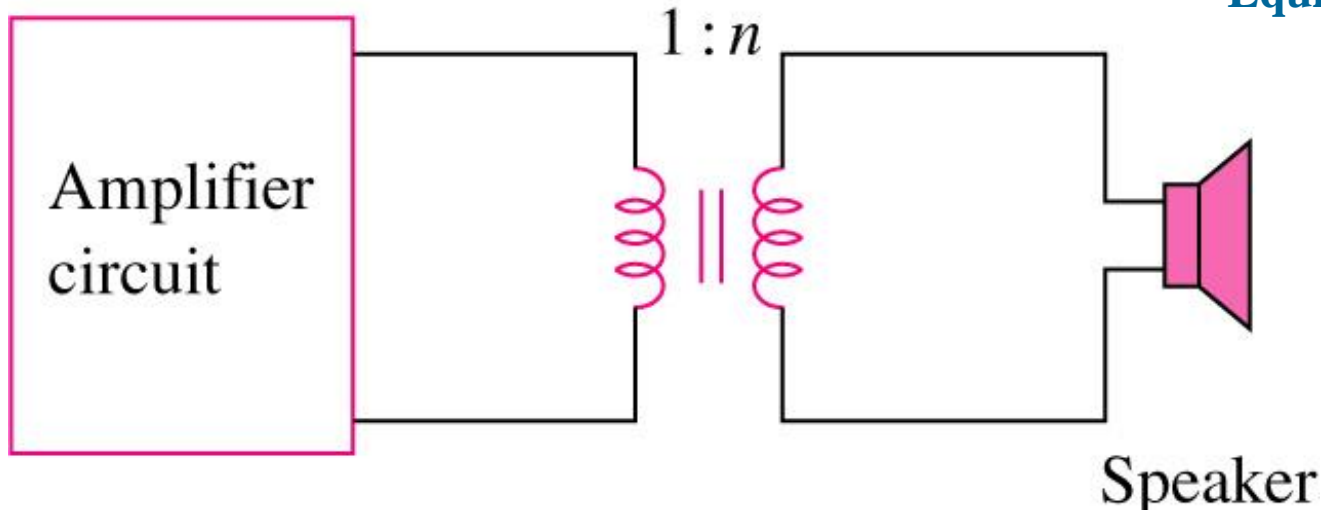


Example 5

Calculate the turns ratio of an ideal transformer required to match a 100Ω load to a source with internal impedance of $2.5\text{k}\Omega$. Find the load voltage when the source voltage is 30V .

Ans: $n = 0.2$; $V_L = 3\text{V}$

13.6 Applications (5)

- A typical power distribution system

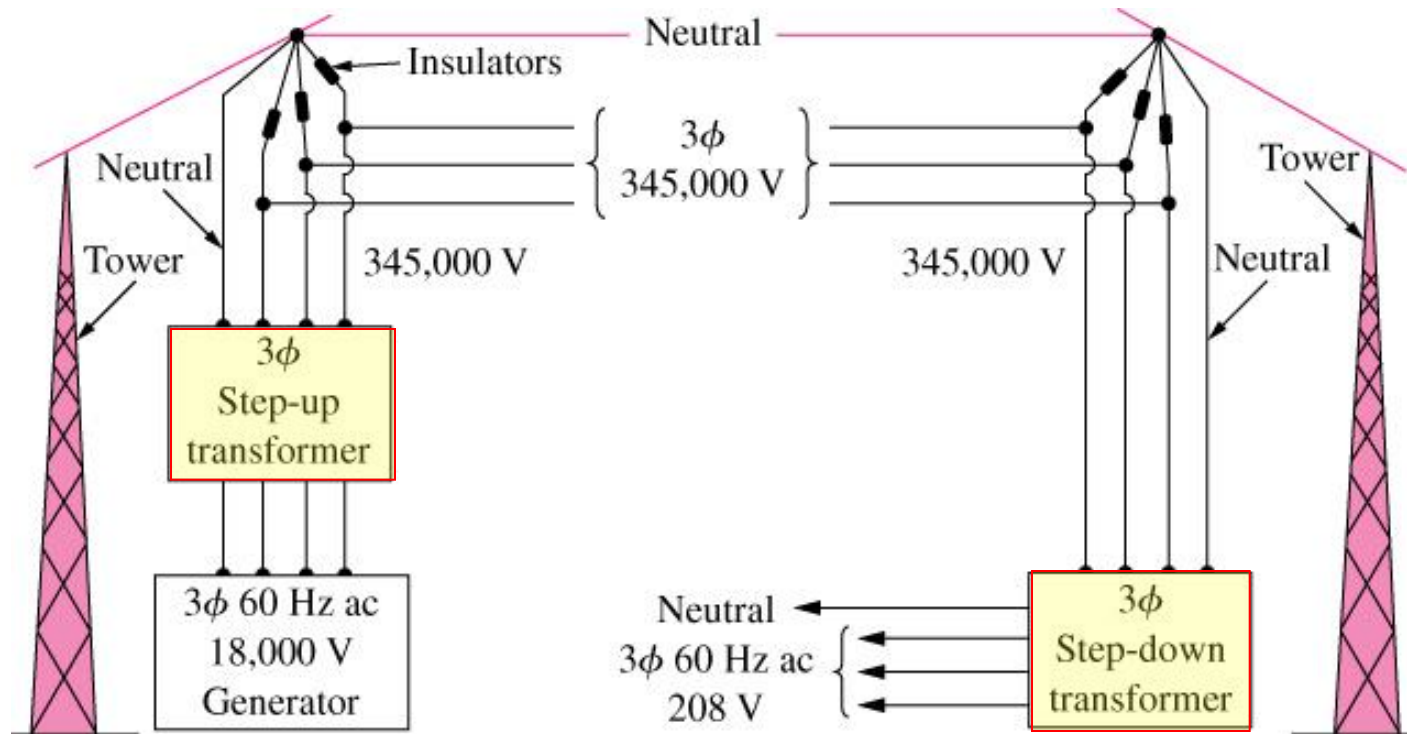

Handouts

Example 4

An ideal transformer is rated at 2400/120V, 9.6 kVA, and has 50 turns on the secondary side.

Calculate:

- (a) the turns ratio,
- (b) the number of turns on the primary side, and
- (c) the current ratings for the primary and secondary windings.

Ans:

- (a) This is a step-down transformer, $n=0.05$**
- (b) $N_1 = 1000$ turns**
- (c) $I_1 = 4A$ and $I_2 = 80A$**

Example 5

Calculate the turns ratio of an ideal transformer required to match a 100Ω load to a source with internal impedance of $2.5\text{k}\Omega$. Find the load voltage when the source voltage is 30V .

Ans: $n = 0.2$; $V_L = 3\text{V}$