

ENGR12

Chapter 2 Basic Laws

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Basic Laws - Chapter 2

2.1 Ohm's Law.

2.2 Nodes, Branches, and Loops.

2.3 Kirchhoff's Laws.

2.4 Series Resistors and Voltage Division.

2.5 Parallel Resistors and Current Division.

2.6 Wye-Delta Transformations.


2.1 Ohms Law (1)

- Ohm's law states that the voltage across a resistor is directly proportional to the current I flowing through the resistor.
- Mathematical expression for Ohm's Law is as follows:

$$v = iR = (2)(10) = \underline{\underline{20V}}$$

- Two extreme possible values of R : **0 (zero)** and **∞ (infinite)** are related with two basic circuit concepts: **short circuit** and **open circuit**.

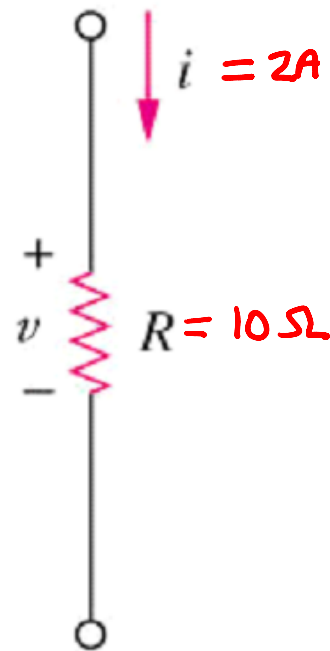if $R=0$, $v = iR = 0$ for all i (short)
if $R=\infty$, $i = \frac{v}{R} = 0$ for all v (open)



2.1 Ohms Law (2)


- Conductance is the ability of an element to conduct electric current; it is the reciprocal of resistance R and is measured in mhos or siemens.

$$G = \frac{1}{R} = \frac{i}{v}$$

-if $R = 10 \text{ k}\Omega$

$$G = \frac{1}{R} = .0001 \text{ }\Omega^{-1} \text{ or } .0001 \text{ S}$$

- The power dissipated by a resistor:

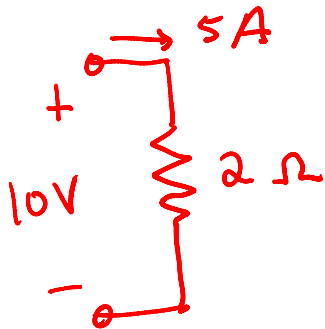


$$p = \underbrace{v}_i i = i^2 R = \frac{v^2}{R}$$

$$= (10)5 = (5^2)(2) = \frac{10^2}{2} = 50 \text{ W}$$

Always
Positive
for Resistors

Find Currents I1 and I2

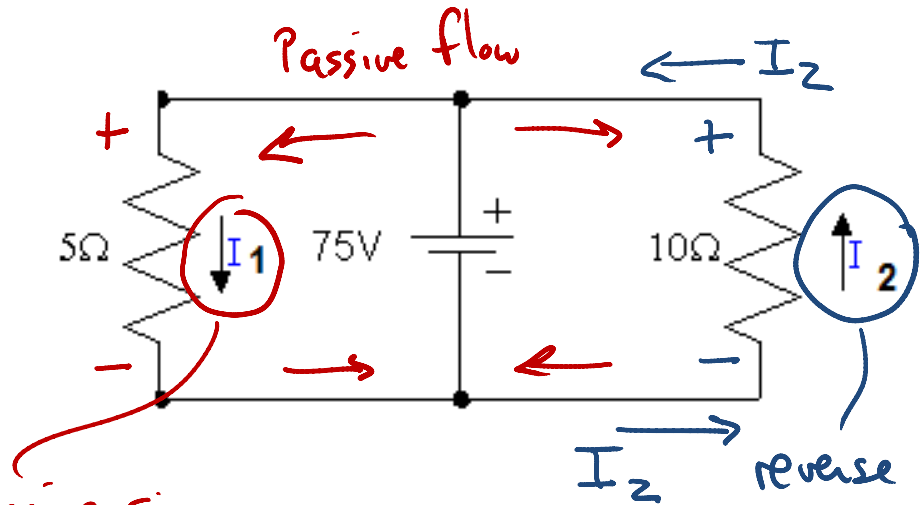

Passive Sign

$$v = iR$$

$$I_1 = \frac{75}{5} = 15A$$

$$I_2 = -\frac{75}{10} = -7.5A$$

reverse of Passive Sign
this is "Active Sign" convention

Ohm's Law
for ASC:
 $v = -iR$

TIP whenever you label i, v on a Resistor use PSC, then $v = iR$

$$i_1 = 15A \quad i_2 = -7.5A$$

Find Power dissipated in each resistor

Passive Sign


$$P_1 = iV = 15(75) = 1125 \text{ W}$$

$P_1 > 0 \rightarrow$ absorbing

Active Sign


$$P_2 = -iV = -(-7.5)(75) = 562.5 \text{ W}$$

$P_2 > 0 \rightarrow$ absorbing

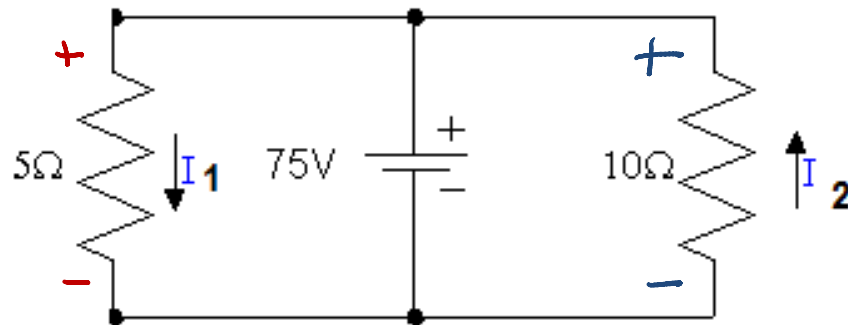

Shorts and Open Circuits


- Short Circuit: $R = 0 \text{ Ohm}$

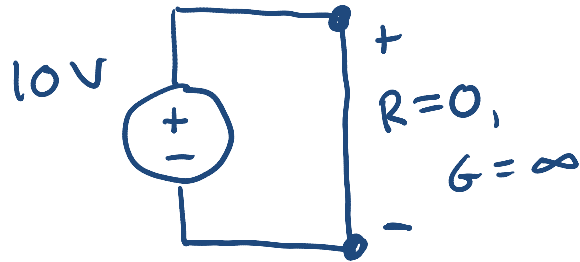

$$I = \frac{V}{R} = \frac{10}{0} = \infty !!$$

In practice, wire gets very hot
may melt - how fuses work

- Open Circuit: $R = \infty \text{ Ohm}$

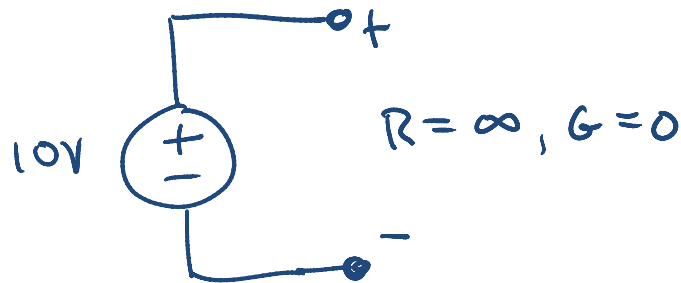

$$I = \frac{V}{R} = \frac{10}{\infty} = 0 !!$$

no current will flow across an
open circuit


2.2 Nodes, Branches and Loops (1)

- A **branch** represents a single element such as a voltage source or a resistor.
- A **node** is the point of connection between two or more branches.
- A **loop** is any closed path in a circuit.
- A network with b branches, n nodes, and l independent loops will satisfy the fundamental theorem of network topology:

$$b = l + n - 1$$

2.2 Nodes, Branches and Loops (2)

Example 1

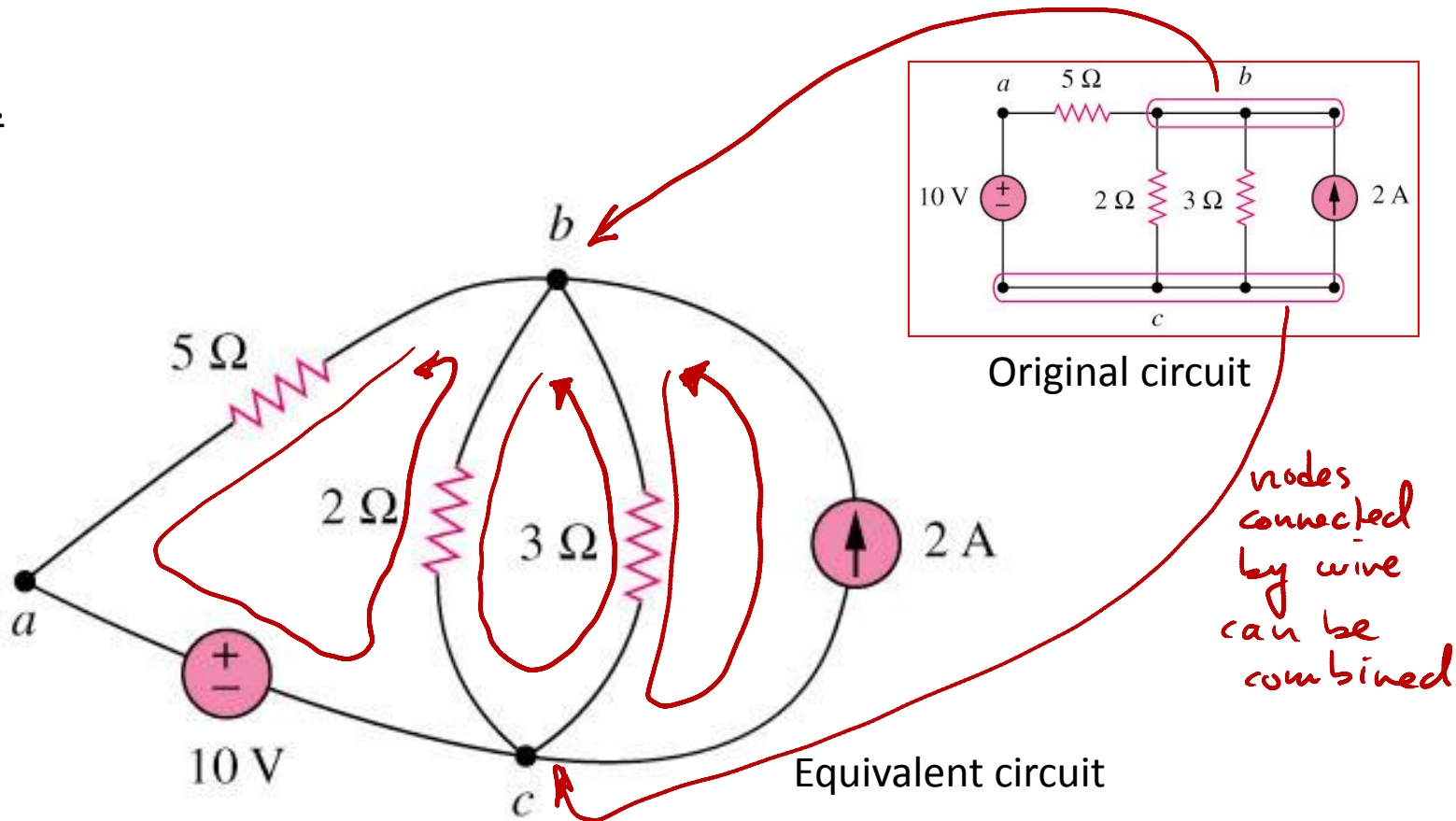


How many branches, nodes and loops are there?

$$5 = 3 + 3 - 1$$

2.2 Nodes, Branches and Loops (3)

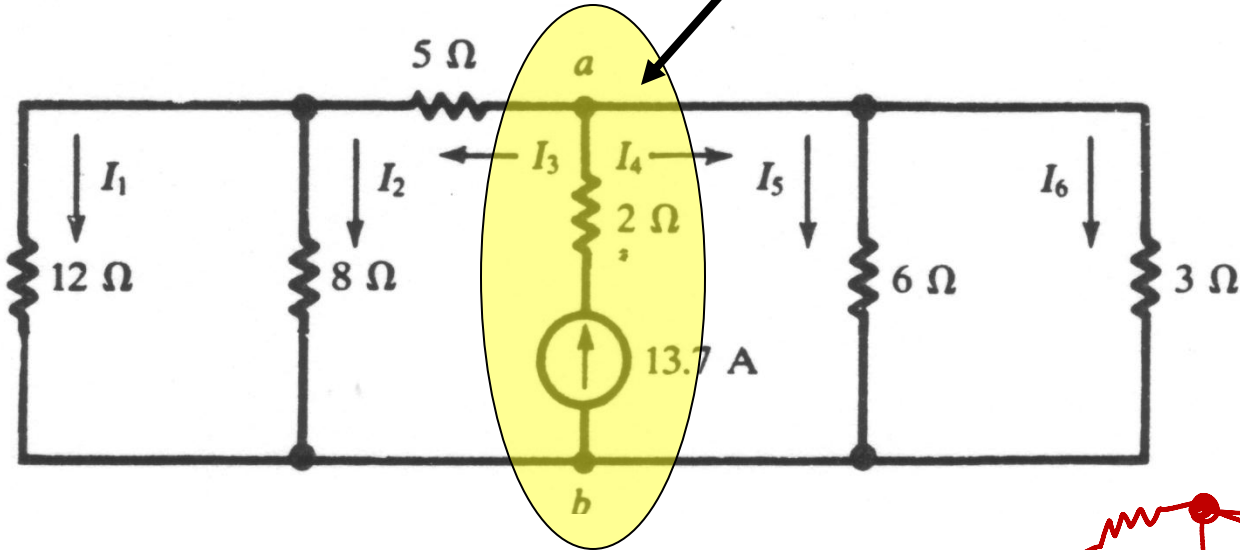Example 2


Should we consider it as one branch or two branches? *either way is fine*



How many branches, nodes and loops are there?



not combined : $7 = 4 + 4 - 1$

combined : $6 = 3 + 4 - 1$

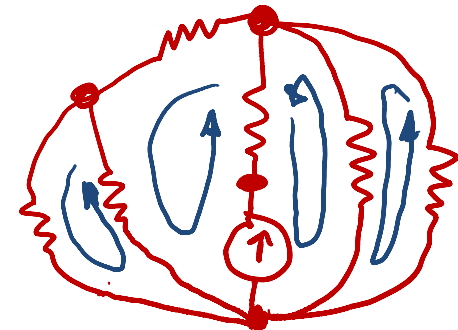

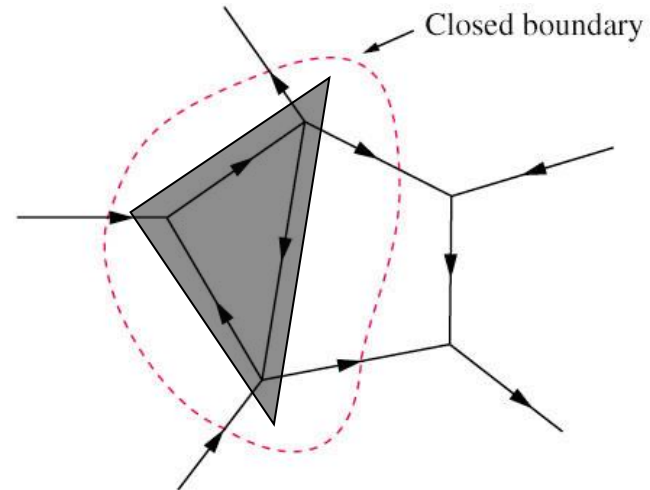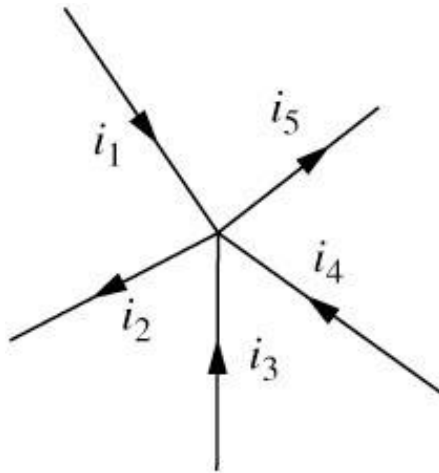2.3 Kirchhoff's Laws (1)

- Kirchhoff's current law (KCL) states that the algebraic sum of currents entering a node (or a closed boundary) is zero.



Mathematically,


$$\sum_{n=1}^N i_n = 0$$

2.3 Kirchhoff's Laws (2)

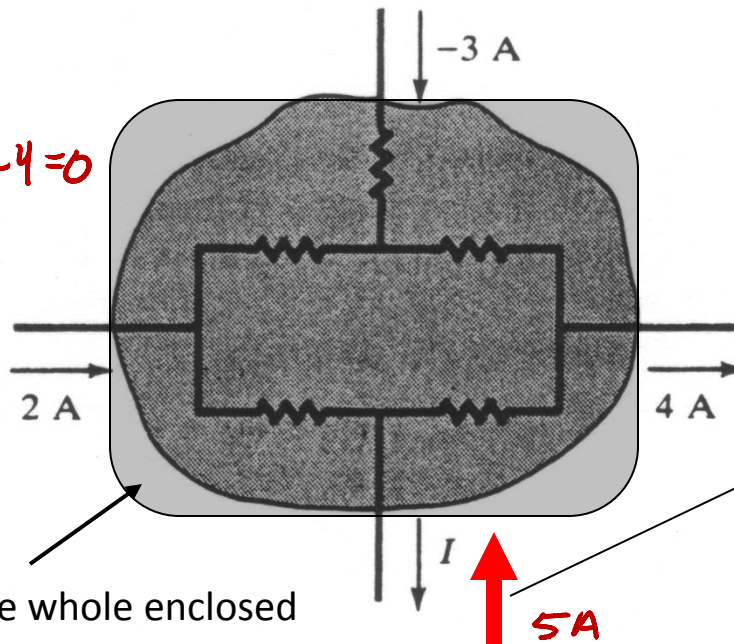Example 4

- Determine the current I for the circuit shown in the figure below.
(Here we choose to use positive for outbound currents)

KCL
 $\sum i_n = 0$
 $I - 2 - (-3) + 4 = 0$
 $I = -5A$



This indicates that the actual current for I is flowing in the opposite direction.

We can consider the whole enclosed area as one "node".

Determine the current through each of the resistors in this circuit.

KCL at A (using + for entering currents)

$$10 - i_1 - 5 = 0$$


$$i_1 = 5 \text{ mA}$$

KCL at B

$$5 + i_2 = 0$$


$$i_2 = -5 \text{ mA}$$

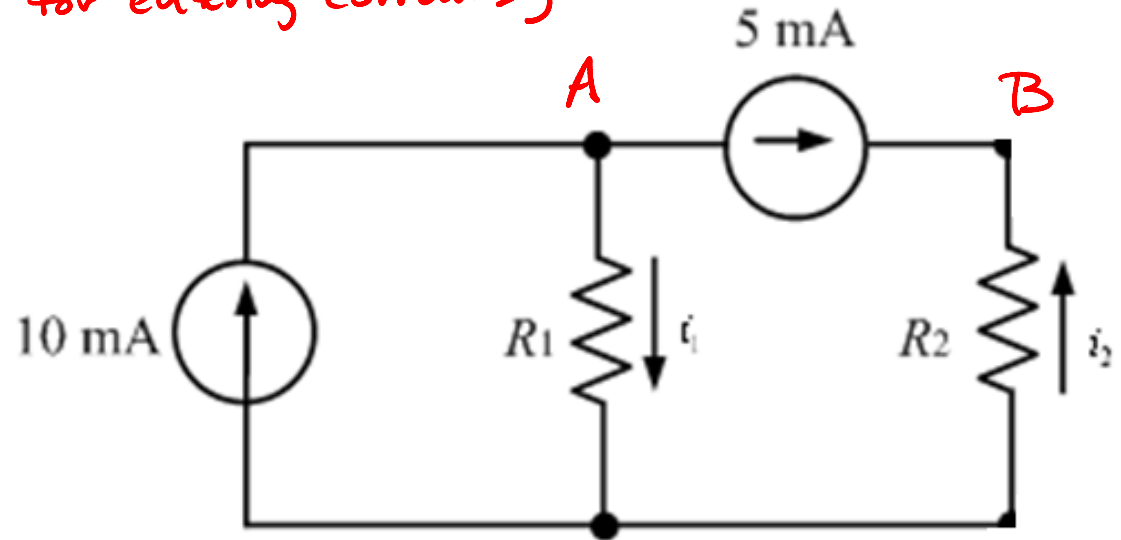→ All components in a branch have same current



$$i_1 = 5 \text{ mA} \quad i_2 = -5 \text{ mA}$$

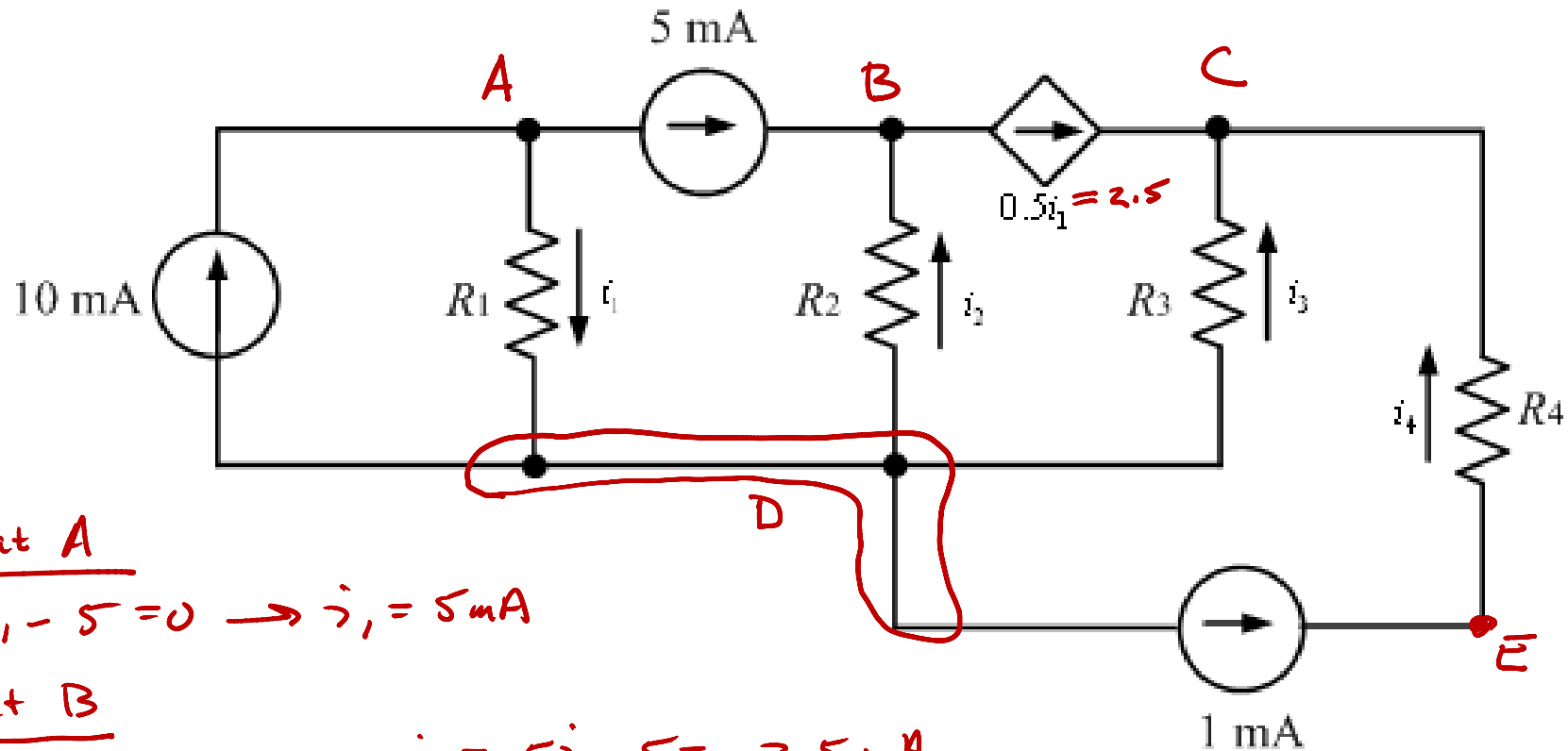Problem 1 Determine the current through each of the resistors in this circuit.



KCL at A

$$10 - i_1 - 5 = 0 \rightarrow i_1 = 5 \text{ mA}$$

KCL at B

$$5 + i_2 - 0.5i_1 = 0 \rightarrow i_2 = 0.5i_1 - 5 = -2.5 \text{ mA}$$

KCL at C

$$2.5 + i_3 + i_4 = 0$$

$$i_3 = -3.5 \text{ mA}$$

KCL at E


$$-i_4 + 1 = 0 \rightarrow i_4 = 1 \text{ mA}$$

$$i_1 = 5 \text{ mA}, \quad i_2 = -2.5 \text{ mA}, \quad i_3 = -3.5 \text{ mA}, \quad i_4 = 1 \text{ mA}$$

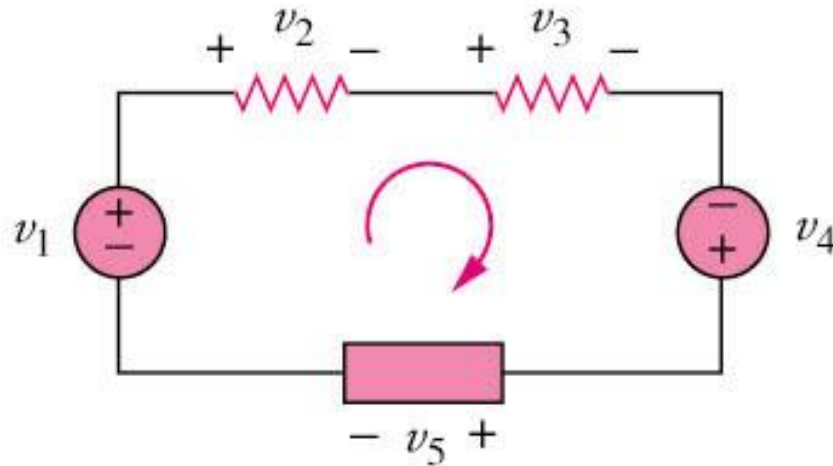2.3 Kirchhoff's Laws (3)

- Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.

Convention: use first sign you encounter for each element:
use clockwise path (OK to change but be consistent!)




Mathematically,
$$\sum_{m=1}^M v_n = 0 = -v_1 + v_2 + v_3 - v_4 + v_5$$

2.3 Kirchhoff's Laws (4)

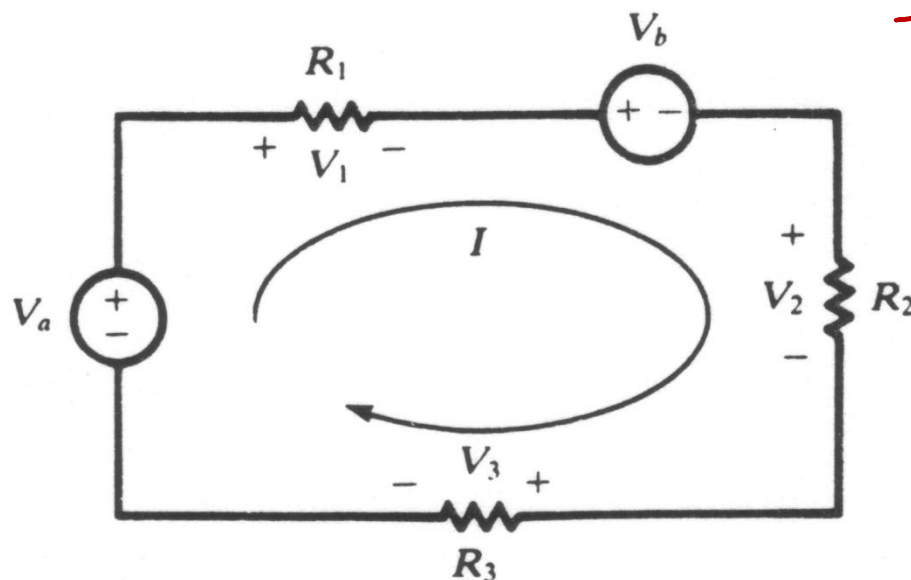Example 5

- Applying the KVL equation for the circuit of the figure below.
(travelling clockwise, and using the 1st sign on each component we encounter along the path)




$$-V_a + V_1 + V_b + V_2 + V_3 = 0$$

Find the voltage across resistor R2.

KVL on outer loop:


$$-10 + 5 + v_2 = 0$$

$$v_2 = 5 \text{ V}$$

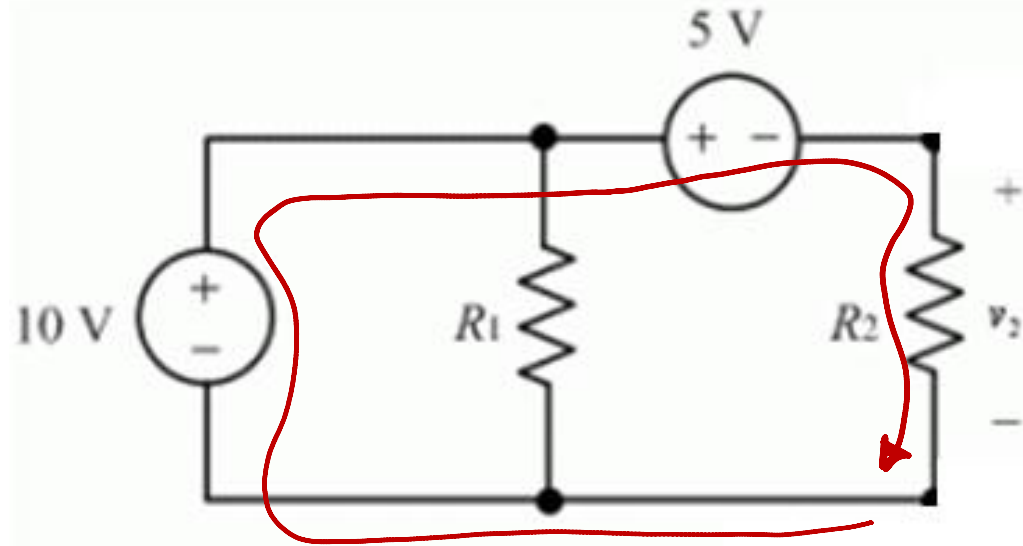

$$v_2 = 5 \text{ V}$$

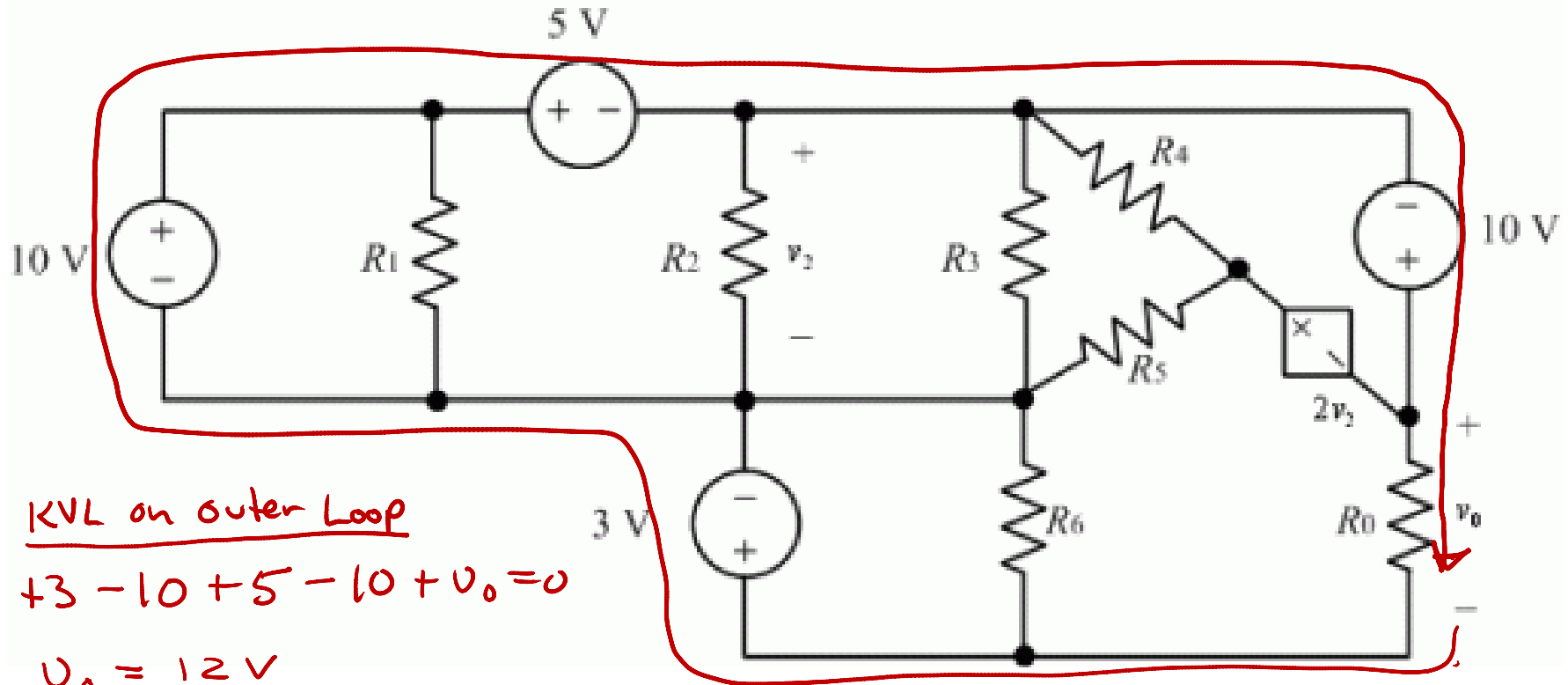Problem 1 Find the voltage across resistor R_0 .



KVL on outer Loop

$$+3 - 10 + 5 - 10 + v_0 = 0$$


$$\underline{v_0 = 12V}$$

KCL and KVL in one circuit

Find the value of V_0 .

Plan

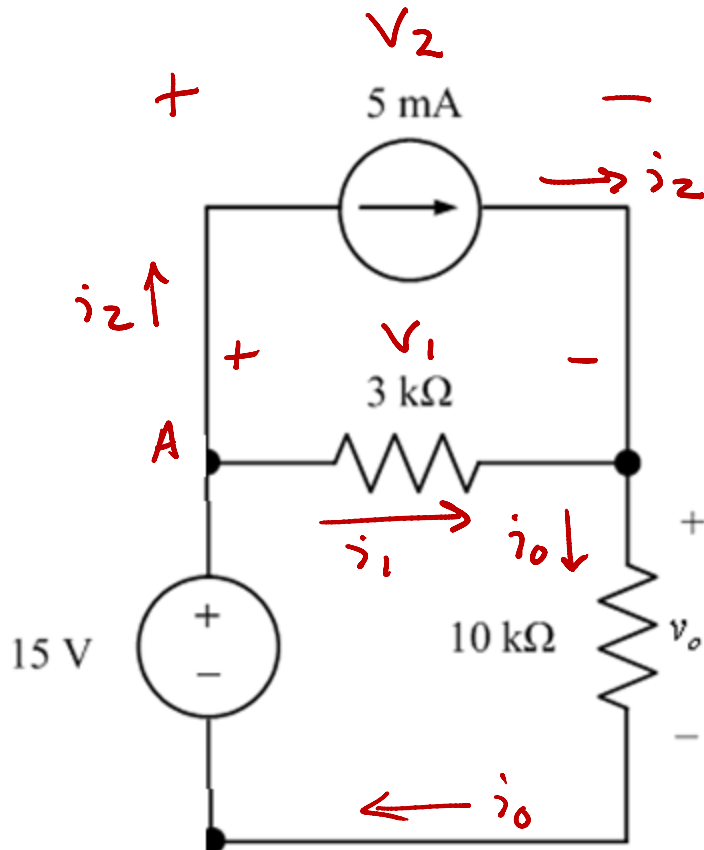- 1) Label all unknowns (use Psc!)
- 2) Write all OL, KVL, KCL equations
- 3) Solve system of eqns



① OL

a) $V_1 = 3 i_1$

b) $V_0 = 10 i_0$

② KVL

a) $-V_1 + V_2 = 0 \rightarrow V_1 = V_2$

b) $-15 + V_1 + V_0 = 0$

c) $-15 + V_2 + V_0 = 0$

③ KCL

a) $i_0 - i_1 - i_2 = 0 \rightarrow i_0 - i_1 = 5$


b) $i_2 - 5 = 0 \rightarrow i_2 = 5$

④ Substitute 1a + 1b
into 2b

$$\begin{array}{l} 10 i_0 + 3 i_1 = 15 \\ i_0 - i_1 = 5 \end{array} \left. \begin{array}{l} \\ \end{array} \right\} \begin{array}{l} 3 \times (3a) + 4 \\ \rightarrow 13 i_0 = 30, i_0 = 2.308 \\ V_0 = 10 i_0 = \underline{\underline{23.1V}} \end{array}$$

$v_0 = 23.1 \text{ V}$

Given i_o is 1A, Find i_1

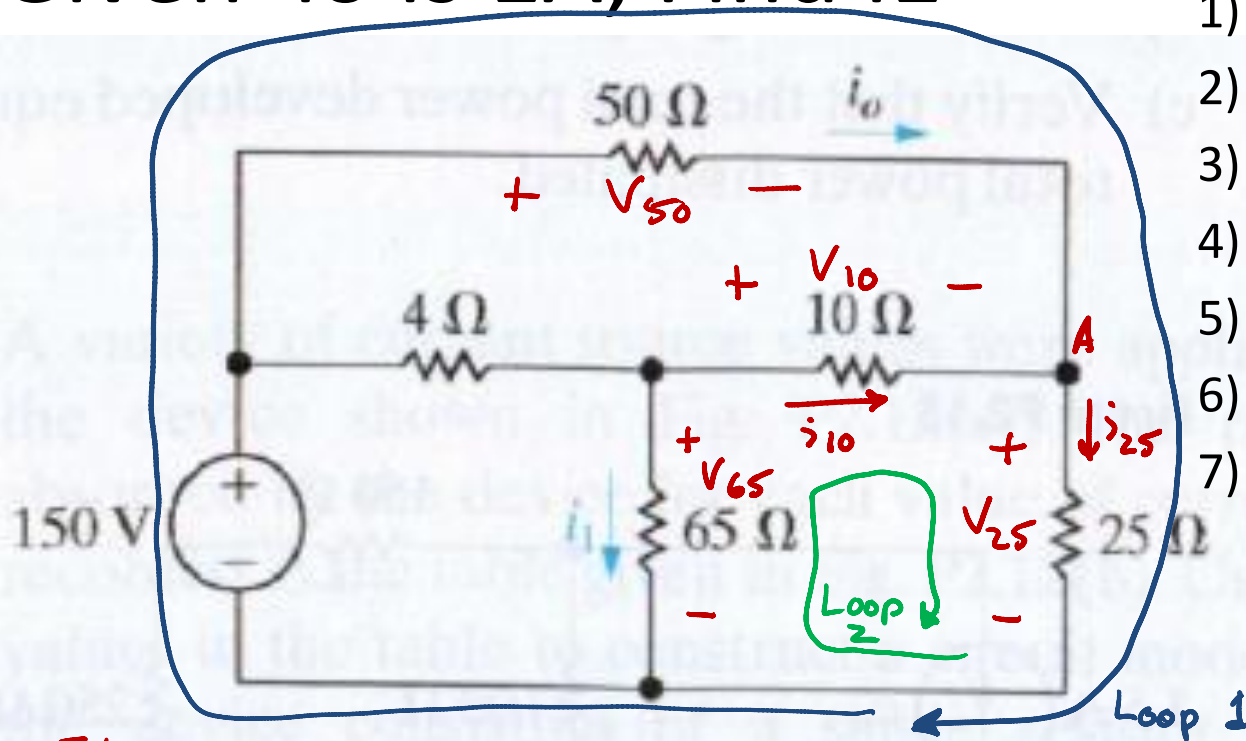

Plan

- 1) Knowing i_o use OL to find V_{50}
- 2) Use KVL to find V_{25} (Loop 1)
- 3) Use OL to find i_{25}
- 4) Use KCL to find i_{10} (Node A)
- 5) Use OL to find V_{10}
- 6) Use KVL to find V_{65} (Loop 2)
- 7) Use OL to find i_1

Step

$$1) V_{50} = 50 i_o = 50V$$

$$2) -150 + V_{50} + V_{25} = 0 \rightarrow V_{25} = 100V$$

$$3) i_{25} = V_{25} / 25 = 4A$$

$$4) i_o + i_{10} - i_{25} = 0 \rightarrow i_{10} = i_{25} - i_o = 3A$$


$$5) V_{10} = i_{10} (10) = 30V$$

$$6) -V_{65} + V_{10} + V_{25} = 0 \rightarrow V_{65} = 30 + 100 = 130V$$

$$7) i_1 = V_{65} / 65\Omega = 2A \quad \checkmark$$

$i_1 = 2A$

Is the interconnection valid?

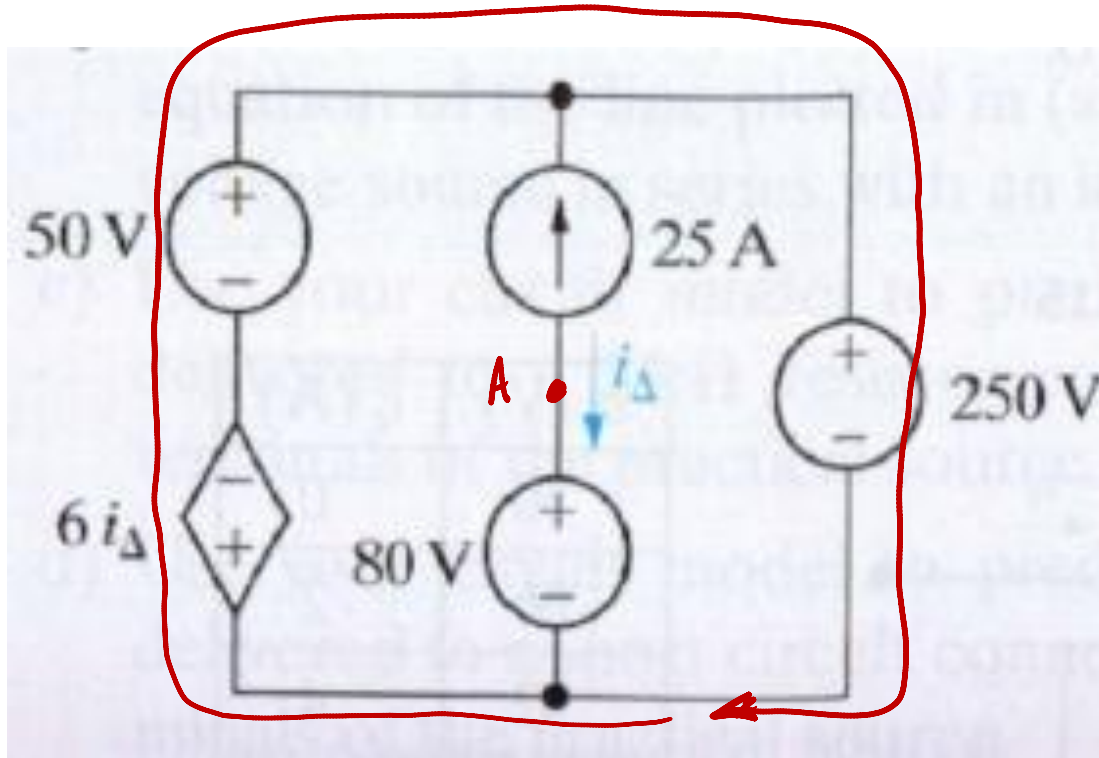

KCL at A

$$i_{\Delta} + 25A = 0 \rightarrow i_{\Delta} = -25A$$


KVL outer loop

$$6i_{\Delta} - 50 + 250 = 0$$

$$i_{\Delta} = \frac{-200}{6} = -33.3 \neq -25$$

\therefore Interconnect NOT valid

Find v if $i_x = -3\text{A}$

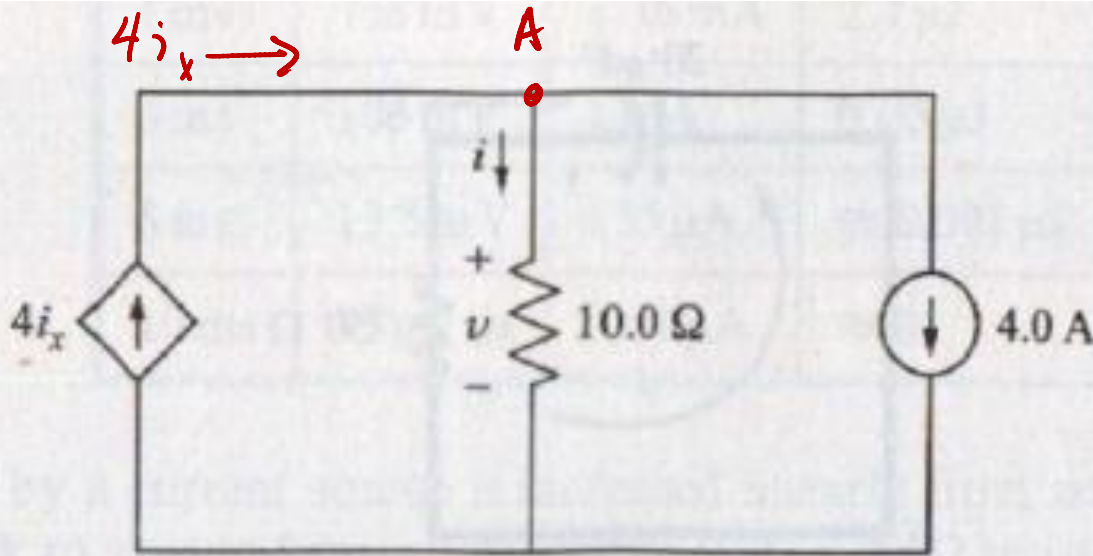

KCL at A

$$4i_x = i + 4$$


$$-12 = i + 4$$

$$i = -16\text{A}$$

OL

$$v = 10i = \underline{\underline{-160\text{V}}}$$

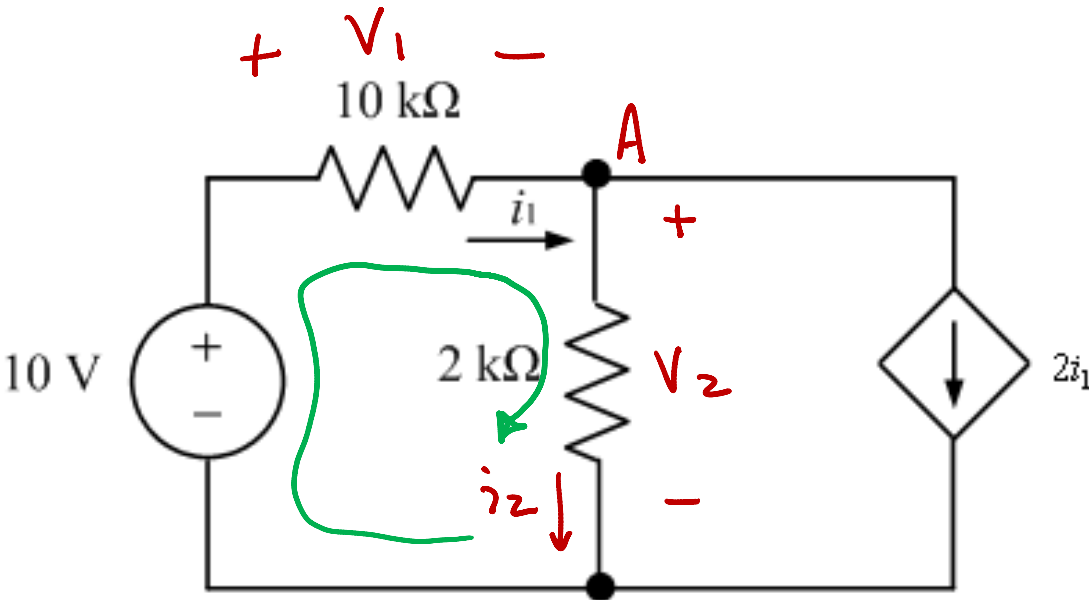Problem 2 Find the current through the 10 kΩ resistor.



KCL at A

$$i_1 = i_2 + 2i_1 \rightarrow i_2 = -i_1$$

KVL

$$-10 + V_1 + V_2 = 0$$

OL

$$V_1 = 10 i_1$$

$$V_2 = 2 i_2 = -2 i_1$$

Solving


$$V_1 + V_2 = 10$$

$$10 i_1 - 2 i_1 = 10$$

$$i_1 = \frac{10}{12} = \underline{\underline{.833 \text{ mA}}}$$

Further Drills on KCL/KVL

Find I

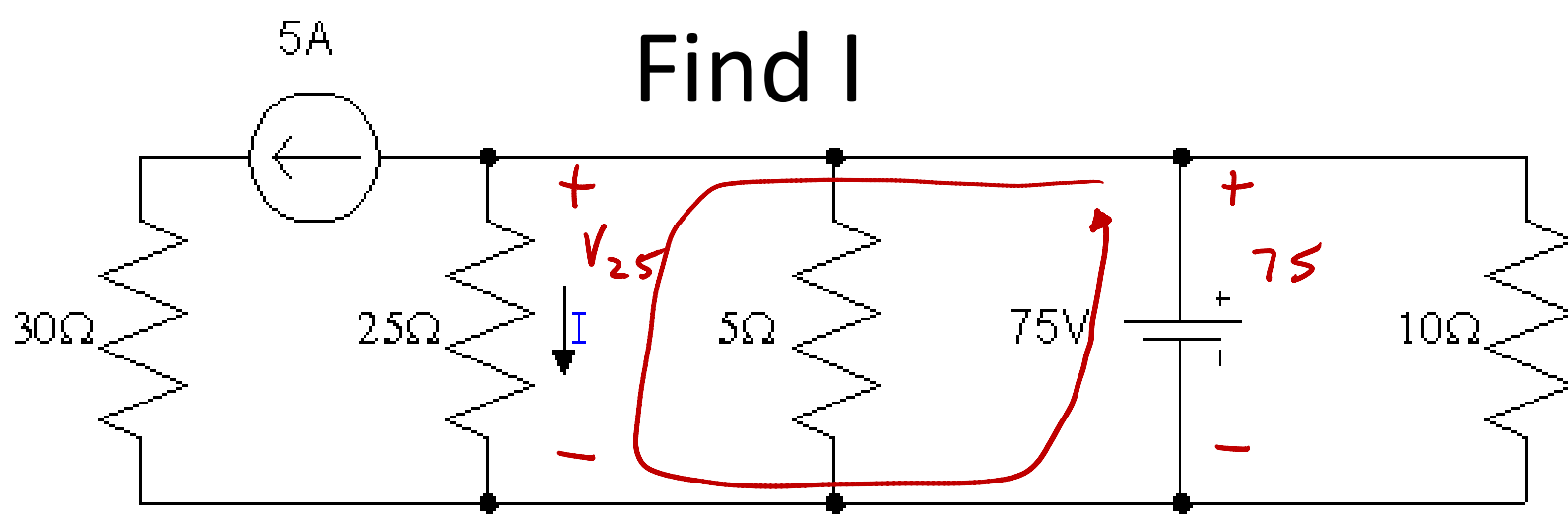


KVL

$$-75 + V_{25} = 0 \rightarrow V_{25} = 75V$$

OL

$$I = \frac{V_{25}}{25} = \underline{\underline{3A}}$$

Find I

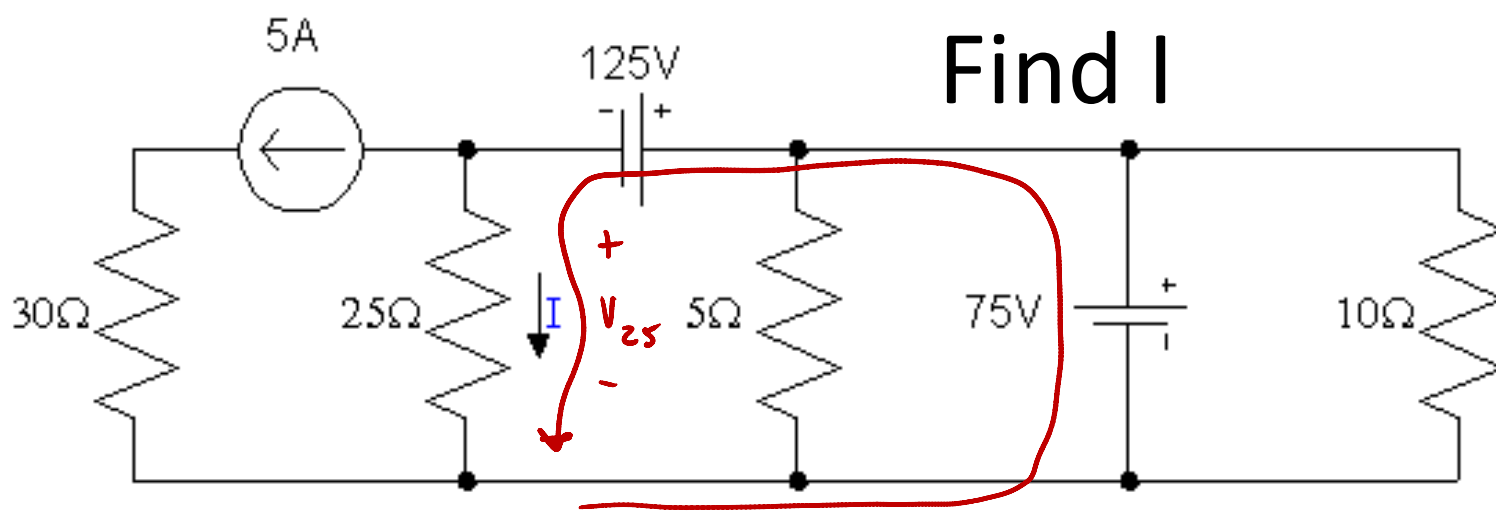

KVL


$$-75 + 125 + V_{25} = 0 \rightarrow V_{25} = -50$$

OL

$$I = \frac{-50}{25} = \underline{\underline{-2A}}$$

Find V

$$\underline{OL}$$
$$V = 10(5) = \underline{\underline{50V}}$$

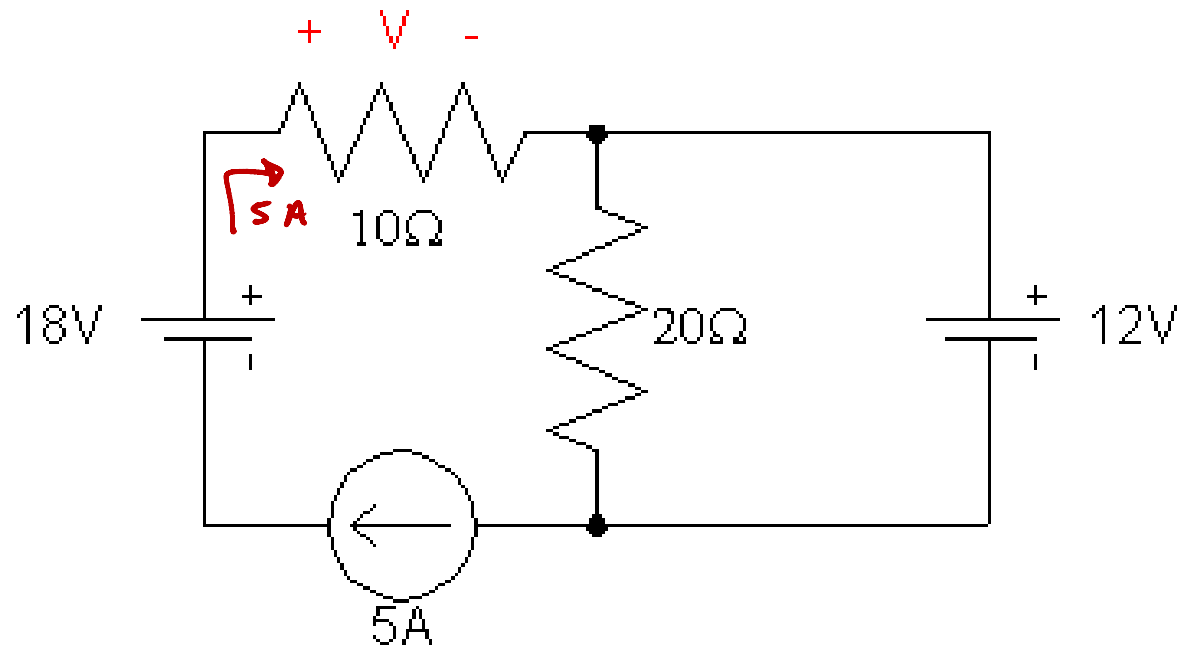


Find V

KCL at SuperNode A

$$-5 + i = 0$$

$$i = 5A$$

$$V = 5(10) = 50V$$

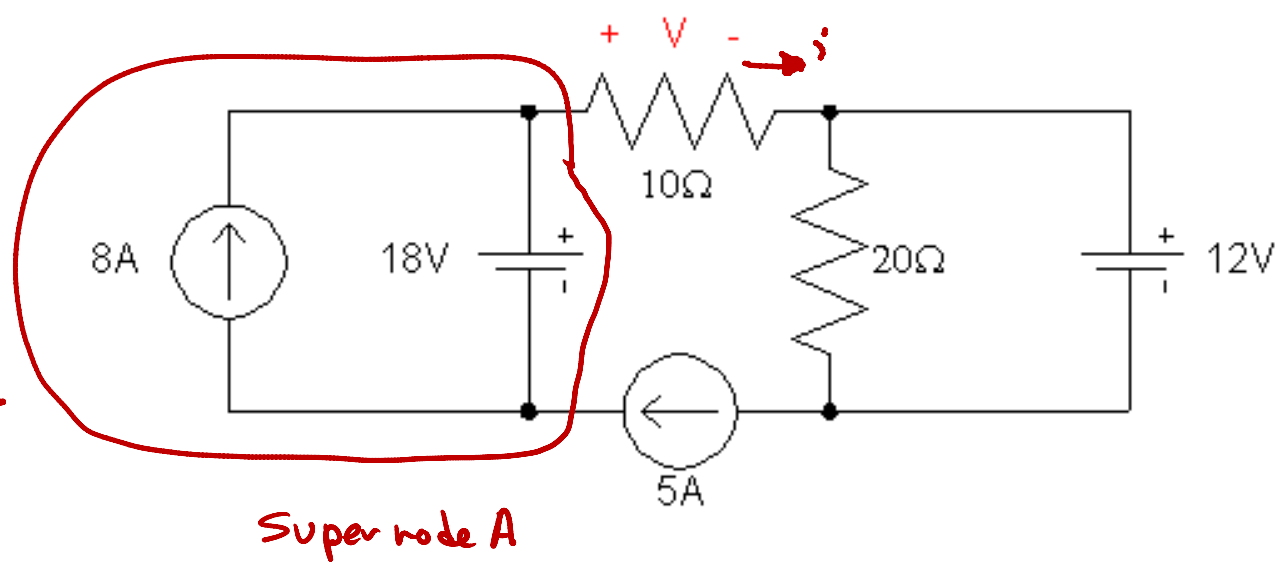


Find V

KCL S.N.A


$$5 - 11 - i = 0$$

$$i = -6A$$

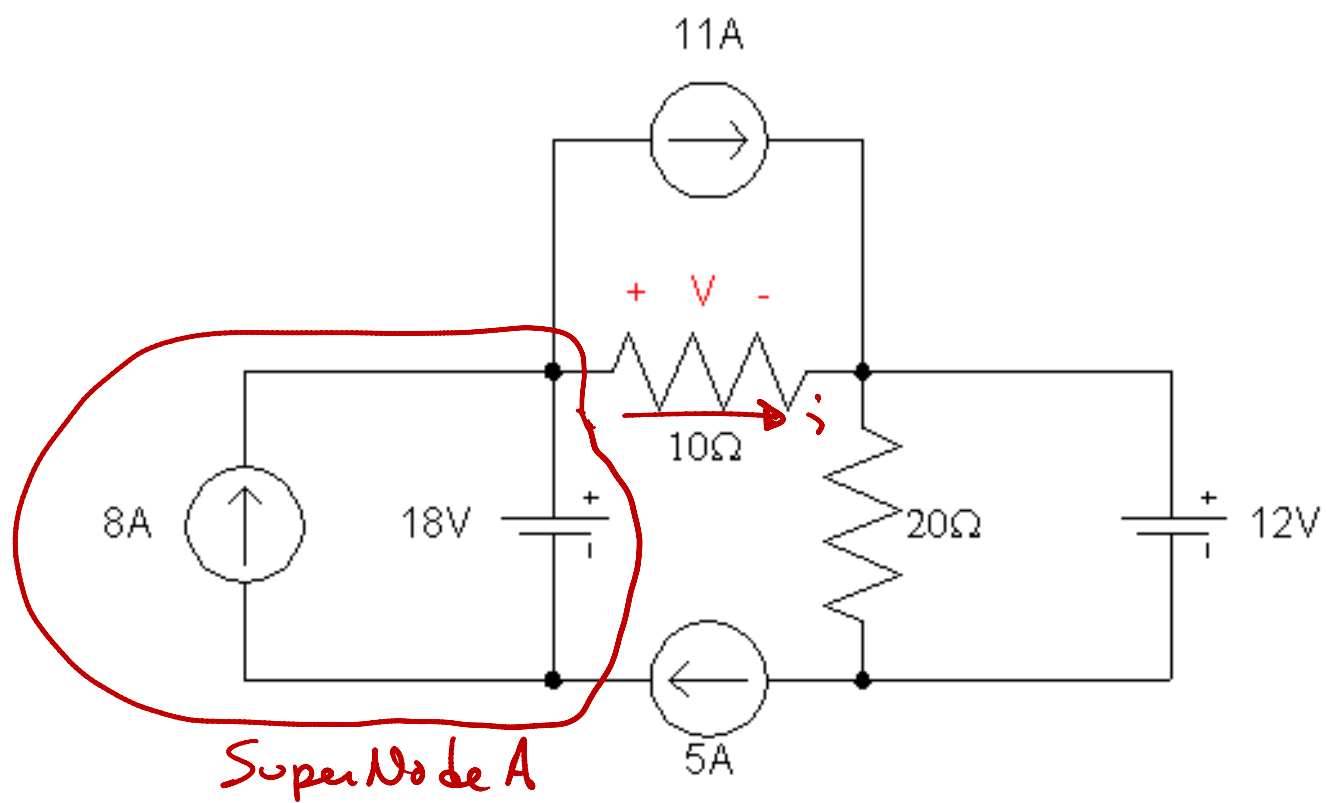
$$V = 10(-6) = \underline{\underline{-60V}}$$



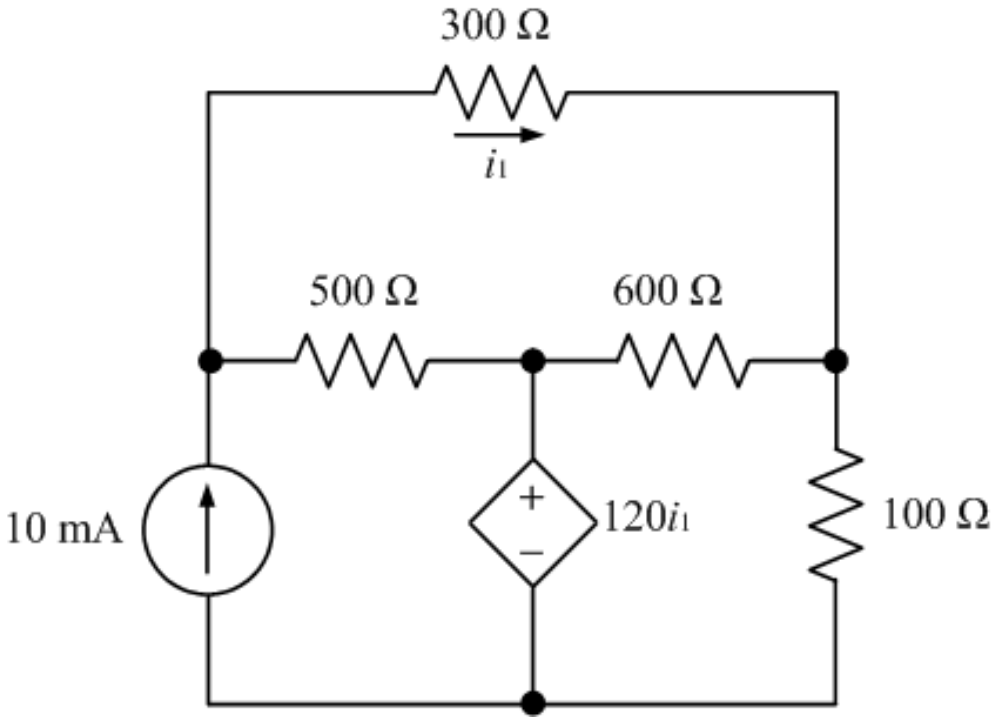Problem 3 Find the current through the $300\ \Omega$ resistor. HARD!!



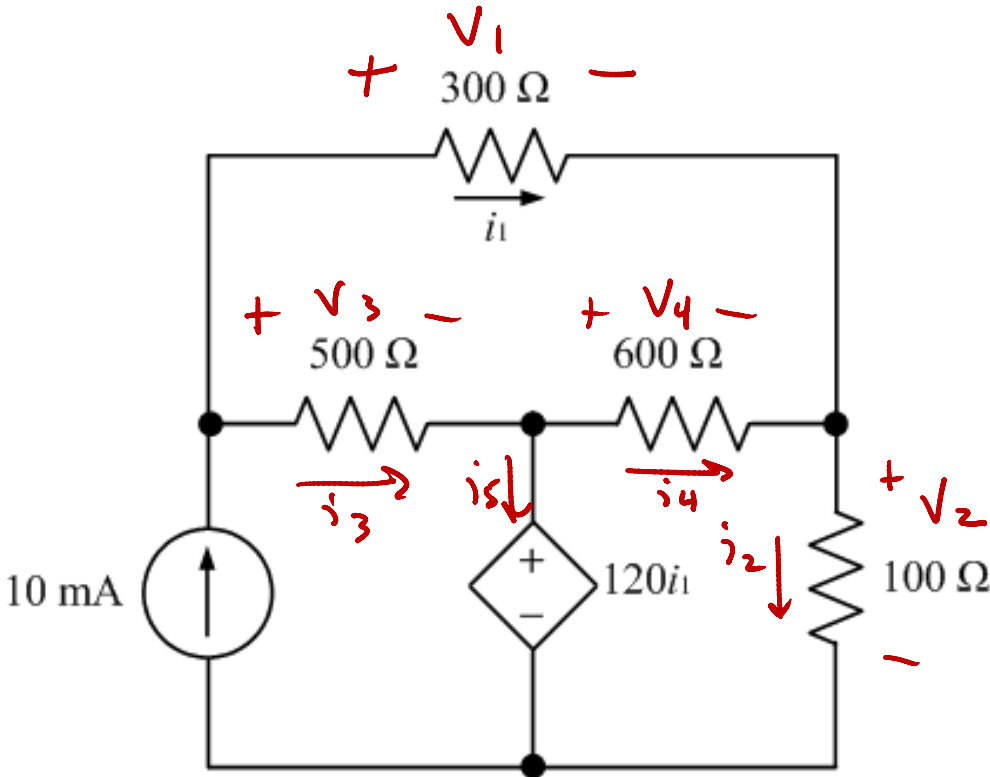Problem 3 Find the current through the 300 Ω resistor. HARD!!



<u>KCL</u>	<u>KVL/OL</u>
$i_1 + i_3 = 10 \text{ mA}$	$-120i_1 - 500i_3 + 300i_1$
$i_1 + i_4 = i_2$	$+ 100i_2 = 0$
$i_4 + i_5 = i_3$	$-120i_1 + 600i_4 + 100i_2 = 0$

System of Eqs

$$\begin{array}{rcl}
 -120i_1 + 100i_2 + & & + 600i_4 + & = 0 \\
 180i_1 + 100i_2 - 500i_3 & & & = 0 \\
 i_1 & + & i_3 & = 10 \\
 i_1 - i_2 & & + i_4 & = 0 \\
 & & - i_3 + i_4 + i_5 & = 0
 \end{array}$$

Matrix Form


$$A = \begin{bmatrix} -120 & 100 & 0 & 600 & 0 & 0 \\ 180 & 100 & -500 & 0 & 0 & 0 \\ 1 & 0 & 1 & 0 & 0 & 0 \\ 1 & -1 & 0 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 & 1 \end{bmatrix}$$

$$b = \begin{bmatrix} 0 \\ 0 \\ 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$I = A \setminus b = \begin{bmatrix} 6.39 \\ 6.57 \\ 3.61 \\ 0.18 \\ 3.43 \end{bmatrix} \text{ mA}$$


Handouts Day 1

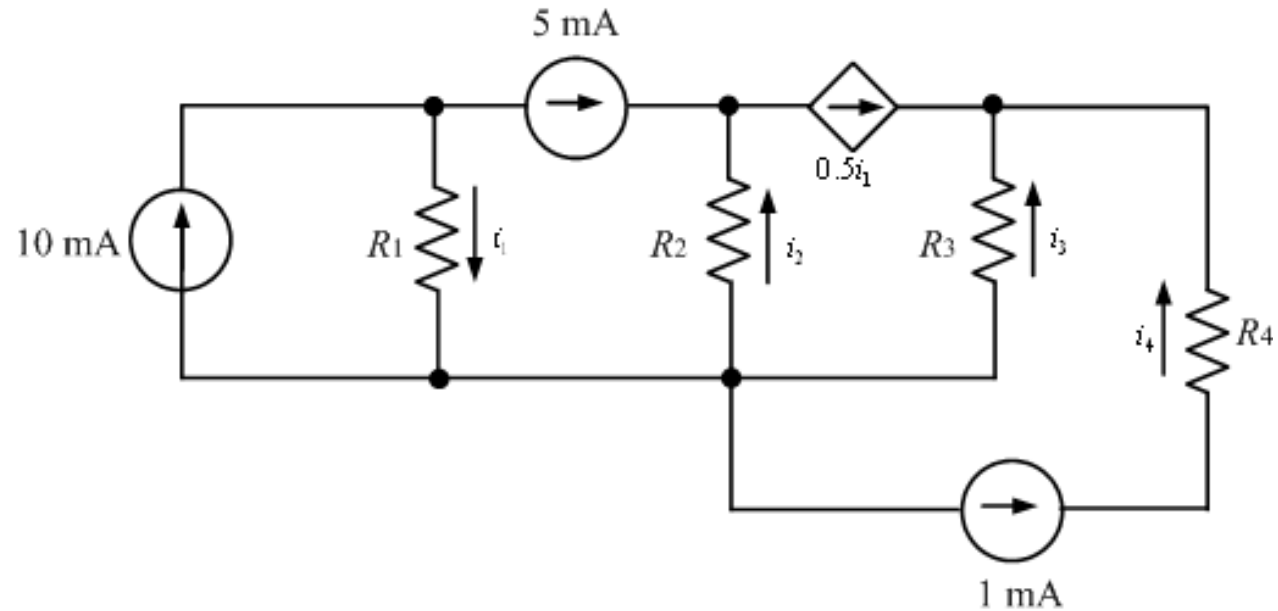1) Problem 1 Determine the current through each of the resistors in this circuit.




$$i_1 = 5\text{mA}, \quad i_2 = -2.5\text{ mA}, \quad i_3 = -3.5\text{ mA}, \quad i_4 = 1\text{ mA}$$

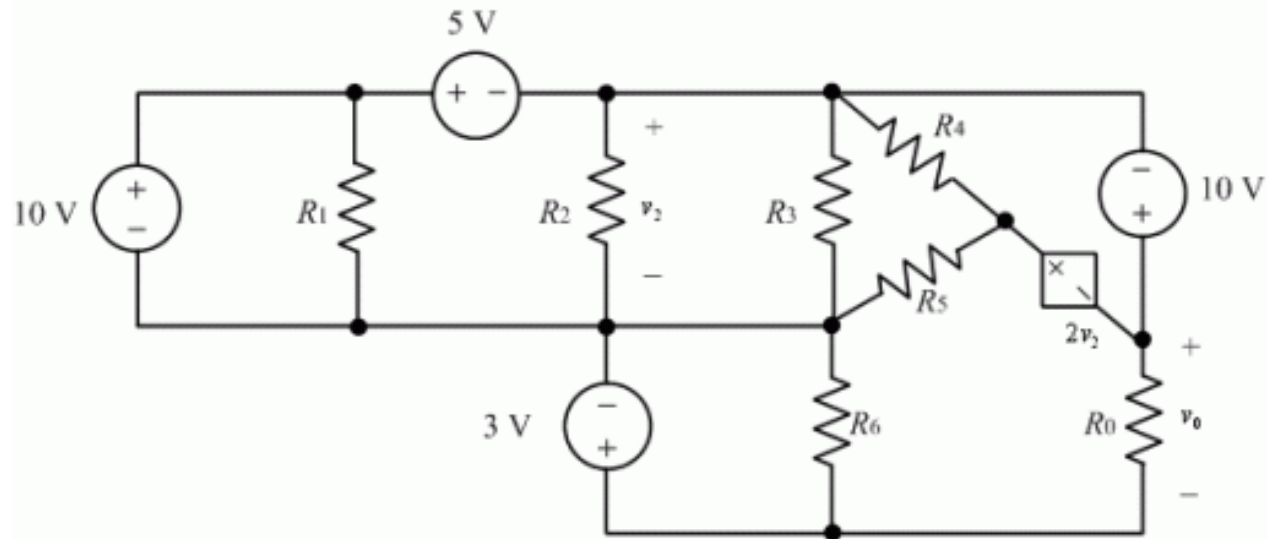2) Problem 1 Find the voltage across resistor R_0 . (12V)




3) KCL and KVL in one circuit

Find the value of v_0 .

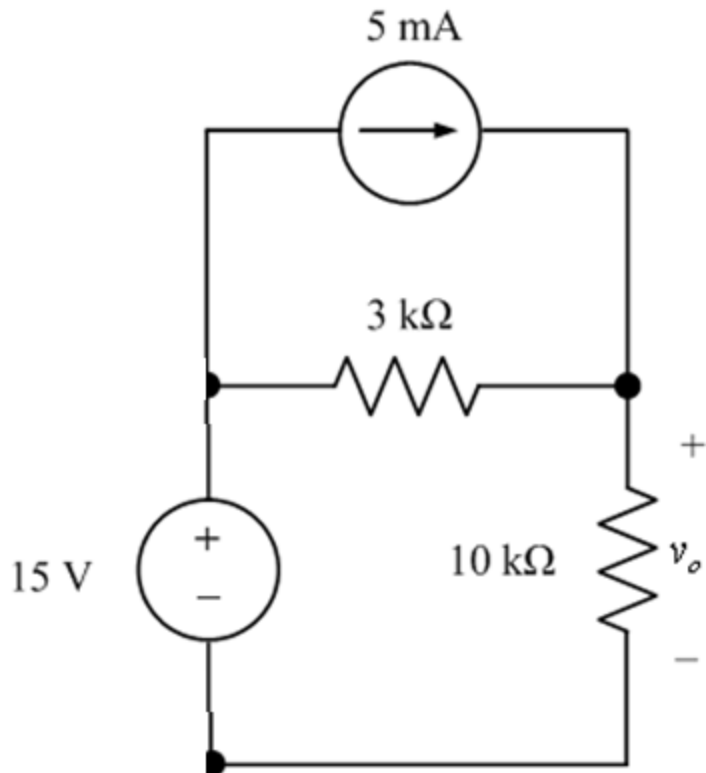

$$v_0 = 23.1 \text{ V}$$


4) If i_o is 1A, Find i_1

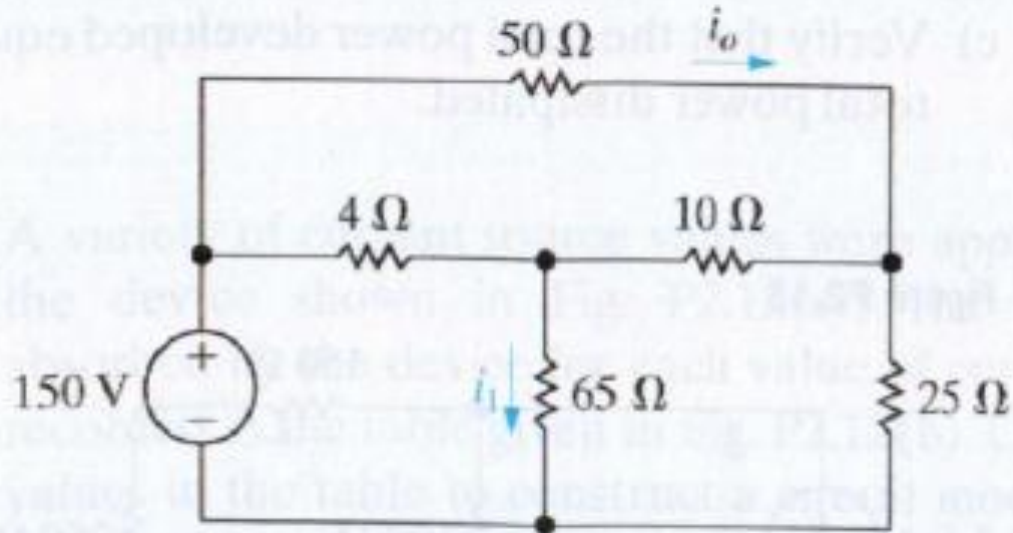

$i_1 = 2A$


Handouts Day 2

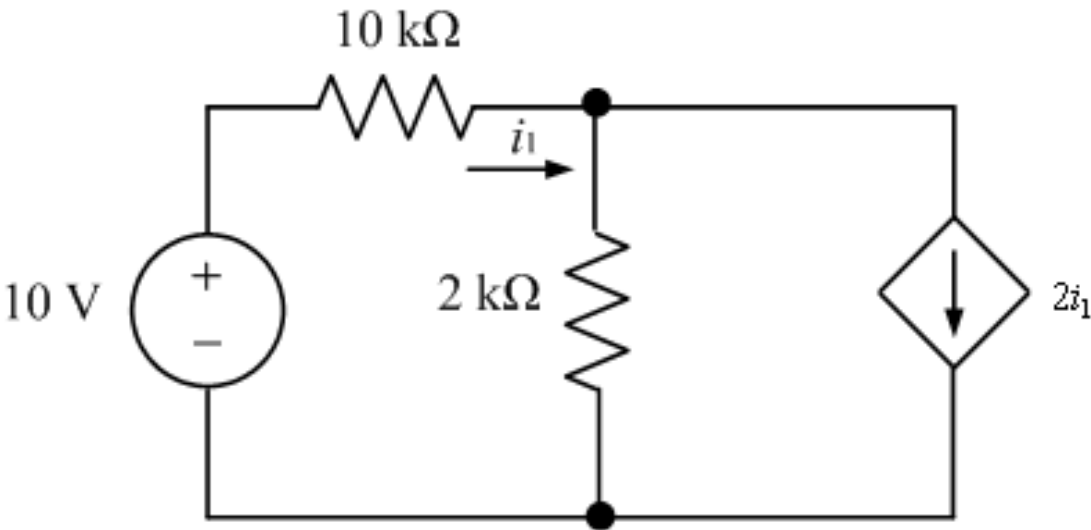1) Problem 2 Find the current through the $10\text{ k}\Omega$ resistor.




2)

Find I (3A)

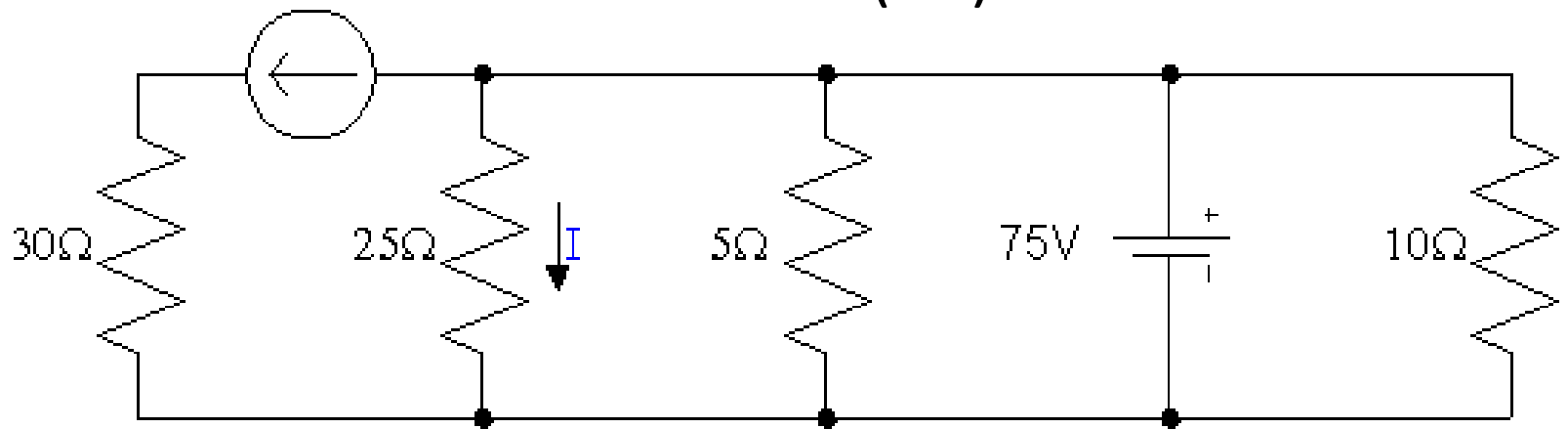

3)

Find V

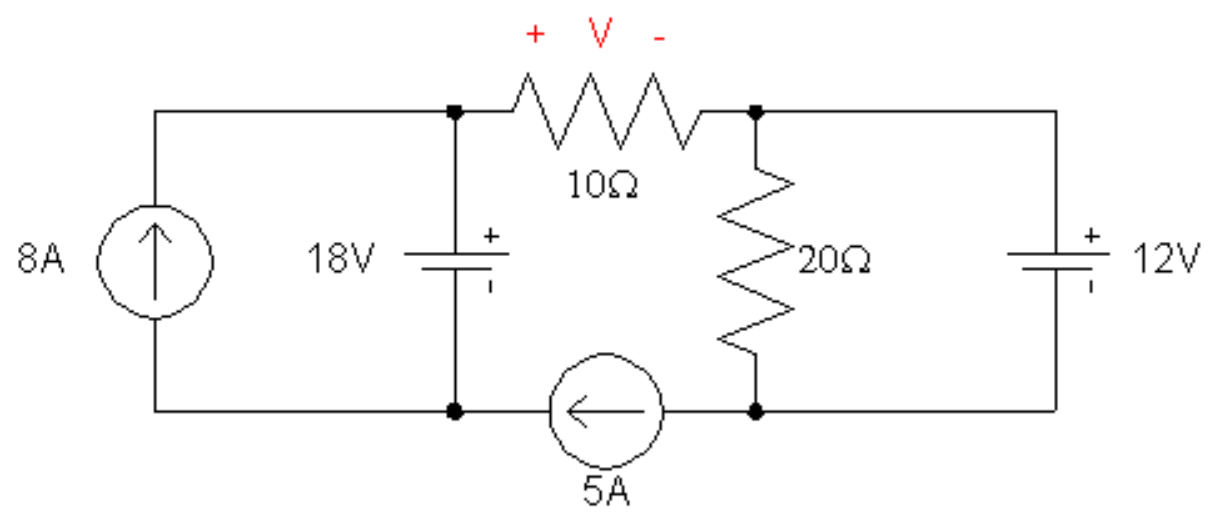

4)

Find V

