
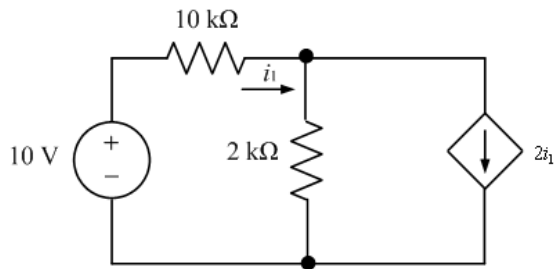


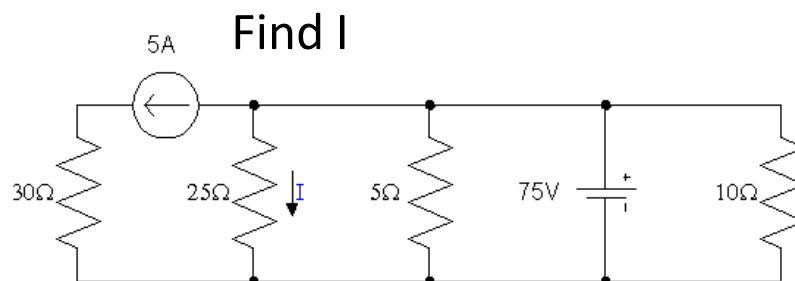
1) Problem 2 Find the current through the $10\text{ k}\Omega$ resistor.



2)



3)
Find V

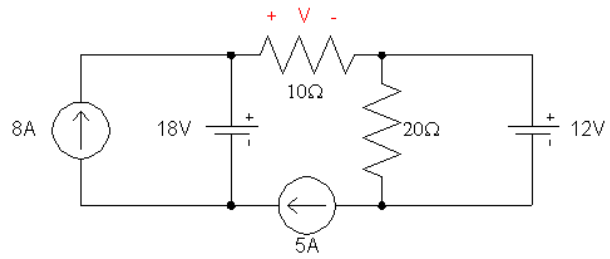

4)
Find V

