
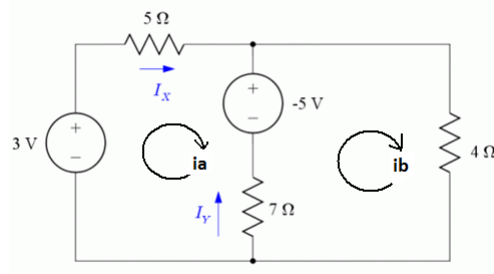


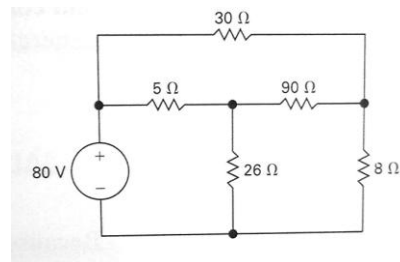
- 1) Use mesh analysis to determine I_a and I_b
 $I_a = 639 \text{ mA}$; $I_b = -48 \text{ mA}$
 Then find BRANCH currents I_x , I_y (639, -687)



- 2) Find a) three mesh currents, [5,2.5,2]
 b) Power of 80V source (-400W del)



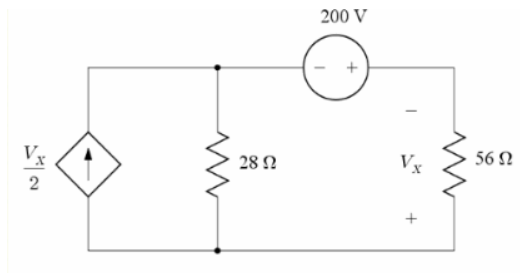3) Use MC to find V_x . [$V_x = -12.9 \text{ V}$]



4) Use SUPERMESH to find the i_a , i_b and power associated with each voltage source.

$i_a = 6.12 \text{ mA}$, $i_b = -5.88 \text{ mA}$, $P_{1.5} = 9.18 \text{ mW}$; $P_{3.0} = 17.6 \text{ mW}$

