
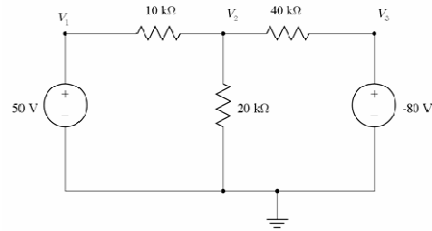


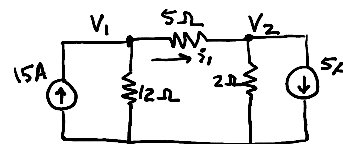
1) Cleo:Problem 1 Write 1 NV eq at V_2 and solve



- 2) Use NV to find v_1 , v_2 and i_1 (60,10,10)
 b) how much power delivered by 15A src? (-900W, del)
 c) how about 5A source? (50W absorb)



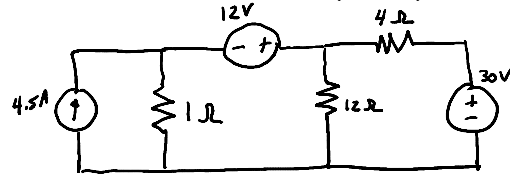3) Write a Supernode NV to find V_1 , V_2 (6,18)



4) Find v_1 , v_2 , i_x (16,10,6/5)

