

Circuit Theory

Chapter 4

Circuit Theorems


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Circuit Theorems - Chapter 4

- 4.1 Motivation
- 4.2 Linearity Property
- 4.3 Superposition
- 4.4 Source Transformation
- 4.5 Thevenin's Theorem
- 4.6 Norton's Theorem
- 4.7 Maximum Power Transfer

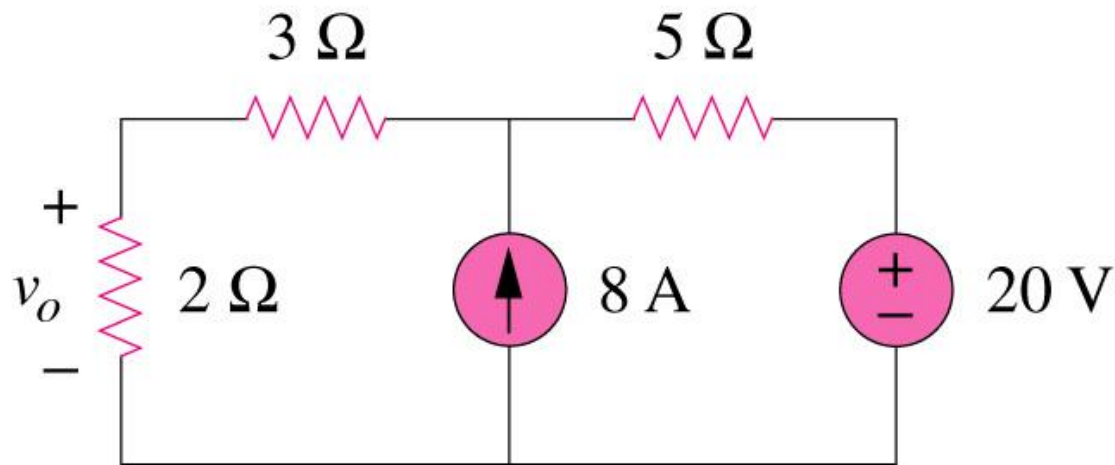4.1 Motivation (1)

If you are given the following circuit, are there any other alternative(s) to determine the voltage across 2Ω resistor?



What are they? And how?

Can you work it out by inspection?

4.2 Linearity Property (1)

It is the property of an element describing a linear relationship between cause and effect.

A linear circuit is one whose output is linearly related (or directly proportional) to its input.

Homogeneity (scaling) property

$$\begin{array}{ccc} \begin{array}{c} \text{Input} \\ \downarrow \\ \mathbf{v} = \mathbf{i} R \\ \downarrow \\ \text{Output} \end{array} & \longrightarrow & \begin{array}{c} \text{scaled} \\ \text{Input} \\ \mathbf{kv} = \mathbf{ki} R \\ \downarrow \\ \text{scaled output} \end{array} \end{array}$$

Additive property

$$\begin{array}{ccc} \begin{array}{c} \text{Input 1} \\ \downarrow \\ \mathbf{v}_1 = \mathbf{i}_1 R \end{array} & \text{and} & \begin{array}{c} \text{Input 2} \\ \downarrow \\ \mathbf{v}_2 = \mathbf{i}_2 R \end{array} \\ \longrightarrow & \mathbf{v} = (\mathbf{i}_1 + \mathbf{i}_2) R = \mathbf{v}_1 + \mathbf{v}_2 & \end{array}$$

Output is sum of individual outputs

4.3 Superposition Theorem (1)

A gift of the Additive property of **Linearity**.



It states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltage across (or currents through) that element due to EACH independent source acting alone.

The principle of superposition helps us to analyze a linear circuit with more than one independent source by calculating the contribution of each independent source separately.

4.3 Superposition Theorem (2)


We consider the effects of 8A and 20V one by one, then add the two effects together for final v_o .

Effect of 8A SRC

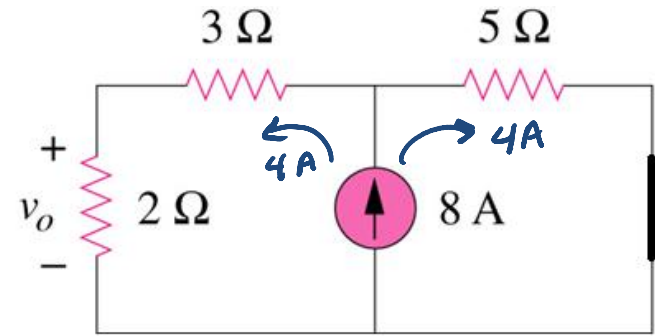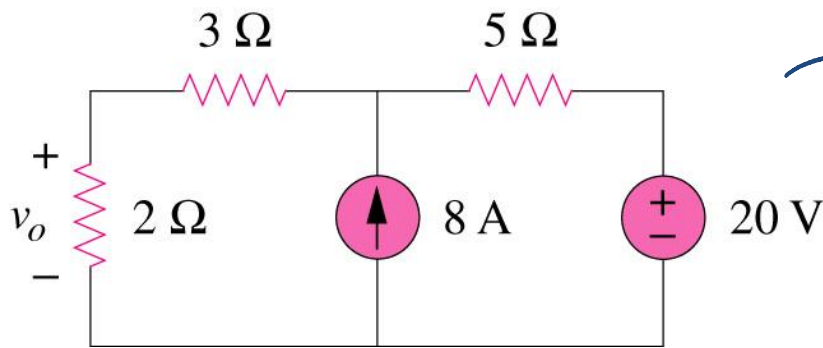

$$V_o = 4(2) = 8$$

Effect of 20V SRC

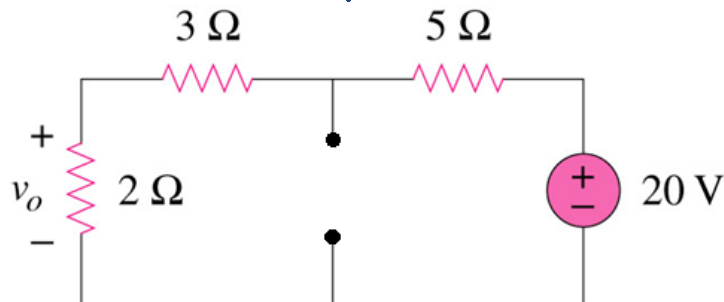

$$V_o = \left(\frac{2}{2+3+5} \right) 20 = 4$$

$$\text{Total } v_o = 8 + 4 = \underline{\underline{12V}}$$

4.3 Superposition Theorem (3)

Steps to apply superposition principle

1. Turn off all independent sources except one source. Find the output (voltage or current) due to that active source using nodal or mesh analysis.
2. Repeat step 1 for each of the other independent sources.
3. Find the total contribution by adding algebraically all the contributions due to the independent sources.

4.3 Superposition Theorem (4)


Two things have to be keep in mind:

1. When we say turn off all other independent sources:
 - Independent voltage sources are replaced by 0 V (short circuit) and
 - Independent current sources are replaced by 0 A (open circuit).
2. Dependent sources are left intact because they are controlled by circuit variables.

4.3 Superposition Theorem (5)

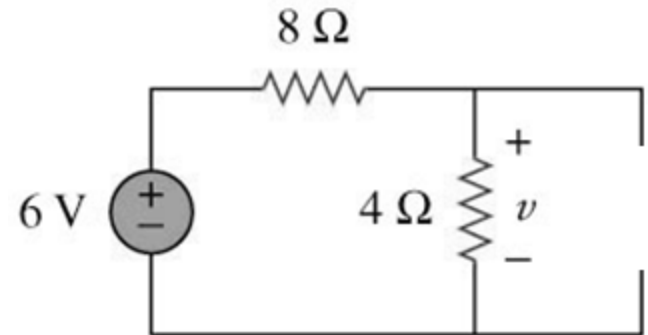
Example 2

Use the superposition theorem to find v in the circuit shown below.




$$v = \left(\frac{4}{4+8}\right) 6 = 2\text{V}$$

3A is turned off
by open-circuit

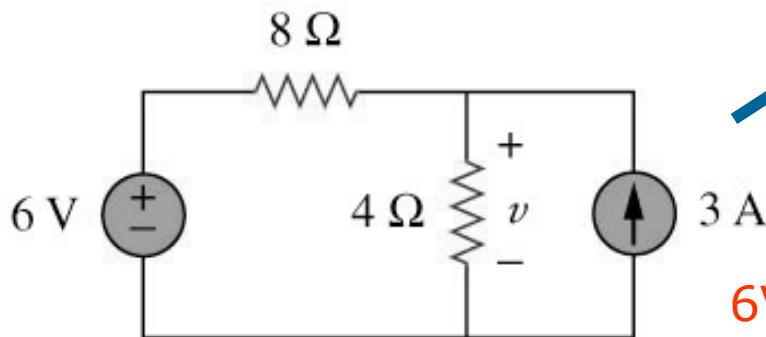


6V is turned off
by short-circuit

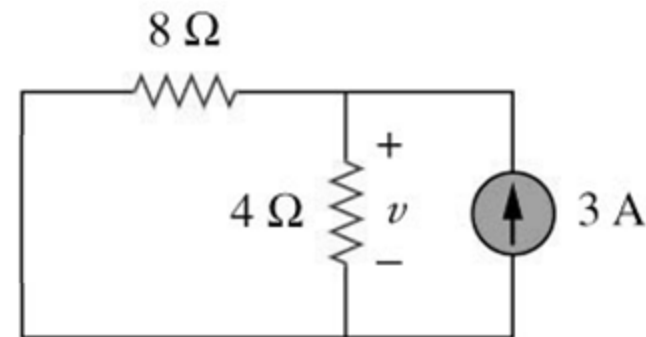


$$v = 3(4 \parallel 8) = 3\left(\frac{32}{12}\right) = 8\text{V}$$

answer $v = 10\text{V} = 2\text{V} + 8\text{V}$


1) Use Superposition to find V_x (3V)

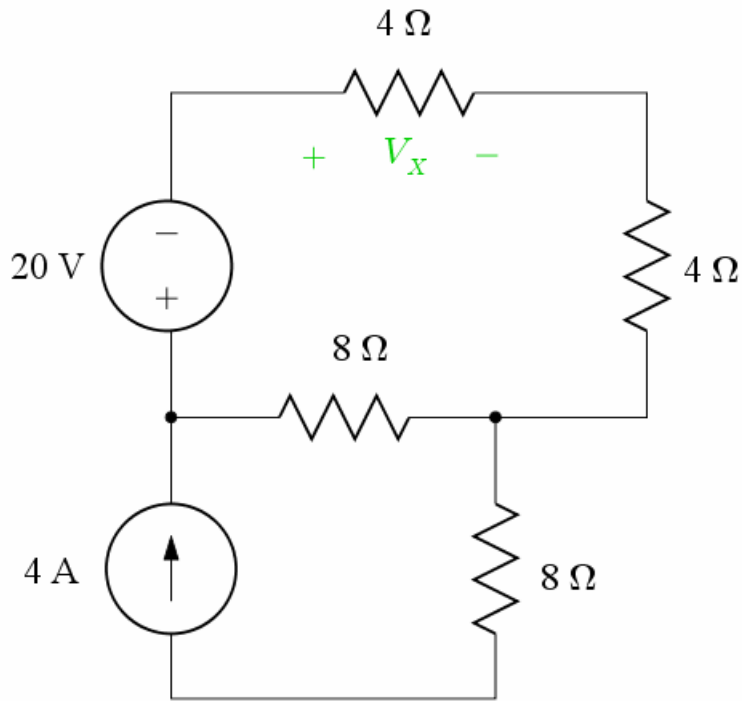

a) Turn off 4A SRC

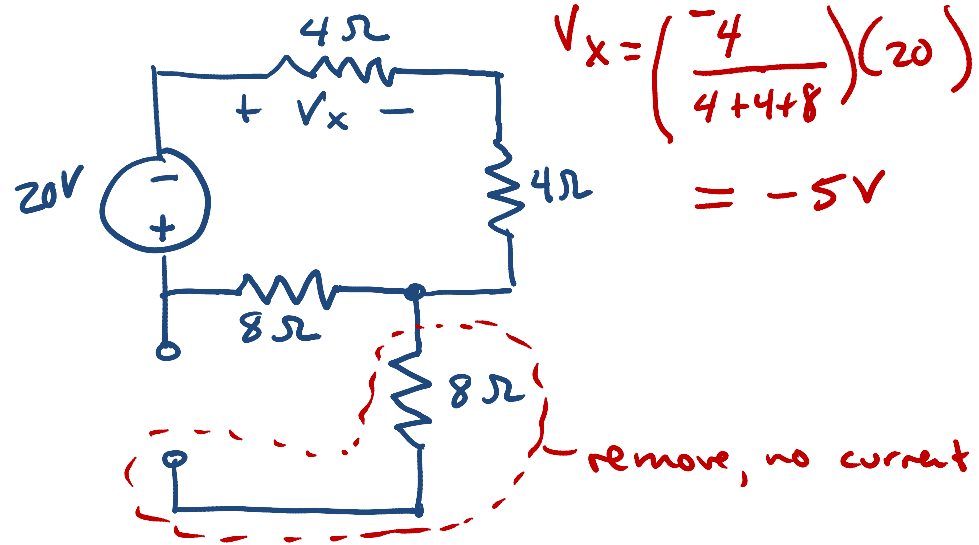

b) Turn off 20V SRC

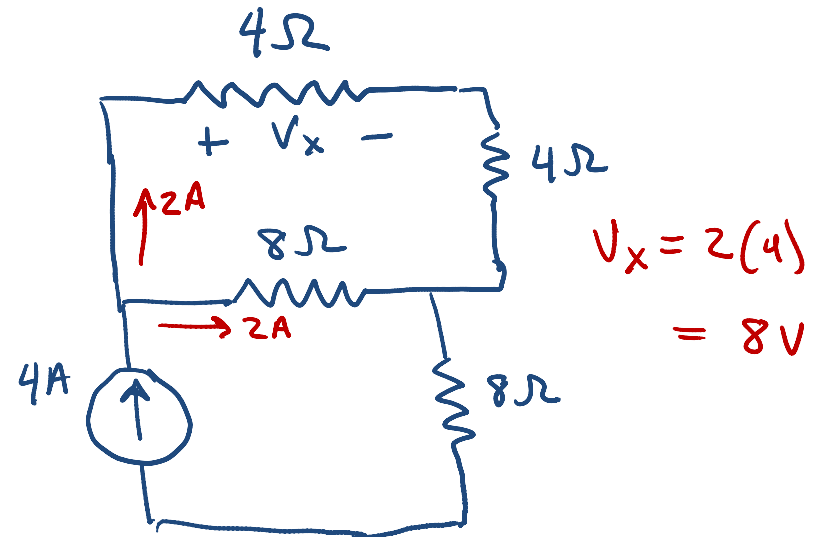


Total $V_x = 8 - 5 = \underline{\underline{3V}}$


4.3 Dependent Sources are not turned off when using the Superposition Theorem

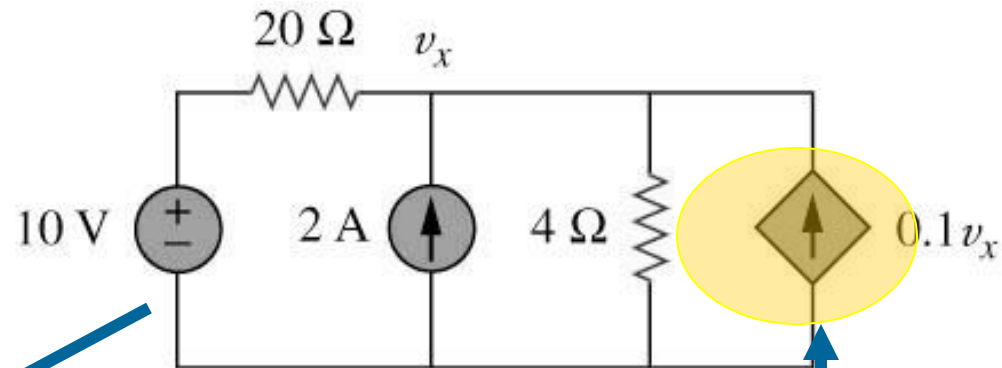Example 3

Use superposition to find v_x in the circuit below.




2A is discarded by open-circuit

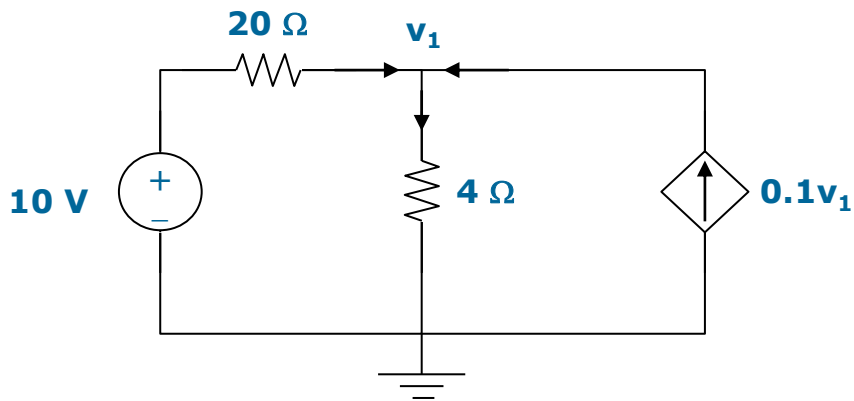

(a)

10V is discarded by open-circuit

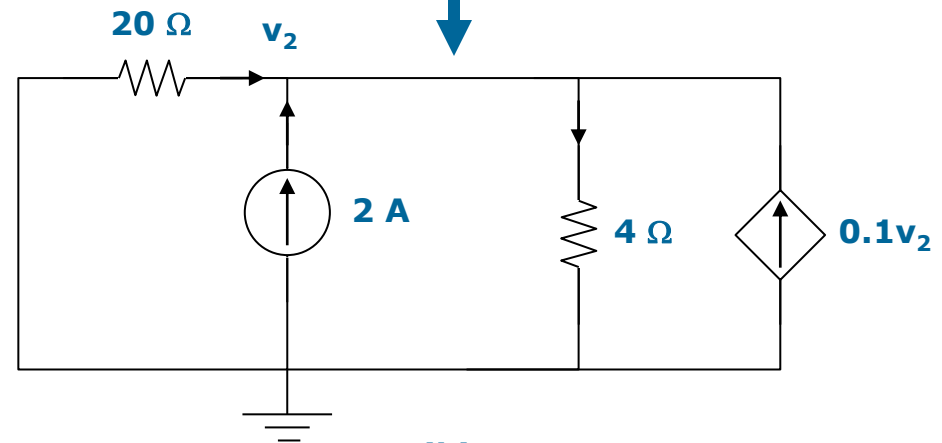


(b)

$*V_x = 12.5V$


4.4 Source Transformation (1)

- An equivalent circuit is one whose v - i characteristics at some terminals (a-b) are identical with the original circuit.
- Source Transformation is the process of replacing a voltage source v_s in series with a resistor R by a current source i_s in parallel with a resistor R , or vice versa.
- The value of i_s or v_s in the replacement circuit is chosen to have the same behavior at the terminals of interest.

4.4 Source Transformation (2)

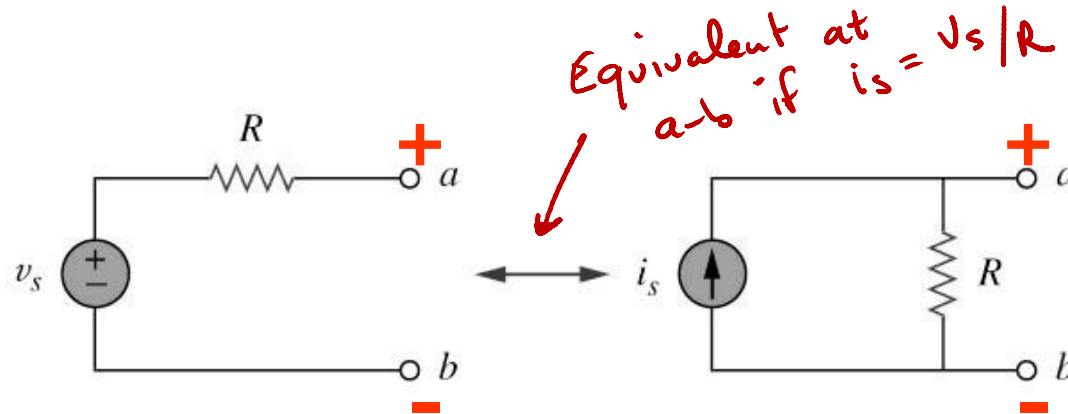


(a) Independent source transform

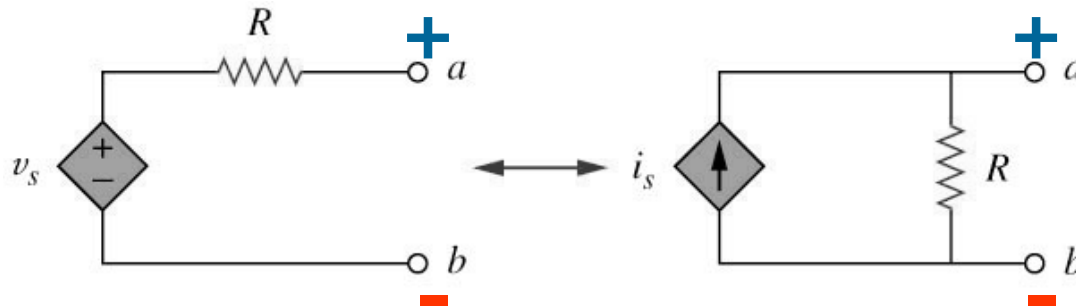

(b) Dependent source transform

- The arrow of the current source is directed toward the positive terminal of the voltage source.
- The source transformation is not possible when $R = 0$ for voltage source and $R = \infty$ for current source.

4.4 Source Transformation Relationship

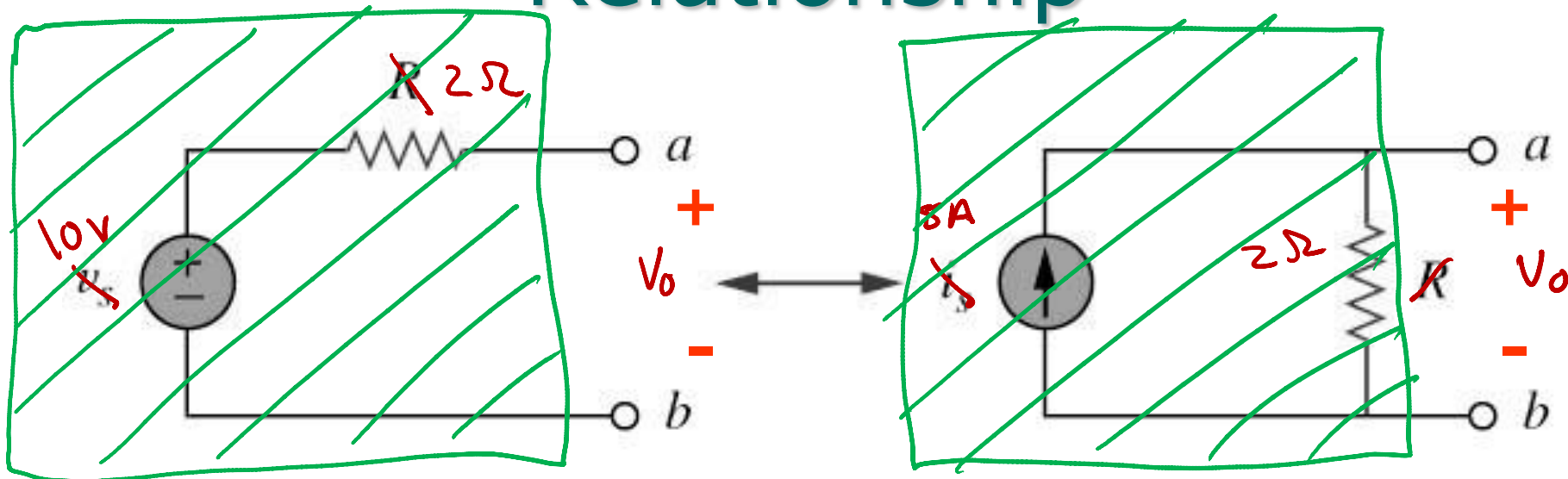

- The two circuits are equivalent **at a-b**

- IF **$v_s = i_s R$** or **$i_s = v_s / R$**


- For example, if $v_s = 10V$ and $R = 2 \text{ Ohm}$

- then $i_s = 5A$ in source transform

- **same effect at a-b !** $V_0 = 10V$ for both ccts !

IF we hide the ccts, we cannot tell which is which
by measuring V or i at a-b

4.4 How does that work exactly?

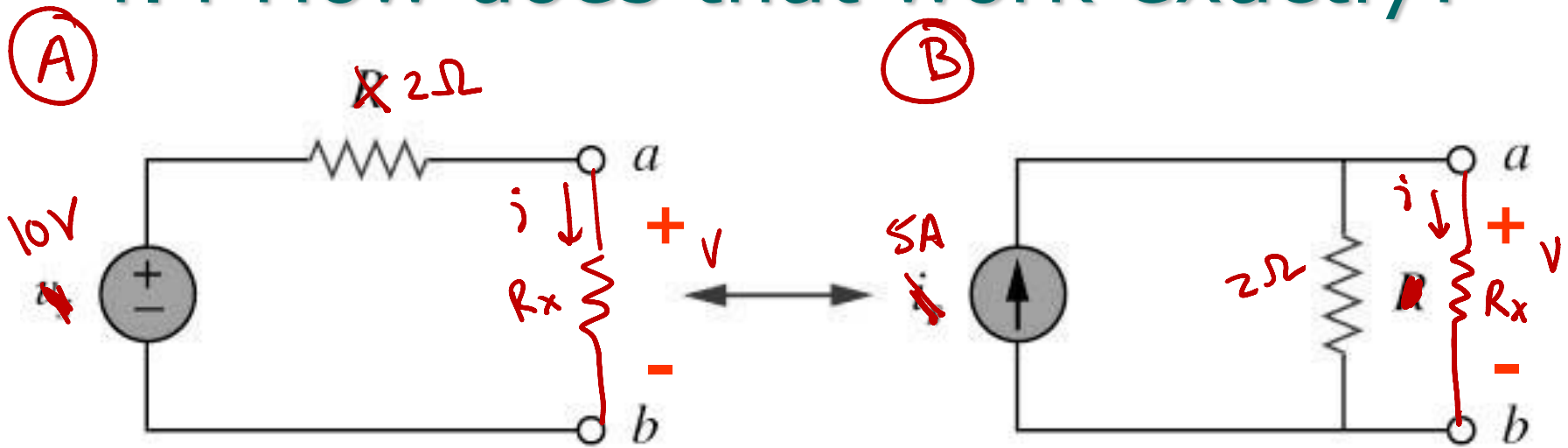

• Let's add a resistor R_x at a-b in both circuits

(A) $v = \left(\frac{R_x}{R_x + 2} \right) 10 \text{ V}$, $i = \frac{10}{R_x + 2} \text{ A}$

(B) $v = 5 (R_x \parallel 2)$, $i = \left(\frac{2}{R_x + 2} \right) 5 \text{ A}$


$= 5 \left(\frac{2 R_x}{R_x + 2} \right)$

∴ Same behavior for all R_x !!


4.4 Source Transformation (3)

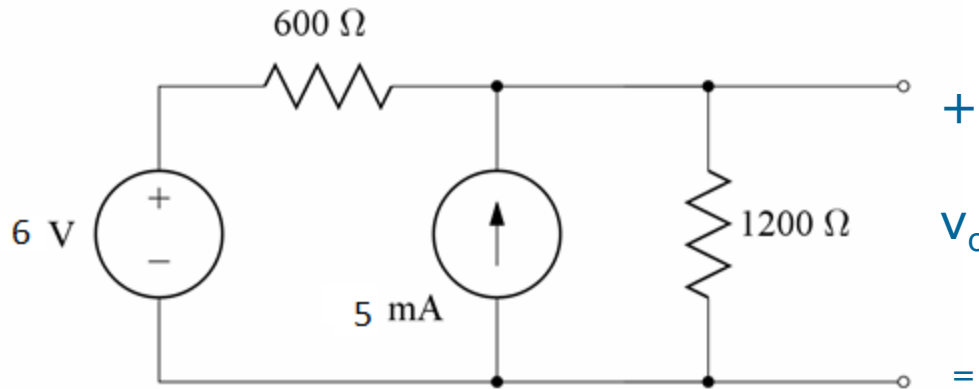Example 4


Find v_o in the circuit shown below using source transformation.



a) Xform $V \rightarrow I$ Src

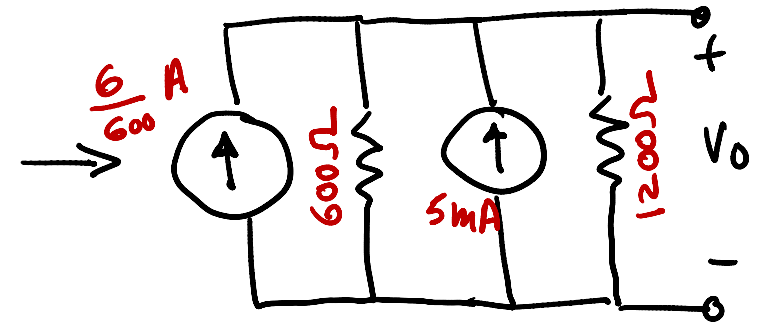


b) Combine parallel R's + I-SRCS

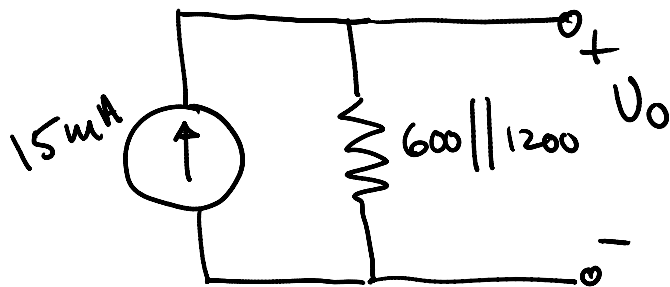


c) Calc v_o

$$V_o = (.015) \left(\frac{600 \cdot 1200}{1800} \right) \\ = \underline{\underline{6V}}$$

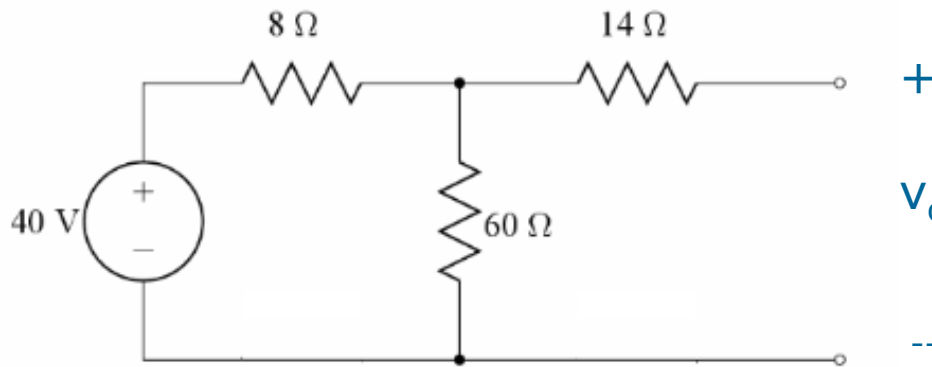
2) Find v_o in the circuit shown below using source transformation.




a) X form $V \rightarrow I$ src

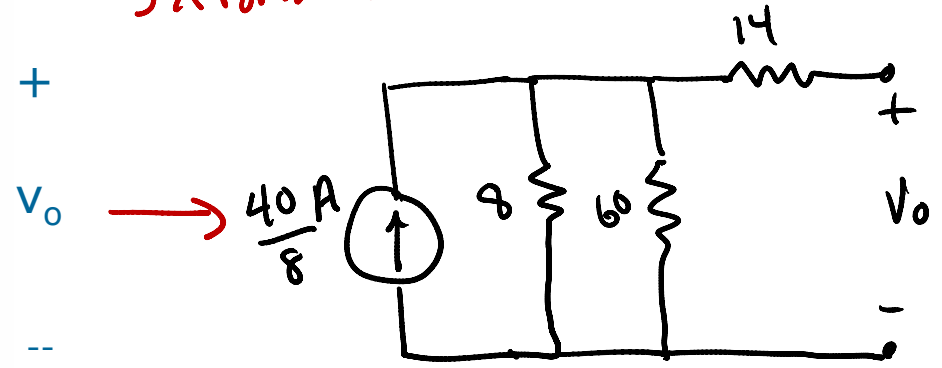

b) Combine || R's

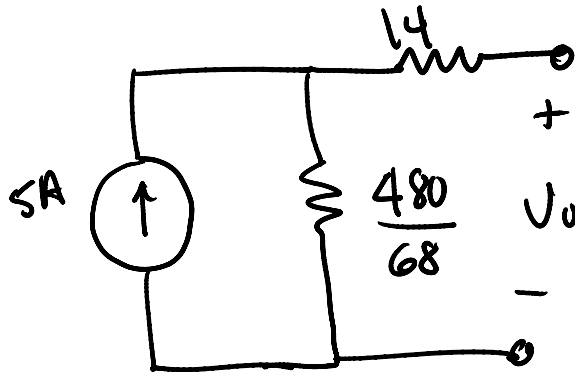

c) X form $I \rightarrow V$ src

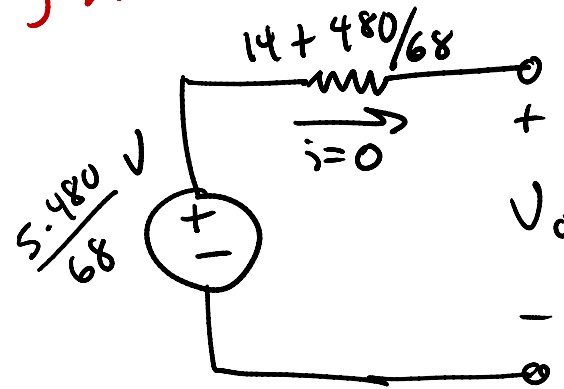


d) Calc v_o

$$v_o = \frac{5 \cdot 480}{68}$$

$$v_o = \underline{\underline{35.29 \text{ V}}}$$


Some other tricks with Source Transform:

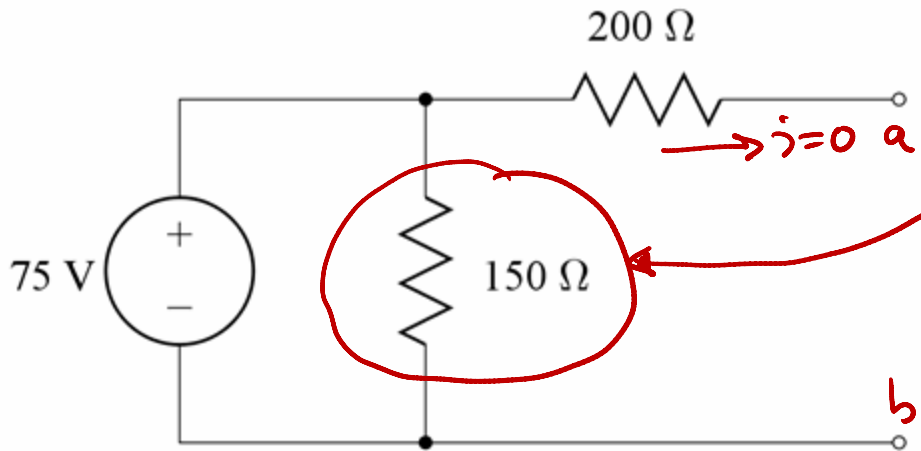Resistors in Parallel with V source can be removed
 Resistors in Series with I source can be removed



Can Remove. Does not affect V_{ab} .
 (Does draw more current from V-Source)

$V_{ab} = 75V$ regardless

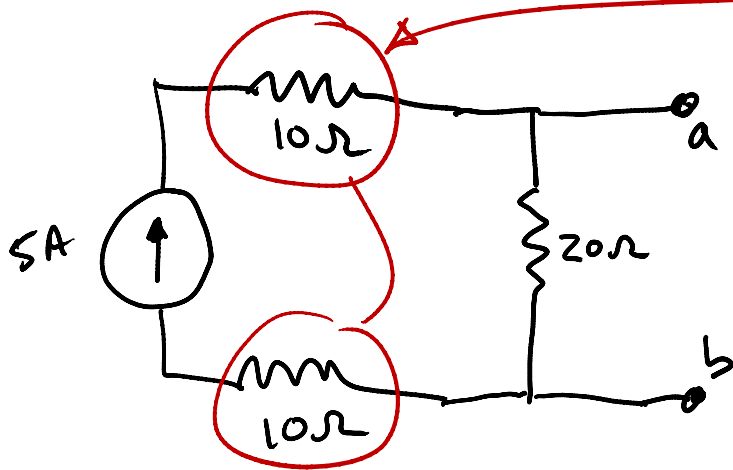

Can remove. Does not affect current flowing thru 20Ω Resistor.




(Does require more voltage from I-Source)

$V_{ab} = 100V$ regardless

Multiple sources in parallel

can be converted to current sources, added and reduced
Likewise, sources in series \rightarrow Voltage sources, added, reduced


Combine I-sources + || R's

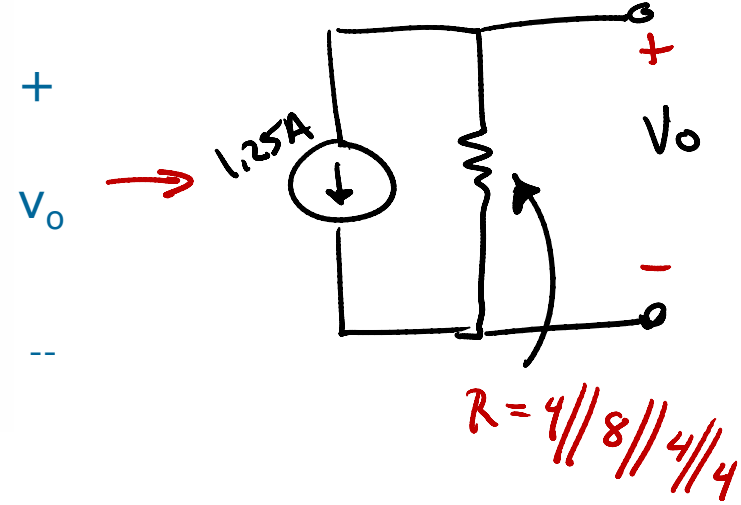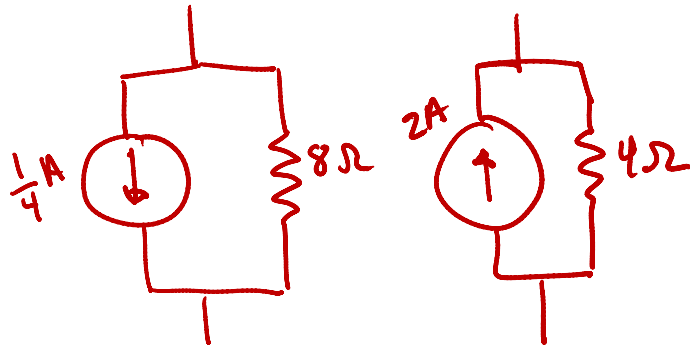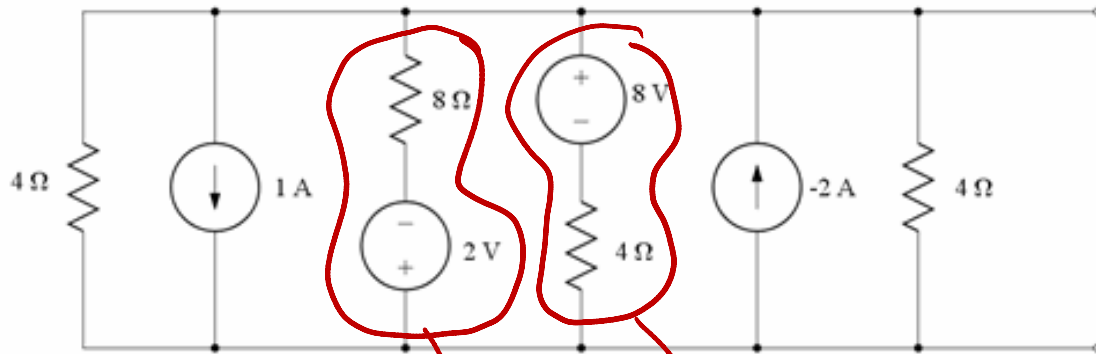

$$\begin{aligned}
 V_o &= -1.25 \left(\frac{32}{12} \parallel 2 \right) \\
 &= -1.25 \left(\frac{16}{\frac{2}{3} + \frac{1}{2}} \right) \\
 &= -1.25 \left(\frac{16}{\frac{7}{6}} \right) = -\frac{40}{7} \\
 &= -5.71 \text{ V}
 \end{aligned}$$

However, Beware "Rebold's Rule"

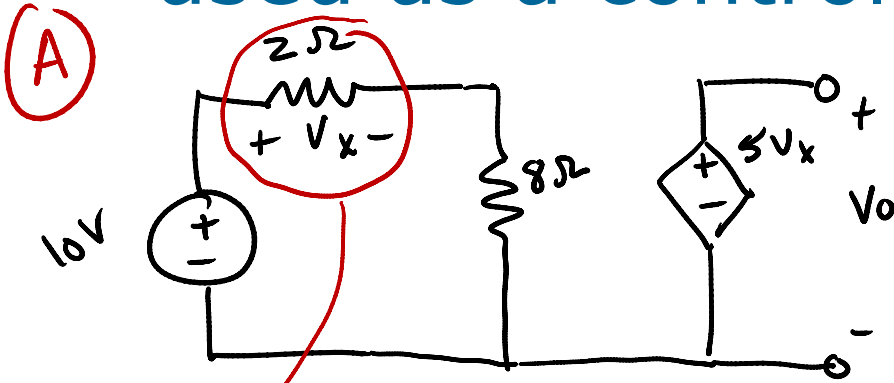- Never Source Transform a Resistor used as a control for a Dependent Src




$$V_x = 10 \left(\frac{2}{10} \right) = 2V$$

$$V_o = 5V_x = 10V$$


This Source Xform has changed a distant cct variable

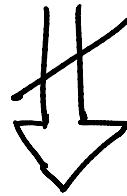this Resistor should not be part of a Xform



$$V_x = 5(2 \parallel 8) = 5 \cdot \frac{16}{10} = 8V$$

$$V_o = 5V_x = 40V !!$$

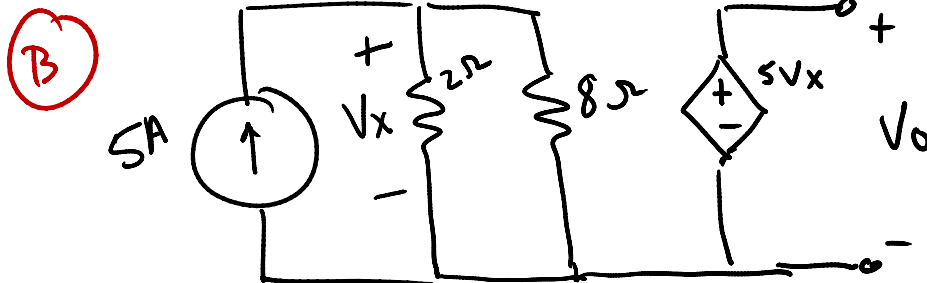


4.5 Thevenin's Theorem (1)


It states that a linear two-terminal circuit (Fig. a) can be replaced by an equivalent circuit (Fig. b) consisting of a voltage source V_{TH} in series with a resistor R_{TH} ,

where

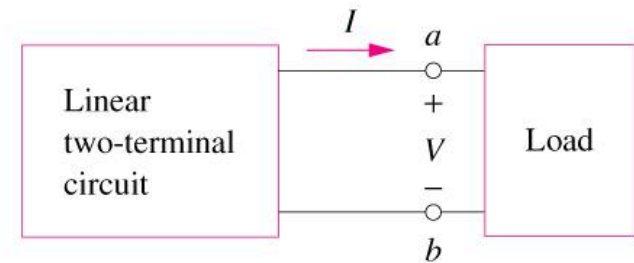- V_{TH} is the open-circuit voltage at the terminals.
- R_{TH} is the input or equivalent resistance at the terminals when the independent sources are turned off, sometimes called the "Lookback Resistance"



(a)

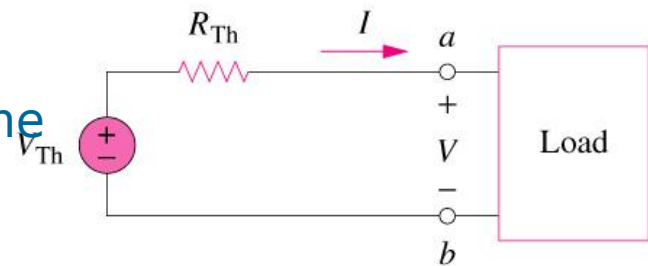


(b)


4.5 Thevenin's Theorem (2)

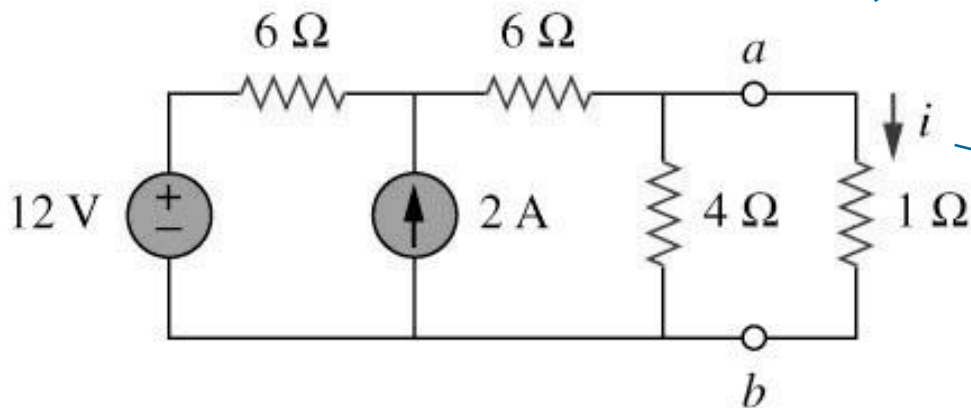Example 5


Using Thevenin's theorem, find the equivalent circuit to the left of the terminals in the circuit shown below. Then find i .



a) Turn off indep Sucs to find R_{Th}




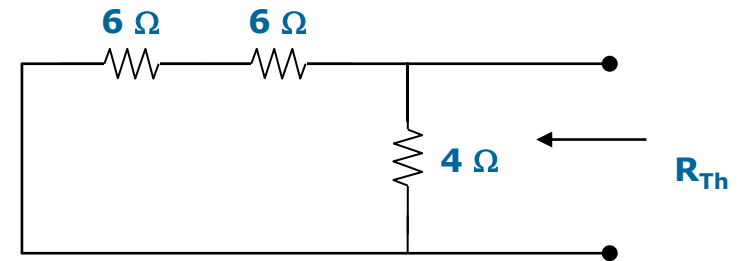


b) Find open-cct V at desired terminals

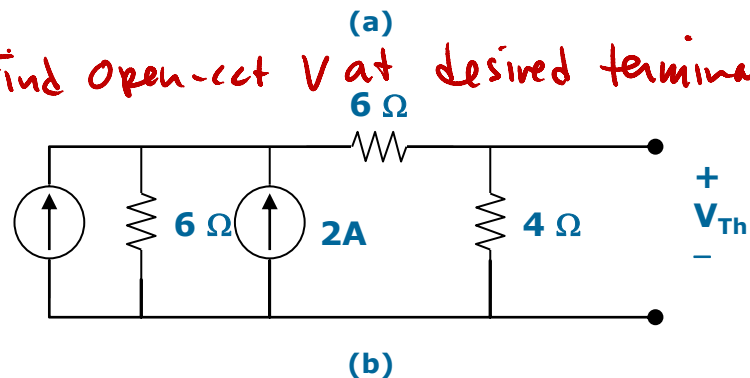


You can use any technique to find V_{th}

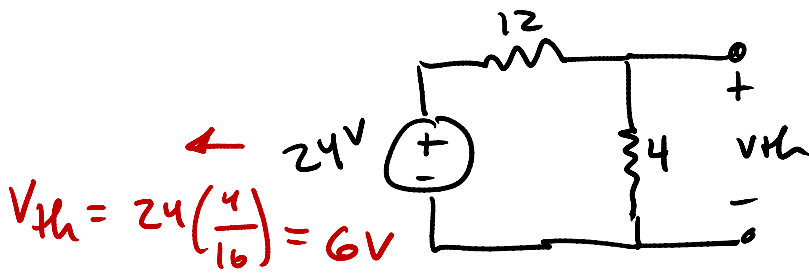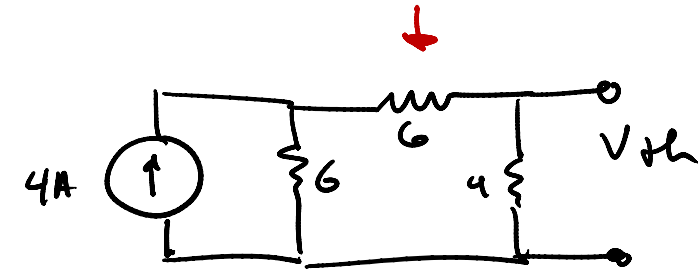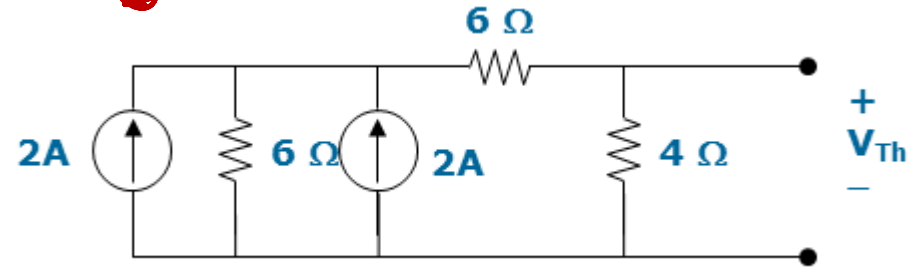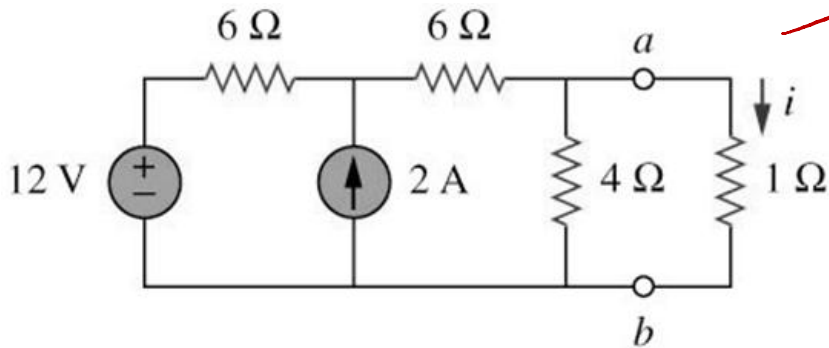
Nodal/Mesh Analysis, Source Xform, KCL/KVL


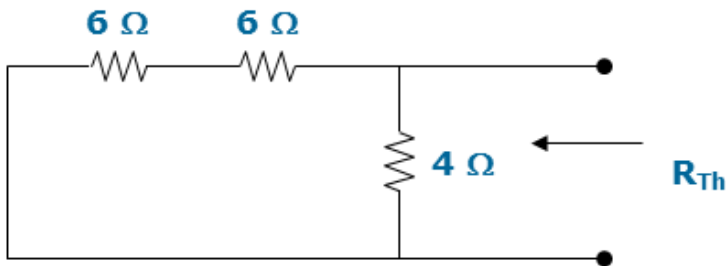
$$R_{th} = 4 \parallel 12 = \frac{48}{16} = \underline{\underline{3}}$$




Thevenin Eq: 3Ω

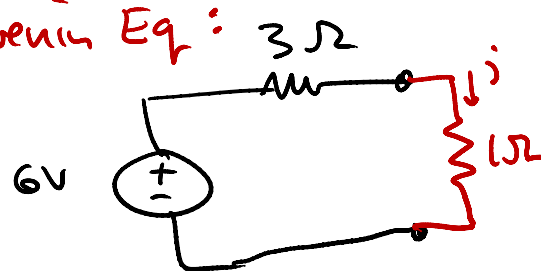

now $i = \frac{6}{4} = 1.5A$

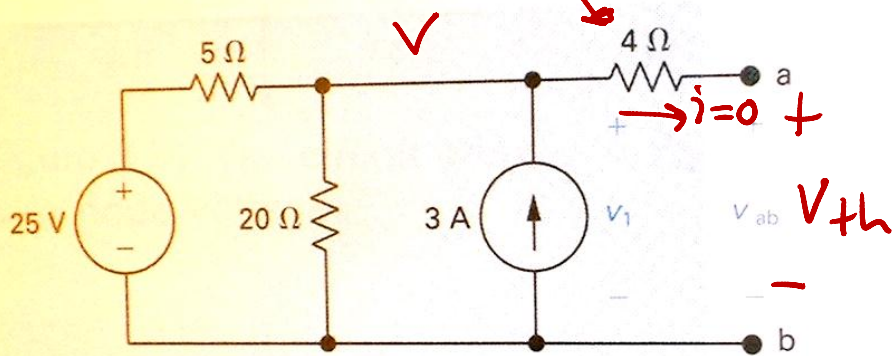3) Find Thevenin Eq at a-b


note how **R4** does not affect V_{oc} ! [$V_{th}=32$, $R_{th}=8$]



Let's use Nodal to find $V = V_{th}$


$$\left(\frac{V-25}{5} + \frac{V}{20} - 3 = 0 \right) \times 20 \rightarrow$$
$$5V = 160, \quad \underline{\underline{V_{th} = 32}}$$

Turn off sources to find R_{th}


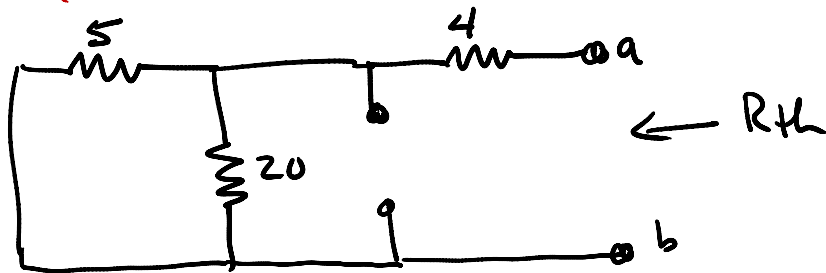


$$R_{th} = 4 + 5 \parallel 20 = \underline{\underline{8 \Omega}}$$

Thevenin Eq:

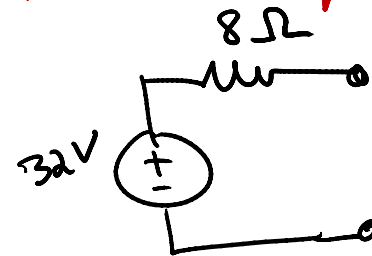

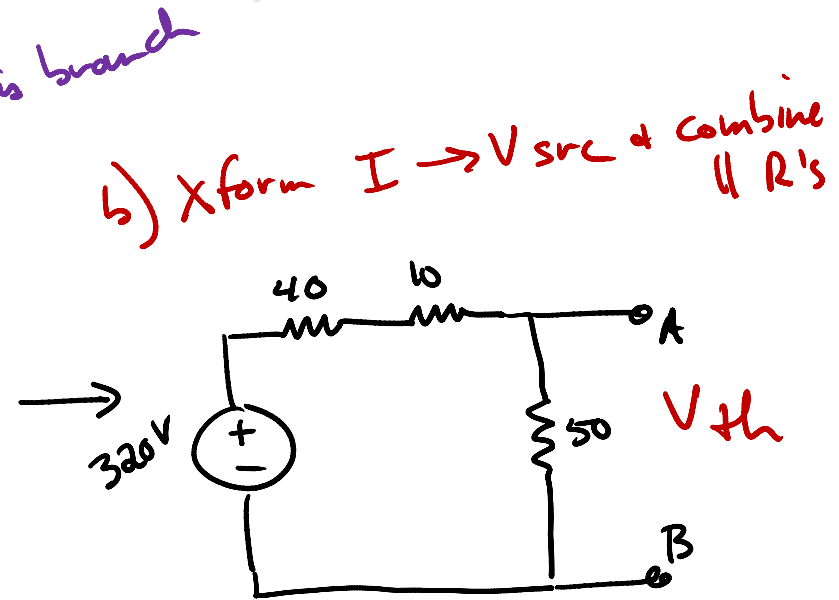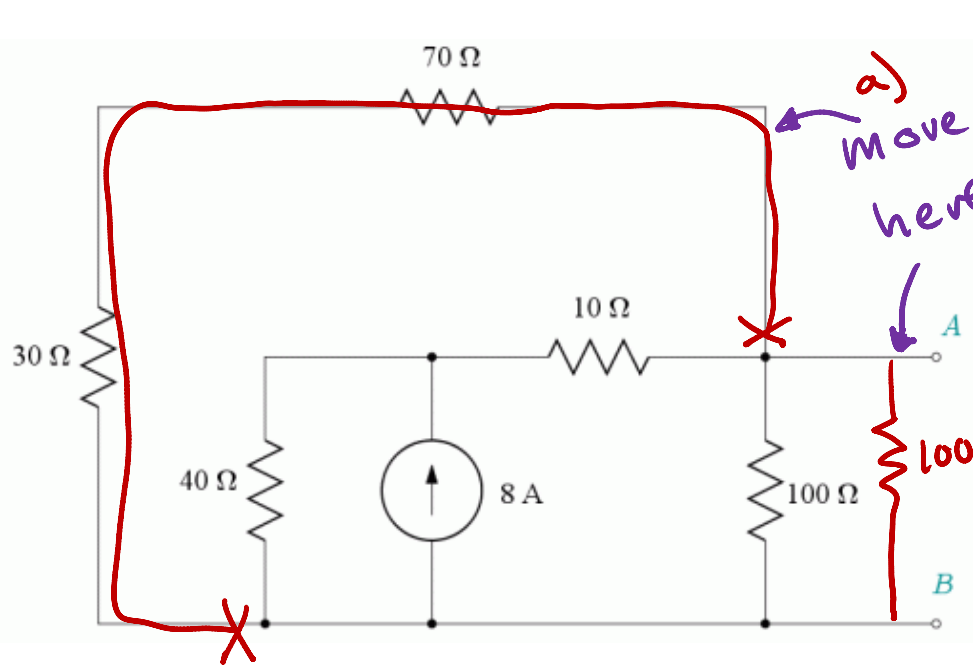4) Find the Thévenin equivalent circuit at the terminals A-B. $R_t = 25\Omega$; $V_t = 160V$




c) Use voltage divider formula

$$V_{th} = \left(\frac{50}{100} \right) 320 = \underline{\underline{160V}}$$

$$R_{th} = 50 \parallel 50 = \underline{\underline{25\Omega}}$$

d) Turn off SRC for R_{th}

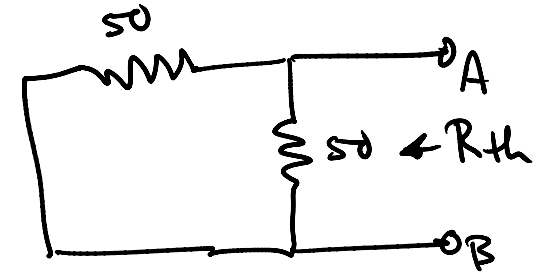


Finding Thevenin Eq with Dependent Sources

- V_{th} is still the open circuit voltage
 - across the terminals of interest
- To find R_{th} ,
 - we CAN turn off Independent Sources
 - we CANNOT turn off Dependent Sources
 - they depend on other circuit variables
 - SOLN: hook up an external source at terminals, find $V_o/I_o = R_{th}$


4.5 Thevenin's Theorem (3)

a) Find V_{th} as before (V_{oc} at a-b)

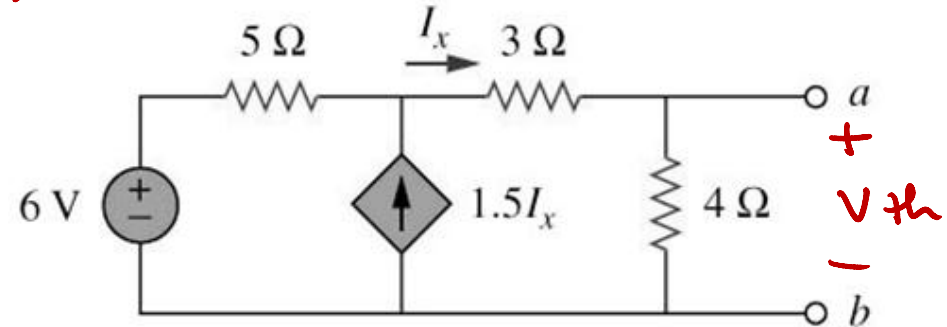


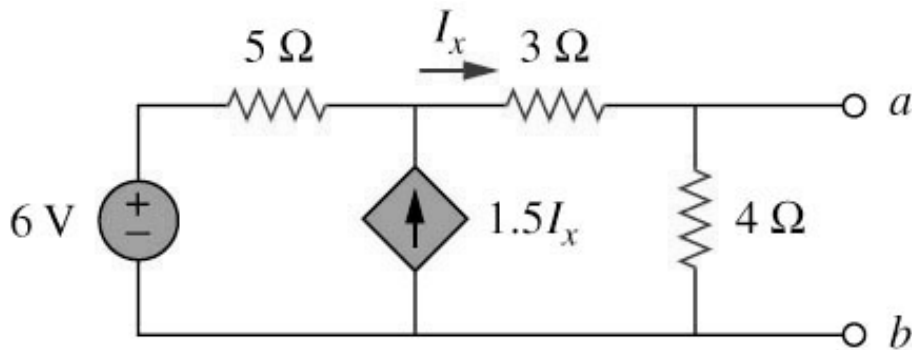Example 6


Find the Thevenin equivalent circuit of the circuit shown below to the left of the terminals.



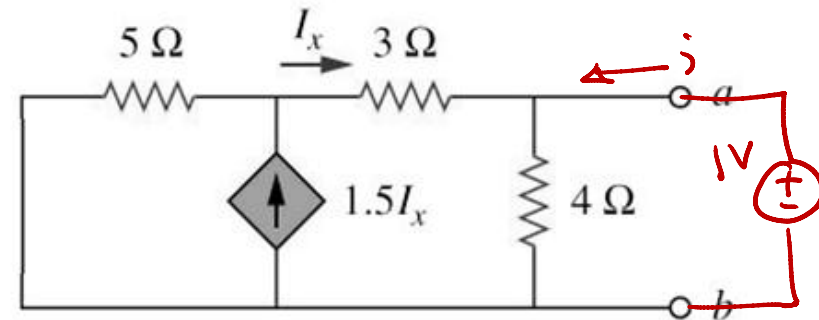b) Find R_{th} by i) turn off indep src
ii) connect external src



Finding V_{th} using Mesh Analysis

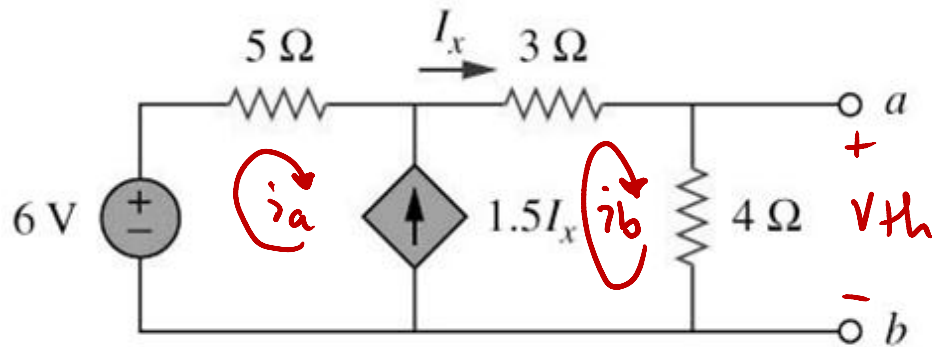

Super mesh:

$$-6 + 5i_a + 3i_b + 4i_b = 0$$

Constraint Eq:

$$i_b - i_a = 1.5I_x = 1.5i_b$$

Also $i_b = I_x$ or, $-0.5i_b = i_a$

Substituting $i_a = -0.5i_b$ into top eq


$$-2.5i_b + 7i_b = 6$$

$$i_b = \frac{6}{4.5} = 1.333$$

$$V_{th} = 4i_b = 5.333V$$

Finding R_{th} in cct with Depend Src

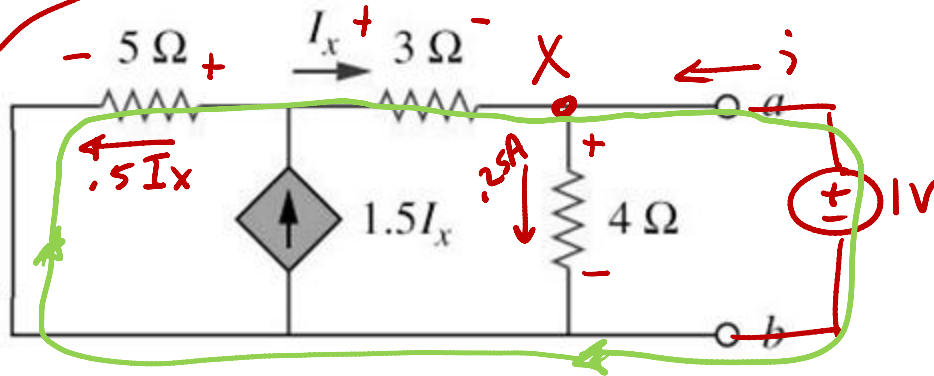- a) Turn off Indep Src b) Connect External Src (1V, could be anything)



c) solve for i

d) $R_{th} = \frac{1V}{i}$

c) KCL at X

$$I_x + i = .25A$$

KVL Green Loop

$$-5(.5I_x) + 3I_x + 1V = 0$$


$$.5I_x = -1$$

$$I_x = -2$$

$$\therefore i = .25A - I_x = 2.25A$$

d) $R_{th} = \frac{1V}{2.25A} = \underline{\underline{.44\Omega}}$

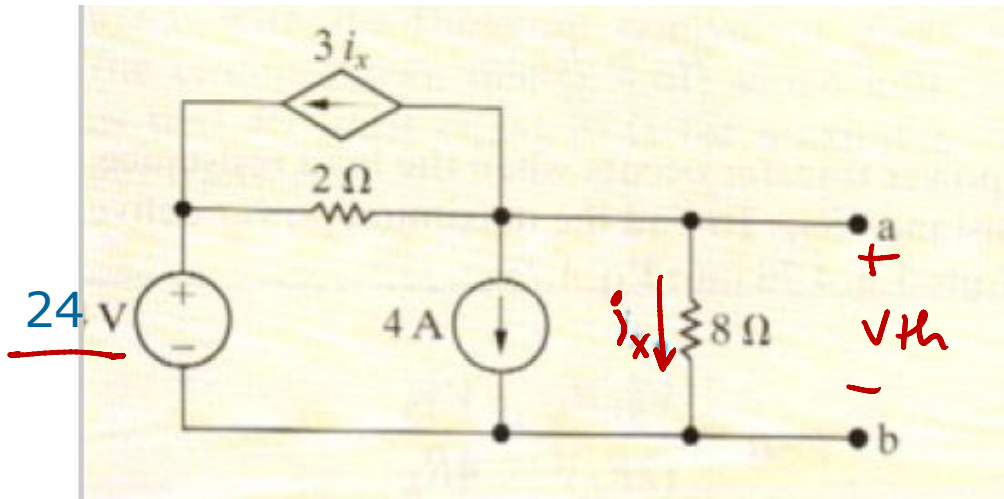5) Find Thevenin at a-b ($V_{th}=8$, $R_{th}=1$)




Nodal Analysis for V_{th}

$$\frac{V_{th}}{8} + 4 + \frac{V_{th} - 24}{2} + 3i_x = 0$$

$$i_x = \frac{V_{th}}{8}$$

$$8V_{th} = 64 \rightarrow V_{th} = \underline{\underline{8V}}$$

External src for R_{th}

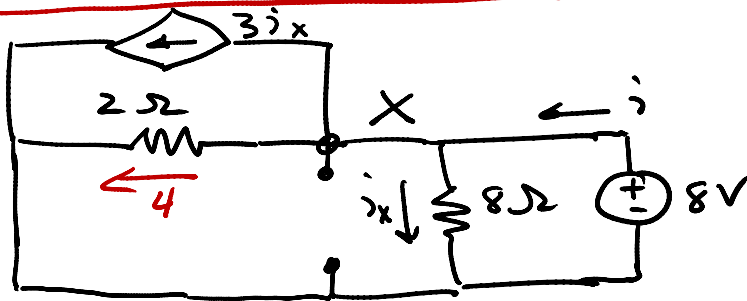


OL
 $i_x = 1A$

KCL at Node X

$$i = 1 + 4 + 3 = 8A \rightarrow R_{th} = \frac{8V}{8A} = \underline{\underline{1\Omega}}$$

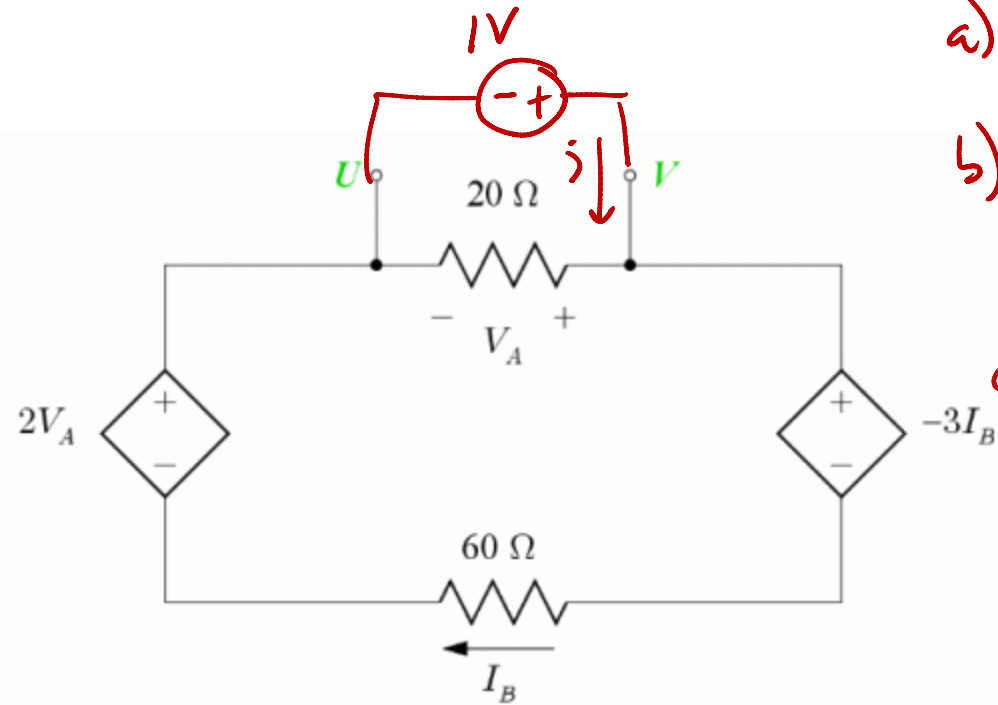6) Find the Thévenin equivalent circuit at the terminals U-V. ($V_{th}=0$, $R_{th} = 9.74$)



a) No Indep Src $\rightarrow V_{th} = 0$

b) Connect 1V Source

$$V_A = 1V$$

c) KVL

$$-2V_A - 1V + (-3I_B) + 60I_B = 0$$

$$57 I_B = 3V$$

$$I_B = \frac{3}{57} A$$

d) KCL at node V

$$i = \frac{1}{20} A + I_B = \frac{1}{20} + \frac{3}{57} = .1026 A$$


$$e) R_{th} = \frac{1V}{.1026A} = \underline{\underline{9.74 \Omega}}$$

4.6 Norton's Theorem (1)


It states that a linear two-terminal circuit can be replaced by an equivalent circuit of a current source I_N in parallel with a resistor R_N ,

Where

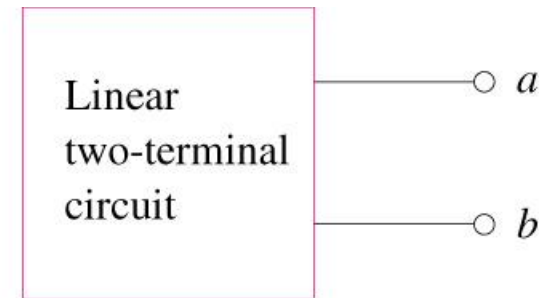- I_N is the short circuit current through the terminals.
- R_N is the input or equivalent resistance at the terminals when the independent sources are turned off.



(a)

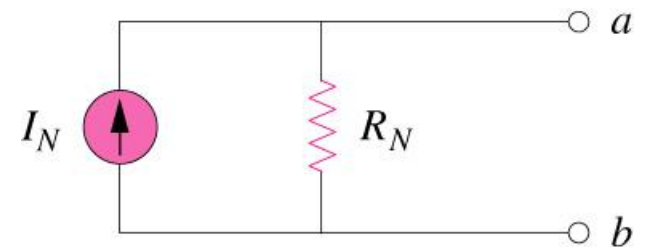


(b)

The Thevenin's and Norton equivalent circuits are related by a source transformation.


4.6 Norton's Theorem (2)

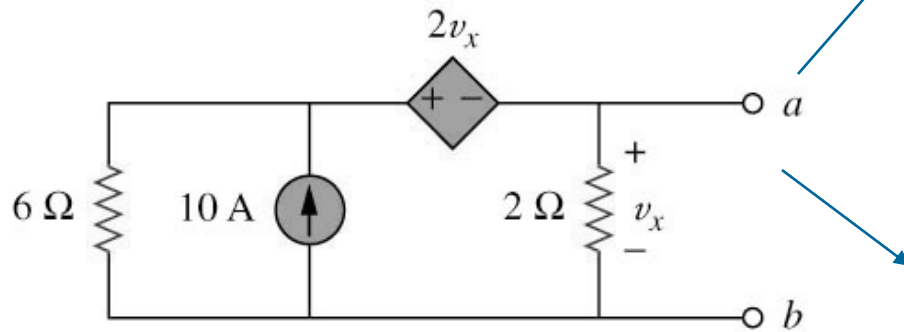Example 7


Find the Norton equivalent circuit of the circuit shown below.



a) Find $R_N = R_{Th}$

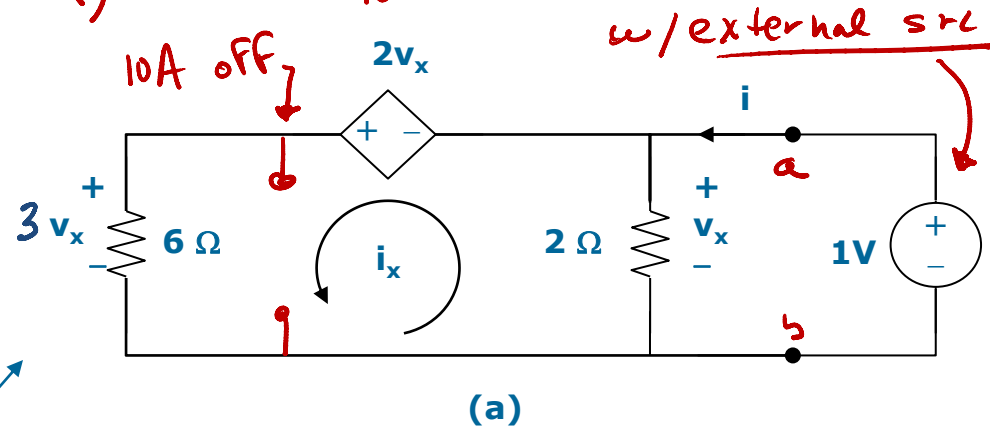


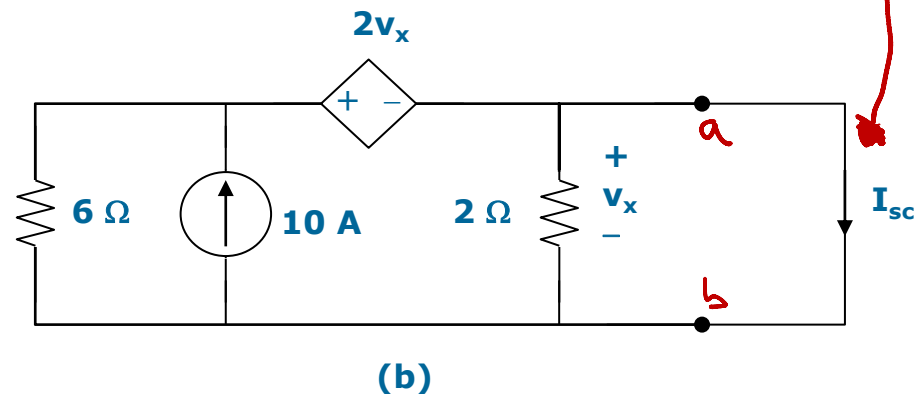b) Find $I_N = I_{sc}$, short circuit current thru a-b



*Refer to in-class illustration, textbook, $R_N = 1\Omega$, $I_N = 10A$.

Finding Norton Eq, previous slide

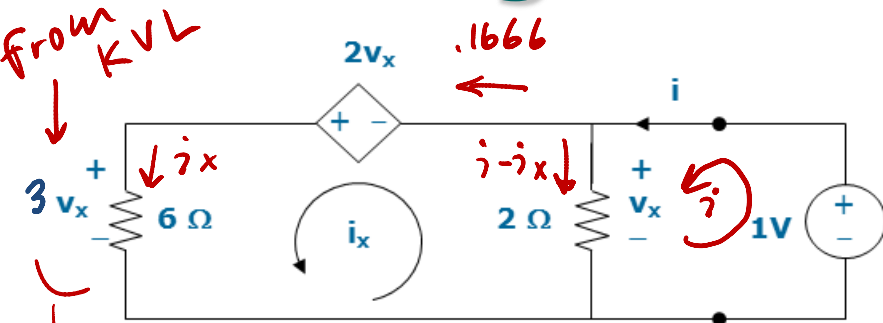

$$V_x = 1V$$



$$i_x = \frac{3V_x}{6} = .5A$$

$$2(i - i_x) = 1V$$

$$i = .5 + i_x = 1A$$

$$R_N = \frac{1V}{1A} = \underline{\underline{1\Omega}}$$

NORTON EQUIV

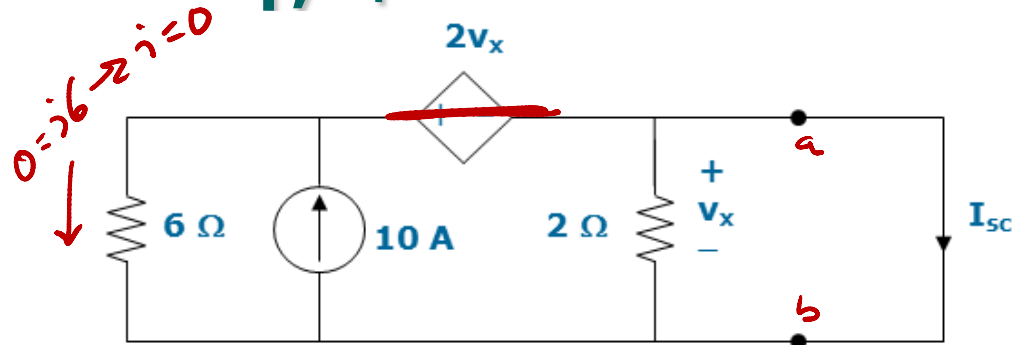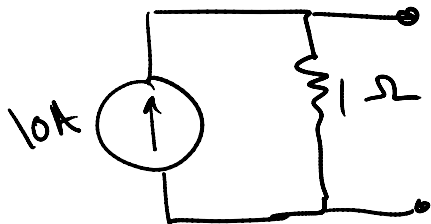


Shorting a-b sets $V_x \equiv 0$
 $+ 2V_x \equiv 0$

All current goes thru a-b
 path of last resistance

$$I_{sc} = 10A = \underline{\underline{I_N}}$$

Thevenin Equiv

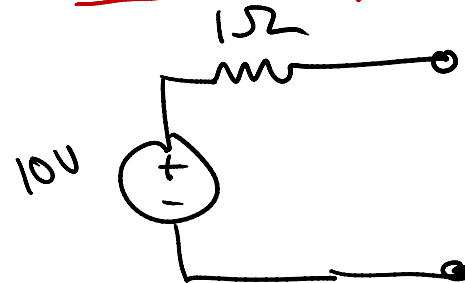

- Or find V_{th} and calculate $I_{sc} = V_{th}/R_{th}$

4.7 Maximum Power Transfer (1)



If the entire circuit is replaced by its Thevenin equivalent except for the load, the power delivered to the load is:

$$P = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

To max power going to R_L ,

$$\text{set } R_L = R_{Th}$$
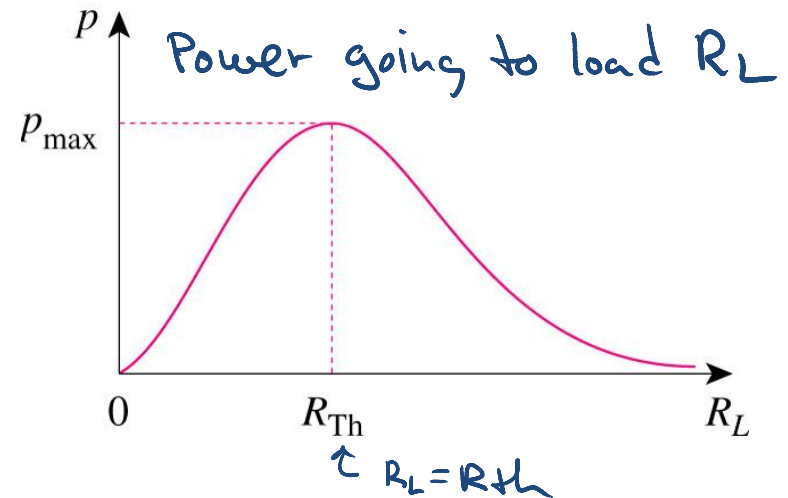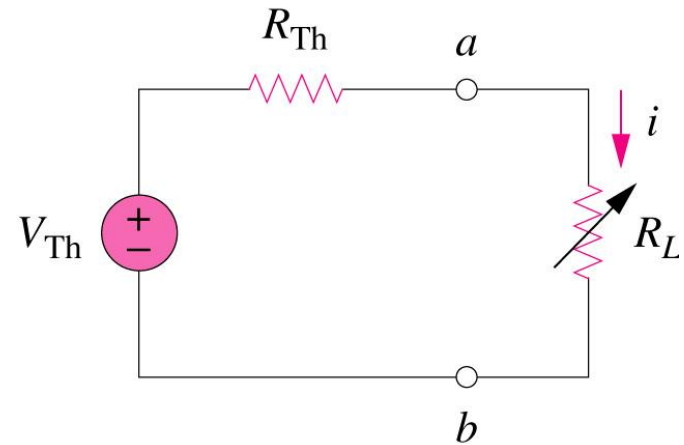
$$\text{then } \underline{\underline{P_{max} = \frac{V_{Th}^2}{4 R_L}}}$$





The power transfer profile with different R_L


4.7 Maximum Power Transfer (2)

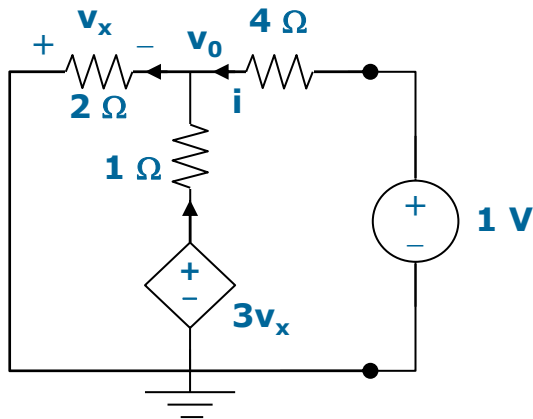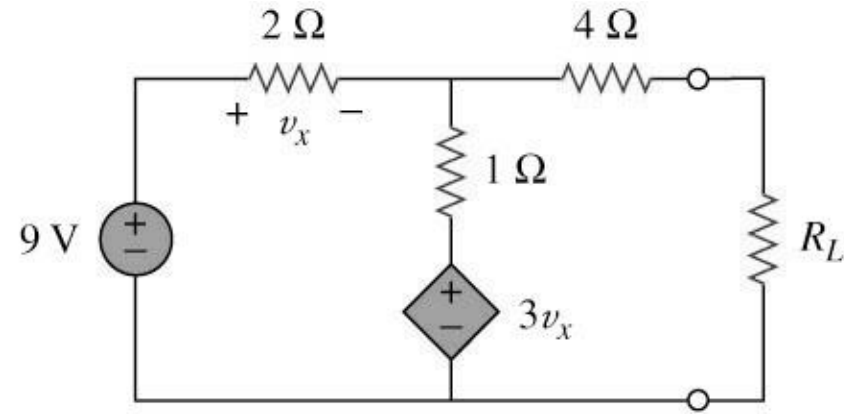Example 8

Determine the value of R_L that will draw the maximum power from the rest of the circuit shown below. Calculate the maximum power.



(a)

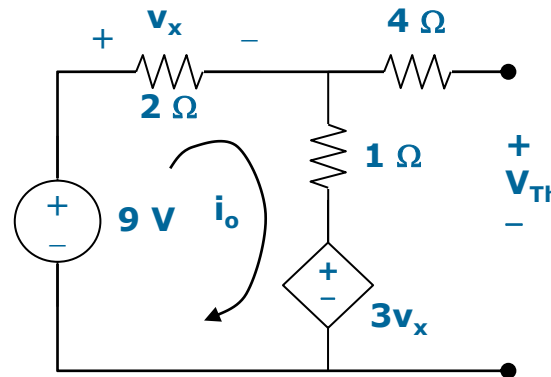

(b)

Fig. a


=> To determine R_{TH}

Fig. b

=> To determine V_{TH}

*Refer to in-class illustration, textbook, $R_L = 4.22\Omega$, $P_m = 2.901W$ 36

a) Find Rth

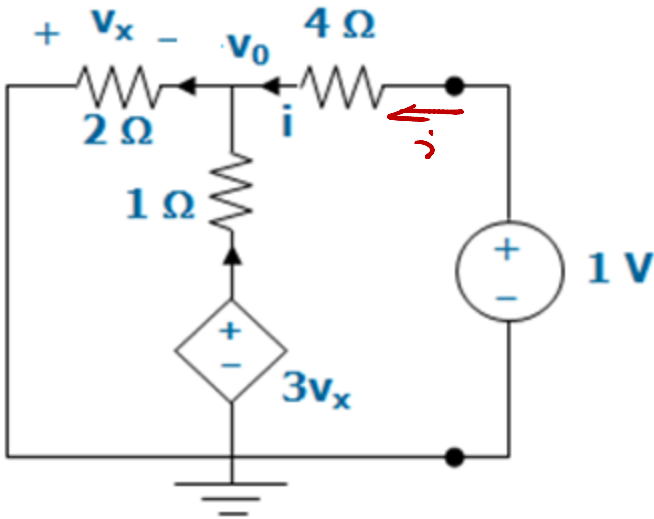

Use Nodal Analysis

$$\frac{v_0}{2} + \frac{v_0 - 3v_x}{1} + \frac{v_0 - 1}{4} = 0$$

$$v_x = -v_0$$

$$19v_0 = 1, \quad v_0 = \frac{1}{19} = .0526 \text{ V}$$

$$i = \frac{1 - v_0}{4} = \frac{1 - .0526}{4} = .2368$$

$$R_{th} = \frac{1}{.2368} = \underline{\underline{4.22 \Omega}}$$

b) Find V_{th}

Use Mesh Analysis

$$-9 + 2i_o + 1i_o + 3v_x = 0$$

$$v_x = 2i_o$$

$$9i_o = 9, \quad i_o = 1A$$


KVL

$$-3v_x - 1i_o + 4(0) + V_{th} = 0$$


$$V_{th} = 3v_x + 1i_o = \underline{\underline{7V}}$$

$$R_L = R_{th} = \underline{\underline{4.22\Omega}}$$
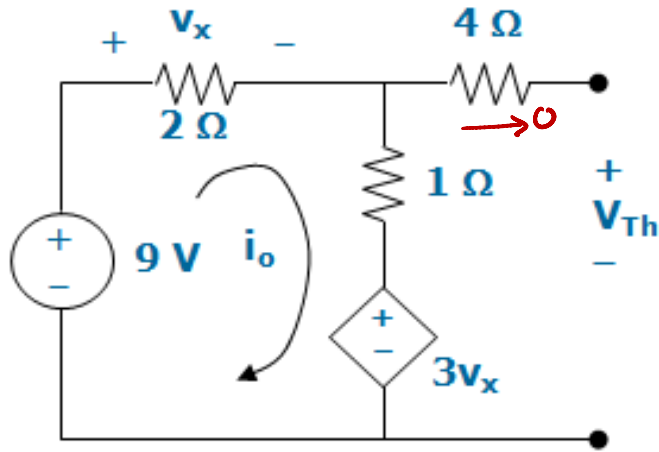
$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{7^2}{4(4.22)} = \underline{\underline{2.901W}}$$




Thevenin Eq Ckt:

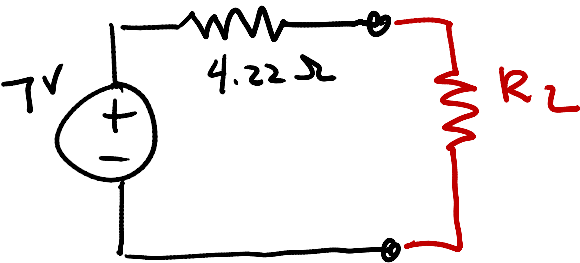

c) Set $R_L = R_{th}$

$$P_{max} = V_{th}^2 / (4R_{th}) \quad [2.901W]$$

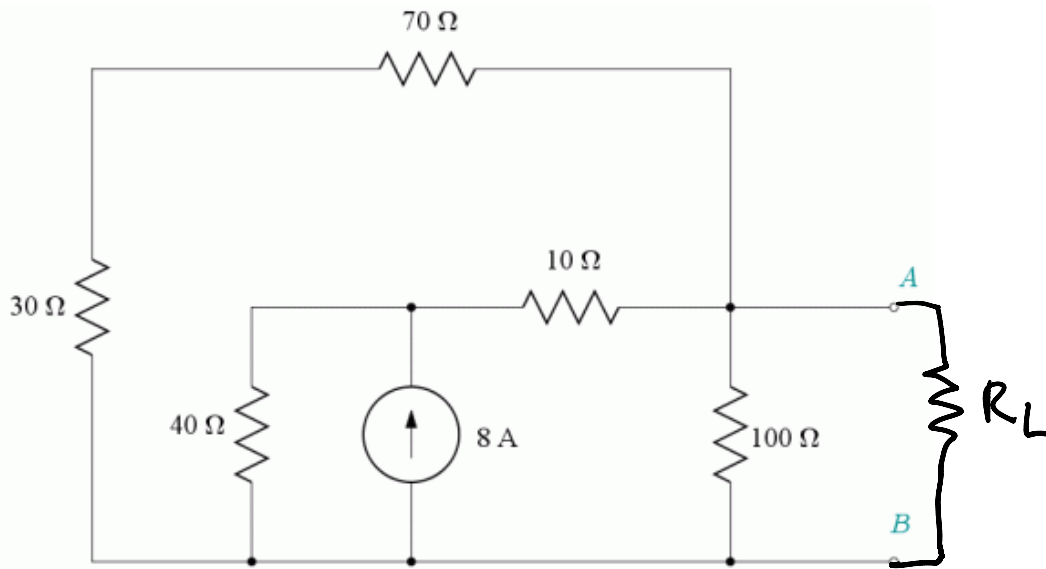7) What is the most power we can deliver to R_L ?
(use V_{th} , R_{th} from prob 4) [256 W]




$$V_{th} = 160 \text{ V}$$

$$R_{th} = 25 \Omega$$

$$\text{Set } R_L = R_{th} = 25 \Omega$$

$$P_{max} = \frac{160^2}{4(25)} = 256 \text{ W}$$

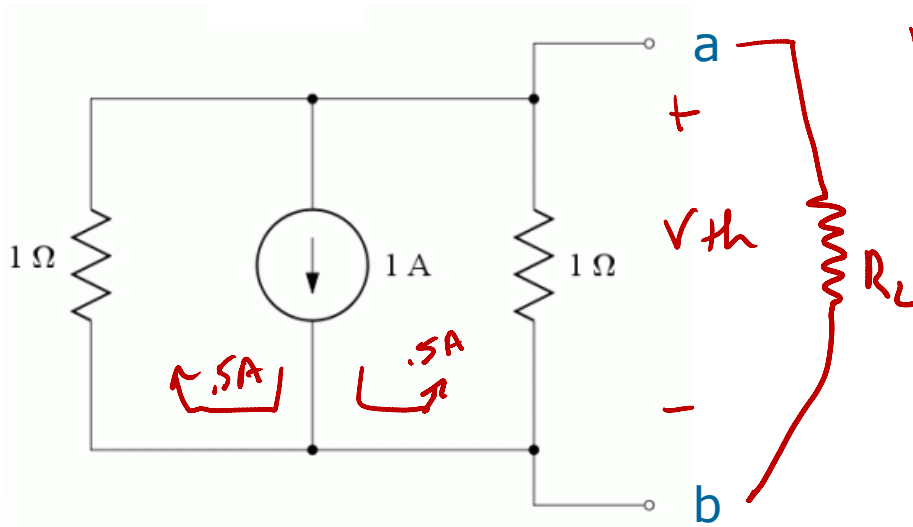
8) Find the Max Power that can be delivered to a load at a-b [125 mW]



$V_{th} = -0.5V$

← Set $R_L = R_{th} = 0.5\Omega$

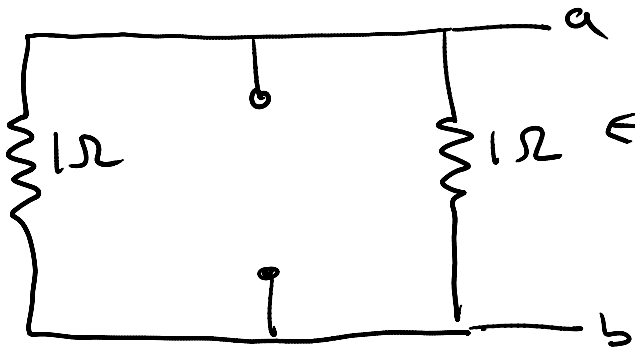$P_{max} = \frac{(-0.5)^2}{4(0.5)} = \underline{\underline{.125W}}$



← $R_{th} = 1 // 1 = 0.5\Omega$

Summary of Thevenin/Norton

- V_{th} = open cct voltage at terminals
- R_{th} = equivalent Resistance seen at terminals when all independent sources turned off
- I_n = current through terminals when they are shorted
- $R_n = R_{th}$
- $I_n = V_{th}/R_{th}$, $V_{th} = I_n * R_n$

Finding R_{thevenin}

- IF Circuit has ONLY Independent Srcs:
 - Option A:
 - Turn off all sources
 - Find equivalent resistance between terminals
 - Option B:
 - Find V_{th} , I_{in} (short circuit current)
 - $R_{\text{th}} = V_{\text{th}}/I_{\text{in}}$

Finding R_{thevenin}


- If Circuit has Dependent + Independent Sources:
 - Option A:
 - Turn off all INDEP sources
 - Connect an External Source to terminals (V_o or I_o)
 - Find the other quantity (I_o or V_o)
 - $R_{\text{th}} = V_o/I_o$
 - Option B:
 - Find V_{th} (open ckt volts), I_{in} (short ckt current)
 - $R_{\text{th}} = V_{\text{th}}/I_{\text{in}}$

Finding Rthevenin


- Circuit has ONLY Dependent Sources:
 - Only Option:
 - Connect an External Source to terminals (V_o or I_o)
 - Find the other quantity (I_o or V_o)
 - $R_{th} = V_o/I_o$

Handouts

1) Use Superposition to find V_x (3V)

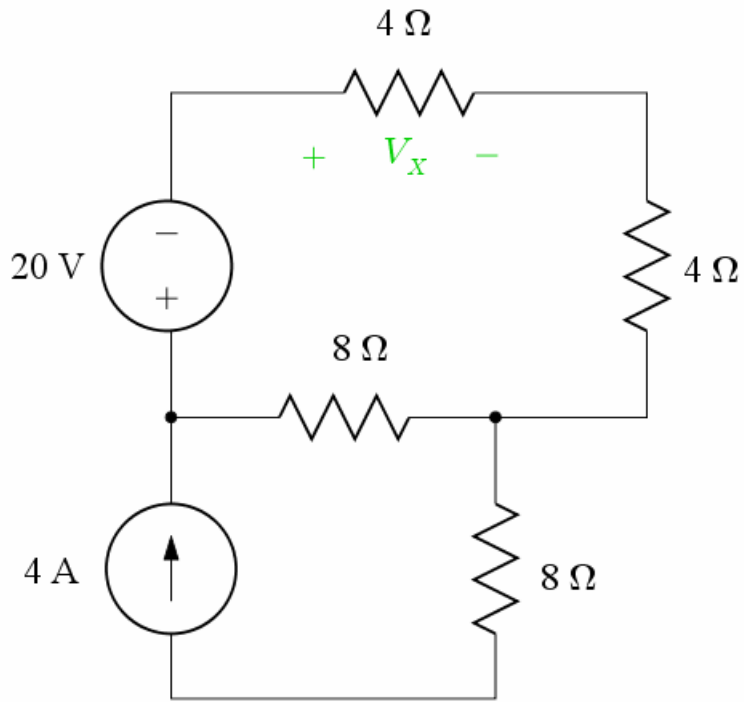


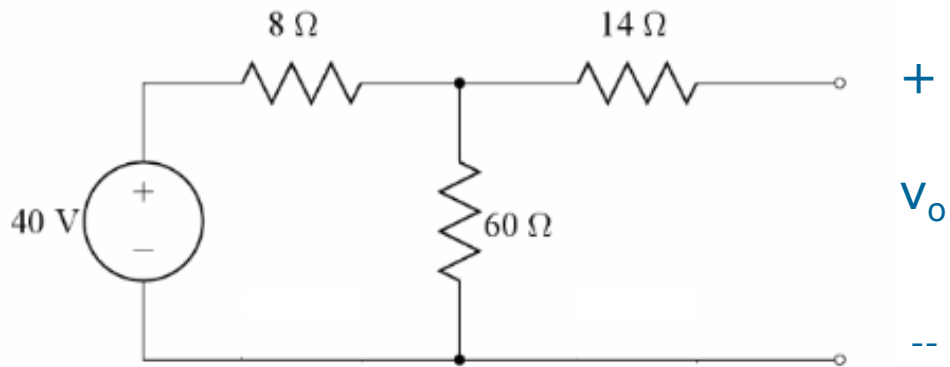2) Find v_o in the circuit shown below using source transformation.




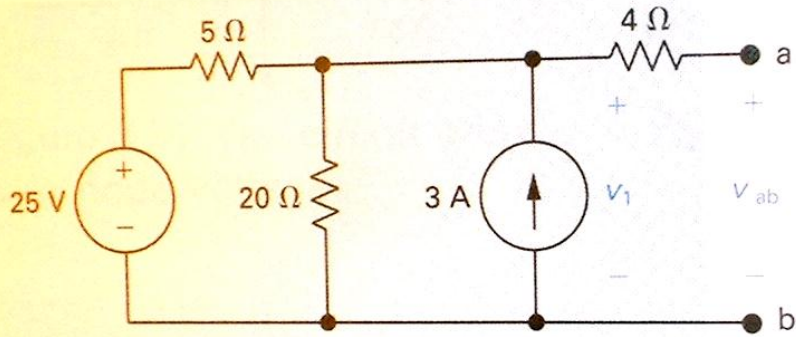3) Find Thevenin Eq at a-b

note how R_4 does not affect V_{oc} ! [$V_{th}=32$, $R_{th}=8$]




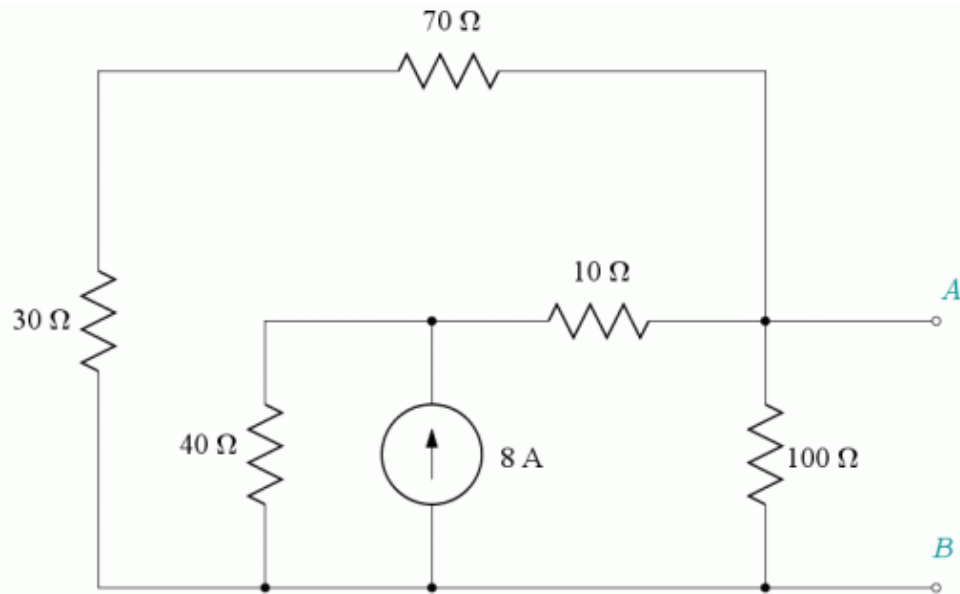4) Find the Thèvenin equivalent circuit at the terminals A-B. $R_t = 25\Omega$; $V_t = 160V$




5) Find Thevenin at a-b ($V_{th}=8$, $R_{th}=1$)


24

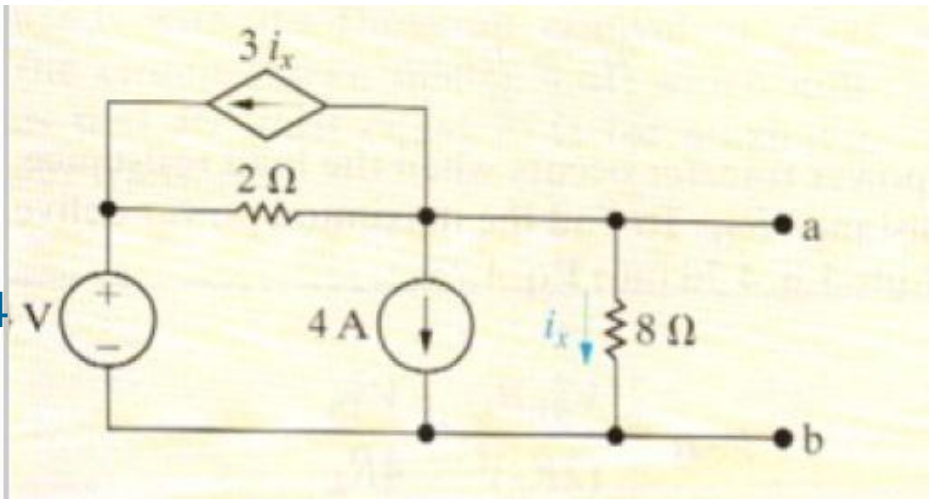

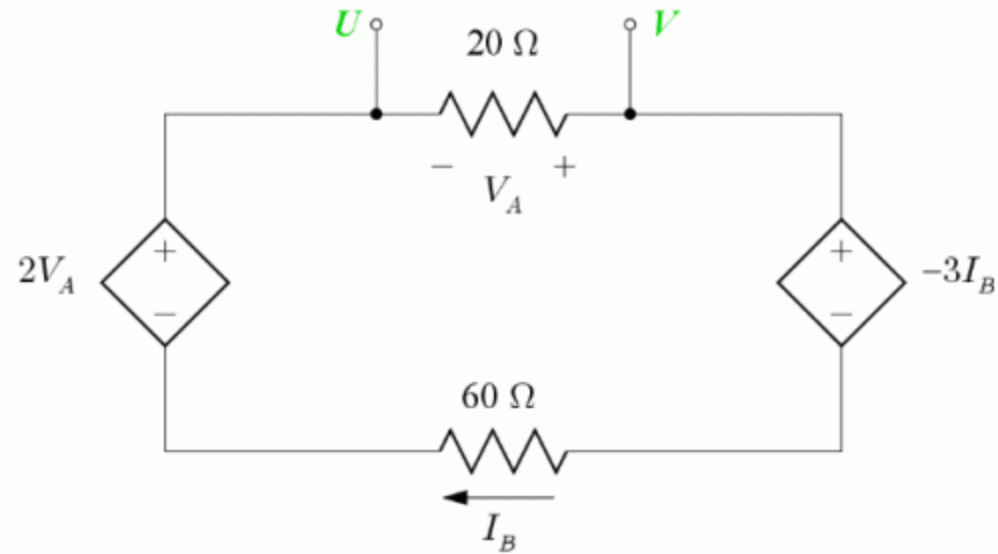6) Find the Thévenin equivalent circuit at the terminals U-V. ($V_{th}=0$, $R_{th} = 9.74$)



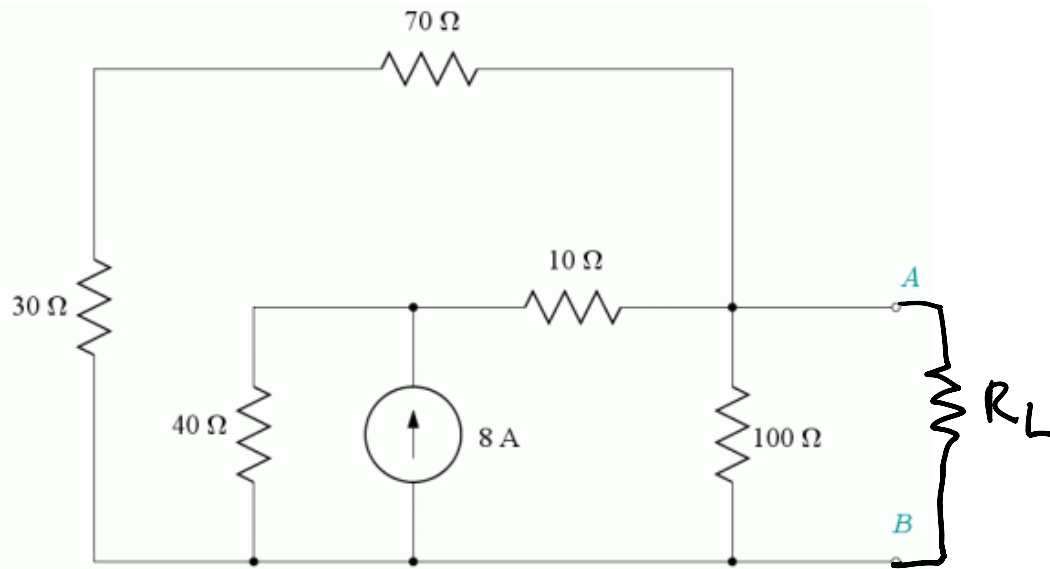7) What is the most power we can deliver to R_L ?
(use V_{th} , R_{th} from prob 4) [256 W]



8) Find the Max Power that can be delivered to a load at a-b [125 mW]

