

# Chapter 5


## The Operational Amplifier

This all came about in the 1930's when Bell Telephone had problems sending telephone signals over long distances....

amplifiers sensitive to temp and humidity →  
variable phone reception
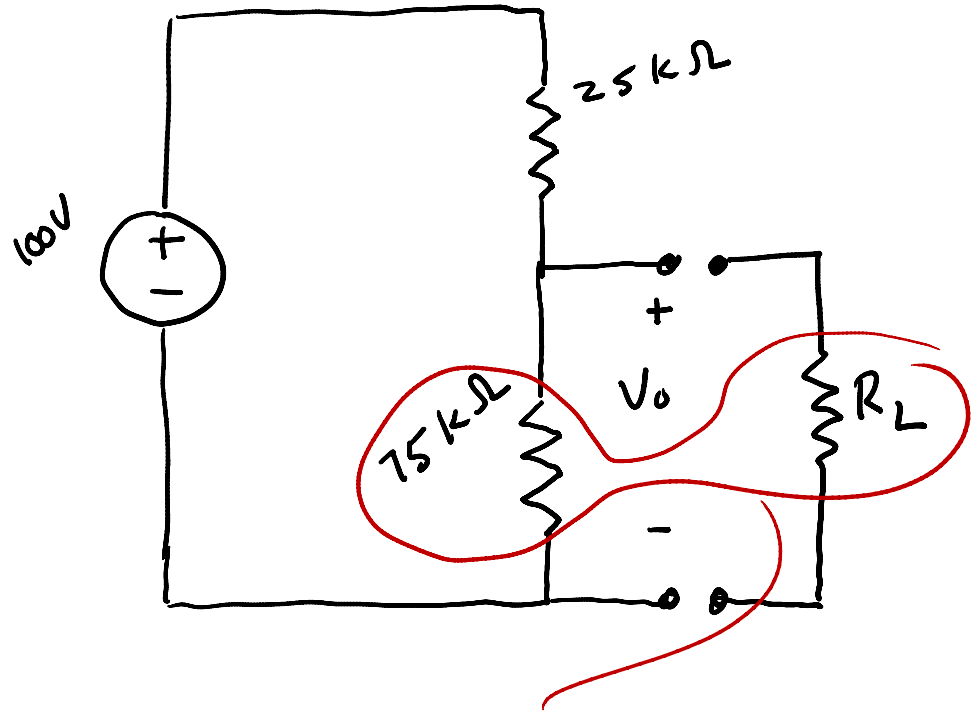
# Recall Voltage divider with Load $R_L$

- "no-load"  $v_o = 75V$
- attach  $R_L = 150k$ ,  
 $v_o$  drops to  $66.6 V$



*Resistors in || are smaller*

- The load "pulls down" the output voltage  
*not good for consumer electronics!*


# Amplifiers

- Amplifiers are devices that magnify signals, and also remain mostly unaffected by changing load resistance. *constant output*
- Amplifiers are used in many instruments and electronic devices (iPod, cell phone, EEG) to boost signals (music, brainwaves) and buffer (isolate) them from loads.

# Agenda


- Basic Amplifier Concepts
- The Op-Amp Model
- How to solve using KCL/KVL
- Standard Op-Amp Circuit Patterns
- Cascaded Op-Amp Circuits

# CircuitLab Model of an Op-Amp

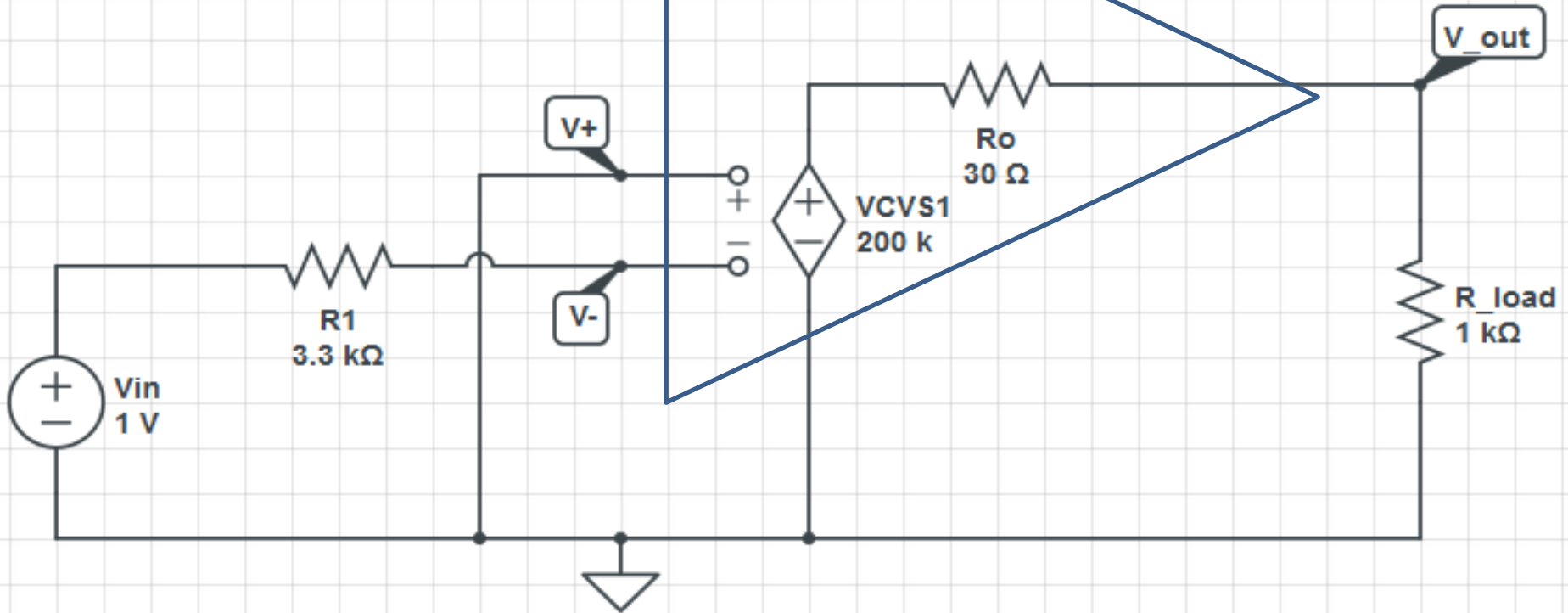

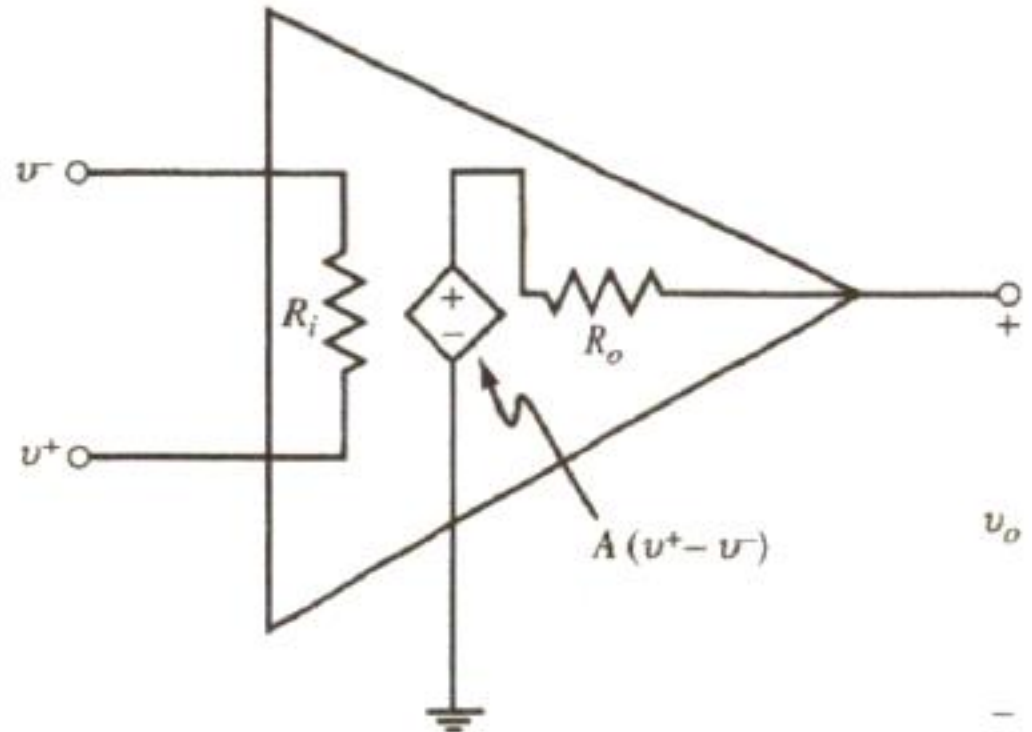
# Non-ideal (realistic) Op-Amp model – use this on Assignment 6 prob5

- Typically:
  - $R_i$  is very large 1M-ohm
  - $R_o$  is small
  - $A$  is  $10^5 - 10^6$
  - model applies to linear range only





# The Operational Amplifier

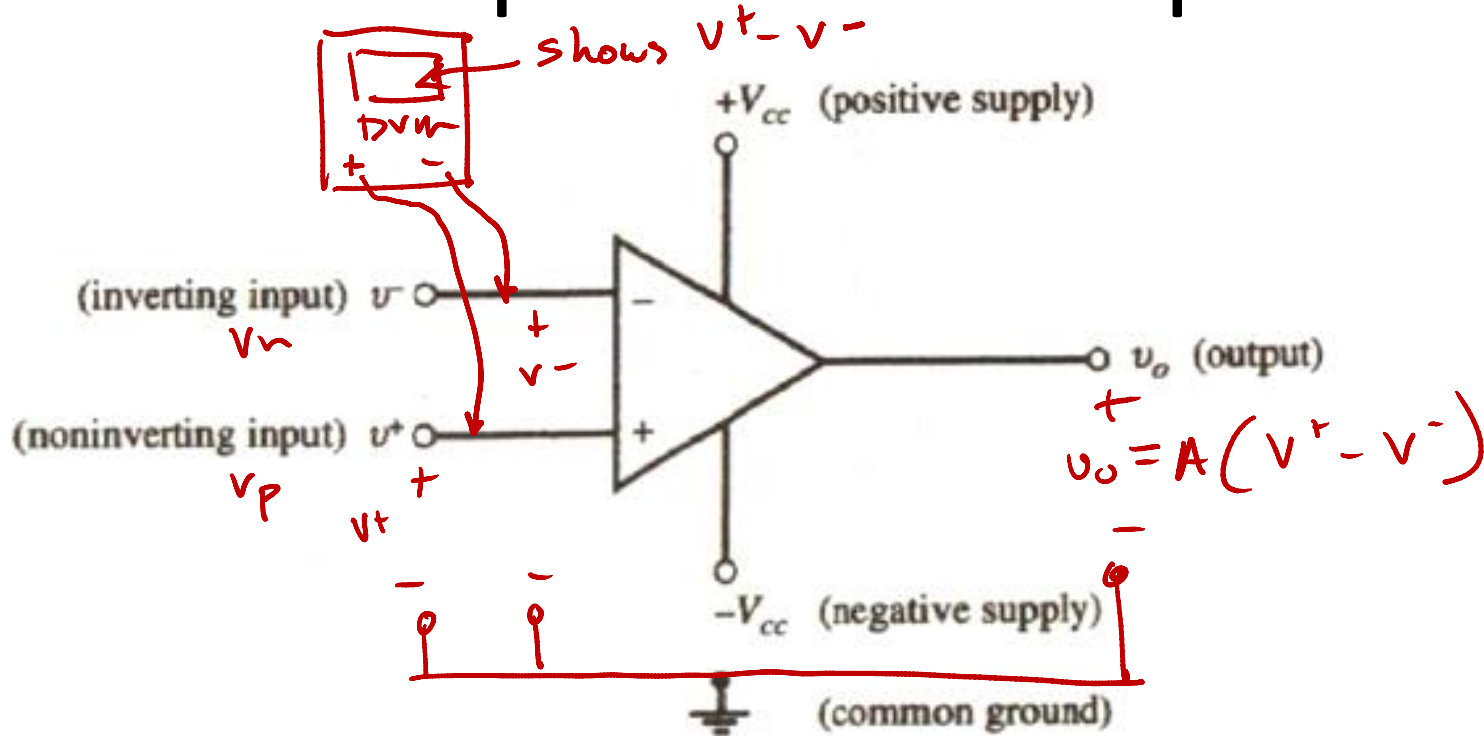



- $v^+$  and  $v^-$  are node voltages relative to ground  
sometimes we use  $v_p$  and  $v_n$
- $v_o = A(v^+ - v^-)$ , ie. A times voltage across the input
- $V_{cc}$ ,  $-V_{cc}$  are power supply inputs, usually  $\pm 15V$
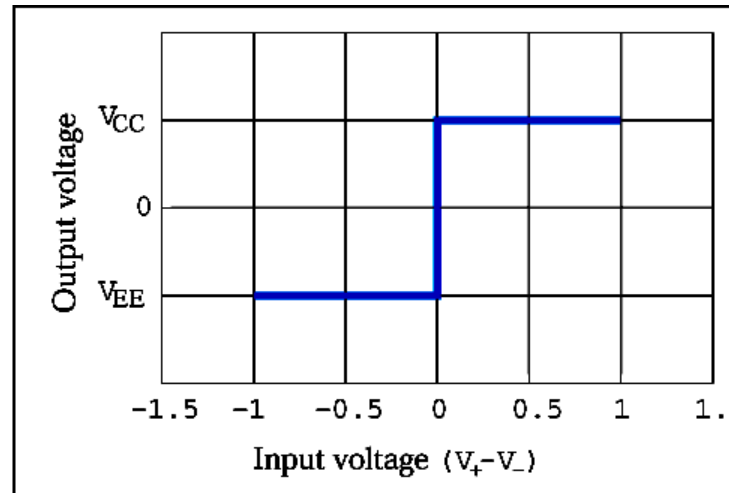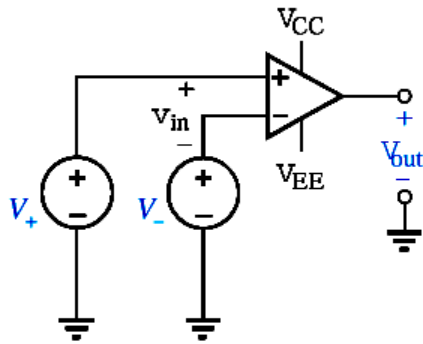
# Op Amps can be used "open loop" outside linear range, $v_+ \neq v_-$

- Ideal Comparator and Transfer Characteristic



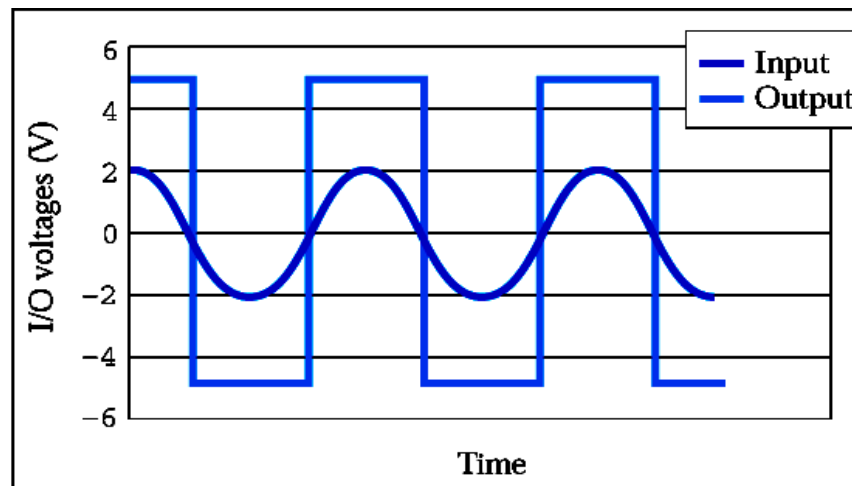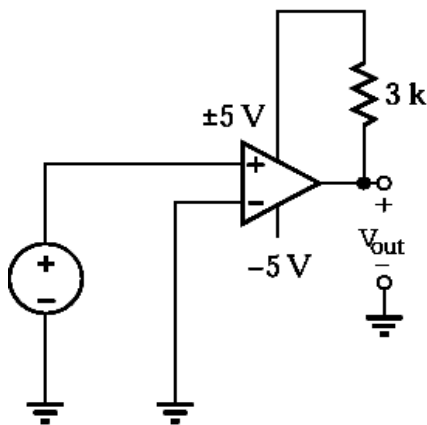- “Zero-Cross” Detector - not so good for telephone use!





# 2 Ways of Using Op-Amps

- “Open Loop”: very high gain amplifier
  - Useful for comparing 2 voltages

*(nonlinear)* – Fixed gain, always at MAX OUTPUT!!

ENGR 12


- “Closed Loop” with negative feedback



*(linear)* – Useful for amplifying, adding, subtracting, differentiation and integration (using capacitors)  
– Variable gain, controlled by resistor selection
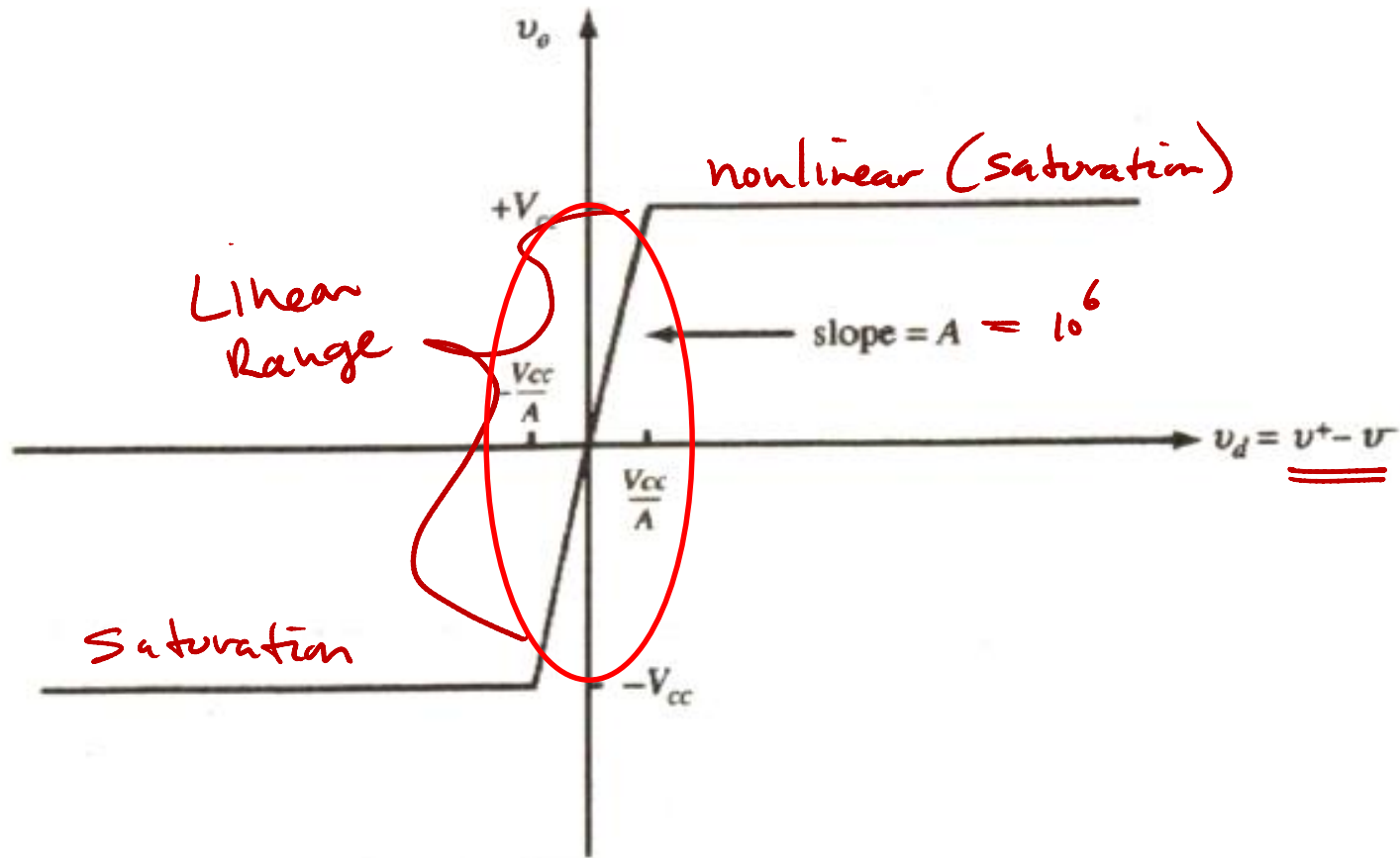
# Linear Operation –


$v_d = v_p - v_n$  is from  $-V_{cc}/A$  to  $+V_{cc}/A$


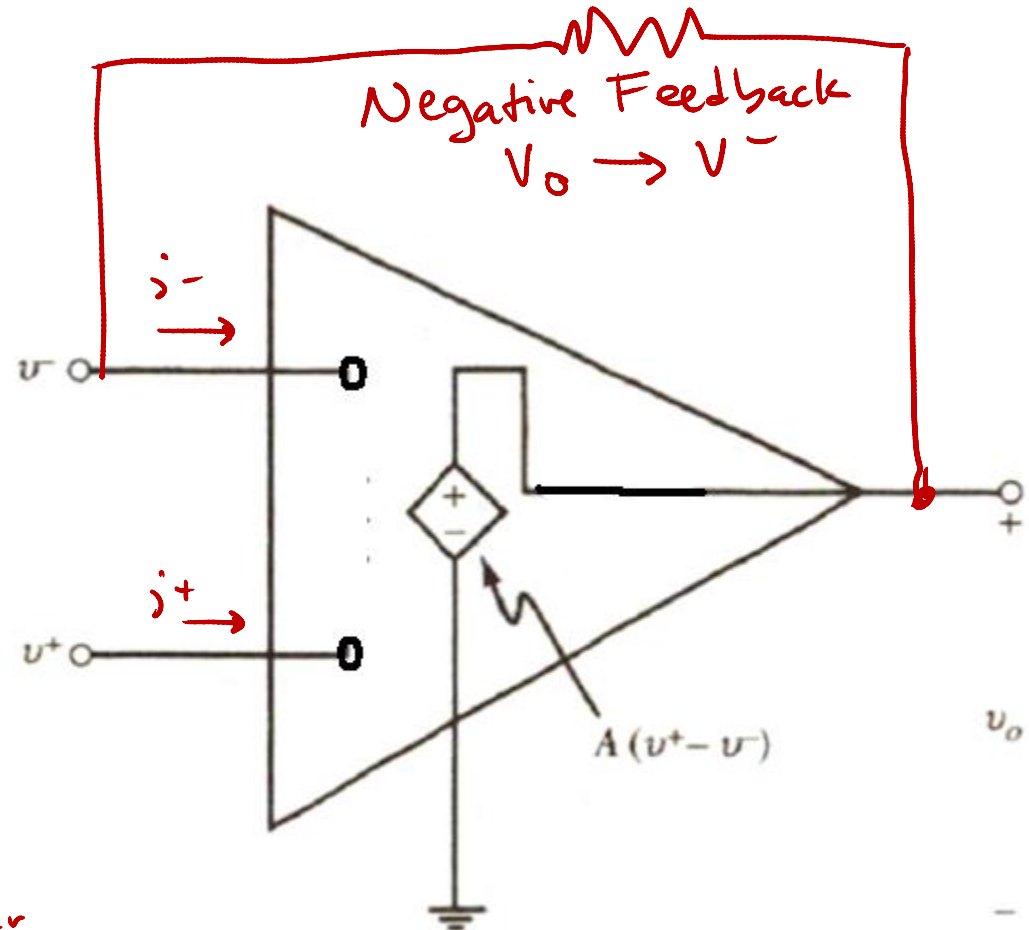
# Ideal Op Amp Model -- Closed Loop

- $R_i = \text{infinity}$
- $R_o = 0$
- $A = \text{infinity}$
  
- $i_+ = i_- = 0$
- $v_+ = v_-$

IF negative feedback  
AND  $v_o$  is within linear  
output range



# Standard Form 1: Inverting Amplifier

Neg feedback ✓  
Linear vo ✓ (limit not given)


$$v_1 = v_2 = 0$$

KCL at Node 1

$$\frac{v_i - v_1}{R_1} + \frac{v_o - v_1}{R_f} = 0$$

$$v_o = -\frac{R_f}{R_1} v_i$$
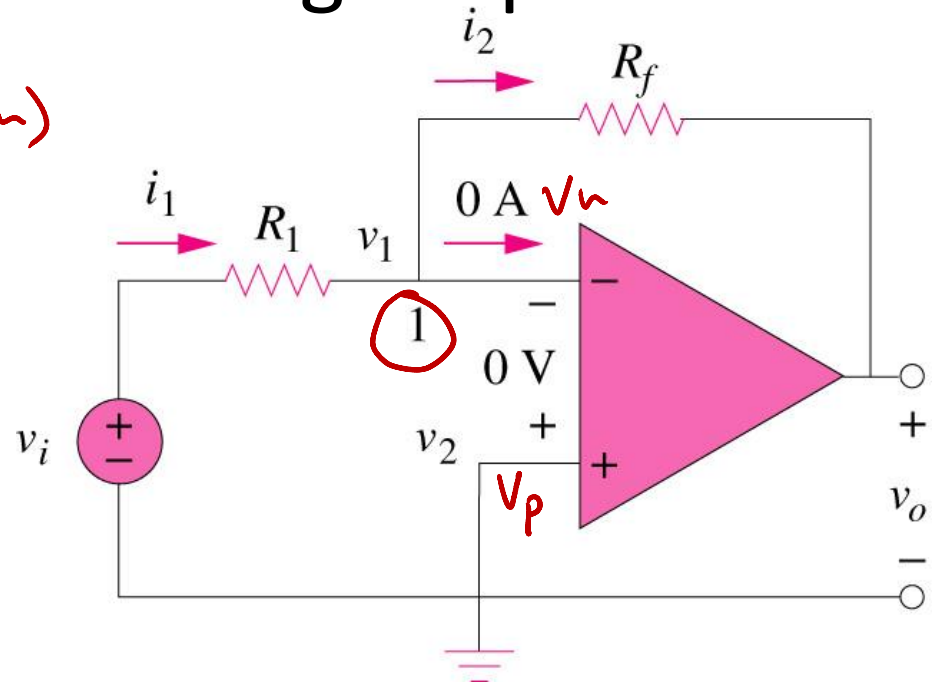
$$\text{Gain} = \frac{v_o}{v_i} = -\frac{R_f}{R_1}$$



$$v_o = -\frac{R_f}{R_1} v_i$$


# Example Inverting Op-Amp Problem

a) Calculate  $V_o$  for

$V_s = 0.4, 2, 3.5, -0.6, -1.6, -2.4$

$$V_o = -\frac{R_f}{R_i} V_s = -\frac{80}{16} V_s = -5 V_s$$

$V_s$	$V_o$
0.4	-2
2	-10
3.5	<del>-17.5</del> -15 limit
-0.6	+3
-1.6	+8
-2.4	<del>+12</del> +10 limit

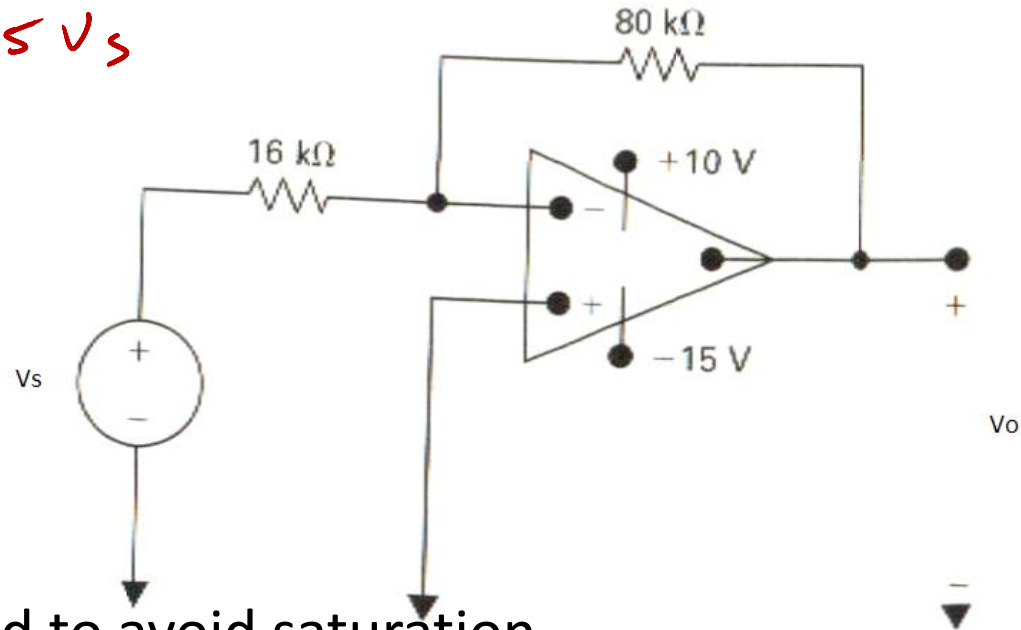

b) Specify the range of  $V_s$  required to avoid saturation

$$+10 = -5 V_s \quad , \quad V_s = -2 V$$

$$-15 = -5 V_s \quad , \quad V_s = +3 V$$

↑  
limits


$$\underline{-2 < V_s < 3}$$

# 1) Problem 1 INVERTING OP AMP

find the voltage  $v_o$  across the  $1\text{k}\Omega$  resistor.  $[-5\text{V}]$

$$V_i = -\frac{15}{3}(2) = -10\text{V}$$
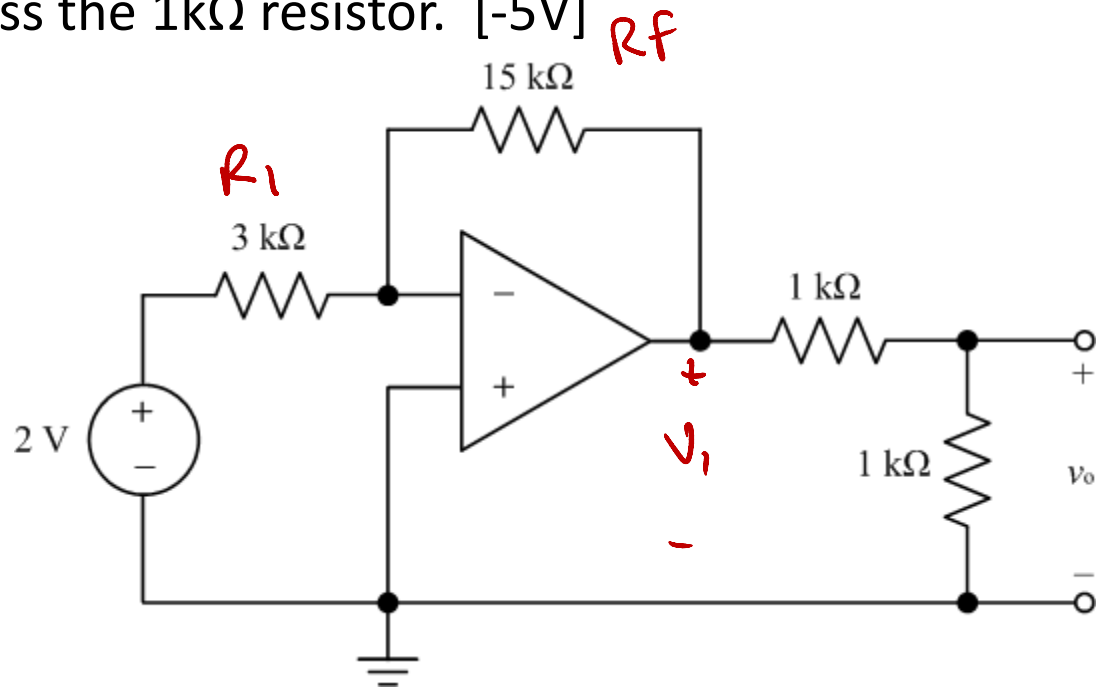
$$V_o = V_i \left(\frac{1}{2}\right) = \underline{\underline{-5\text{V}}}$$



# How to Approach Op-Amp probs

1. Check for negative feedback  
All of our Op-Amp ccts will be “Closed Loop” with negative feedback
2. Assume current flowing into  $V_p/V_n$  terminals of op-amp = 0
3. Assume Op-Amp in linear range  
This means  $V_p$  must =  $V_n$   
otherwise  $A(V_p-V_n)$  takes us to saturation
4. Determine value of  $V_p$
5. Set  $V_n = V_p$
6. Set up nodal equation at  $V_n$  node and solve for  $V_o$
7. Check that  $V_o$  does not exceed power supply voltages  $\pm V_{cc}$  (if given)  
If so, then assumptions 3 and 5 do not hold  
Set  $V_o$  to the power supply voltage and recalculate

If you recognize common forms you can use formulas related to them

- Very helpful in cascaded Op-Amp problems
- Best not to depend too much on these
- You should always be able to go back to KCL/KVL

# Standard Form 2: Summing Amplifier


$$V_n = V_p = 0$$

KCL node a

$$\frac{v_1 - 0}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} - \frac{0 - v_o}{R_f} = 0$$

$$v_o = - \left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$$

Sum of inputs

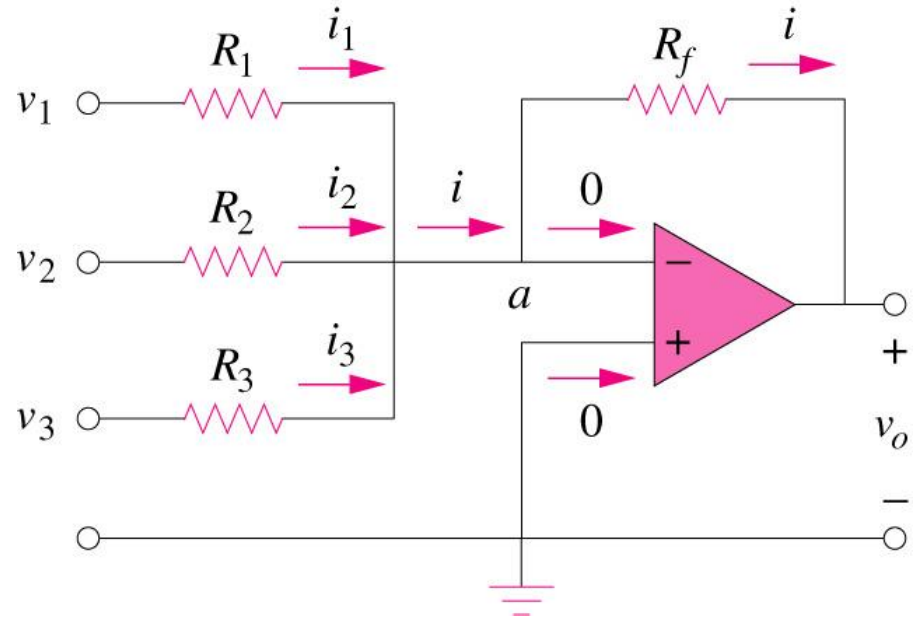

$$v_o = - \left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$$



# Summing Amplifier Example


Calculate  $v_o$  and  $i_o$  in the op amp circuit shown below.

Use formula, or KCL

$$\frac{(2-0)}{5} + \frac{(1-0)}{2.5} - \frac{(0-v_o)}{10} = 0$$

$$v_o = -10 \left( \frac{2}{5} + \frac{1}{2.5} \right) = -8V$$
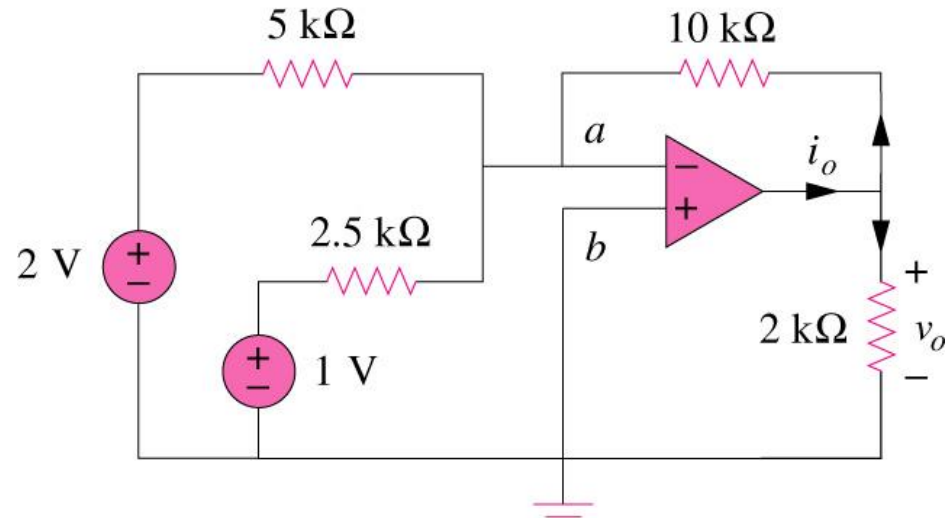
$$i_o = \frac{v_o}{10} + \frac{v_o}{2} = -4.8 \text{ mA}$$



Ans: -8V, -4.8mA

## 2) Problem 2) Summing Op-Amp


Find  $V_o$  in the circuit shown if  $V_a=0.1V$  and  $V_b= 0.25V$  [-7.5]

$$V_o = - \left( \frac{R_f V_1}{R_1} + \frac{R_f V_2}{R_2} \right)$$

$$V_o = - \left( \frac{250}{5} V_a + \frac{250}{25} V_b \right)$$

$$= - (5 + 2.5)$$

$$= -7.5 V$$

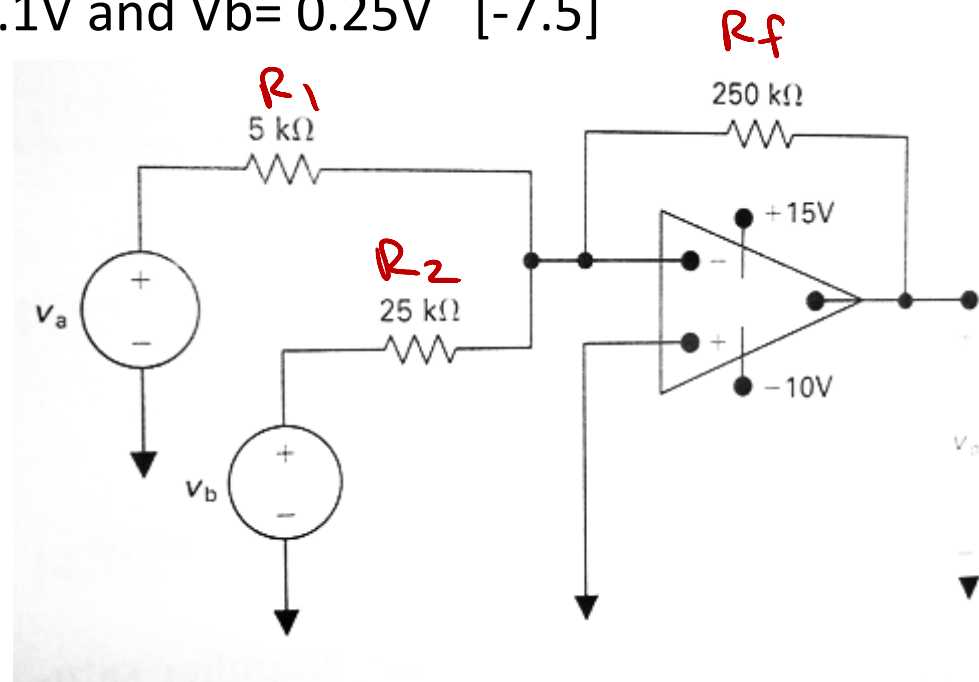

# Standard Form 3: Non-Inverting Amplifier


$$V_1 \equiv V_2 = V_i$$

KCL at  $V_1$

$$\frac{0 - V_1}{R_1} + \frac{V_o - V_1}{R_f} = 0$$

$$V_o = R_f \left( \frac{V_i}{R_1} + \frac{V_i}{R_f} \right)$$

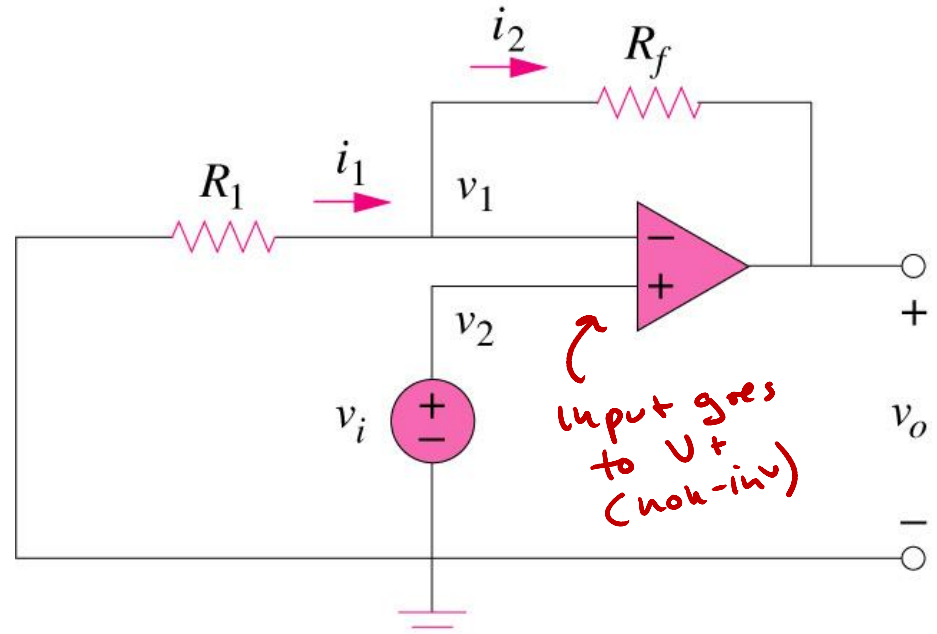
$$V_o = V_i \underbrace{\left( \frac{R_f}{R_1} + 1 \right)}_{\text{Gain} > 1}$$



$$v_o = \left( 1 + \frac{R_f}{R_1} \right) v_i$$
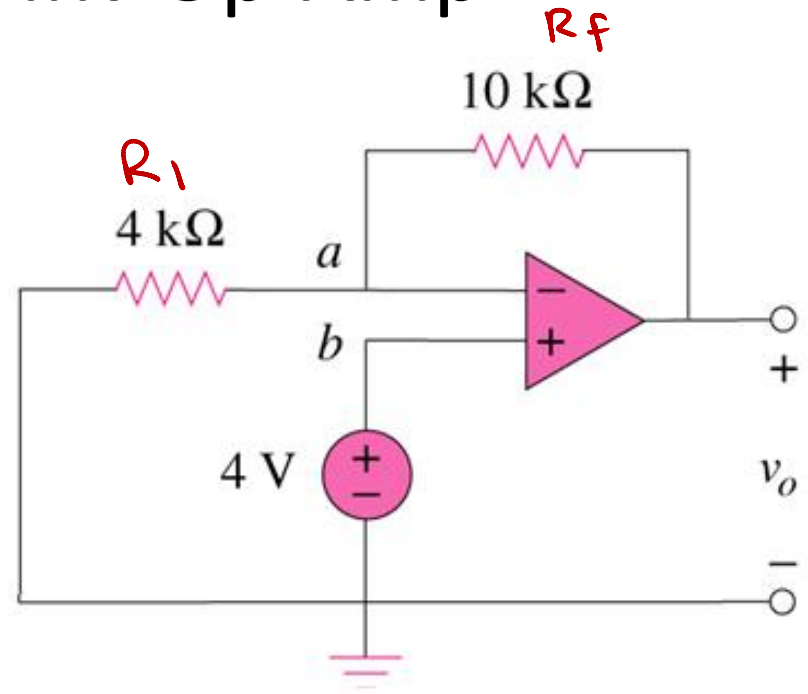
# Find $V_o$ for the Non-Inv Op-Amp

$$\begin{aligned}V_o &= V_i \left( \frac{R_f}{R_1} + 1 \right) \\ &= 4 \left( \frac{10}{4} + 1 \right) \\ &= 14 \text{ V}\end{aligned}$$



### 3) Problem 3) Non-Inverting

Find the output Voltage when  $R_x$  is set to 60k

What  $R_x$  will cause saturation? [4.8V, 75k]

a) Non-inverting

Voltage divider on input

$$V_p = .4 \left( \frac{60}{15+60} \right) = .32V$$

now use formula


$$V_o = V_p \left( \frac{R_f}{R_1} + 1 \right) \\ = .32 \left( \frac{63}{4.5} + 1 \right) = \underline{\underline{4.8V}}$$

b) Total formula for  $V_o$

$$V_o = .4 \left( \frac{R_x}{15+R_x} \right) (15) = +5 \text{ at saturation}$$

Solve for  $R_x$
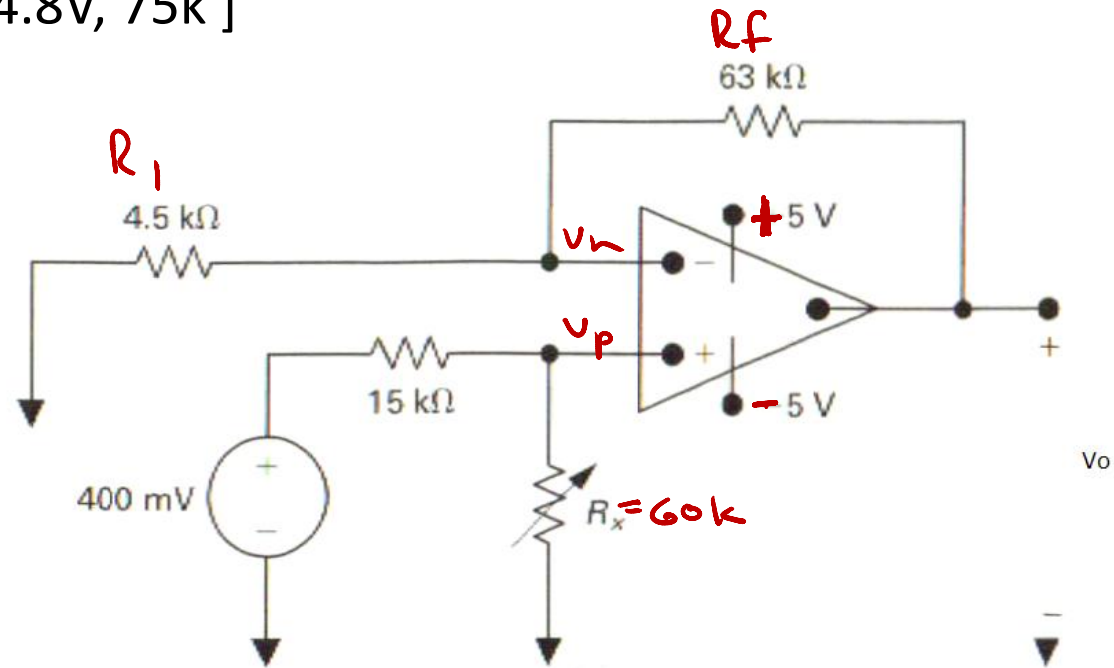
$$R_x (6) = 5(15+R_x), \underline{\underline{R_x = 75k}}$$



# Difference Amplifier

Combine Non- & Inv Formulas:


$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_2 - \frac{R_2}{R_1} V_1$$

If we select

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}, \text{ then}$$

$$V_o = \frac{R_2}{R_1} (V_2 - V_1)$$

A balanced difference amp!

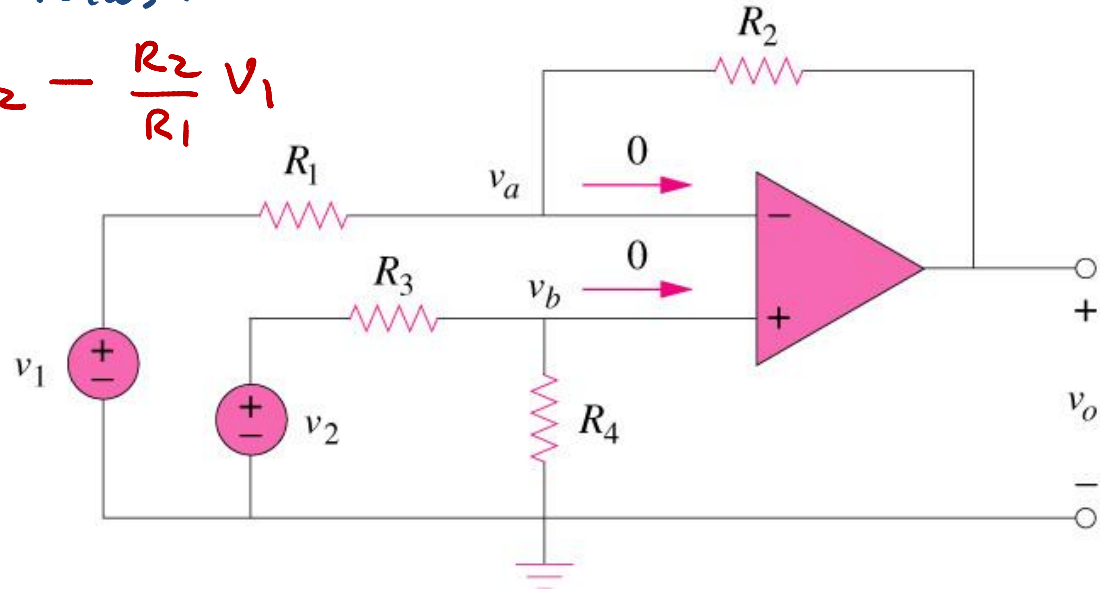


$$v_o = \frac{R_2}{R_1} (v_2 - v_1), \text{ if } \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

Find the output voltage  $v_o$  [-80]

Note:  $\frac{1600}{200} = \frac{8}{1}$
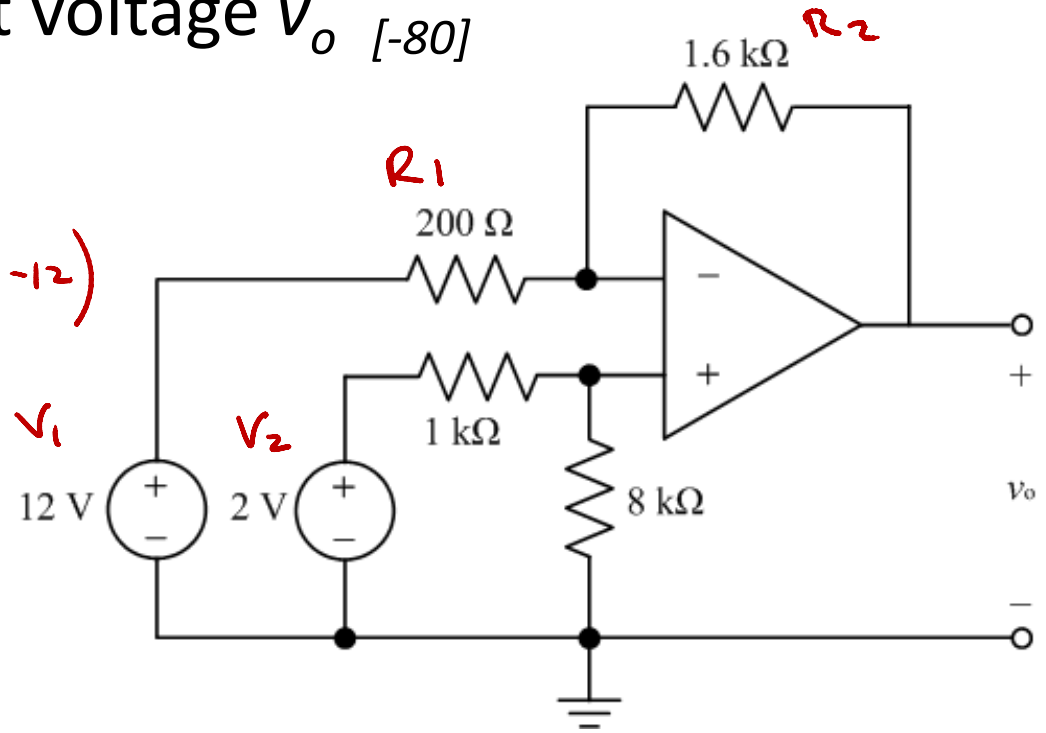
$$\begin{aligned} \therefore v_o &= \frac{R_2}{R_1} (v_2 - v_1) = 8(2 - 12) \\ &= \underline{\underline{-80 \text{ V}}} \end{aligned}$$



# 4) Problem 4 Difference Amplifier

If  $V_b = 4.0\text{V}$ , what values of  $V_a$  will keep linear operation? [ $2 \leq v_a \leq 6$ ]

$$\text{Again, } \frac{50}{10} = \frac{20}{4}$$

$$\therefore V_o = \frac{R_2}{R_1} (V_2 - V_1)$$

$$V_o = 5(V_b - V_a)$$


$$= 5(4 - V_a)$$

Solve for

$$\text{a) } 10 = 5(4 - v_a) \rightarrow v_a = \frac{(20 - 10)}{5} = 2$$

$$\text{b) } -10 = 5(4 - v_a) \rightarrow v_a = \frac{(20 + 10)}{5} = 6$$


$$\underline{2 < v_a < 6}$$

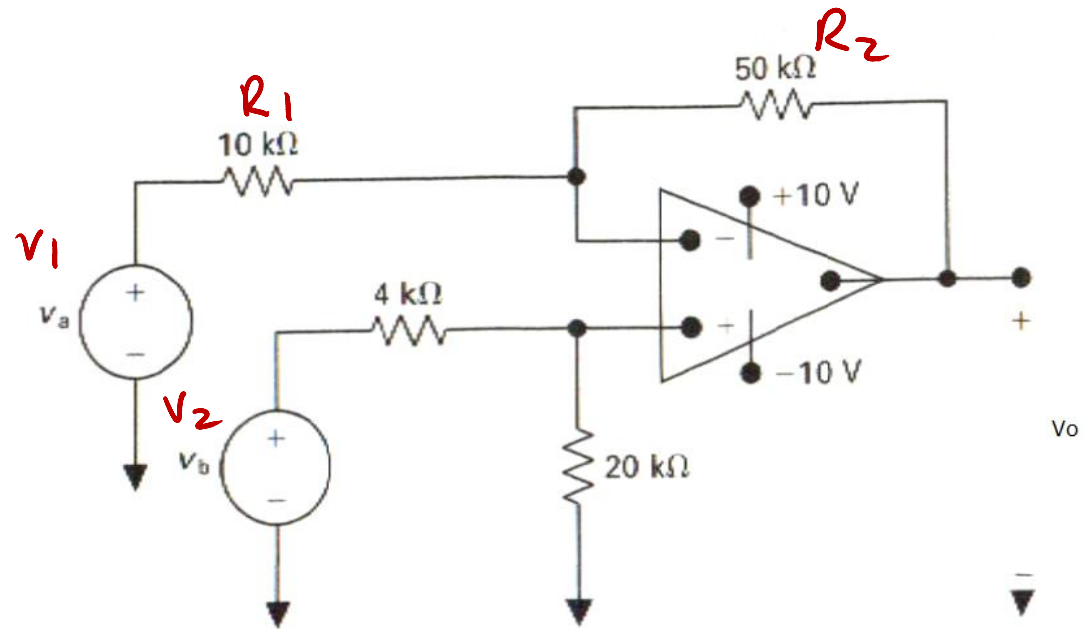


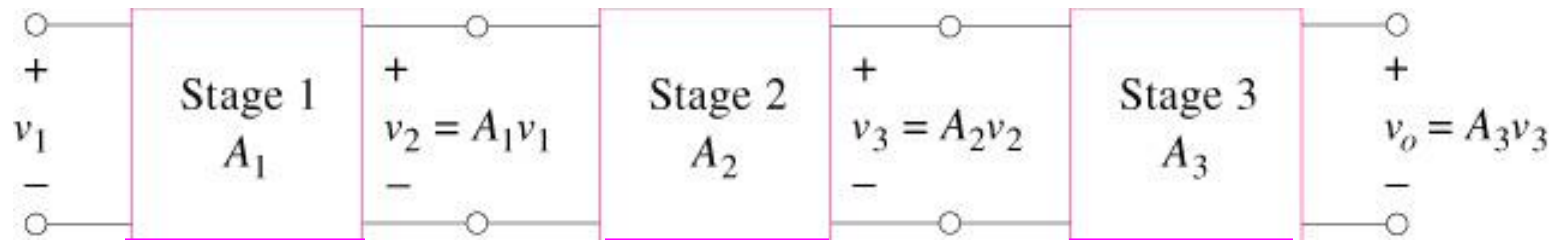
# Cascaded Op Amps

- A head-to-tail arrangement of two or more op amp circuits such that the output to one is the input of the next.



- Total Gain is the product of all stages

$$Gain = \frac{v_o}{v_i} = A_1 A_2 A_3$$

# Another way to make a Difference Amp

Find the formula for  $V_o$  in the circuit below.

Inverting Op-Amp


$$V_a = -\frac{3R_3}{R_3} V_2 = -3V_2$$

Summing Op-Amp

$$V_o = -\left(\frac{5R_1}{5R_1} V_a + \frac{5R_1}{R_1} V_1\right)$$

$$= -(-3V_2 + 5V_1)$$


$$V_o = 5V_1 - 3V_2$$

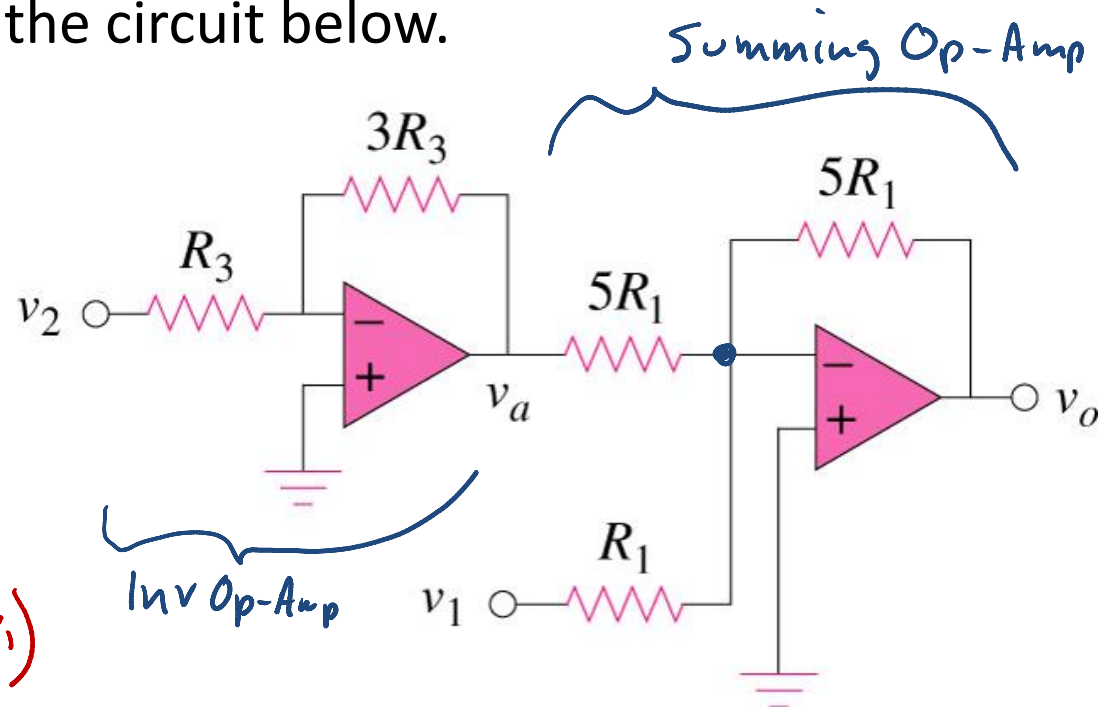

Ans:

$$v_o = -5v_1 + 3v_2$$

Find the output voltage  $v_o$  [900 V]

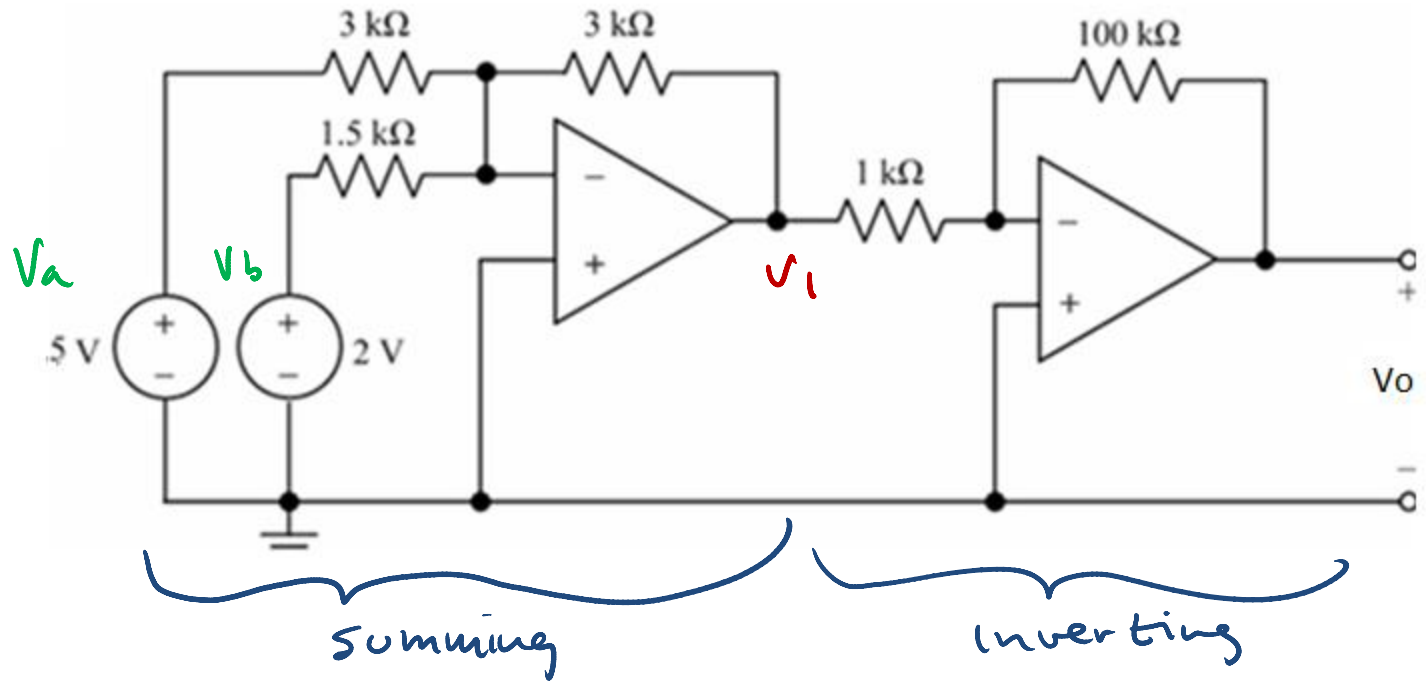

Summing

$$v_1 = -\left(\frac{3}{3}(5) + \frac{3}{1.5}(2)\right) = -9$$

Inverting

$$v_o = -\frac{100}{1} v_1 = \underline{900\text{ V}} \text{ (assuming not saturated!)}$$

$$\text{Total Gain} = 100(v_a + 2v_b)$$

Find  $v_o$  and  $i_o$  in the circuit shown below.

Non-Inv A

$$V_a = \left(1 + \frac{R_{fa}}{R_{la}}\right) 20 \text{ mV}$$

$$= 5(.02) = .1 \text{ V}$$

Non-Inv B


$$V_o = \left(1 + \frac{R_{fb}}{R_{lb}}\right) V_a$$

$$= (3.5)(.1) = \underline{\underline{.35 \text{ V}}}$$

$$\text{Total Gain} = \left(1 + \frac{R_{fa}}{R_{la}}\right) \left(1 + \frac{R_{fb}}{R_{lb}}\right) = (5)(3.5) = 17.5$$

Finding  $i_o$
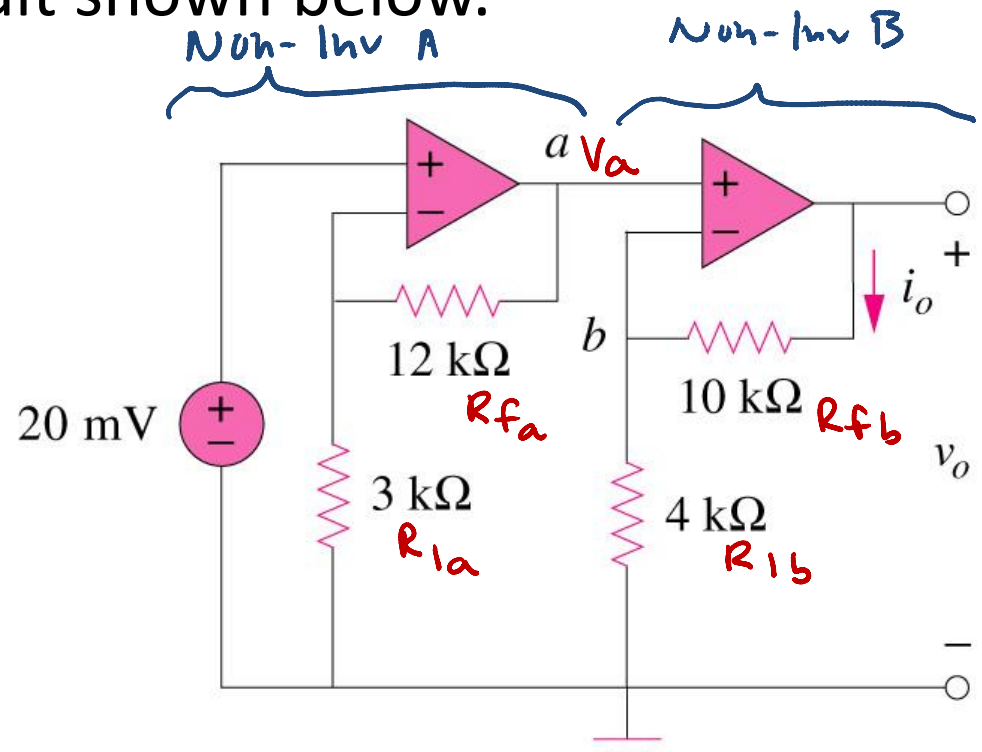
$$\text{OL: } i_o = \frac{V_o}{14 \text{ k}} = \frac{.35}{14000} = \underline{\underline{25 \mu\text{A}}}$$



If  $v_1 = 1V$  and  $v_2 = 2V$ , find  $v_o$  in the op amp circuit shown below.

C

$$V_o = -\left(\frac{10}{5} v_a + \frac{10}{15} v_b\right)$$


A

$$v_a = -\frac{6}{2} v_1$$

B

$$v_b = -\frac{8}{4} v_2$$


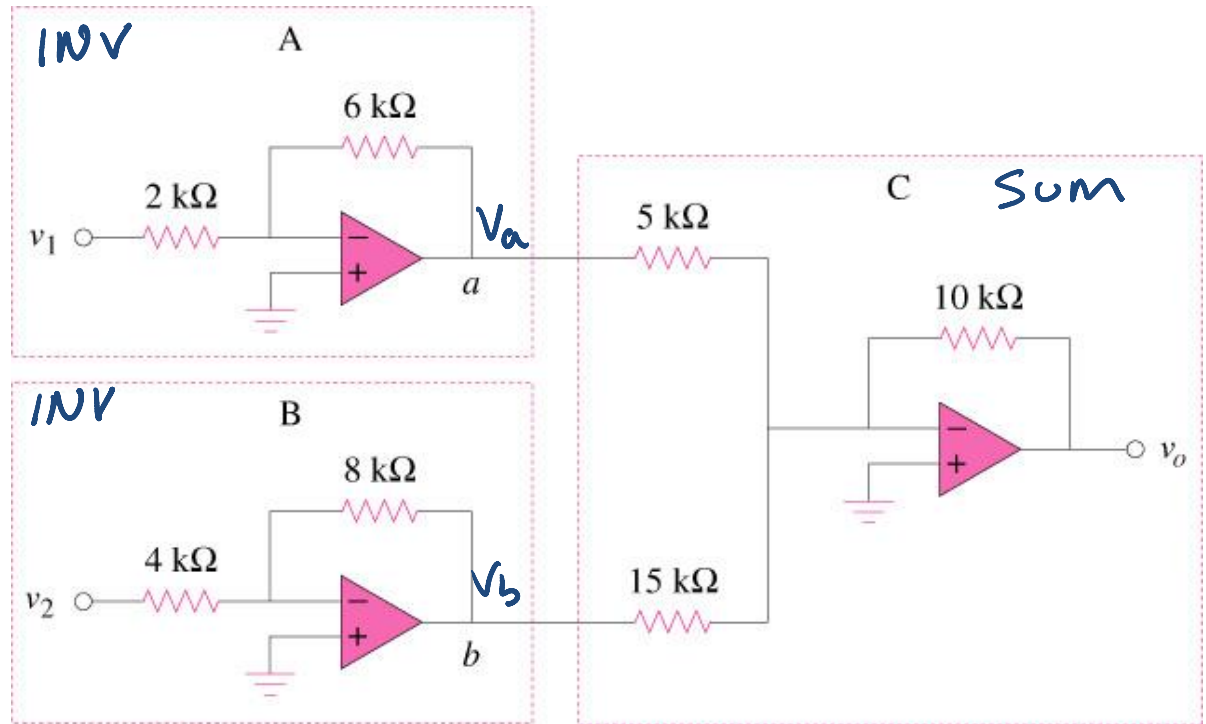
$$\begin{aligned} \therefore V_o &= 3v_1 + \frac{8}{3}v_2 \\ &= 3 \cdot 1 + \frac{8}{3} \cdot 2 = \underline{\underline{8.667 V}} \end{aligned}$$


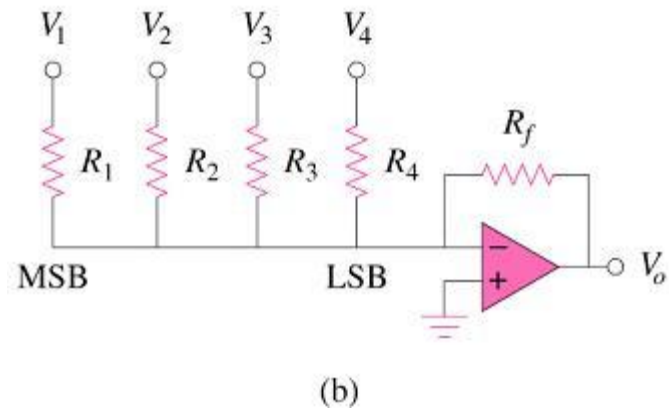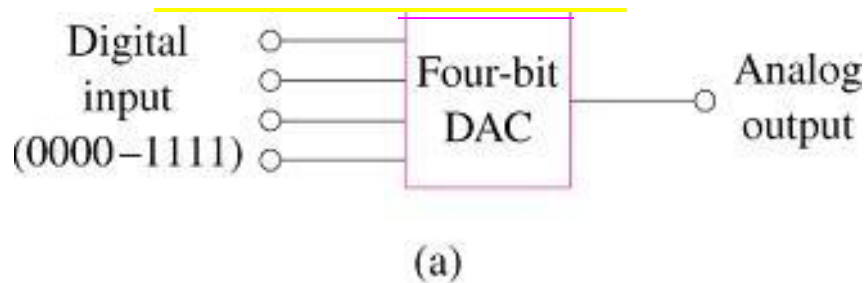
# 5.5 Application

- Digital-to Analog Converter (DAC) : a device which transforms digital signals into analog form.

Four-bit DAC: (a) block diagram (b) binary weighted ladder type



where

$V_1$  - MSB,  $V_4$  - LSB

$V_1$  to  $V_4$  are either 0 or 1 V

# 5.5 DAC Example


For the circuit shown below, calculate  $v_o$  if  $v_1=0V, v_2=1V$  and  $v_3 = 1V$ .

Summing Op-Amp

$$V_o = - \left( \frac{10}{10} v_1 + \frac{10}{20} v_2 + \frac{10}{40} v_3 \right)$$

$$= - (.5 + .25)$$

$$= - .75V$$

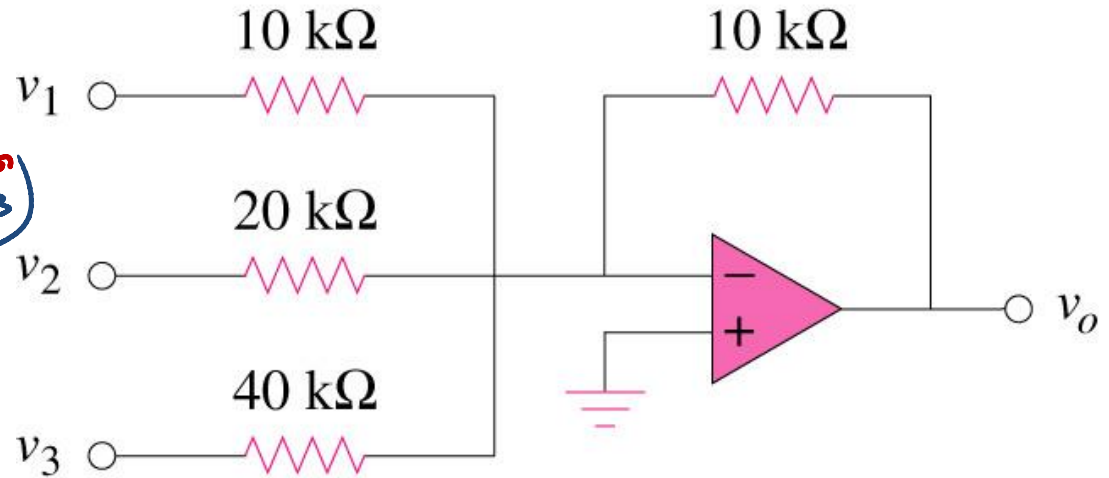


Ans:-0.75V

# Handouts



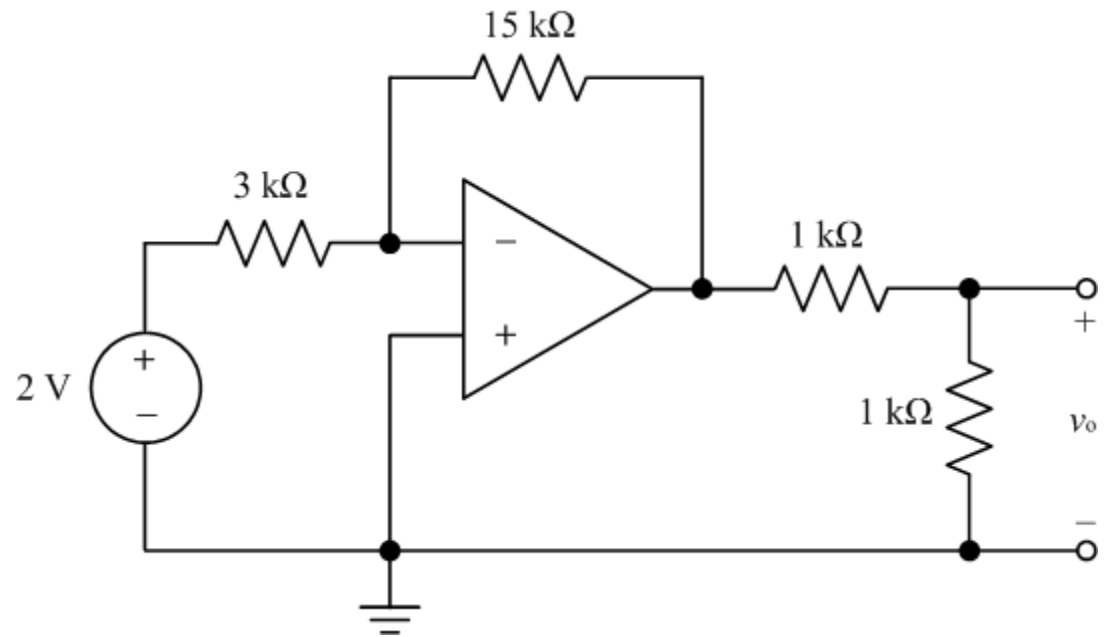
# 1) Problem 1 INVERTING OP AMP

find the voltage  $v_o$  across the  $1\text{k}\Omega$  resistor. [-5V]



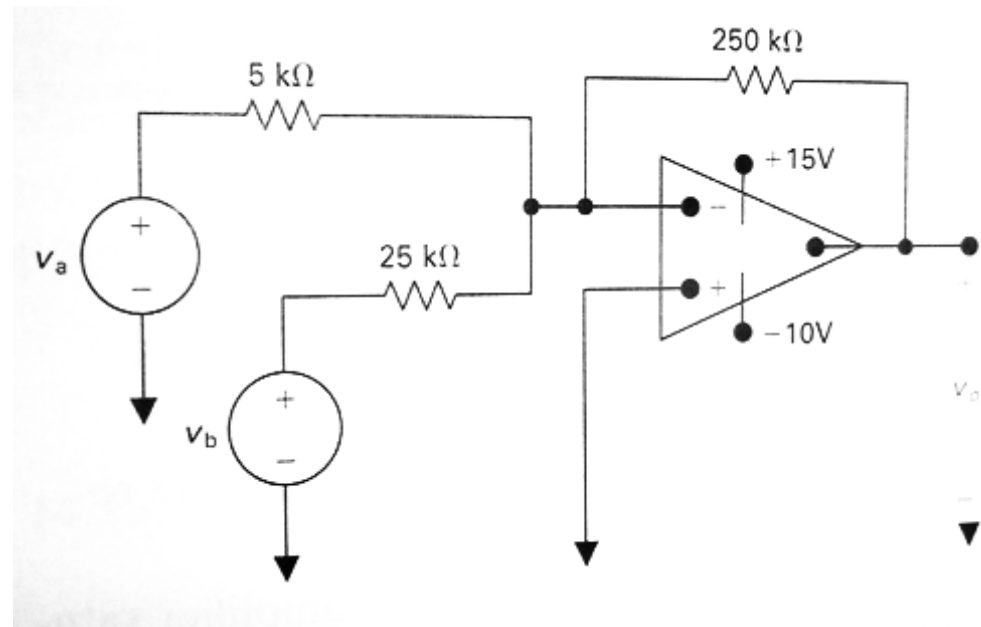
## 2) SUMMING OP-AMP

Find  $V_o$  in the circuit shown if  $V_a=0.1V$  and  $V_b= 0.25V$  [-7.5]




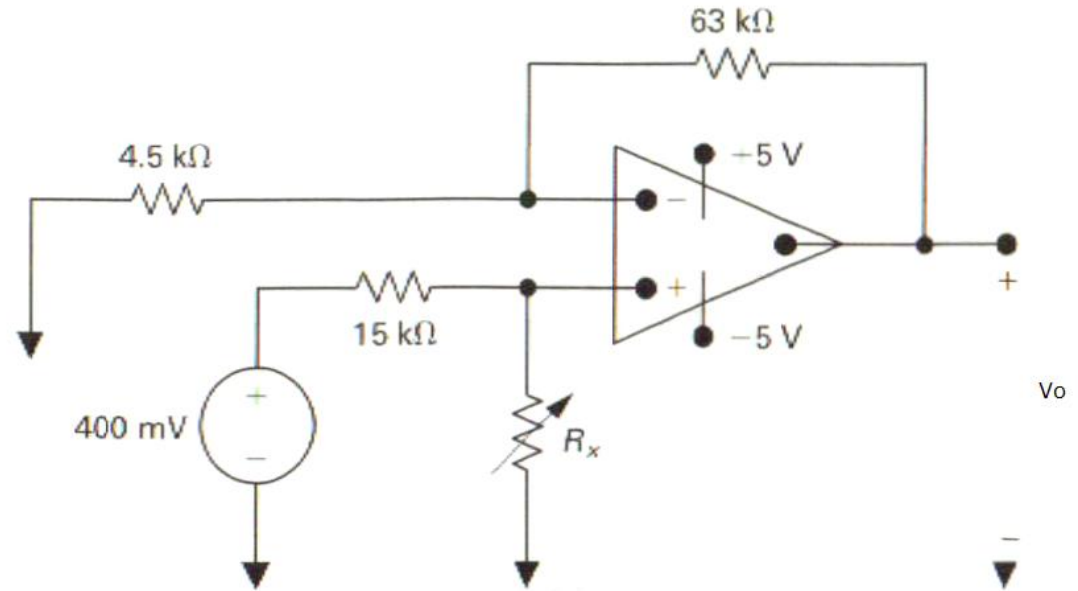3) NON INVERTING Find the output Voltage when  $R_x$  is set to 60k  
What  $R_x$  will cause saturation? [4.8V, 75k]



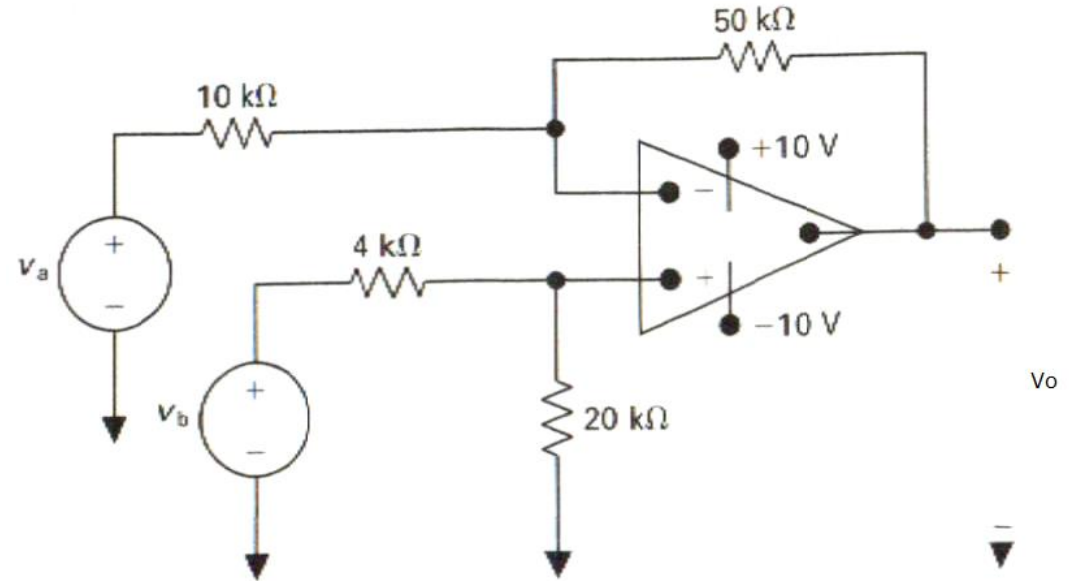
# 4) Problem 4 Difference Amplifier

If  $V_b=4.0\text{V}$ , what values of  $V_a$  will keep linear operation? [ $2 \leq v_a \leq 6$ ]


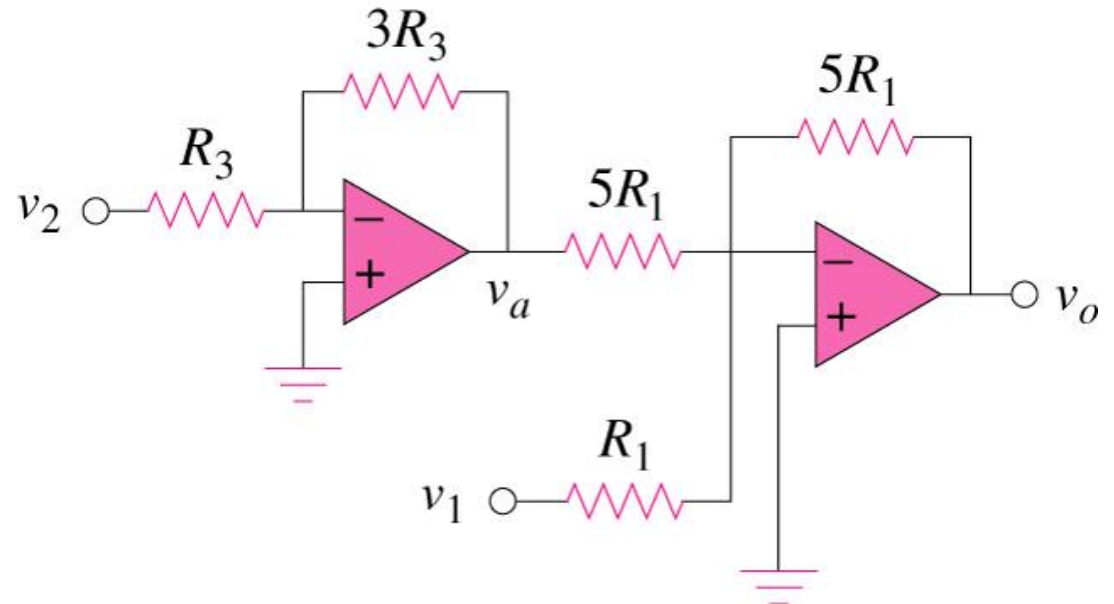
# 5. Another way to make a Difference Amp


Find the formula for  $V_o$  in the circuit below.




Ans:

$$v_o = -5v_1 + 3v_2$$

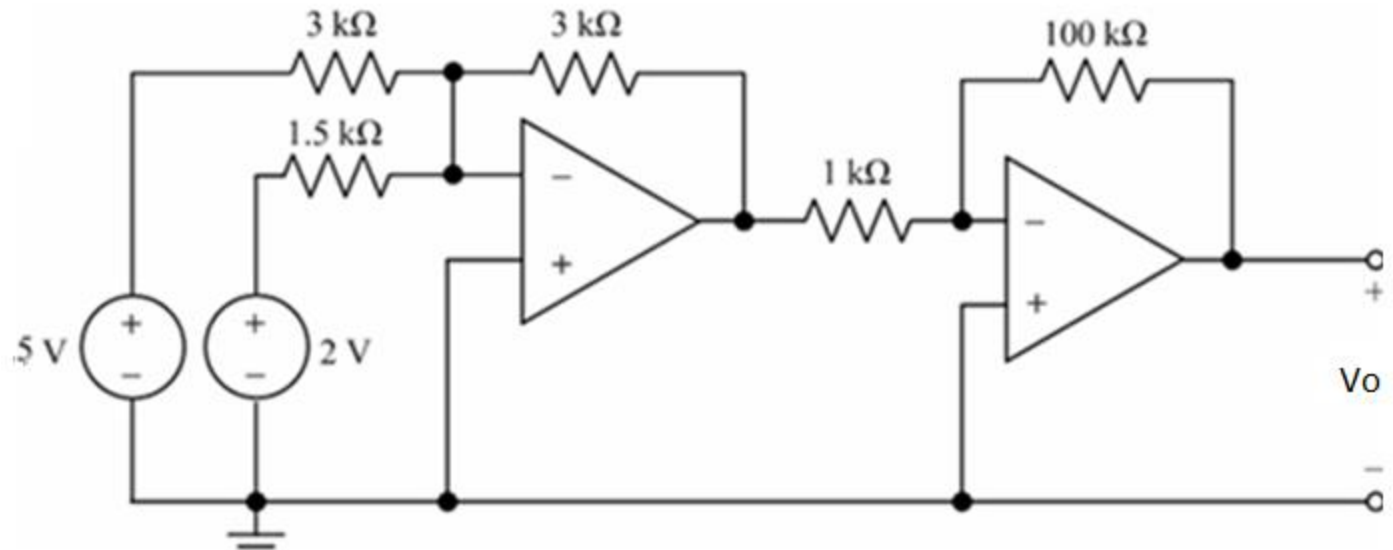6. Find the output voltage  $v_o$  [900 V]



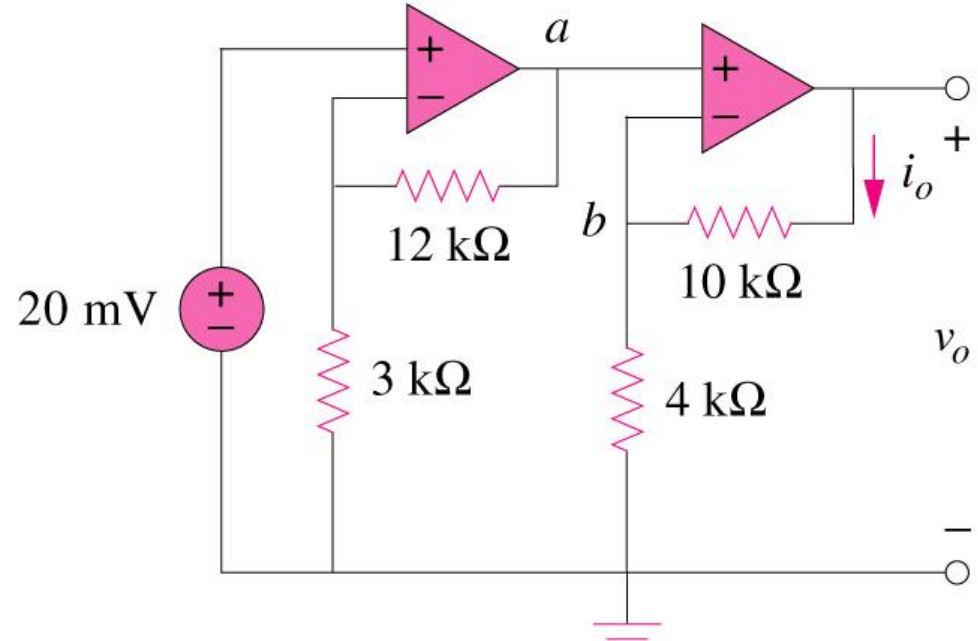7. Find  $v_o$  and  $i_o$  in the circuit shown below.



Ans: 350mV, 25μA 39

# How to Approach Op-Amp probs

1. Check for negative feedback  
All of our Op-Amp ccts will be “Closed Loop” with negative feedback
2. Assume current flowing into  $V_p/V_n$  terminals of op-amp = 0
3. Assume Op-Amp in linear range  
This means  $V_p$  must =  $V_n$   
otherwise  $A(V_p-V_n)$  takes us to saturation
4. Determine value of  $V_p$
5. Set  $V_n = V_p$
6. Set up nodal equation at  $V_n$  node and solve for  $V_o$
7. Check that  $V_o$  does not exceed power supply voltages  $\pm V_{cc}$  (if given)  
If so, then assumptions 3 and 5 do not hold  
Set  $V_o$  to the power supply voltage and recalculate

If you recognize common forms you can use formulas related to them

- Very helpful in cascaded Op-Amp problems
- Best not to depend too much on these
- You should always be able to go back to KCL/KVL