

Circuit Theory

Chapter 7

First-Order Circuits

**see "Derivation" link for more
information**

First-Order Circuits


Chapter 7

"Natural Response"

- 7.1 The Source-Free RC Circuit
- 7.2 The Source-Free RL Circuit
- 7.3 Unit-step Function
- 7.4 Step Response of an RC Circuit
- 7.5 Step Response of an RL Circuit

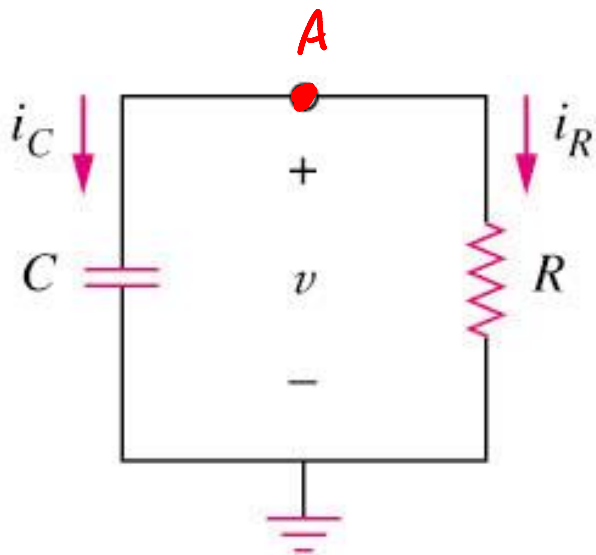7.1 The Source-Free RC Circuit (1)

- A **first-order circuit** is characterized by a first-order differential equation.



KCL at Node A

$$i_C + i_R = 0$$

$$\frac{Cdv}{dt} + \frac{v}{R} = 0$$


Capacitor Law

Ohm's Law

- Apply Kirchhoff's laws to purely resistive circuit results in algebraic equations.
- Apply the laws to RC and RL circuits produces differential equations.

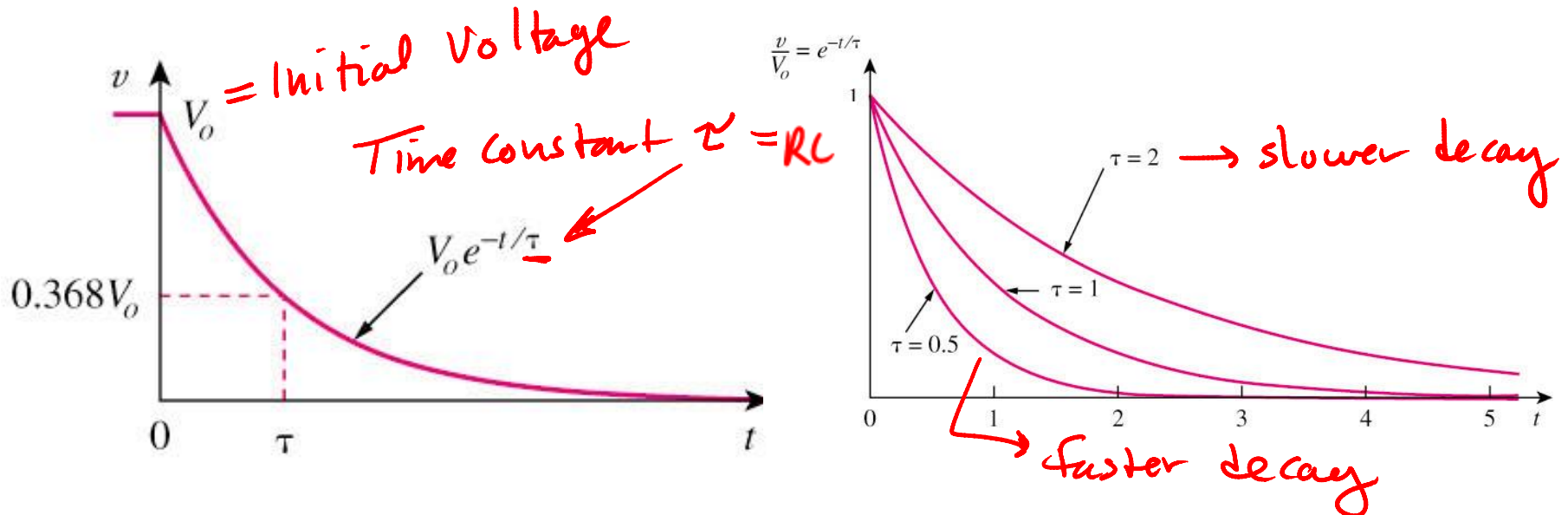7.1 The Source-Free RC Circuit (2)

- The **natural response** of a circuit refers to the behavior (in terms of voltages and currents) of the circuit itself, with no external sources of excitation.




- The **time constant** τ of a circuit is the time required for the response to decay by a factor of $1/e$ or 36.8% of its initial value.
- v decays **faster** for small τ and **slower** for large τ .

7.1 The Source-Free RC Circuit (3)

The key to working with a source-free RC circuit is finding:

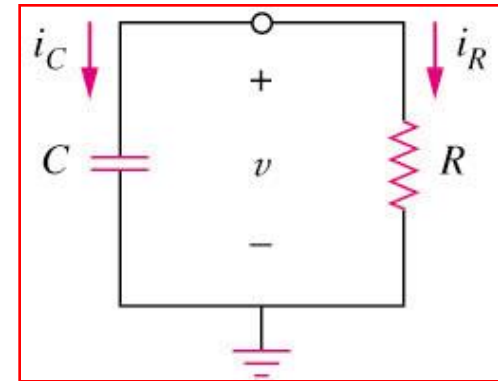a) V_0 b) τ

$$v(t) = V_0 e^{-t/\tau} \quad \text{where} \quad \tau = RC$$



1. The initial voltage $v(0) = V_0$ across the capacitor.
2. The time constant $\tau = RC$.

7.1 Source-Free RC Circuit (4)

Example 1

Refer to the circuit below, determine v_C , v_x , and i_o for $t \geq 0$.

Assume that $v_C(0) = 30 \text{ V} = V_0$

$$\tau = R_{ab}C = (8 + 12 \parallel 6) \left(\frac{1}{3}\right)$$

$$= (8 + 4) \left(\frac{1}{3}\right) = 4 \text{ seconds}$$


$$\therefore v_C(t) = V_0 e^{-t/\tau} = \underline{\underline{30 e^{-0.25t}}}$$

v_x divides v_C

$$v_x = \left(\frac{12 \parallel 6}{12 \parallel 6 + 8}\right) v_C = \frac{4}{12} v_C = \frac{1}{3} v_C = 10 e^{-0.25t}$$

$$\text{KCL } i_o + \frac{v_x}{12} + \frac{v_x}{6} = 0, \quad i_o = -\frac{v_x}{4} = -2.5 e^{-0.25t}$$

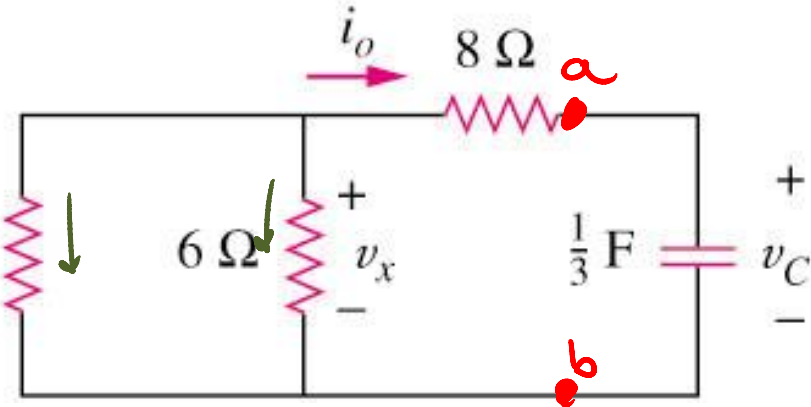Answer: $v_C = 30 e^{-0.25t} \text{ V}$; $v_x = 10 e^{-0.25t}$; $i_o = -2.5 e^{-0.25t} \text{ A}$



OR $i_o = i_C = C \frac{dv_C}{dt}$

$i_o = \left(\frac{1}{3}\right) \left(-\frac{1}{4}\right) 30 e^{-0.25t}$

SAME 6

7.1 Source-Free RC Circuit (5)

Example 2

The switch in circuit below is opened at $t = 0$, find $v(t)$ for $t \geq 0$.

PLAN


A) Find V_0 , Voltage across parallel resistors (Voltage divider)

$$V_0 = 24 \left(\frac{12 \parallel 4}{6 + 12 \parallel 4} \right) = \frac{24(3)}{6+3} = \underline{\underline{8V}}$$

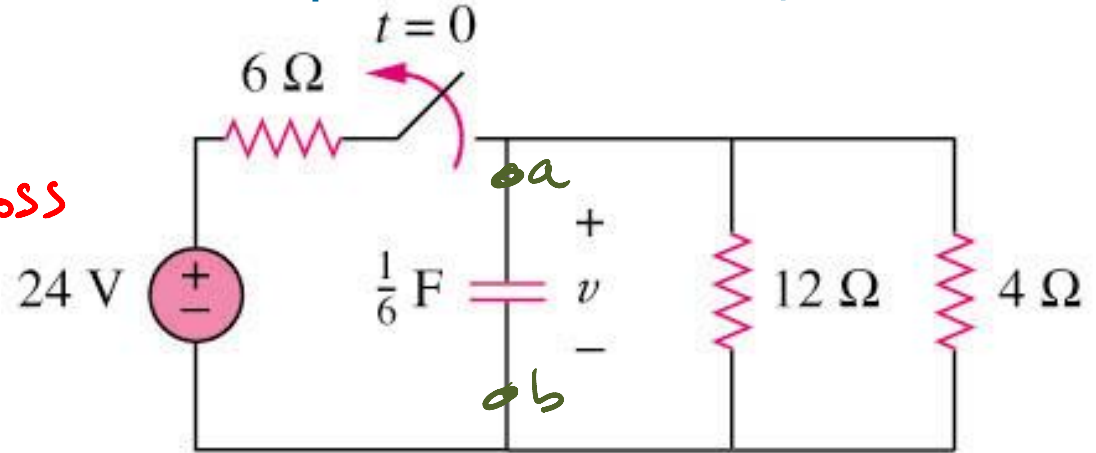B) Find τ for $t \geq 0$, R_{ab} seen by capacitor (switch open)

$$R_{ab} = 12 \parallel 4 = 3 \Omega, \quad C = \frac{1}{6} F \rightarrow \tau = (3) \left(\frac{1}{6} \right) = 0.5$$

$$c) \quad v(t) = V_0 e^{-t/\tau} = 8 e^{-t/0.5} = \underline{\underline{8e^{-2t}}}$$




Answer: $V(t) = 8e^{-2t} V$ ⁷

7.2 The Source-Free RL Circuit (1)

- A **first-order RL circuit** consists of a inductor L (or its equivalent) and a resistor (or its equivalent)

$$\underline{KVL} \quad v_L + v_R = 0$$

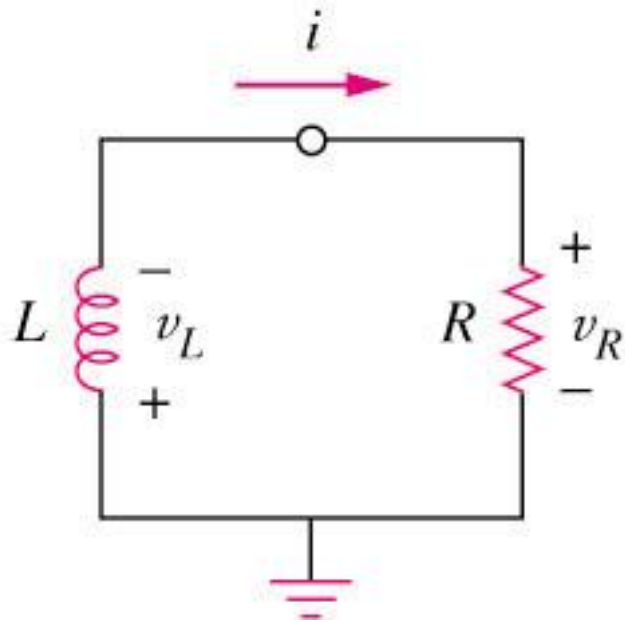

$$L \frac{di}{dt} + iR = 0$$

Inductor Law

Ohm's Law


Solving

$$\frac{di}{i} = -\frac{R}{L} dt \rightarrow i(t) = I_0 e^{-t/\tau}$$

Initial Current

time constant

7.2 The Source-Free RL Circuit (2)

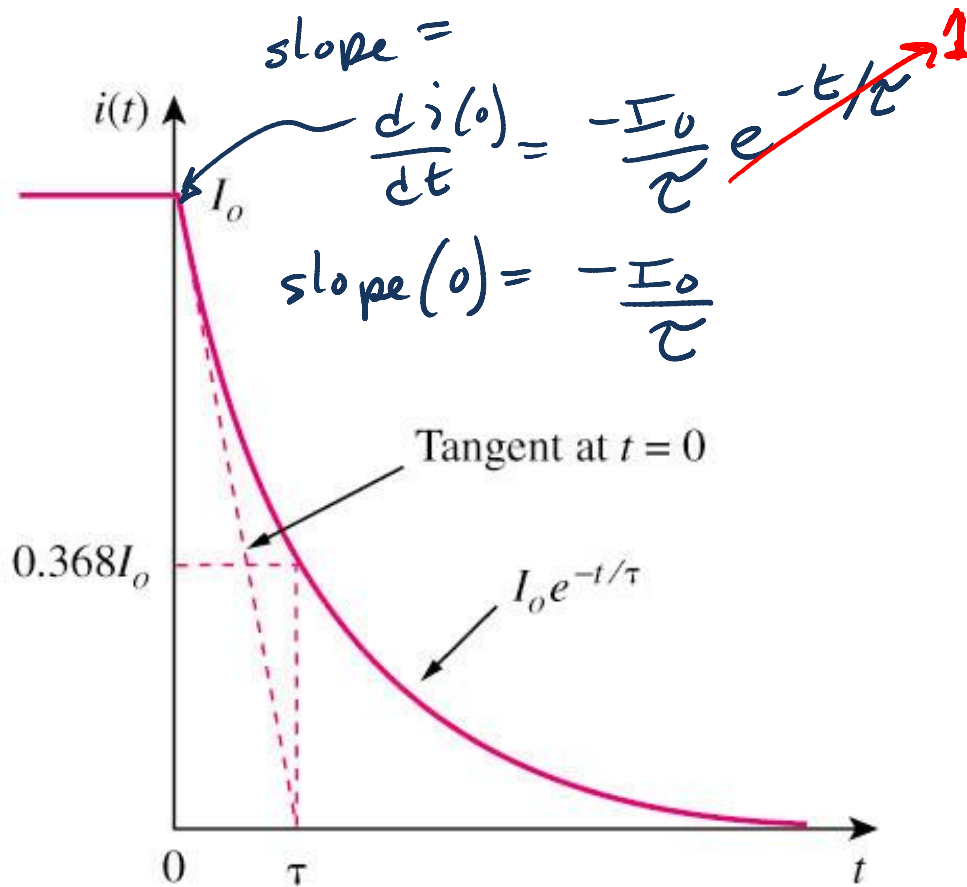


- The **time constant** τ of a circuit is the time required for the response to decay by a factor of $1/e$ or 36.8% of its initial value.
- $i(t)$ decays **faster** for small τ and **slower** for large τ .
- The general form is very similar to a RC source-free circuit.

7.2 The Source-Free RL Circuit (3)

Comparison between a RL and RC circuit


A RL source-free circuit
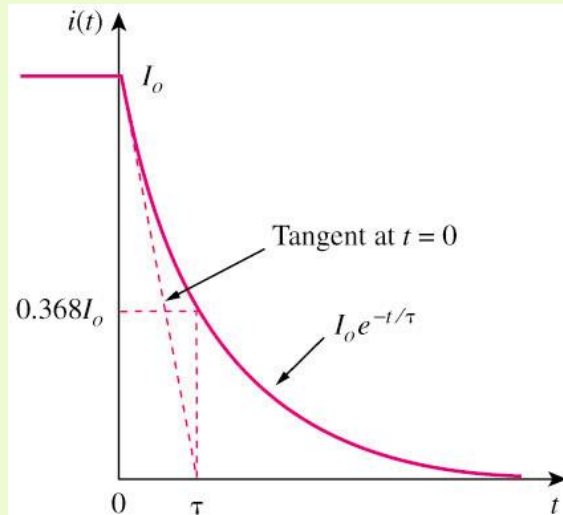
$$i(t) = I_0 e^{-t/\tau} \quad \text{where} \quad \tau = \frac{L}{R}$$



A RC source-free circuit
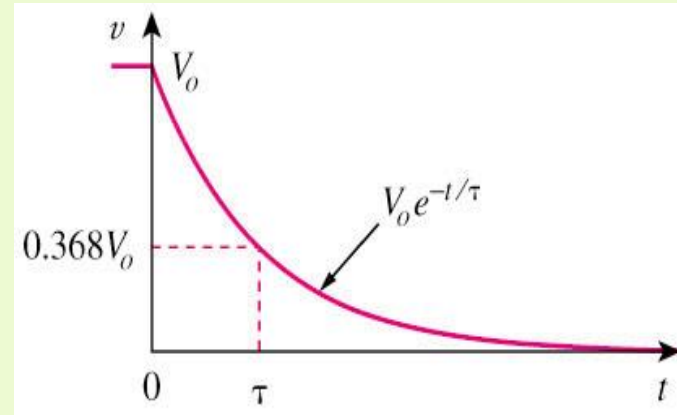
$$v(t) = V_0 e^{-t/\tau} \quad \text{where} \quad \tau = RC$$



7.2 The Source-Free RL Circuit (4)

The key to working with a source-free RL circuit is finding:


a) I_0 , initial current

b) τ

$$i(t) = I_0 e^{-t/\tau}$$

where

$$\tau = \frac{L}{R}$$

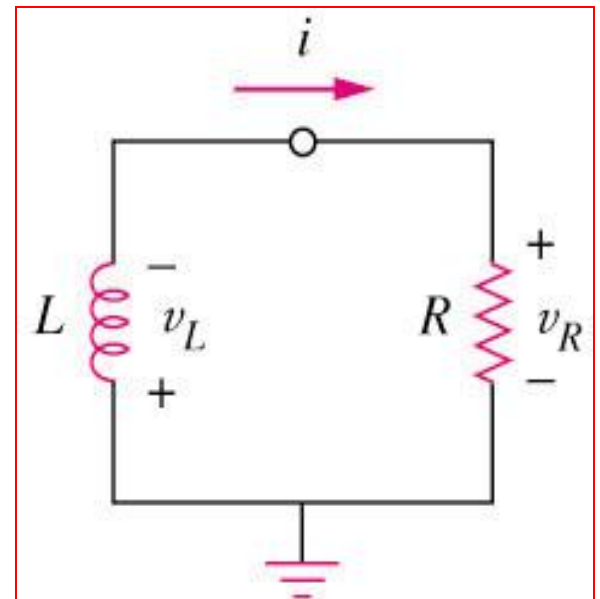

1. The initial voltage $i(0) = I_0$ through the inductor.
2. The time constant $\tau = L/R$.

7.2 The Source-Free RL Circuit (5)

Example 3

Find i and v_x in the circuit.

Assume that $i(0) = 5$ A.


$$i(t) = I_0 e^{-t/\tau} = 5e^{-t/\tau}$$

$$\tau = \frac{L}{R}$$

$$R = R_{ab} \text{ with Inductor Removed}$$
$$= 15 \parallel (7+3) = 6 \Omega$$

$$\tau = \frac{\frac{1}{6}}{\frac{1}{6}} = \frac{1}{36} \text{ sec}$$
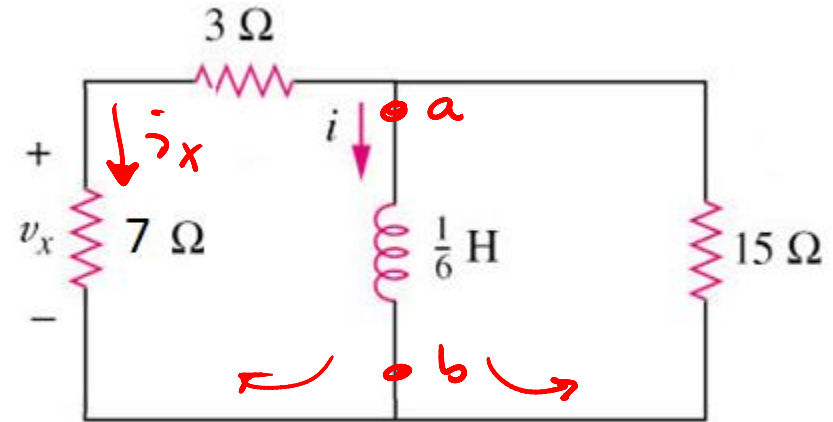
$$\therefore i(t) = 5e^{-36t} \text{ A}$$



Current Divider

$$i_x = -i \left(\frac{15}{10+15} \right)$$
$$= -3e^{-36t}$$

$$V_x = 7i_x = -21e^{-36t}$$

Answer: $i(t) = 5e^{-36t}$ A 12

7.2 The Source-Free RL Circuit (6)

Example 4


For the circuit, find $i(t)$ for $t > 0$.

A) $t < 0 \rightarrow$ Switch closed

Assume L is a short

Solve for I_0


(redraw circuit)

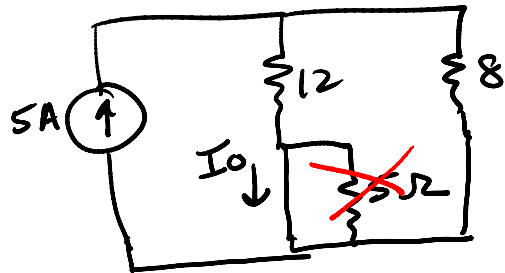


$$I_0 = 5A \left(\frac{8}{12+8} \right) = 2A$$

B) $t > 0 \rightarrow$ Switch open, Find R_{ab} with L removed

(redraw circuit)

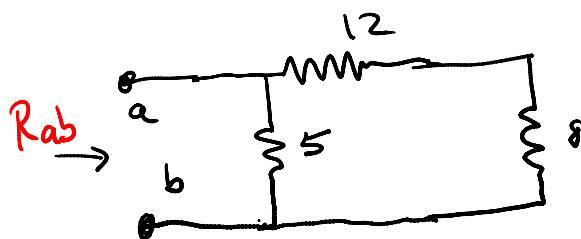

$$R_{ab} = 5 // (12 + 8) = 4\Omega$$

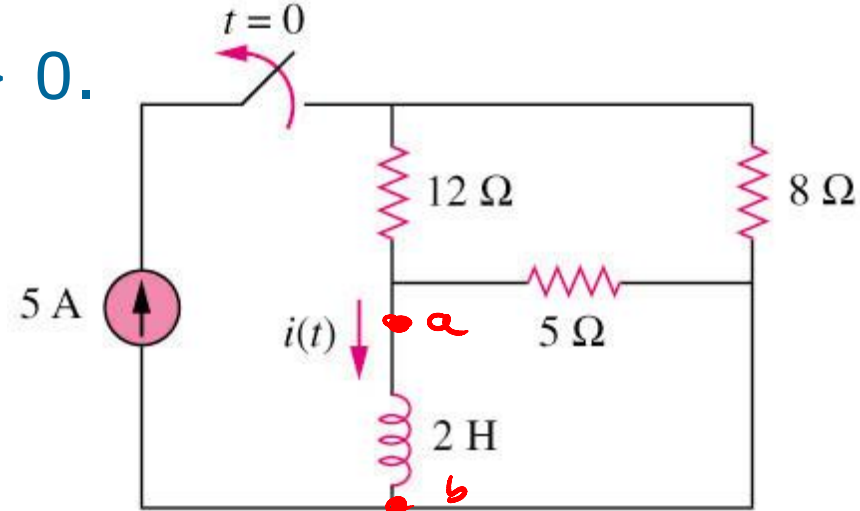

$$c) \tau = \frac{L}{R} = \frac{2}{4} = \frac{1}{2} s$$


$$d) i(t) = I_0 e^{-t/\tau} = 2 e^{-2t} A$$

Answer: $i(t) = 2e^{-2t} A$

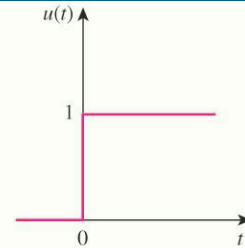
7.3 Unit-Step Function (1)

- The **unit step function** $u(t)$ is 0 for negative values of t and 1 for positive values of t .


$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$


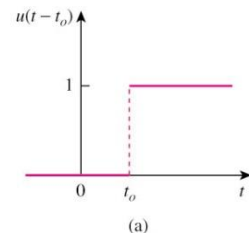
$$u(t - t_o) = \begin{cases} 0, & t < t_o \\ 1, & t > t_o \end{cases}$$



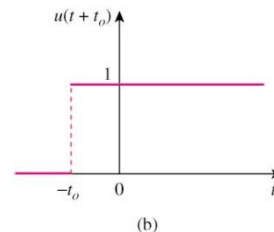
$$u(t + t_o) = \begin{cases} 0, & t < -t_o \\ 1, & t > -t_o \end{cases}$$




7.3 Unit-Step Function (2)

Represent an abrupt change for:

1. voltage source.

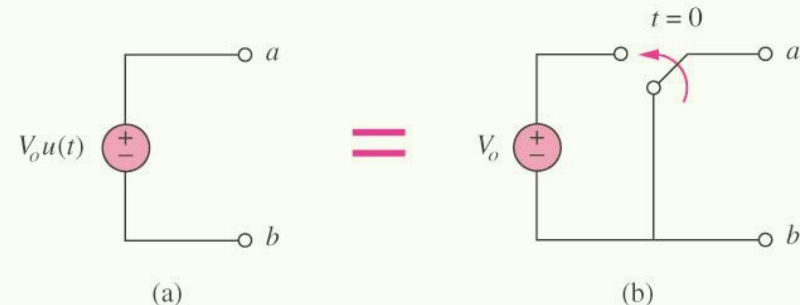


2. for current source:

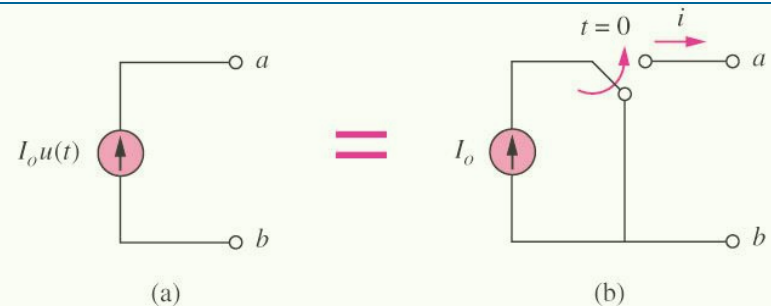

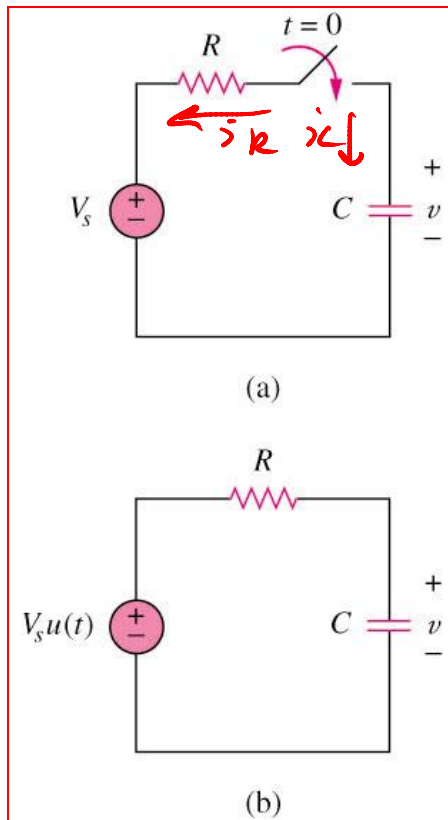7.4 The Step-Response of a RC Circuit (1)

- The **step response** of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source.



- Initial condition:**

$$v(0^-) = v(0^+) = V_0$$

- Applying KCL, $i_C + i_R = 0$

$$C \frac{dv}{dt} + \frac{(v - V_s) u(t)}{R} = 0$$


or

$$\frac{dv}{dt} = - \frac{v - V_s}{RC} u(t)$$

- Where $u(t)$ is the unit-step function

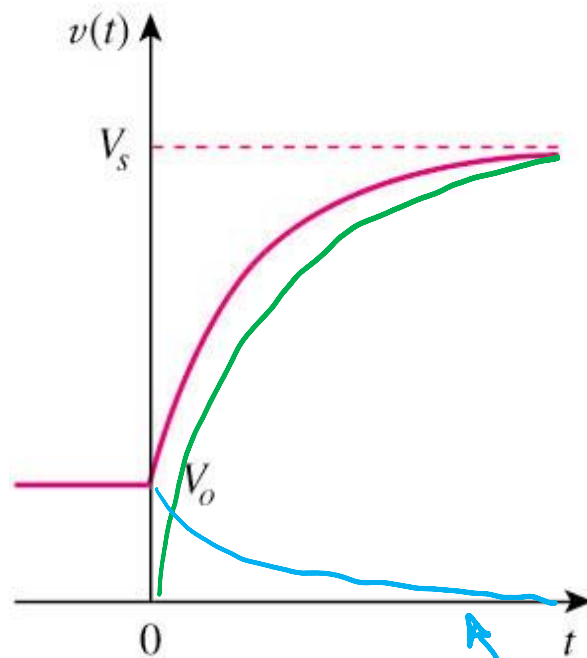7.4 The Step-Response of a RC Circuit (2)

- Integrating both sides and considering the initial conditions, the solution of the equation is:



$$v(t) = \begin{cases} V_0 & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

Final value
at $t \rightarrow \infty$

Initial value
at $t = 0$

Source-free
Response

Complete Response = Natural response
(stored energy)

+ Forced Response
(independent source)

= $V_0 e^{-t/\tau}$

+ $V_s(1 - e^{-t/\tau})$

7.4 The Step-Response of a RC Circuit (3)

Three steps to find out the step response of an RC circuit:

1. The initial capacitor voltage $v(0)$.
2. The final capacitor voltage $v(\infty)$ or, the final DC voltage across C.
3. The time constant τ .

$$v(t) = v(\infty) + [v(0+) - v(\infty)]e^{-t/\tau}$$


Note: The above method is a short-cut method. You may also determine the solution by setting up the circuit formula directly using KCL, KVL, ohms law, capacitor and inductor VI laws.

7.4 Step-Response of a RC Circuit (4)

Example 5


Find $v(t)$ for $t > 0$ in the circuit in below. Assume the switch has been open for a long time and is closed at $t = 0$.

Calculate $v(t)$ at $t = 0.5$.

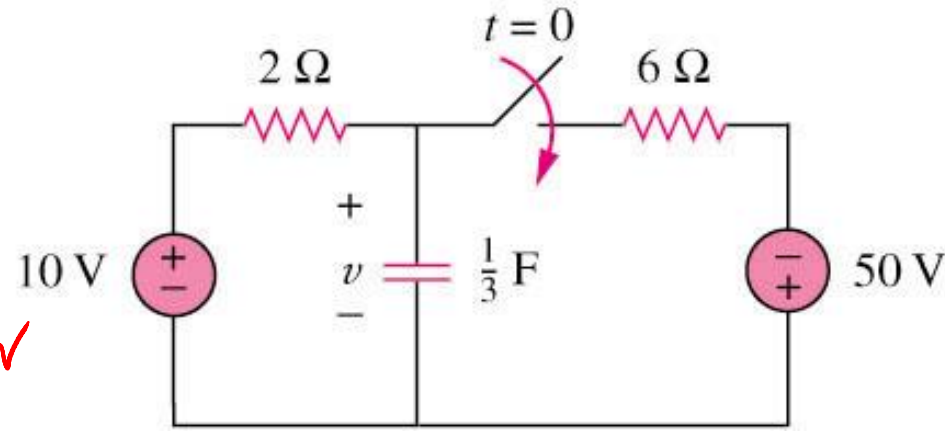


1) $t < 0$

C is an open at 10V
Find V_0

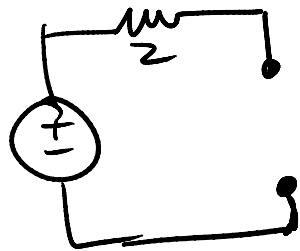

2) as $t \rightarrow \infty$

C is an open at 10V
Find V_f

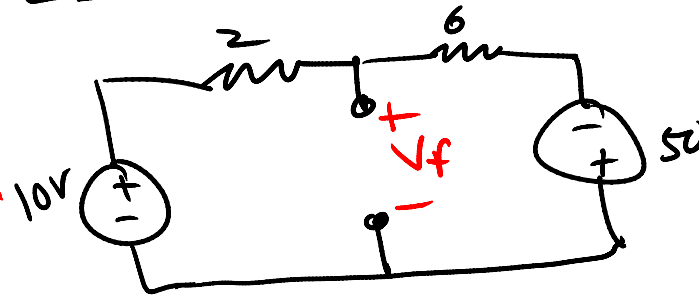

Nodal Analysis

$$\frac{V_f - 10}{2} + \frac{V_f - (-50)}{6} = 0$$

$$3V_f - 30 + V_f + 50 = 0$$

$$V_f = -5V$$


3) Find $\tau = RC = (2/6) \frac{1}{3} = \frac{12}{24} = \frac{1}{2} s$

4) $v(t) = V_f + (V_0 - V_f)e^{-t/\tau}$, $v(t) = -5 + (10 - (-5))e^{-2t}$

Answer: $v(t) = 15e^{-2t} - 5$ and $v(0.5) = 0.5182V$

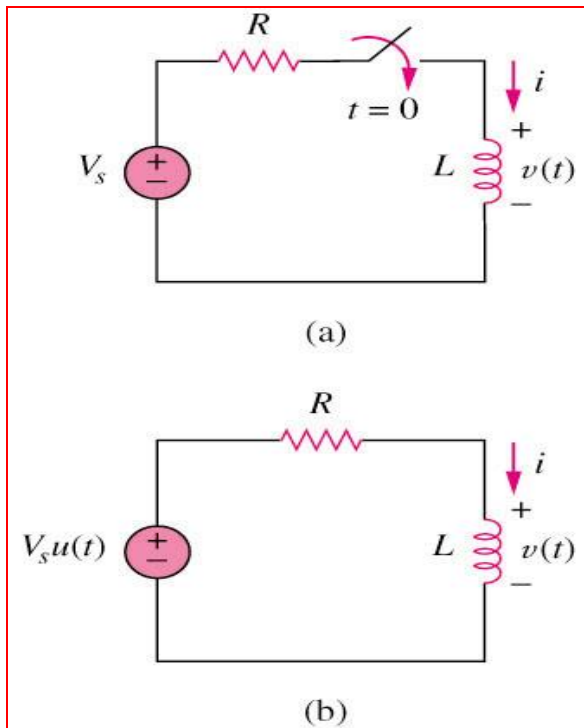7.5 The Step-response of a RL Circuit (1)

- The **step response** of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source.



- Initial current**
 $i(0^-) = i(0^+) = I_0$
- Final inductor current**
 $i(\infty) = V_s/R$
- Time constant $\tau = L/R$

$$i(t) = \frac{V_s}{R} + (I_0 - \frac{V_s}{R}) e^{-\frac{t}{\tau}} u(t)$$

I_f I_0 I_f

7.5 The Step-Response of a RL Circuit (2)

Three steps to find out the step response of an RL circuit:

1. The initial inductor current $i(0)$ at $t = 0+$.
2. The final inductor current $i(\infty)$.
3. The time constant τ .

$$i(t) = i(\infty) + [i(0+) - i(\infty)] e^{-t/\tau}$$

Note: The above method is a short-cut method. You may also determine the solution by setting up the circuit formula directly using KCL, KVL, ohms law, capacitor and inductor VI laws.

7.5 The Step-Response of a RL Circuit (4)

Example 6



The switch in the circuit shown below has been closed for a long time. It opens at $t = 0$.

Find $i(t)$ for $t > 0$.

1) $t < 0$, L is short ckt

Find I_0


$$I_0 = 3A$$

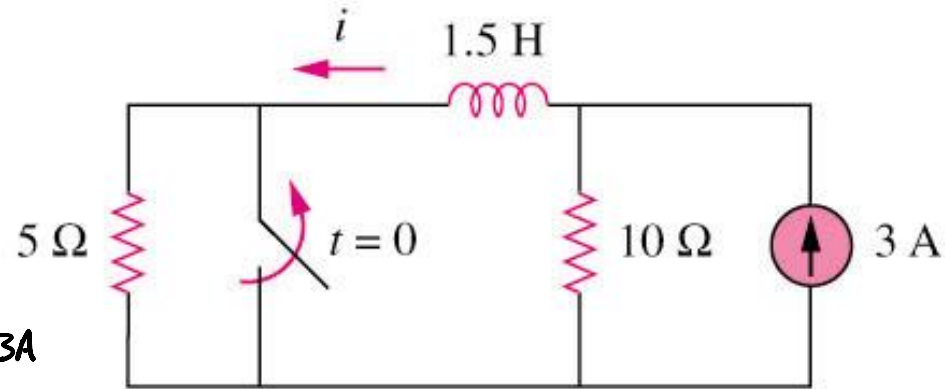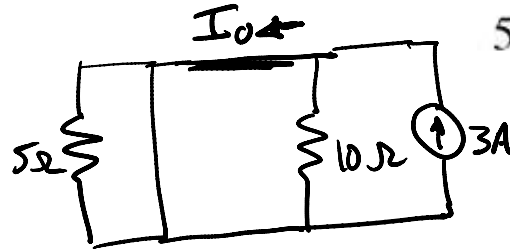

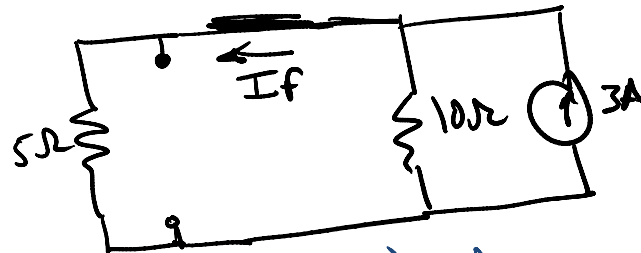2) $t \rightarrow \infty$, L is a short ckt

Find I_f

$$I_f = 3 \left(\frac{10}{5+10} \right) = 2A$$



3) Req for $t > 0$

$$R = 5 + 10 = 15\Omega$$

$$4) \tau = \frac{L}{R} = \frac{1.5}{15} = 0.1s$$

$$5) i(t) = I_f + (I_0 - I_f)e^{-t/\tau}$$

$$i(t) = 2 + (3 - 2)e^{-10t} =$$

Answer: $i(t) = 2 + e^{-10t}$


Handouts

7.1 Source-Free RC Circuit (4)

Example 1

Refer to the circuit below, determine v_C , v_x , and i_o for $t \geq 0$.

Assume that $v_C(0) = 30$ V.

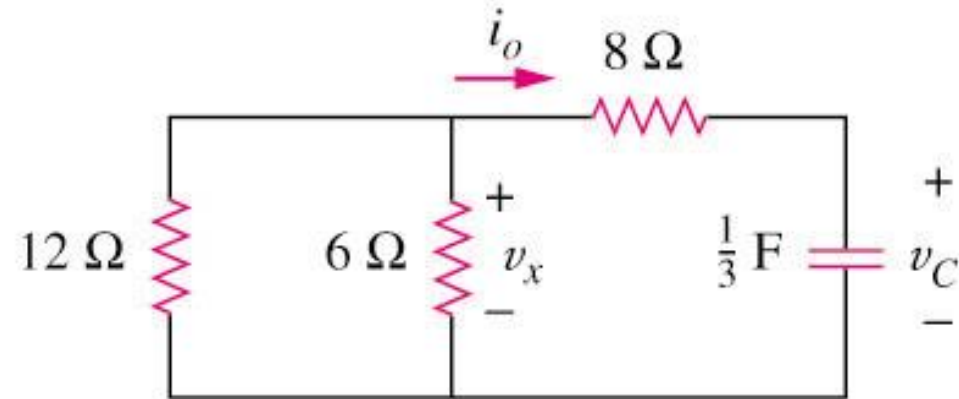


Answer: $v_C = 30e^{-0.25t}$ V ; $v_x = 10e^{-0.25t}$; $i_o = -2.5e^{-0.25t}$ A

7.1 Source-Free RC Circuit (5)

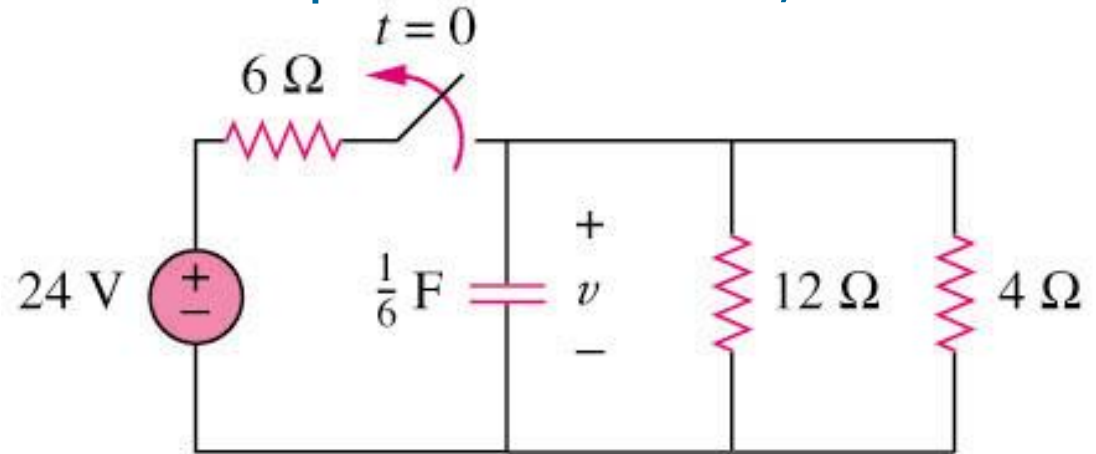Example 2

The switch in circuit below is opened at $t = 0$, find $v(t)$ for $t \geq 0$.




Answer: $V(t) = 8e^{-2t}$ V ²⁵

7.2 The Source-Free RL Circuit (5)

Example 3

Find i and v_x in the circuit.

Assume that $i(0) = 5$ A.

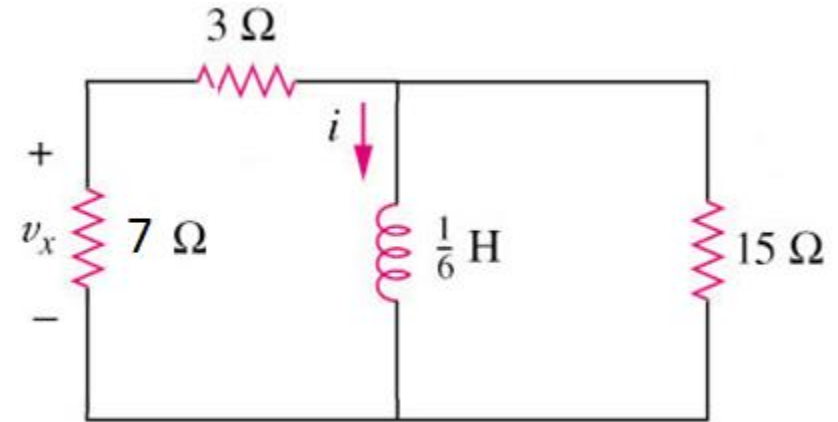


Answer: $i(t) = 5e^{-36t}$ A 26

7.2 The Source-Free RL Circuit (6)

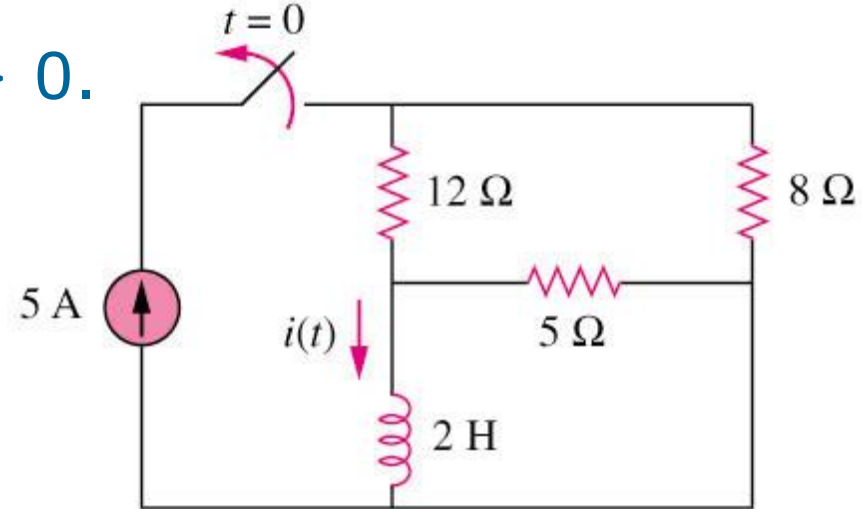Example 4

For the circuit, find $i(t)$ for $t > 0$.




Answer: $i(t) = 2e^{-2t}\ \text{A}$

7.4 Step-Response of a RC Circuit (4)

Example 5

Find $v(t)$ for $t > 0$ in the circuit in below. Assume the switch has been open for a long time and is closed at $t = 0$.

Calculate $v(t)$ at $t = 0.5$.

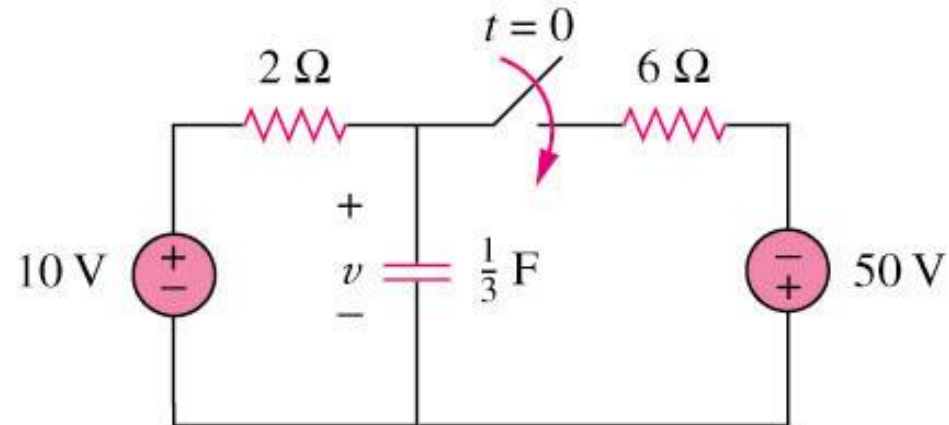


Answer: $v(t) = 15e^{-2t} - 5$ and $v(0.5) = 0.5182V$ 28

7.5 The Step-Response of a RL Circuit (4)

Example 6

The switch in the circuit shown below has been closed for a long time. It opens at $t = 0$.

Find $i(t)$ for $t > 0$.

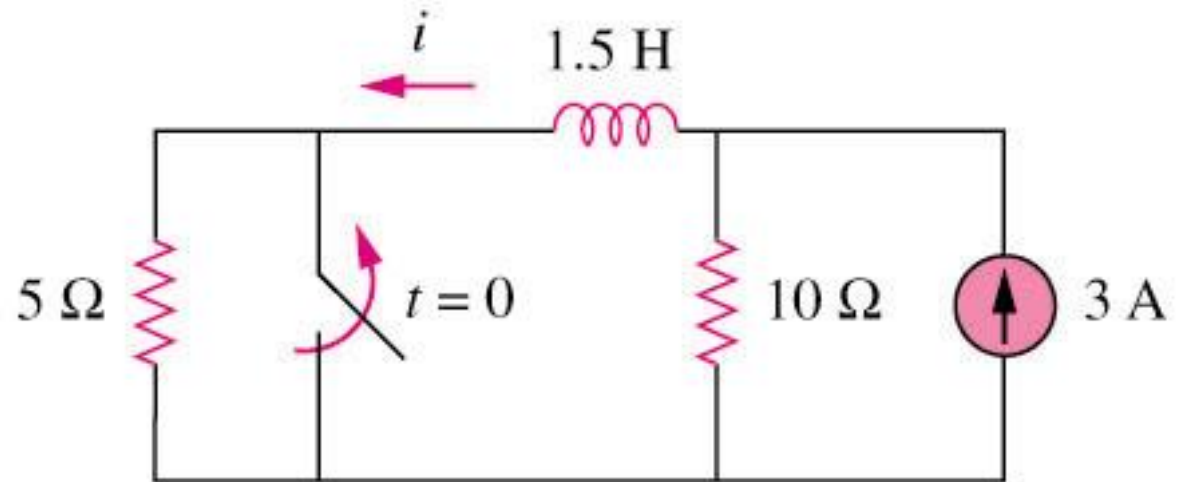

Answer: $i(t) = 2 + e^{-10t}$ 29