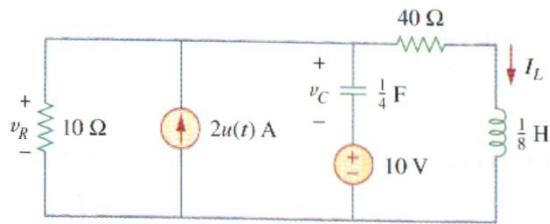


**8.3** Refer to the circuit shown in Fig. 8.64. Calculate:

- $i_L(0^+)$ ,  $v_C(0^+)$ , and  $v_R(0^+)$ ,
- $di_L(0^+)/dt$ ,  $dv_C(0^+)/dt$ , and  $dv_R(0^+)/dt$ ,
- $i_L(\infty)$ ,  $v_C(\infty)$ , and  $v_R(\infty)$ .



The  $2u(t)$  source is OFF for  $t < 0$  and ON for  $t > 0$ .

**ANSWER**

- $i_L(0+) = 0 \text{ A}$   
 $v_C(0+) = -10 \text{ V}$   
 $v_R(0+) = 0 \text{ V}$
- $di_L(0+)/dt = 0$   
 $dv_C(0+)/dt = 8 \text{ V/s}$   
 $dv_R(0+)/dt = 8 \text{ V/s}$
- $i_L(\infty) = 0.4 \text{ A}$   
 $v_C(\infty) = 6 \text{ V}$   
 $v_R(\infty) = 16 \text{ V}$

**8.4** In the circuit of Fig. 8.65, find:

- $v(0^+)$  and  $i(0^+)$ ,
- $dv(0^+)/dt$  and  $di(0^+)/dt$ ,
- $v(\infty)$  and  $i(\infty)$ .

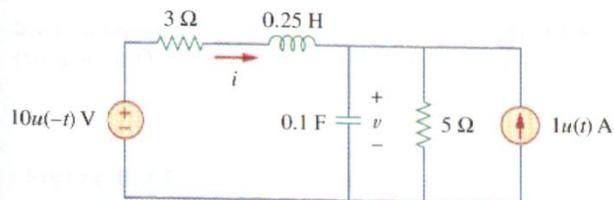


Figure 8.65

The  $10u(-t)$  source is ON for  $t < 0$  and OFF for  $t > 0$

The  $1u(t)$  source is OFF for  $t < 0$  and ON for  $t > 0$

**ANSWER**

- $v(0+) = 6.25 \text{ V}$   
 $i(0+) = 1.25 \text{ A}$
- $dv(0+)/dt = 10 \text{ V/s}$   
 $di(0+)/dt = -40 \text{ A/s}$
- $v(\infty) = 1.875 \text{ V}$   
 $i(\infty) = 0.625 \text{ V}$

**8.5** Refer to the circuit in Fig. 8.66. Determine:

- (a)  $i(0^+)$  and  $v(0^+)$ ,
- (b)  $di(0^+)/dt$  and  $dv(0^+)/dt$ ,
- (c)  $i(\infty)$  and  $v(\infty)$ .

**ANSWER**

- a)  $i(0+) = v(0+) = 0$
- b)  $di(0+)/dt = 0$   
 $dv(0+)/dt = 16 \text{ V/s}$
- c)  $i(\infty) = 1.6 \text{ A}$   
 $v(\infty) = 9.6 \text{ V}$

