

Circuit Theory

Chapter 8

Second-Order Circuits

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Second-Order Circuits




Chapter 8

- 8.1 Examples of 2nd order RLC circuit
- 8.2 The source-free series RLC circuit
- 8.3 The source-free parallel RLC circuit
- 8.4 Step response of a series RLC circuit
- 8.5 Step response of a parallel RLC

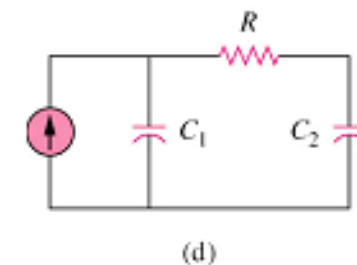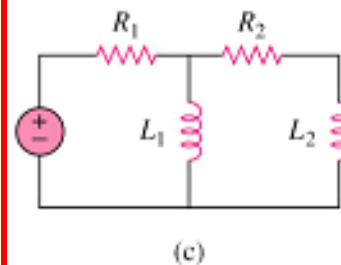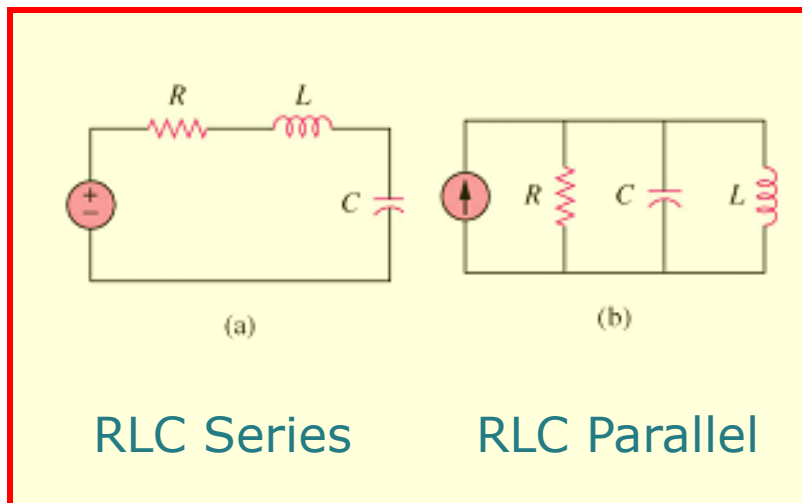8.1 Examples of Second Order RLC circuits

What is a 2nd order circuit?

A second-order circuit is characterized by a second-order differential equation. It consists of resistors and the equivalent of two energy storage elements.



An RLC circuit contains both an inductor and a capacitor


- These circuits have a wide range of applications, including oscillators and frequency filters
- They can also model automobile suspension systems, temperature controllers, airplane responses, etc.




RLC circuits

A very common use of inductors is as part of a **tuned circuit**. For instance, each slider on a graphic equalizer selects out a range of frequencies from the audio spectrum, and controls how much gain there should be for those frequencies. A later stage recombines the various frequency bands.

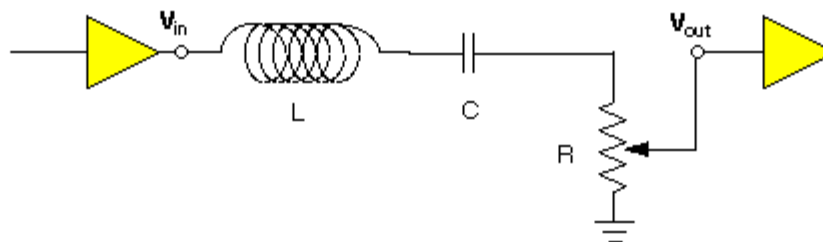RLC (Resistor-Inductor-Capacitor) circuits are a common way of extracting a frequency range. Here's part of a typical circuit:



8.2 Source-Free Series RLC Circuits (1)

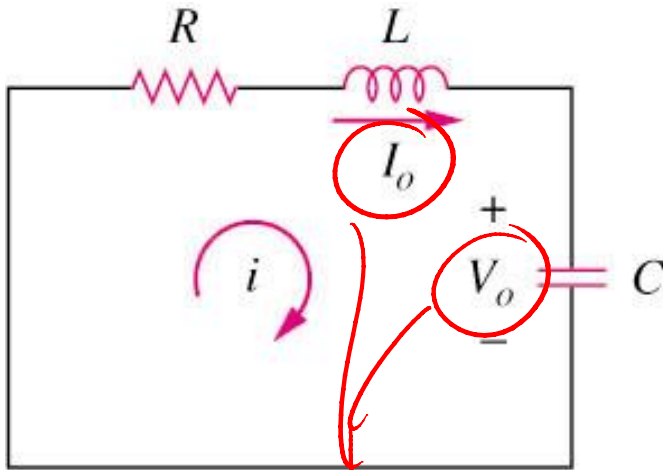

- The solution of the source-free series RLC circuit is called the natural response of the circuit.
- The circuit is excited by the energy initially stored in the capacitor and inductor.

$$\text{energy} = \frac{1}{2}LI_0^2 + \frac{1}{2}CV_0^2$$

**The 2nd
order of
expression**

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

How to derive and how to solve?

Derivation

Series RLC circuit

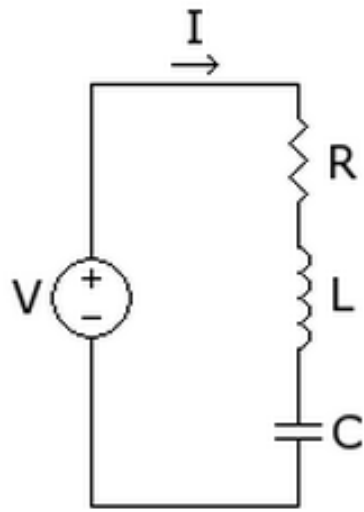


Figure 1. RLC series circuit

V - the voltage of the power source

I - the current in the circuit

R - the resistance of the resistor

L - the inductance of the inductor

C - the capacitance of the capacitor

From KVL,

$$v_R + v_L + v_C = v(t)$$

where v_R , v_L , v_C are the voltages across R, L and C respectively and $v(t)$ is the time varying voltage from the source. Substituting in the [constitutive equations](#),

$$Ri(t) + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^{\tau=t} i(\tau) d\tau = v(t)$$

For the case where the source is an unchanging voltage, differentiating and dividing by L leads to the second order differential equation:

$$\frac{d^2 i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = 0$$

This can usefully be expressed in a more generally applicable form:

$$\frac{d^2 i(t)}{dt^2} + 2\alpha \frac{di(t)}{dt} + \omega_0^2 i(t) = 0$$

8.2 Source-Free Series RLC Circuits (3)

There are three possible solutions for the following 2nd order differential equation:

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

$$\Rightarrow \frac{d^2 i}{dt^2} + 2\alpha \frac{di}{dt} + \omega_0^2 i = 0$$

General 2nd order Form

where

Neper Freq

$$\alpha = \frac{R}{2L}$$

and

Natural or Resonant Freq

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

The types of solutions for $i(t)$ depend on the relative values of α and ω .

To solve (1) $\frac{d^2i}{dt^2} + 2\alpha \frac{di}{dt} + \omega_0^2 i = 0$

- Assume a solution of the form

$$i(t) = Ae^{st}$$

- Then $\frac{di}{dt} = sAe^{st}$ and $\frac{d^2i}{dt^2} = s^2Ae^{st}$

- Substitute into (1), $s^2Ae^{st} + 2\alpha sAe^{st} + \omega_0^2Ae^{st} = 0$

- And divide out the common terms
to get $s^2 + 2\alpha s + \omega_0^2 = 0$ (the characteristic eqn)

- Solve for s: $s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$

- s has either 2 real, 1 real, or 2 complex solutions

8.2 Source-Free Series RLC Circuits (4)

There are three possible solutions for the following 2nd order differential equation:

$$\frac{d^2i}{dt^2} + 2\alpha \frac{di}{dt} + \omega_0^2 i = 0$$

$$\alpha = \frac{R}{2L} \quad \text{and} \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

1. If $\alpha > \omega_0$, over-damped case

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \text{where} \quad s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

2. If $\alpha = \omega_0$, critical damped case

$$i(t) = (A_2 + A_1 t) e^{-\alpha t} \quad \text{where} \quad s_{1,2} = -\alpha$$

3. If $\alpha < \omega_0$, under-damped case

$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) \quad \text{where} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

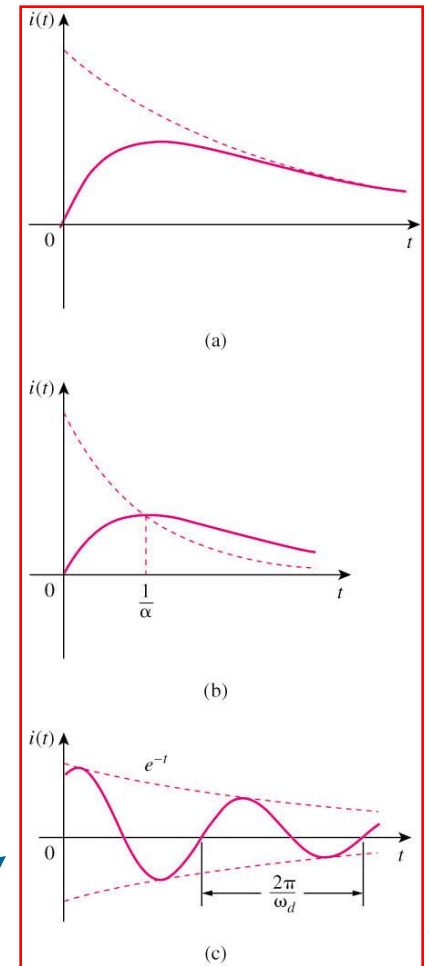
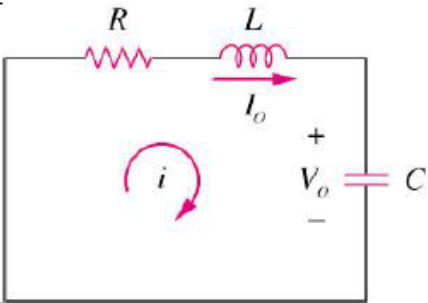



Table 1: Natural Response of Series RLC

Circuit			
Diff-Eq	$\frac{d^2i}{dt^2} + 2\alpha \frac{di}{dt} + \omega_0^2 i = 0$ $\alpha = \frac{R}{2L} \quad \text{and} \quad \omega_0 = \sqrt{\frac{1}{LC}}$		
Damping	Over: $\omega_0^2 < \alpha^2$	Under: $\omega_0^2 > \alpha^2$	Critical: $\omega_0^2 = \alpha^2$
Form of Soln	$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$	$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$	$i(t) = A_1 t e^{-\alpha t} + A_2 e^{-\alpha t}$
Roots	$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$	$s_{1,2} = -\alpha \pm j\omega_d, \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$	$s_{1,2} = -\alpha$
Boundary Conditions	$i(0+) = A_1 + A_2$ $\frac{di(0+)}{dt} = s_1 A_1 + s_2 A_2$	$i(0+) = B_1$ $\frac{di(0+)}{dt} = -\alpha B_1 + \omega_d B_2$	$i(0+) = A_2$ $\frac{di(0+)}{dt} = A_1 - \alpha A_2$

1a) Source-Free Series RLC

If $R = 10 \Omega$, $L = 5 \text{ H}$, and $C = 2 \text{ mF}$, find α , ω_0 , s_1 and s_2 .

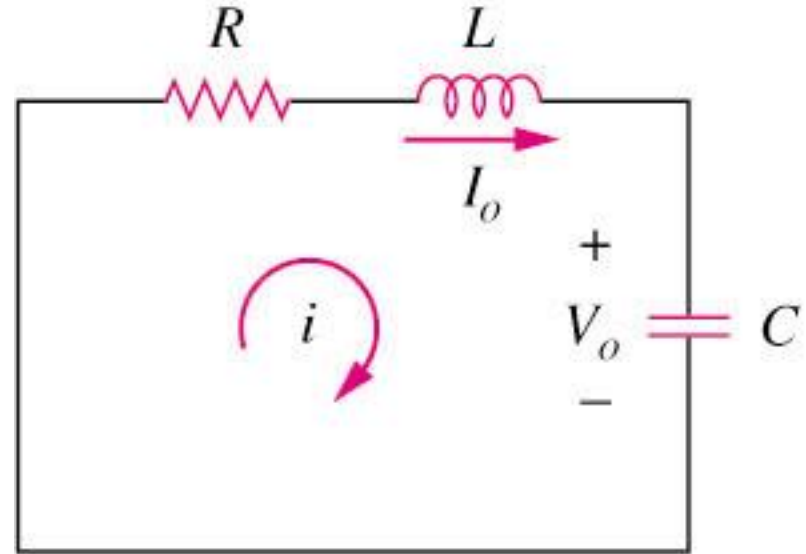What type of natural response will the circuit have?



$$\alpha = \frac{R}{2L} = \frac{10}{2(5)} = 1 \text{ Np/s}$$
$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(5)(.002)}} = \frac{1}{\sqrt{.01}} = 10 \text{ Rad/s}$$


} $\omega_0 > \alpha \rightarrow$
Underdamped

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$s_1 = -1 + \sqrt{1 - 10^2} = -1 + j 9.95$$
$$s_2 = -1 - j 9.95$$

Answer: underdamped ¹¹

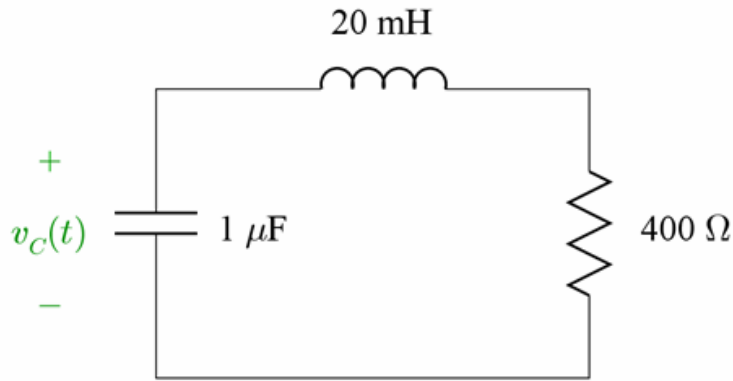1b) determine the qualitative form of the response as being either overdamped, underdamped, or critically damped.




Overdamped

$$\alpha = \frac{R}{2L} = \frac{400}{2(.02)} = 10,000 \text{ Np/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{[(.02)(1 \times 10^{-6})]^{1/2}}$$

$$= 7071 \text{ Rad/s}$$

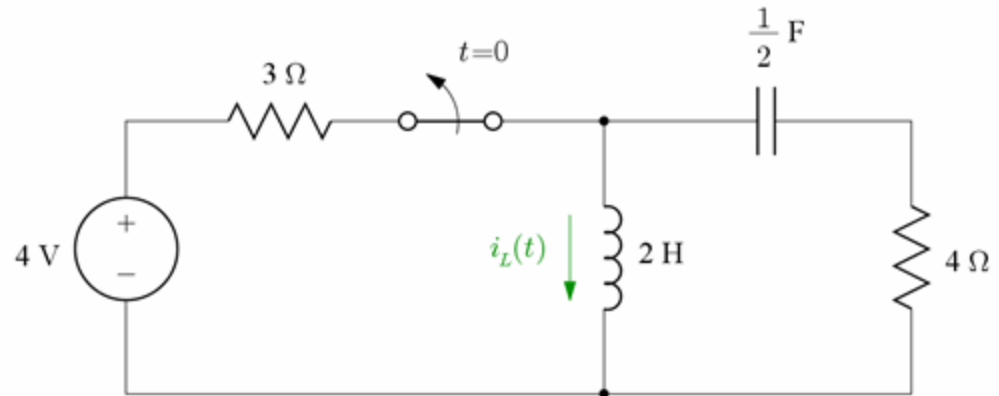$\alpha > \omega_0 \rightarrow$ overdamped



Critically damped

$$\alpha = \frac{R}{2L} = \frac{4}{2(2)} = 1 \text{ Np/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{[(2)(.5)]^{1/2}} = 1 \text{ Rad/s}$$


$\alpha = \omega_0 \rightarrow$
critically damped

2) Source-Free Series RLC

The circuit shown has reached steady state at $t = 0^-$. The capacitor is uncharged.

If the make-before-break switch moves to position b at $t = 0$, calculate $i(t)$ for $t > 0$.

1) Find α , ω_0 + damping behavior

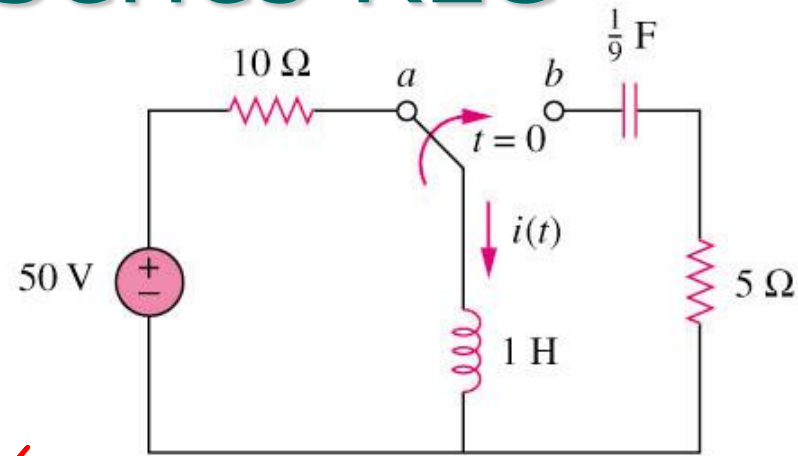

$$\alpha = \frac{R}{2L} = \frac{5}{2(1)} = \underline{\underline{2.5}} \quad \left. \begin{array}{l} \omega_0 > \alpha \\ \therefore \text{underdamped} \end{array} \right\}$$


$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(1)(1/9)}} = \underline{\underline{3}} \quad \left. \begin{array}{l} \omega_0 > \alpha \\ \therefore \text{underdamped} \end{array} \right\} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{9 - 6.25} = \underline{\underline{1.658}}$$

2) Solve for initial conditions a) $i_L(0^+)$ + b) $\frac{di_L(0^+)}{dt}$

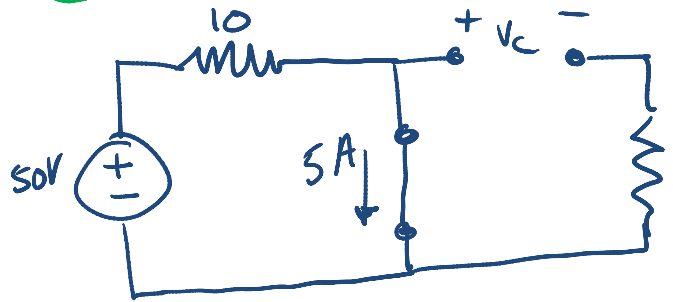a) $i_L(0^+) \equiv i_L(0^-) = \frac{50V}{10\Omega} = 5A$

(Inductor is a short at $t=0^-$)

Circuit at $t=0^-$
 $L \rightarrow$ short ckt
 $C \rightarrow$ open ckt



b) Inductor Law: $V_L = L \frac{di_L}{dt} \rightarrow \frac{di_L}{dt}(0^+) = \frac{V_L(0^+)}{L}$


Redraw ckt at $t=0^+$ with $L \rightarrow I_0$ & $C \rightarrow V_0$

KVL

$$-V_L(0^+) + 0 - (5A)(5\Omega) = 0$$

$$V_L(0^+) = -25V$$
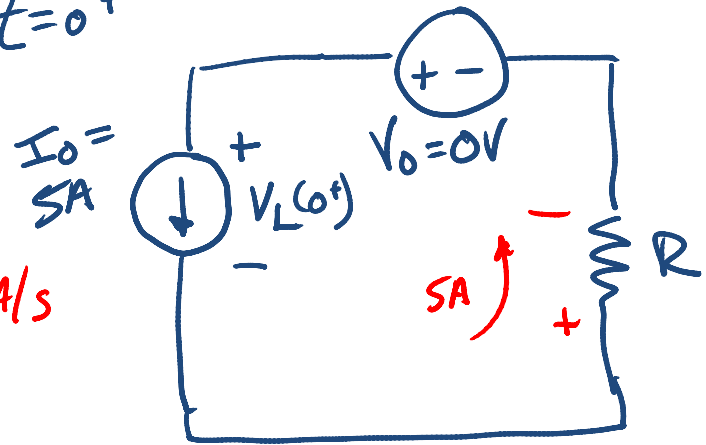
$$\frac{di_L}{dt}(0^+) = \frac{V_L(0^+)}{L} = \frac{-25}{1} = -25A/s$$



3) Solve for B_1, B_2 (see table handout)

$$B_1 = i_L(0^+) = 5$$

$$-\alpha B_1 + \omega B_2 = \frac{di_L(0^+)}{dt} = -25A/s$$


$$-(2.5)(5) + (1.658)B_2 = -25 \rightarrow B_2 = \frac{-12.5}{1.658} = -7.539$$

4) Compile Solution $i_L(t) = e^{-2.5t} (5 \cos 1.658t - 7.539 \sin 1.658t)$

Answer: $i(t) = e^{-2.5t} [5 \cos 1.6583t - 7.538 \sin 1.6583t] A$

```
t = 0:0.01:4;  
f=exp(-2.5*t).*(5*cos(1.6583*t)-7.538*sin(1.6583*t));  
plot(t,f)
```


$\dot{i}_2(t)$,
A

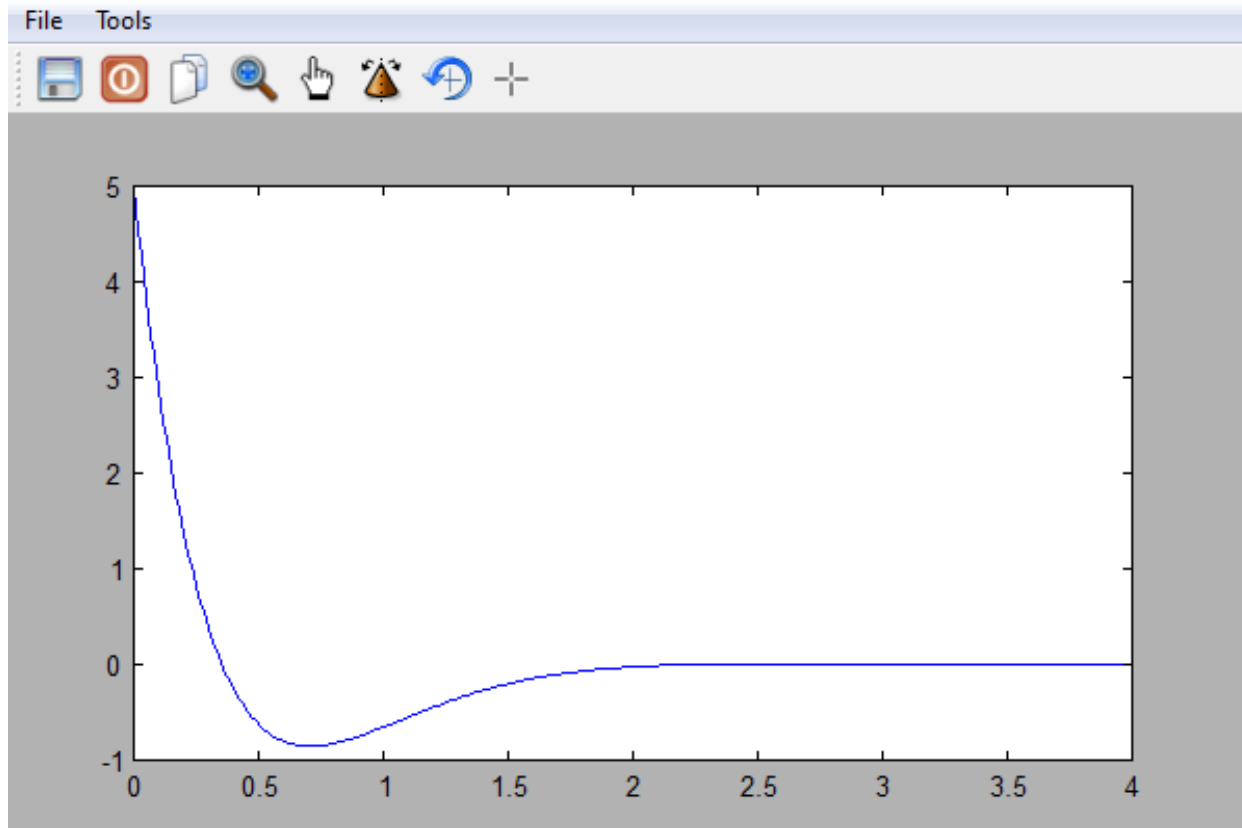

t, Sec


`plot(t(2:end),diff(f)./diff(t))`

$\frac{dL(t)}{dt}$
A/s

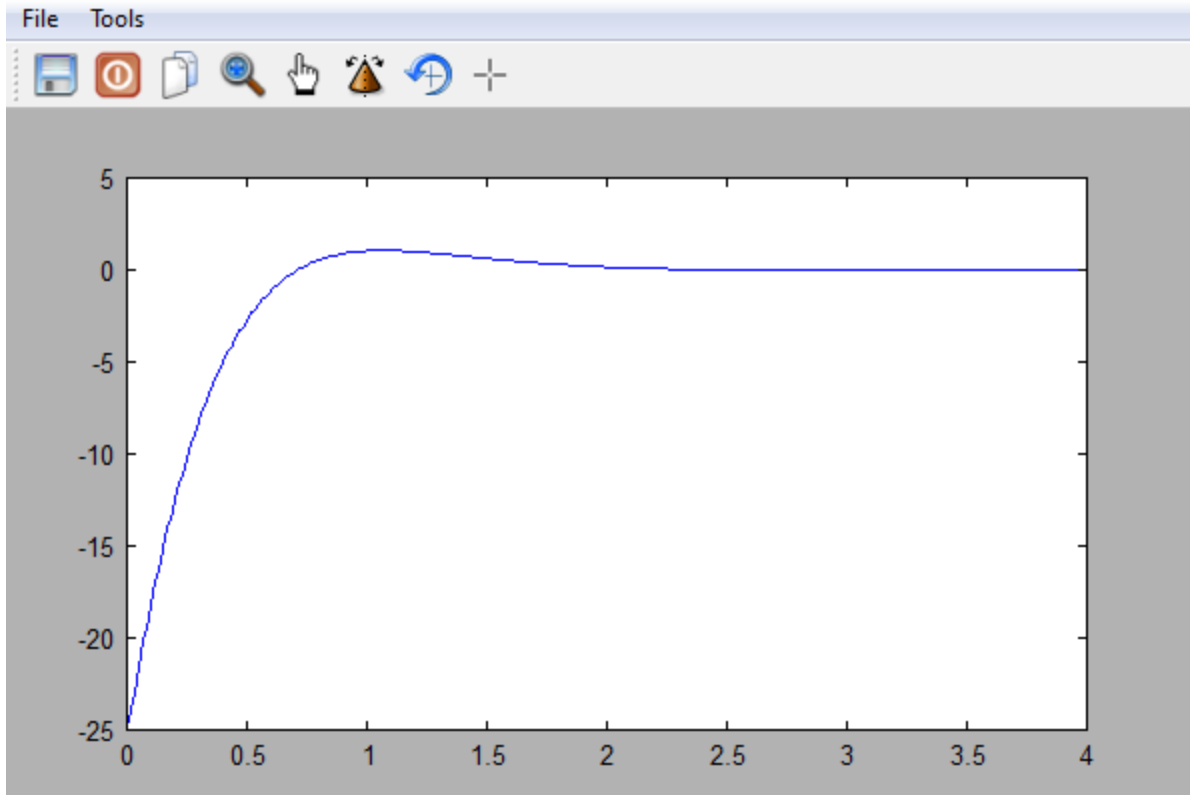

t, s

8.3 Source-Free Parallel RLC Circuits

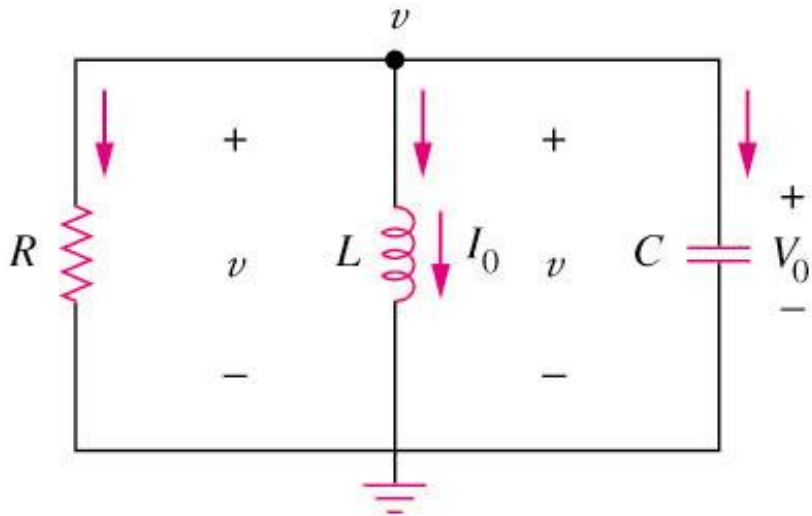

Let

$$i(0) = I_0 = \frac{1}{L} \int_{-\infty}^0 v(t) dt$$

$$v(0) = V_0$$

Apply KCL to the top node:

$$\frac{v}{R} + \frac{1}{L} \int_{-\infty}^t v dt + C \frac{dv}{dt} = 0$$

Taking the derivative with respect to t and dividing by C

The 2nd order equation

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

8.3 Source-Free Parallel RLC Circuits

There are three possible solutions for the following 2nd order differential equation:

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

how using v_c as variable

$$\Rightarrow \frac{d^2 v}{dt^2} + 2\alpha \frac{dv}{dt} + \omega_0^2 v = 0$$

General 2nd order Form

where

$$\alpha = \frac{1}{2RC} \quad \text{and} \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

↳ vs series RLC, where $\alpha = \frac{R}{2L}$

The types of solutions for $i(t)$ depend on the relative values of α and ω .

8.3 Source-Free Parallel RLC Circuits

There are three possible solutions for the following 2nd order differential equation:

$$\frac{d^2v}{dt^2} + 2\alpha \frac{dv}{dt} + \omega_0^2 v = 0$$

1. If $\alpha > \omega_0$, over-damped case

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \text{ where } s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

2. If $\alpha = \omega_0$, critical damped case

$$v(t) = (A_2 + A_1 t) e^{-\alpha t} \text{ where } s_{1,2} = -\alpha$$

3. If $\alpha < \omega_0$, under-damped case

$$v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) \text{ where } \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

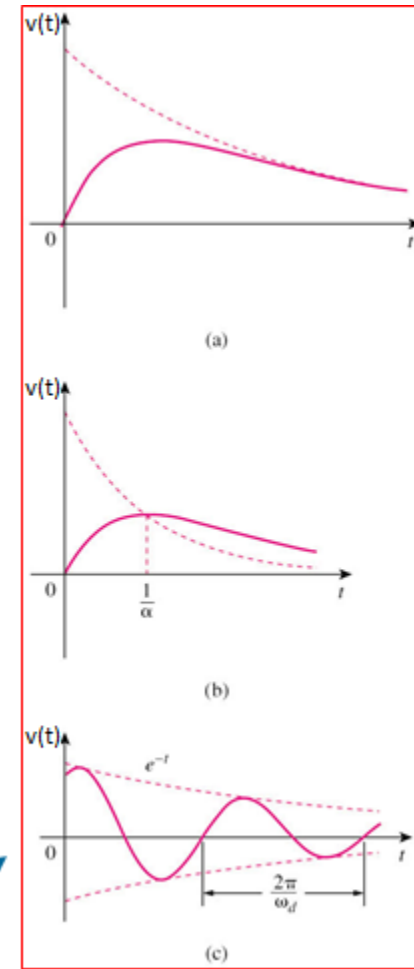
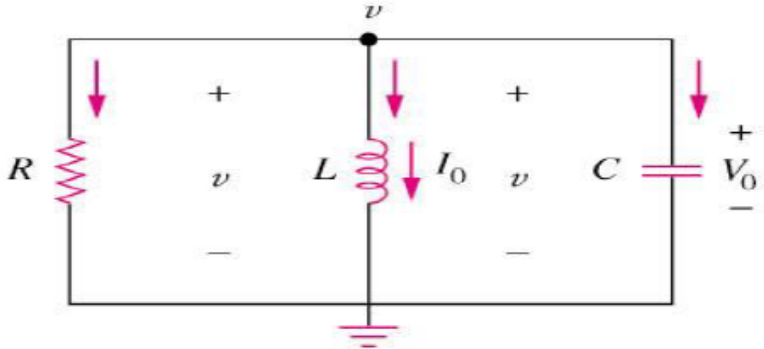


Table 3: Natural Response of Parallel RLC

Circuit			
Diff-Eq	$\frac{d^2v}{dt^2} + 2\alpha \frac{dv}{dt} + \omega_0^2 v = 0 \quad \text{where} \quad \alpha = \frac{1}{2RC} \quad \text{and} \quad \omega_0 = \sqrt{\frac{1}{LC}}$		
Damping	Over: $\omega_0^2 < \alpha^2$	Under: $\omega_0^2 > \alpha^2$	Critical: $\omega_0^2 = \alpha^2$
Form of Soln	$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$	$v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$	$v(t) = (A_2 + A_1 t) e^{-\alpha t}$
Roots	$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$	$s_{1,2} = -\alpha \pm j\omega_d, \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$	$s_{1,2} = -\alpha$
Boundary Conditions	$v(0+) = A_1 + A_2$ $\frac{dv(0+)}{dt} = \frac{i_c(0+)}{C} = s_1 A_1 + s_2 A_2$	$v_c(0+) = B_1$ $\frac{dv(0+)}{dt} = \frac{i_c(0+)}{C} = -\alpha B_1 + \omega_d B_2$	$v(0+) = A_2$ $\frac{dv(0+)}{dt} = \frac{i_c(0+)}{C} = A_1 - \alpha A_2$

3) Source-Free Parallel RLC Circuit

Find $v(t)$ for $t > 0$.

1) Find α , ω_0 + damping behavior

$$\alpha = \frac{1}{2RC} = \frac{1}{2(20)(.004)} = 6.25$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{[10(.004)]^{1/2}} = 5$$

$\alpha > \omega_0 \rightarrow$ over damped $\rightarrow \begin{cases} s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -6.25 + 3.75 = -2.5 \\ s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -6.25 - 3.75 = -10 \end{cases}$

2) Solve for initial conditions a) $V(0^+)$ + b) $\frac{dV(0^+)}{dt}$

a) $V(0^+) \equiv V(0^-) = 0V$



(Inductor is a short at $t=0^-$)

Capacitor \rightarrow

$$i_C(0^+) = i_C(0^-) = 2A$$

Redraw Ckt at $t=0^-$

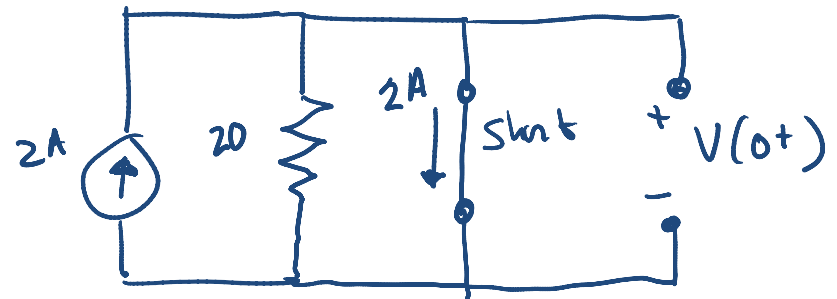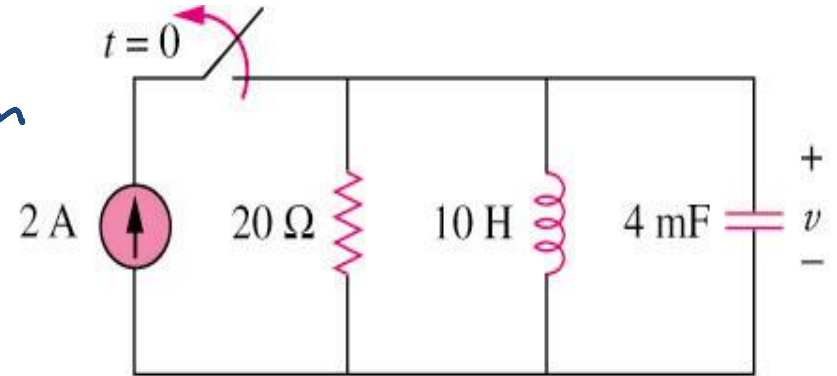$L \rightarrow$ short
 $C \rightarrow$ open




b) Capacitor Law: $i_c = C \frac{dV_c}{dt} \rightarrow \frac{dV_c(0^+)}{dt} = \frac{i_c(0^+)}{C}$

Redraw ckt at $t=0^+$, with $L \rightarrow I_0$ & $C \rightarrow V_0$

KCL

$$i_c(0^+) = -2A$$
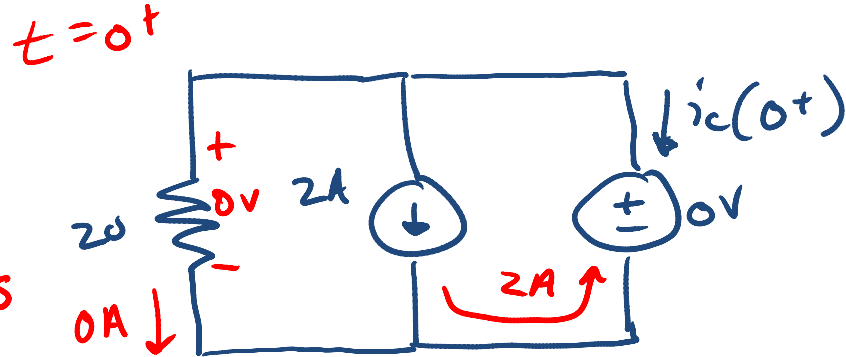
$$\frac{dV_c(0^+)}{dt} = \frac{-2A}{.004F} = -500V/s$$



3) Solve for A_1, A_2 (see table handout)

$$A_1 + A_2 = V(0^+) = 0 \rightarrow A_2 = -A_1$$

$$s_1 A_1 + s_2 A_2 = \frac{dV}{dt}(0^+) = -500 = -2.5A_1 - 10A_2$$

$$10A_1 - 2.5A_1 = -500, \quad 7.5A_1 = -500, \quad A_1 = -66.67, \\ A_2 = +66.67$$


4) Assemble final solution:

$$V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} = -66.67 e^{-2.5t} + 66.67 e^{-10t}$$

Answer: $V(t) = \underline{66.67(e^{-10t} - e^{-2.5t}) V}$

```
t = 0:0.01:4;  
f = 66.67*(exp(-10*t)-exp(-2.5*t)) ;  
plot(t,f)  
axis([0 3 -35 5])
```


$v(t)$
Volts

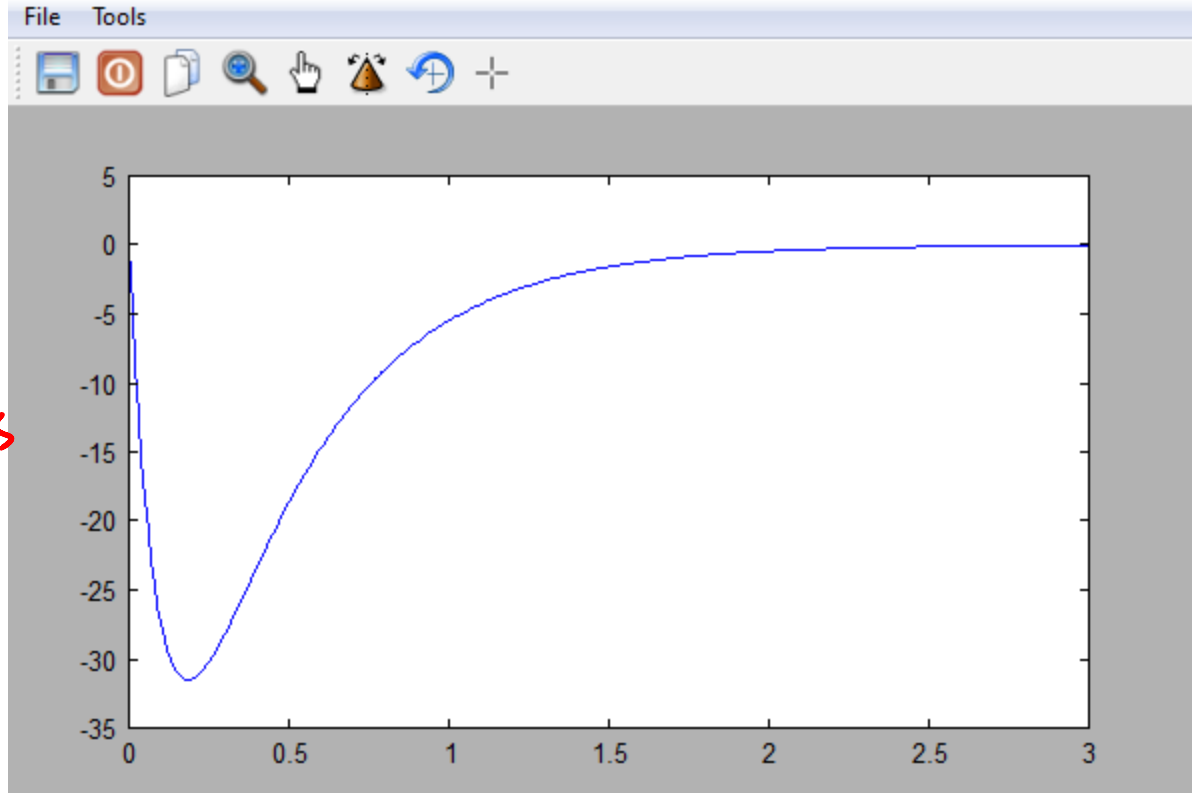

t, sec

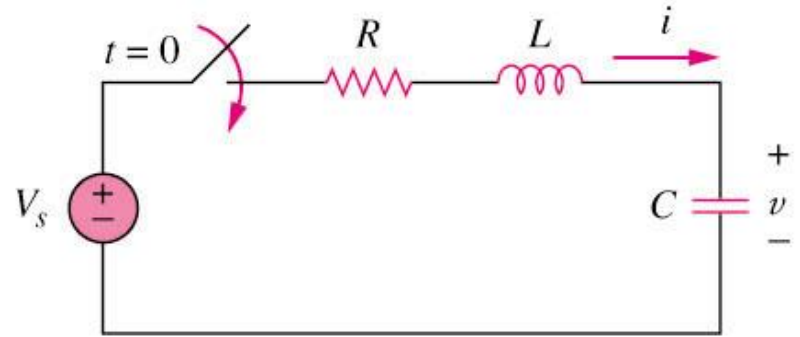8.4 Step-Response Series RLC

- The step response is obtained by the sudden application of a dc source.



KVL

$$V_s = Ri + L \frac{di}{dt} + v$$

But

$$i = C \frac{dv}{dt}$$

Substitute, div by LC

**The 2nd
order
expression**

$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{v_s}{LC}$$

The above equation has the same form as the equation for source-free series RLC circuit.

- The same coefficients (important in determining the frequency parameters).
- Different circuit variable in the equation.

8.4 Step-Response Series RLC Circuits (2)

The solution of the equation should have two components: the transient response $v_t(t)$ & the steady-state response $v_{ss}(t)$:

$$v(t) = v_t(t) + v_{ss}(t)$$

- The transient response v_t is the same as that for source-free case


$$v_t(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{over-damped})$$

$$v_t(t) = (A_1 + A_2 t) e^{-\alpha t} \quad (\text{critically damped})$$

$$v_t(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t) \quad (\text{under-damped})$$


- The steady-state response is the final value of $v(t)$
 - $v_{ss}(t) = v(\infty)$
- The values of A_1 and A_2 are obtained from the initial conditions:
 - $v(0)$ and $dv(0)/dt$.

Table 2: Step Response of Series RLC

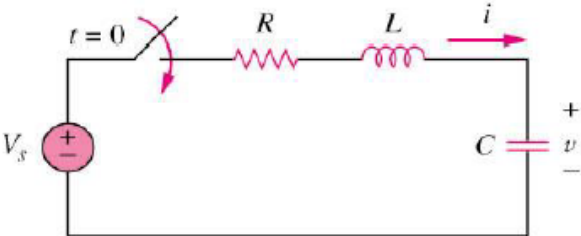Circuit			
Diff-Eq	$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{v_s}{LC}$ $\alpha = \frac{R}{2L} \quad \text{and} \quad \omega_0 = \sqrt{\frac{1}{LC}}$		
Damping	Over: $\omega_0^2 < \alpha^2$	Under: $\omega_0^2 > \alpha^2$	Critical: $\omega_0^2 = \alpha^2$
Form of Soln	$v(t) = v(\infty) + A_1 e^{s_1 t} + A_2 e^{s_2 t}$	$v(t) = v(\infty) + e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$	$v(t) = v(\infty) + A_1 t e^{-\alpha t} + A_2 e^{-\alpha t}$
Roots	$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$	$s_{1,2} = -\alpha \pm j\omega_d, \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$	$s_{1,2} = -\alpha$
Boundary Conditions	$v(0+) = v(\infty) + A_1 + A_2$ $\frac{dv(0+)}{dt} = s_1 A_1 + s_2 A_2$	$v(0+) = v(\infty) + B_1$ $\frac{dv(0+)}{dt} = -\alpha B_1 + \omega_d B_2$	$v(0+) = v(\infty) + A_2$ $\frac{dv(0+)}{dt} = A_1 - \alpha A_2$

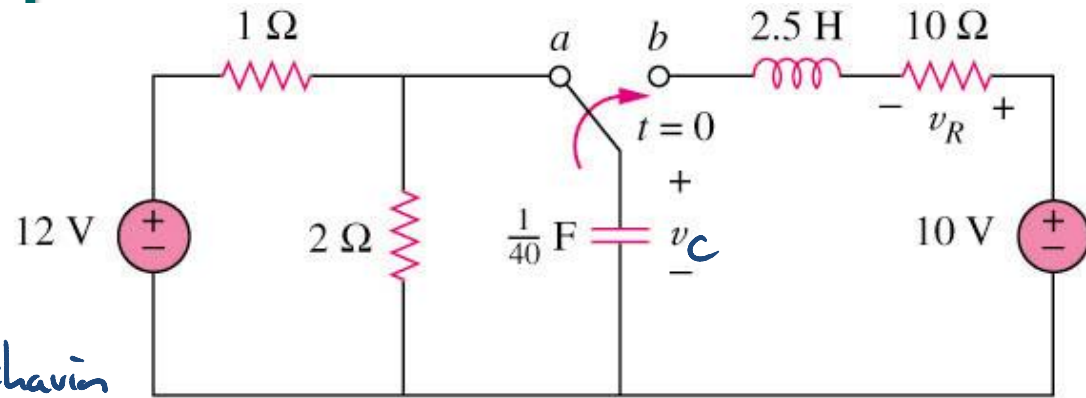4) Step-Response Series RLC

Having been in position a for a long time, the switch in the circuit below is moved to position b at $t = 0$. Find $v(t)$ and $v_R(t)$ for $t > 0$.



1) Find α , ω_0 + damping behavior

$$\alpha = \frac{R}{2L} = \frac{10}{(2)(2.5)} = 2$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\left(\frac{2.5}{40}\right)^{\frac{1}{2}}} = 4$$

$\omega_0 > \alpha \rightarrow$ underdamped

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \underline{\underline{3.46}}$$


2) Solve for initial + final conditions a) $v_C(0^+)$, b) $\frac{dv_C(0^+)}{dt}$, c) $v_C(\infty)$

Redraw cct at $t=0^-$

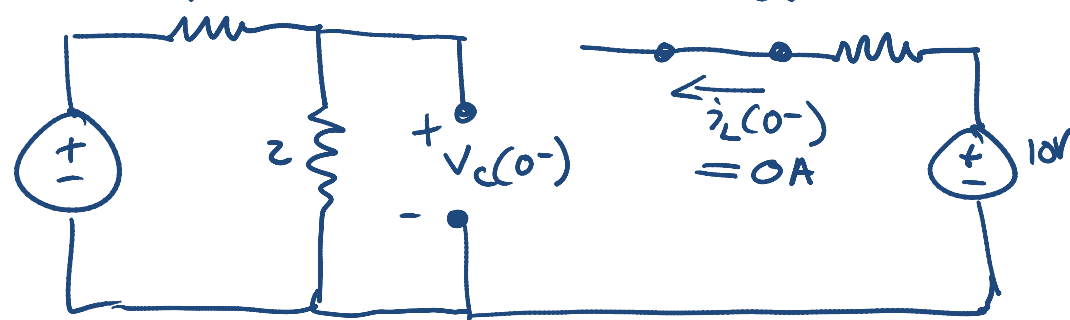a) $v_C(0^+) \equiv v_C(0^-)$

$$= 12 \left(\frac{2}{2+1} \right) = \underline{\underline{8V}}$$

$i_L(0^+) \equiv i_L(0^-) = \underline{\underline{0A}}$




$$b) \frac{dV_c(t)}{dt} = \frac{i_c(t)}{C}$$

$$C \rightarrow 8V$$

$$L \rightarrow 0A$$

(Redraw
Cct at
 $t=0^+$)

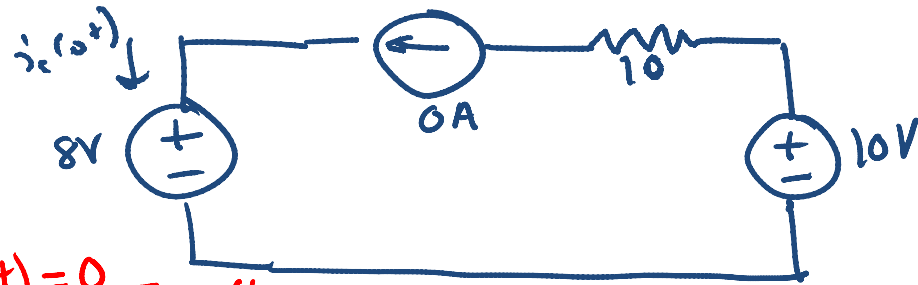


$$i_c(t) = 0A \text{ (Inductor)}, \frac{dV_c(t)}{dt} = \frac{0}{C} = 0V/s$$

$$c) V_c(\infty) = 10V$$

$$C \rightarrow \text{open}$$

$$L \rightarrow \text{short}$$

(Redraw
cct at
 $t=\infty$)

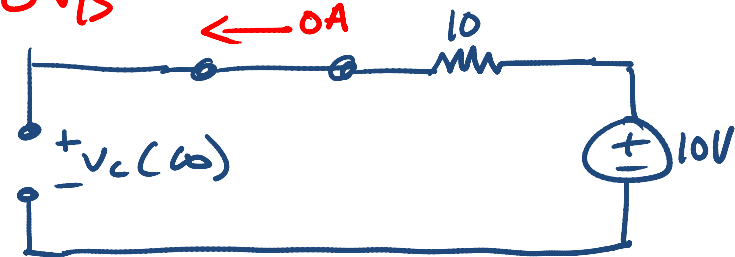

3) Solve for B_1, B_2

$$V_c(t) = V_c(\infty) + B_1 \rightarrow B_1 = V_c(t) - V_c(\infty) = 8 - 10 = \underline{\underline{-2V}}$$

$$\frac{dV_c(t)}{dt} = 0 = -\alpha B_1 + \omega B_2 = -(2)(-2) + 3.46 B_2 = 0$$

$$B_2 = \frac{-4}{3.46} = -1.15$$

4) Assemble final solution

$$V_c(t) = V_c(\infty) + e^{-\alpha t} (B_1 \cos \omega t + B_2 \sin \omega t)$$

$$= 10 + e^{-2t} (-2 \cos(3.46t) - 1.15 \sin(3.46t))$$


$$V_R(t) = R i_c(t) = R dV_c(t)/dt$$

Answer: $v(t) = \underline{\underline{\{10 + [(-2\cos 3.464t - 1.1547\sin 3.464t)e^{-2t}]\}} V}$

$$V_R(t) = \underline{\underline{[2.31\sin 3.464t]e^{-2t} V}}$$


```
t = 0:0.01:4;  
f = 10+(-2*cos(3.464*t)-1.1547*sin(3.464*t))*exp(-2*t);  
plot(t,f)
```


V(t)
Volts

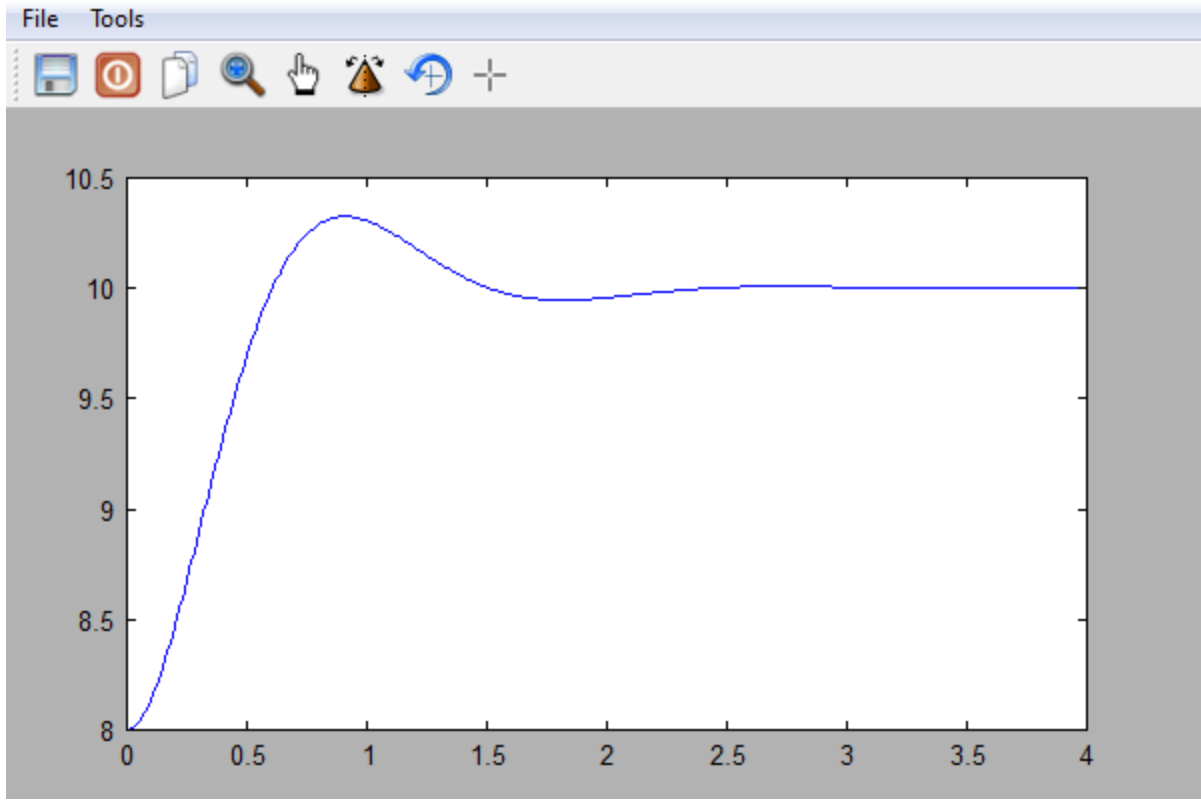

t, sec

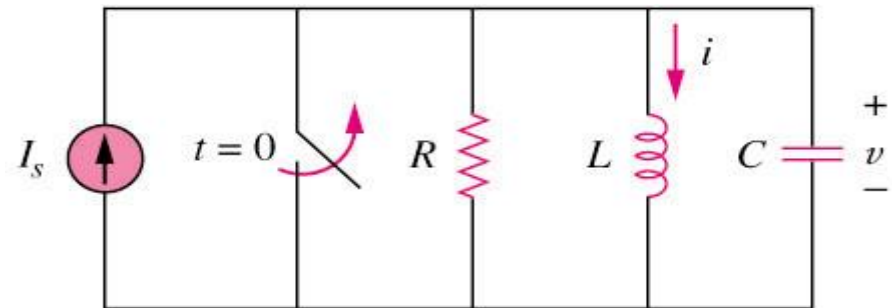8.5 Step-Response Parallel RLC Circuits (1)

- The step response is obtained by the sudden application of a dc source.



**The 2nd
order
expression**

$$\frac{d^2i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC}$$

It has the same form as the equation for source-free parallel RLC circuit.

- The same coefficients (important in determining the frequency parameters).
- Different circuit variable in the equation.

8.5 Step-Response Parallel RLC Circuits (2)

The solution of the equation should have two components: the transient response $i_t(t)$ & the steady-state response $i_{ss}(t)$:

$$i(t) = i_t(t) + i_{ss}(t)$$

- The transient response i_t is the same as that for source-free case


$$i_t(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{over-damped})$$

$$i_t(t) = (A_1 + A_2 t) e^{-\alpha t} \quad (\text{critical damped})$$

$$i_t(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t) \quad (\text{under-damped})$$


- The steady-state response is the final value of $i(t)$.
 - $i_{ss}(t) = i(\infty) = I_s$
- The values of A_1 and A_2 are obtained from the initial conditions:
 - $i(0)$ and $di(0)/dt$.

Table 4: Step Response of Parallel RLC

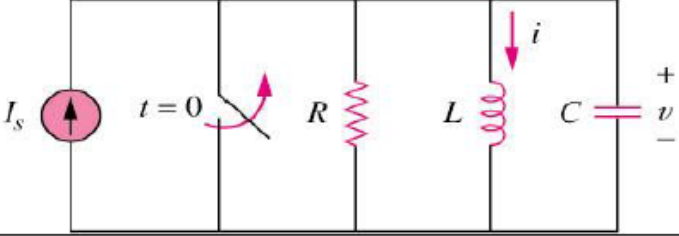Circuit			
Diff-Eq	$\frac{d^2i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC}$ <p style="text-align: right;">where $\alpha = \frac{1}{2RC}$ and $\omega_0 = \sqrt{\frac{1}{LC}}$</p>		
Damping	Over: $\omega_0^2 < \alpha^2$	Under: $\omega_0^2 > \alpha^2$	Critical: $\omega_0^2 = \alpha^2$
Form of Soln	$i(t) = i(\infty) + A_1 e^{s_1 t} + A_2 e^{s_2 t}$	$i(t) = i(\infty) + e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$	$i(t) = i(\infty) + A_1 t e^{-\alpha t} + A_2 e^{-\alpha t}$
Roots	$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$	$s_{1,2} = -\alpha \pm j\omega_d$, $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$	$s_{1,2} = -\alpha$
Boundary Conditions	$i(0+) = i(\infty) + A_1 + A_2$ $\frac{di(0+)}{dt} = \frac{v_L(0+)}{L} = s_1 A_1 + s_2 A_2$	$i(0+) = i(\infty) + B_1$ $\frac{di(0+)}{dt} = \frac{v_L(0+)}{L} = -\alpha B_1 + \omega_d B_2$	$i(0+) = i(\infty) + A_2$ $\frac{di(0+)}{dt} = \frac{v_L(0+)}{L} = A_1 - \alpha A_2$

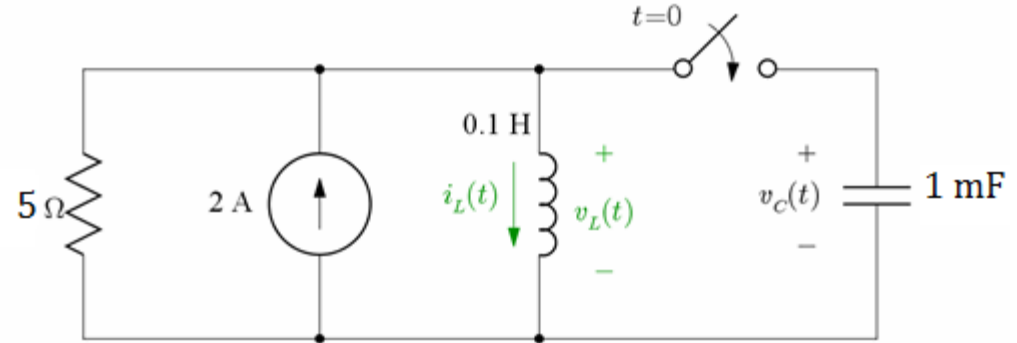5) Step-Response Parallel RLC Cct

Find $i_L(t)$ for $t > 0$,
 given $v_C(0^-) = 10V$, and switch
 has been open a long time
 before closing at $t=0$



1) find α , ω_0 & damping

$$\alpha = \frac{1}{2RC} = \frac{1}{2(5)(0.001)} = 100$$

$$\omega_0 = \frac{1}{\sqrt{L(0.001)}} = 100$$

$\omega_0 = \alpha \rightarrow$ Critically Damped

2) Solve for initial & final conditions ^{a)} $i_L(0^+)$, ^{b)} $\frac{di_L(0^+)}{dt}$, ^{c)} $i_L(\infty)$

a) $i_L(0^+) = 2A$


b) $\frac{di_L(0^+)}{dt} = \frac{V_L(0^+)}{L}$

$V_L(0^+) = V_C(0^+) = 10V$

$\frac{di_L(0^+)}{dt} = \frac{10V}{0.1H} = 100 V/s$

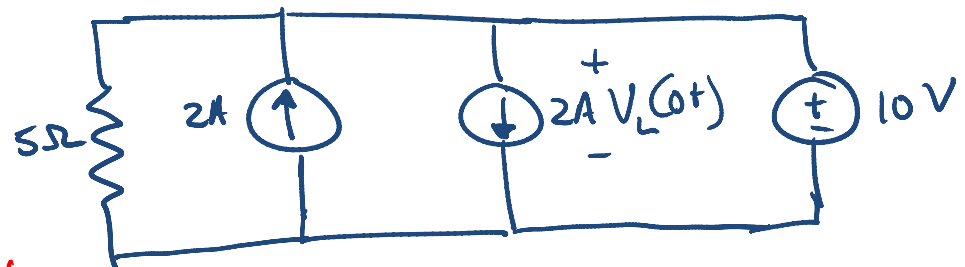c) $i_L(\infty) = 2A$

Redraw at $t=0^+$ $C \rightarrow V_0$, $L \rightarrow I_0$




3) Solve for A_1 & A_2 (table)

$$i_L(0^+) = A_2 + i_L(\infty), \quad A_2 = i_L(0^+) - i_L(\infty) = 0$$

$$\frac{di_L}{dt}(0^+) = A_1 - \alpha A_2 = 100, \quad A_1 = 100$$

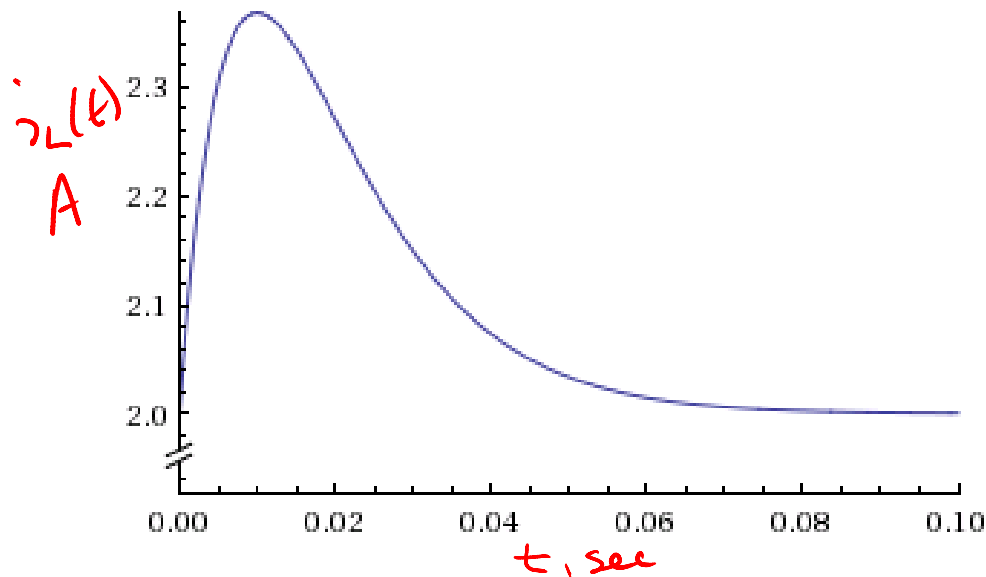4) Assemble final solution


$$\begin{aligned} i_L(t) &= i_L(\infty) + A_1 t e^{-\alpha t} + A_2 e^{-\alpha t} \\ &= 2 + 100 t e^{-100 t} \end{aligned}$$



Answer: $i_L(t) = 2 + 100te^{-100t}, t > 0$

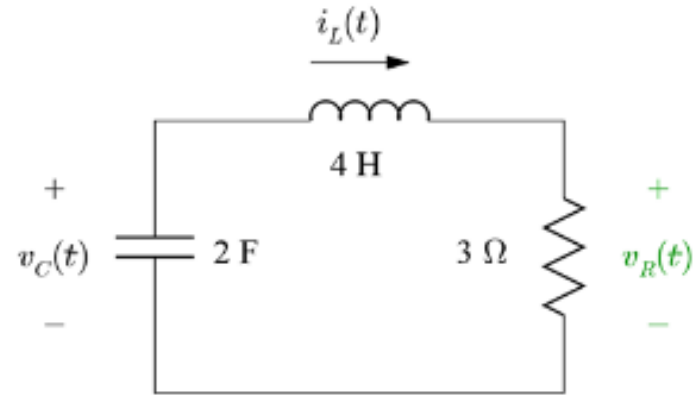6) Determine the initial value of $V_r(t)$, and $dV_r(t)/dt$, and the final value of $V_r(t)$

<http://www.rose-hulman.edu/CLEO/video/player.php?id=34&embed>




$$v_C(0) = 10 \text{ V}$$

$$i_L(0) = 2 \text{ A}$$

$$\frac{dv_C(0^+)}{dt} = \frac{\dot{i}_C}{C} = -\frac{2}{2} = -1 \text{ V/s}$$

$$\frac{d\dot{i}_L(0^+)}{dt} = \frac{V_L}{L} = \frac{4}{4} = 1 \text{ A/s}$$
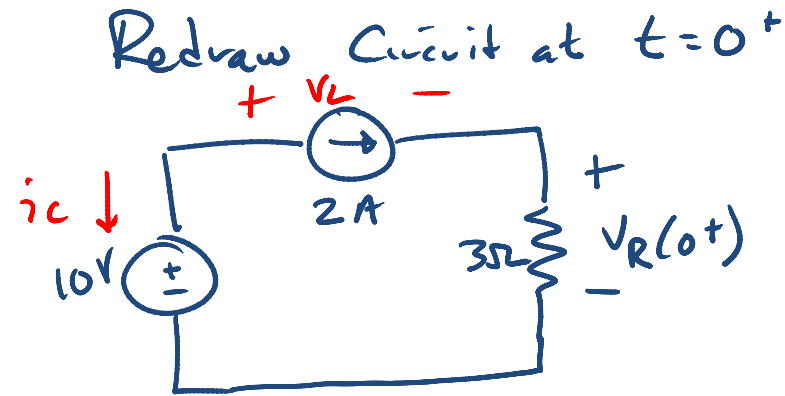
$$\dot{i}_L(\infty) = 0 \text{ (capacitor)}$$



Ohm's Law

$$V_R(0^+) = \dot{i}_R(0^+) 3 = 6 \text{ V}$$

$$\frac{dV_R(0^+)}{dt} = \frac{d\dot{i}_R(0^+)}{dt} 3$$

$$= \frac{d\dot{i}_L(0^+)}{dt} (3)$$


$$= (1)(3) = 3 \text{ A/s}$$

$$V_r(0) = 6 \text{ V}; \quad V_r(\infty) = \dot{i}_R(\infty) (3) = \dot{i}_L(\infty) (3) = 0$$


$$dV_r(0)/dt = 3 \text{ V/s};$$

$$V_r(\text{infinity}) = 0 \text{ V}$$

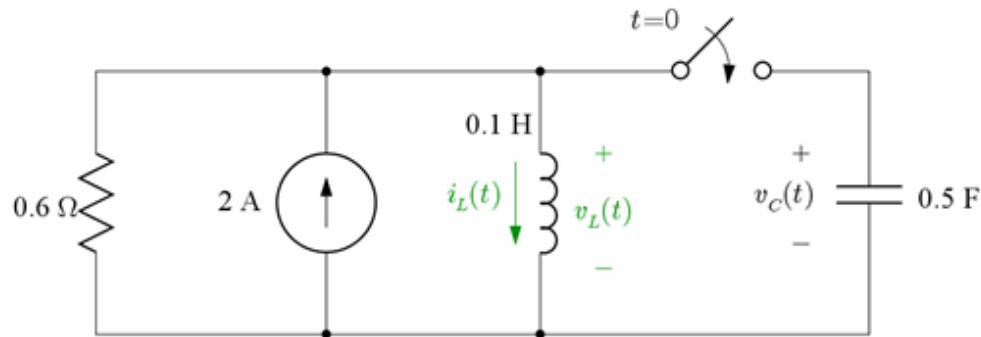7) For both the inductor current and voltage, determine their initial values, the initial values of their derivatives, and their final values. The capacitor has 9 J of stored energy before the switch closes.



$(t = 0^+)$

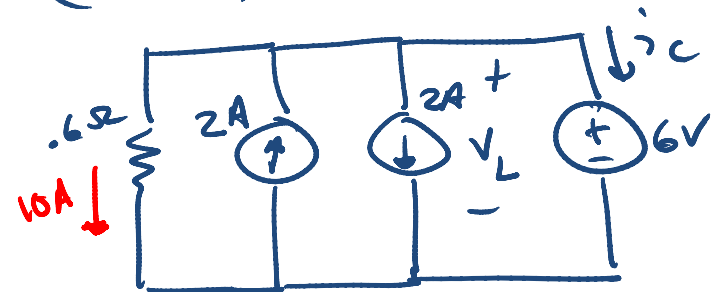

$$W_C = 9 \text{ J} = \frac{C V_C^2}{2} = \frac{.5 V_C^2}{2} \rightarrow V_C^2 = 9(4), \underline{V_C(0^+) = 6V}$$

$$\underline{i_L(0^+) = 2A}$$

$$\frac{di_L(0^+)}{dt} = \frac{V_L(0^+)}{L} = \frac{V_C(0^+)}{L} = \frac{6}{.1} = \underline{60 \text{ A/s}}$$

$$\underline{i_L(\infty) = 2A}$$

$$\frac{dV_C(0^+)}{dt} = \frac{i_C(0^+)}{C} = \frac{-10A}{.5F}$$

$$= \underline{-20 \text{ V/s}}$$

$$\underline{V_C(\infty) = 0V}$$

$$i_L(0) = 2A$$

$$\frac{di_L(0)}{dt} = 60 \text{ A/s}$$

$$i_L(\infty) = 2A$$

$$v_L(0^-) = 0V, v_L(0^+) = 6V$$

$$\frac{dv_L(0)}{dt} = -20 \text{ V/s}$$


$$v_L(\infty) = 0V$$

Handouts


1a) Source-Free Series RLC

If $R = 10 \Omega$, $L = 5 \text{ H}$, and $C = 2 \text{ mF}$, find α , ω_o , s_1 and s_2 .

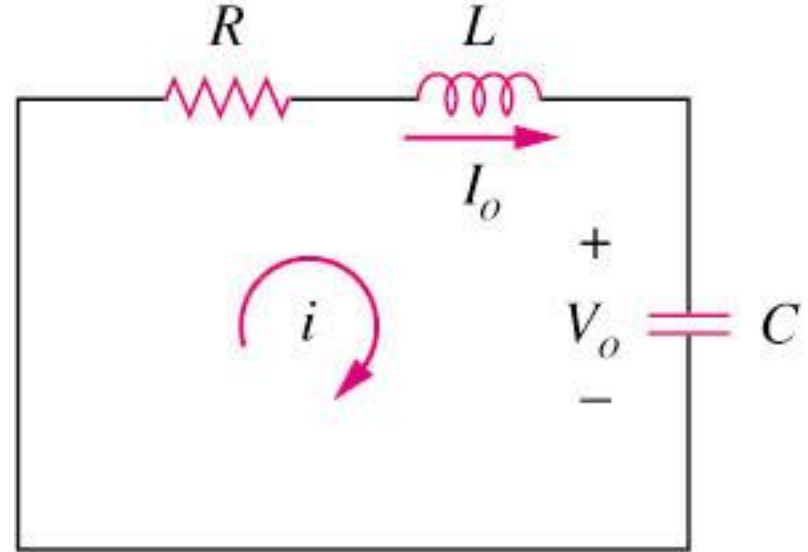
What type of natural response will the circuit have?



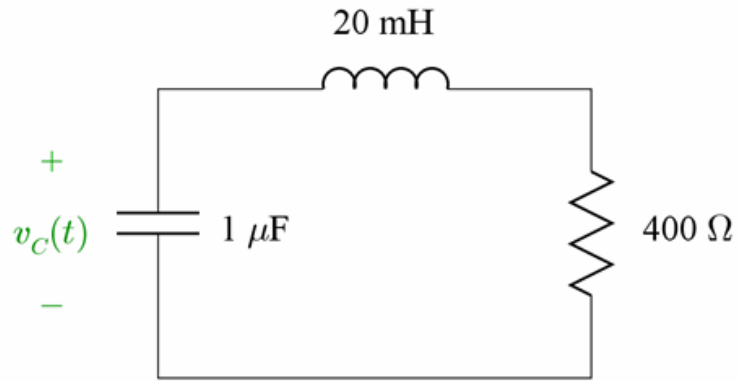1b) determine the qualitative form of the response as being either overdamped, underdamped, or critically damped.



Overdamped

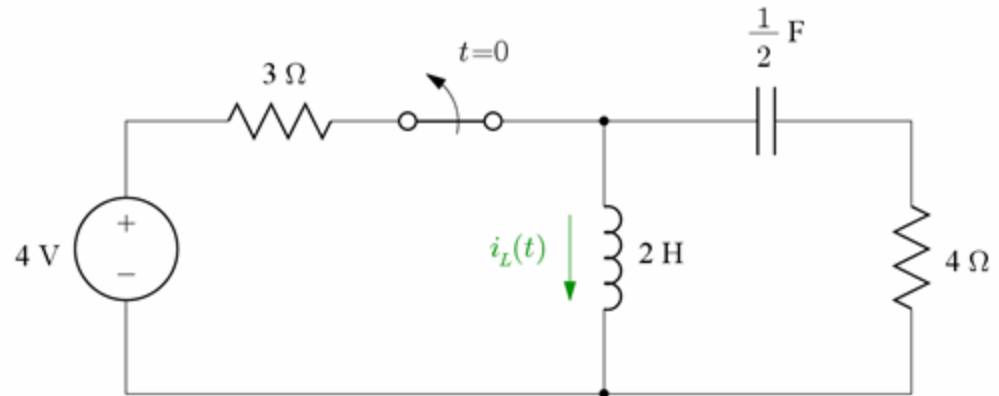


Critically damped

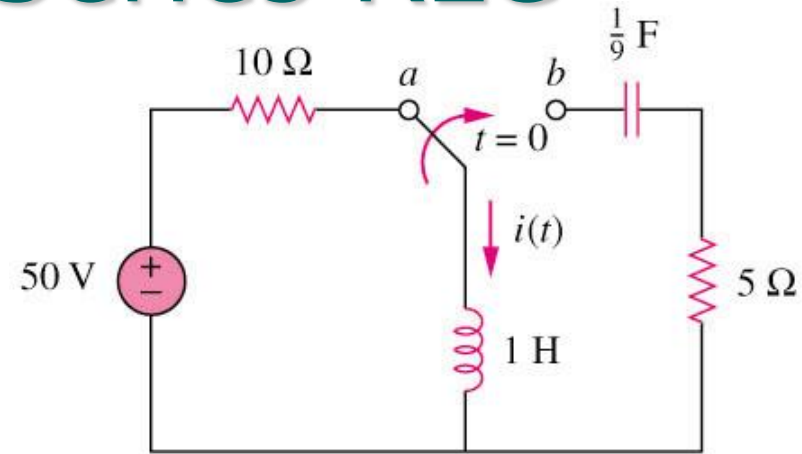2) Source-Free Series RLC

The circuit shown has reached steady state at $t = 0^-$.


If the make-before-break switch moves to position b at $t = 0$, calculate $i(t)$ for $t > 0$.



Answer: $i(t) = \underline{e^{-2.5t}[5\cos 1.6583t - 7.538\sin 1.6583t]} \text{ A}$

3) Source-Free Parallel RLC Circuit


Find $v(t)$ for $t > 0$.

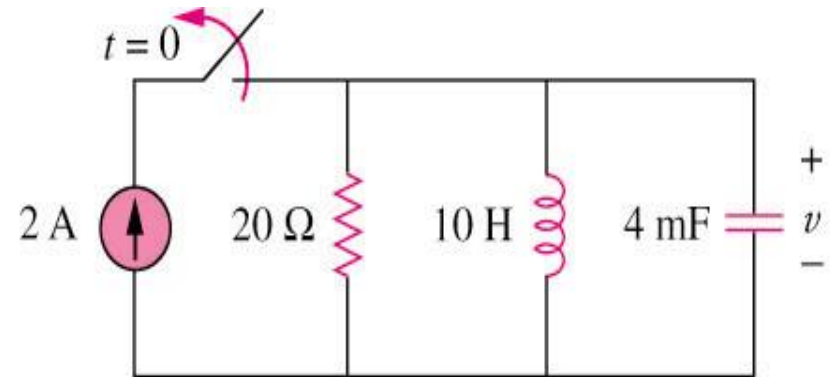

Answer: $v(t) = \underline{\underline{66.67(e^{-10t} - e^{-2.5t}) \text{ V}}}$ 42

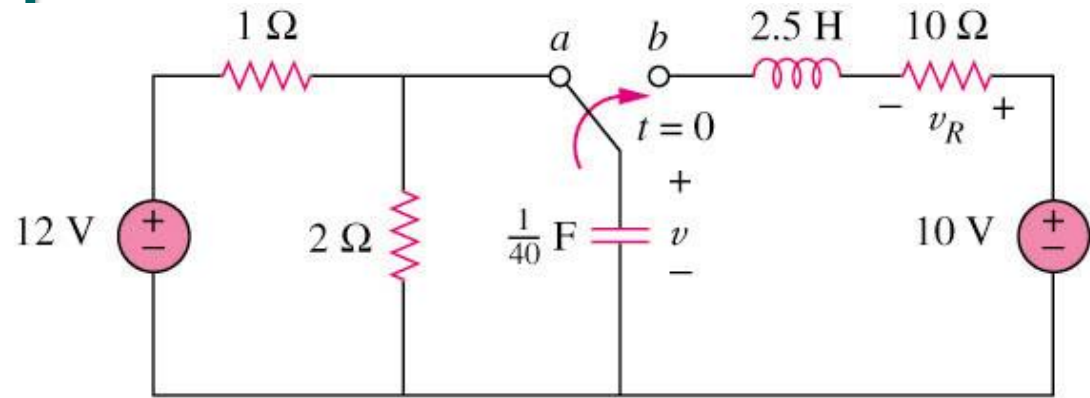4) Step-Response Series RLC

Having been in position a for a long time, the switch in the circuit below is moved to position b at $t = 0$. Find $v(t)$ and $v_R(t)$ for $t > 0$.




Answer: $v(t) = \{10 + [(-2\cos 3.464t - 1.1547\sin 3.464t)e^{-2t}]\}$ V

$$v_R(t) = \underline{[2.31\sin 3.464t]e^{-2t}} \text{ V}$$

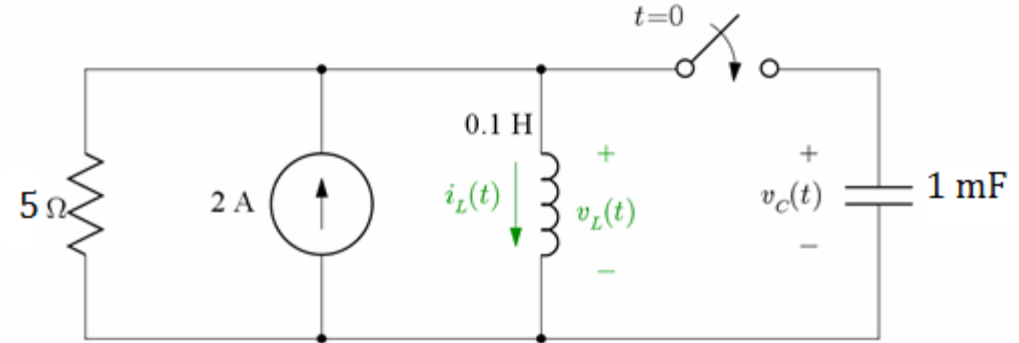5) Step-Response Parallel RLC Cct


Find $i_L(t)$ for $t > 0$,
given $v_c(0^-) = 10\text{V}$, and switch
has been open a long time
before closing at $t = 0$



Answer: $\underline{i_L(t) = 2 + 100te^{-100t}, t > 0}$

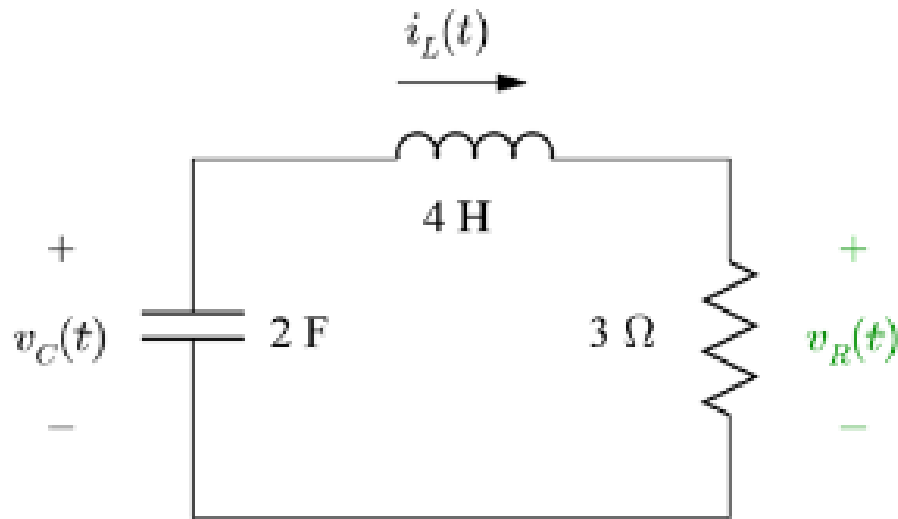6) Determine the initial value of $V_r(t)$, and $dV_r(t)/dt$, and the final value of $V_r(t)$

<http://www.rose-hulman.edu/CLEO/video/player.php?id=34&embed>




$$v_C(0) = 10 \text{ V}$$

$$i_L(0) = 2 \text{ A}$$

$$\begin{aligned} V_r(0) &= 6 \text{ V}; \\ dV_r(0)/dt &= 3 \text{ V/s}; \\ V_r(\text{infinity}) &= 0 \text{ V} \end{aligned}$$

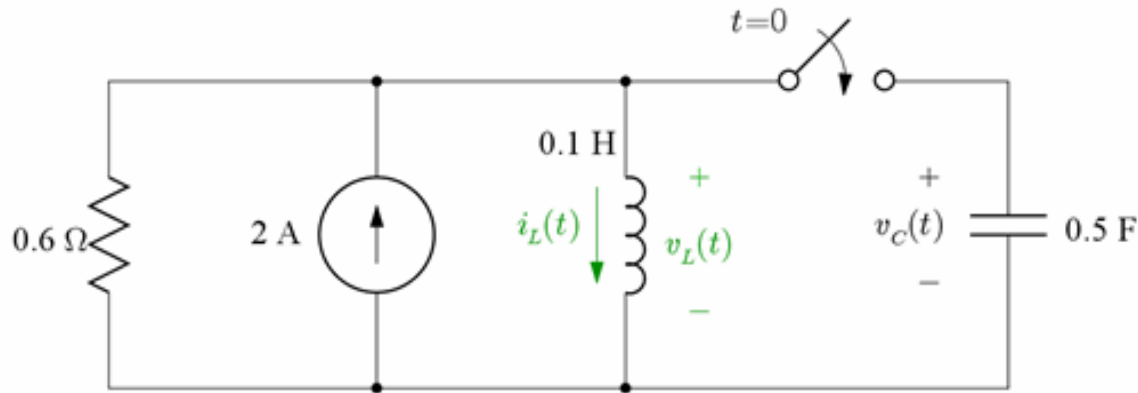7) For both the inductor current and voltage, determine their initial values, the initial values of their derivatives, and their final values. The capacitor has 9 J of stored energy before the switch closes.



$$\begin{array}{ll}
 i_L(0) = 2 \text{ A} & v_L(0^-) = 0 \text{ V}, v_L(0^+) = 6 \text{ V} \\
 \frac{di_L(0)}{dt} = 60 \text{ A/s} & \frac{dv_L(0)}{dt} = -20 \text{ V/s} \\
 i_L(\infty) = 2 \text{ A} & v_L(\infty) = 0 \text{ V}
 \end{array}$$